

# Design Kit

## Class D Audio Amplifier Using IRS2092

# Contents

	<b>Slide #</b>
1. Specification.....	3
• Efficiency.....	4-5
• THD.....	6-7
• Frequency Response.....	8-9
• Note: $P_o[W]$ vs. $V_{in}[V_{PEAK}]$ .....	10
2. Waveforms Evaluations.....	11
3. Simulated vs. Measured Waveforms.....	12-14
4. Voltage Gain – $G_V$ .....	15-16
5. Self Oscillation Frequency.....	17-18
6. Dead time.....	19-21
7. Turn on transient.....	22-25
8. Components stress.....	26-27
9. Power loss in the MOSFETs.....	28
• Standard Model.....	29-30
• Professional Model.....	31-33
• Standard vs. Professional Model.....	34-35
10. Short circuit vs. switching output shutdown.....	36-38
11. Short Circuit Response.....	39-41
12. Capacitor Models.....	42-44
13. Simulated Performance of the circuit with different FETs.....	45-47
14. Simulation Index .....	48



# 1. Specifications

---

## General Test Conditions

Supply Voltage	$\pm 15V$
Load Impedance	8-4 $\Omega$
Self-Oscillating Frequency	400kHz
Gain Setting	24dB

[Simulation folder](#)

## Electrical Data

Output Power	25W	(1kHz, 4 $\Omega$ )
Efficiency	93%	(25W, 4 $\Omega$ )

[\[Efficiency\]](#)


## Audio Performance

Distortion	Less than 0.015%THD	(1kHz, 4 $\Omega$ , 10W)
Frequency Response : 20Hz~20kHz	$\pm 1dB$	(20 ~ 20000 Hz, 4 $\Omega$ , 2V Output)

[\[THD\]](#)

[\[FrqRsp\]](#)
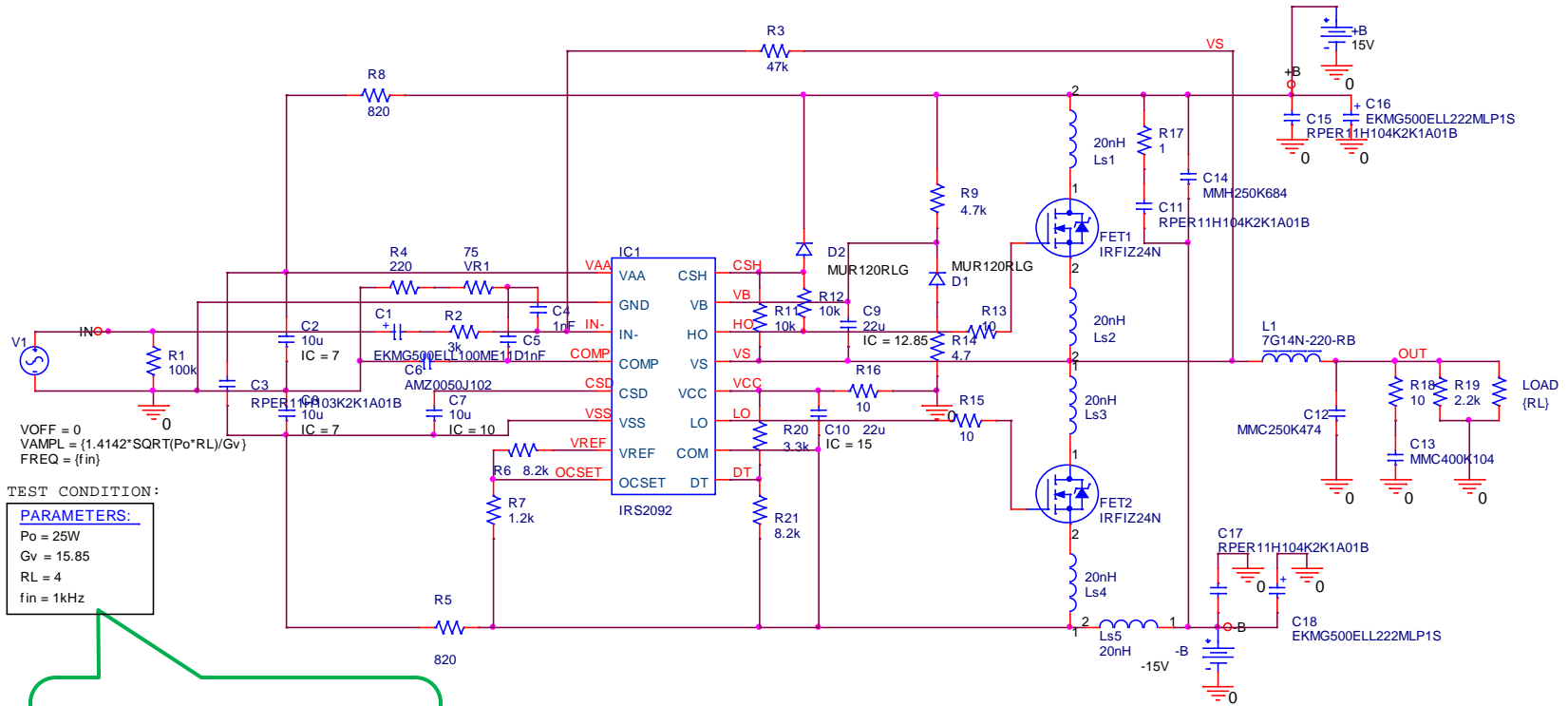
# Specifications : Efficiency Evaluation Circuit



Condition :  
 $P_o = 25[W]$ ,  $4\Omega$  Load

## Analysis

Time Domain (Transient)

Run to time: 3ms

Start saving data after: 1ms

Maximum step size: 100n

Skip the initial transient bias point calculation (SKIPBP)

## .Options

RELTOL: 0.01

VNTOL: 1.0u

ABSTOL: 1.0n

CHGTOL: 0.01p

GMIN: 1.0E-12


ITL1: 500

ITL2: 200


ITL4: 10


 
# Specifications : Efficiency Simulation Result


 
# Specifications : THD Evaluation Circuit



Condition :  
 $f_{in} = 1\text{kHz}$ ,  $P_o = 10\text{[W]}$ ,  
 $4\Omega$  Load

## Analysis

Time Domain (Transient)

Run to time: 3ms

Start saving data after: 0s

Maximum step size: 100n

Skip the initial transient bias point calculation (SKIPBP)

Output File Options...

Perform Fourier Analysis

Center Frequency: 1kHz

Output Variables: V(OUT)

## .Options

RELTOL: 0.01

VNTOL: 1.0u

ABSTOL: 1.0n

CHGTOL: 0.01p

GMIN: 1.0E-12


ITL1: 500

ITL2: 200

ITL4: 10



# Specifications : THD Simulation Result

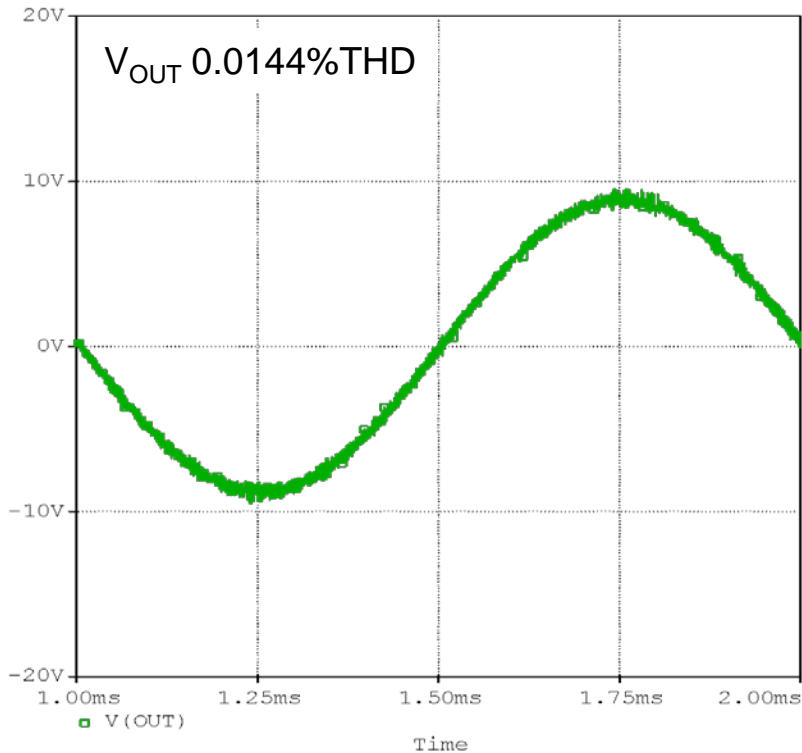


HARMONIC NO	FREQUENCY (HZ)	FOURIER COMPONENT	NORMALIZED COMPONENT	PHASE (DEG)	NORMALIZED PHASE
1	1.00E+03	8.81E+00	1.00E+00	1.79E+02	0.00E+00
2	2.00E+03	4.62E-04	5.25E-05	4.18E+01	-3.15E+02
3	3.00E+03	2.78E-04	3.16E-05	8.49E+01	-4.51E+02
4	4.00E+03	3.23E-04	3.67E-05	6.91E+01	-6.45E+02
5	5.00E+03	3.73E-04	4.23E-05	8.66E+01	-8.06E+02
6	6.00E+03	6.69E-04	7.60E-05	6.10E+01	-1.01E+03
7	7.00E+03	2.85E-04	3.24E-05	8.09E+01	-1.17E+03
8	8.00E+03	4.32E-04	4.91E-05	7.17E+01	-1.36E+03
9	9.00E+03	5.95E-04	6.76E-05	2.70E+01	-1.58E+03

TOTAL HARMONIC DISTORTION = 1.438206E-02 PERCENT


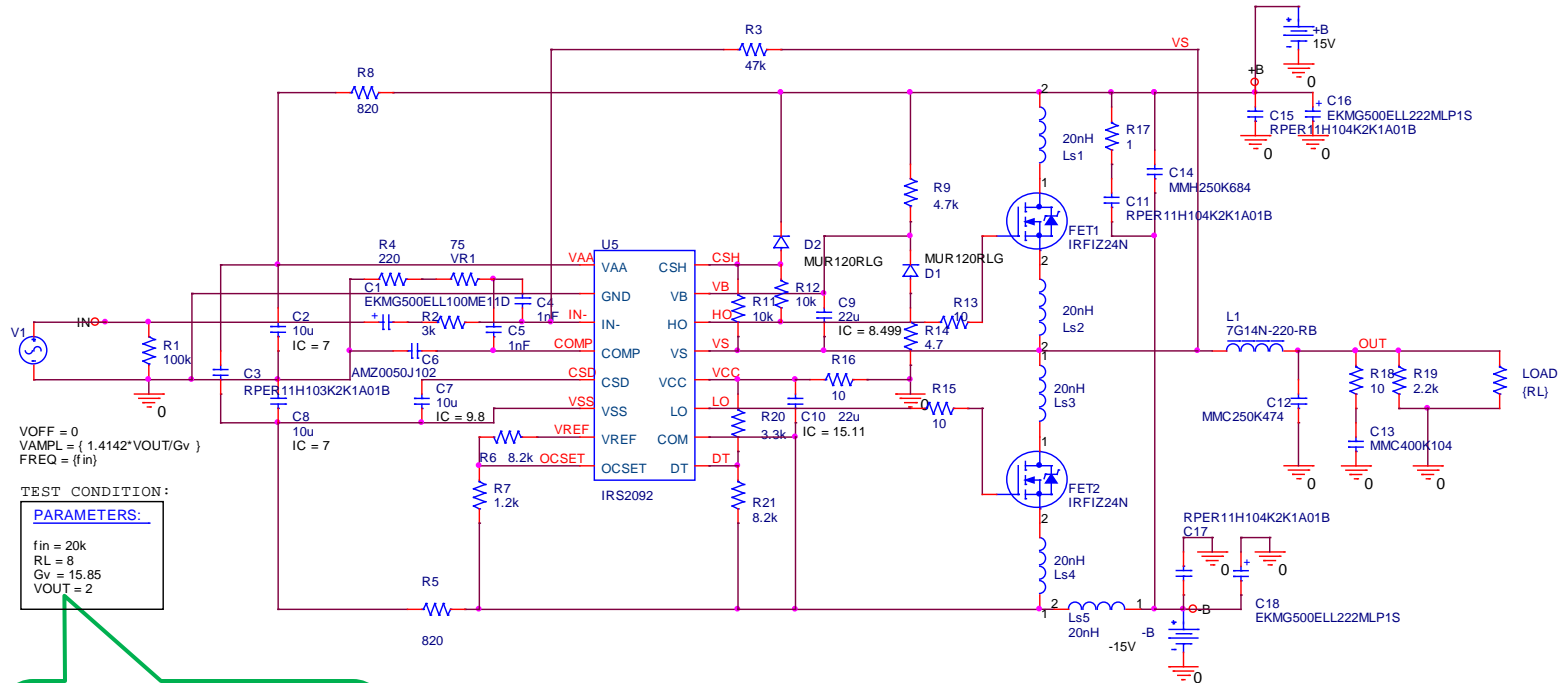
# Specifications : Frequency Response Evaluation Circuit



Condition :  
20 ~ 20000 Hz, 4Ω  
Load, 2V Output

## Analysis

Time Domain (Transient)

Run to time: 2ms

Start saving data after: 0ms

Maximum step size: 100n

Skip the initial transient bias point calculation (SKIPBP)

## Parametric Sweep

Global parameter

Parameter name: RL

Value list: 4, 8

## .Options

RELTOL: 0.01

VNTOL: 1.0u

ABSTOL: 1.0n

CHGTOL: 0.01p

GMIN: 1.0E-12

ITL1: 500


ITL2: 200

ITL4: 10




 
# Specifications : Frequency Response Simulation Result



## Note : $P_O$ [W] vs. $V_{IN}$ [ $V_{PEAK}$ ]

---


$$V_{in} [V_{peak}] = \frac{1.4142 \times \sqrt{P_o \times R_{load}}}{G_v}$$

- ▶  $P_o$  [W] = power output
- ▶  $R_{load}$  [ $\Omega$ ] = Load resistance
- ▶  $G_v$  = Amplifier voltage gain






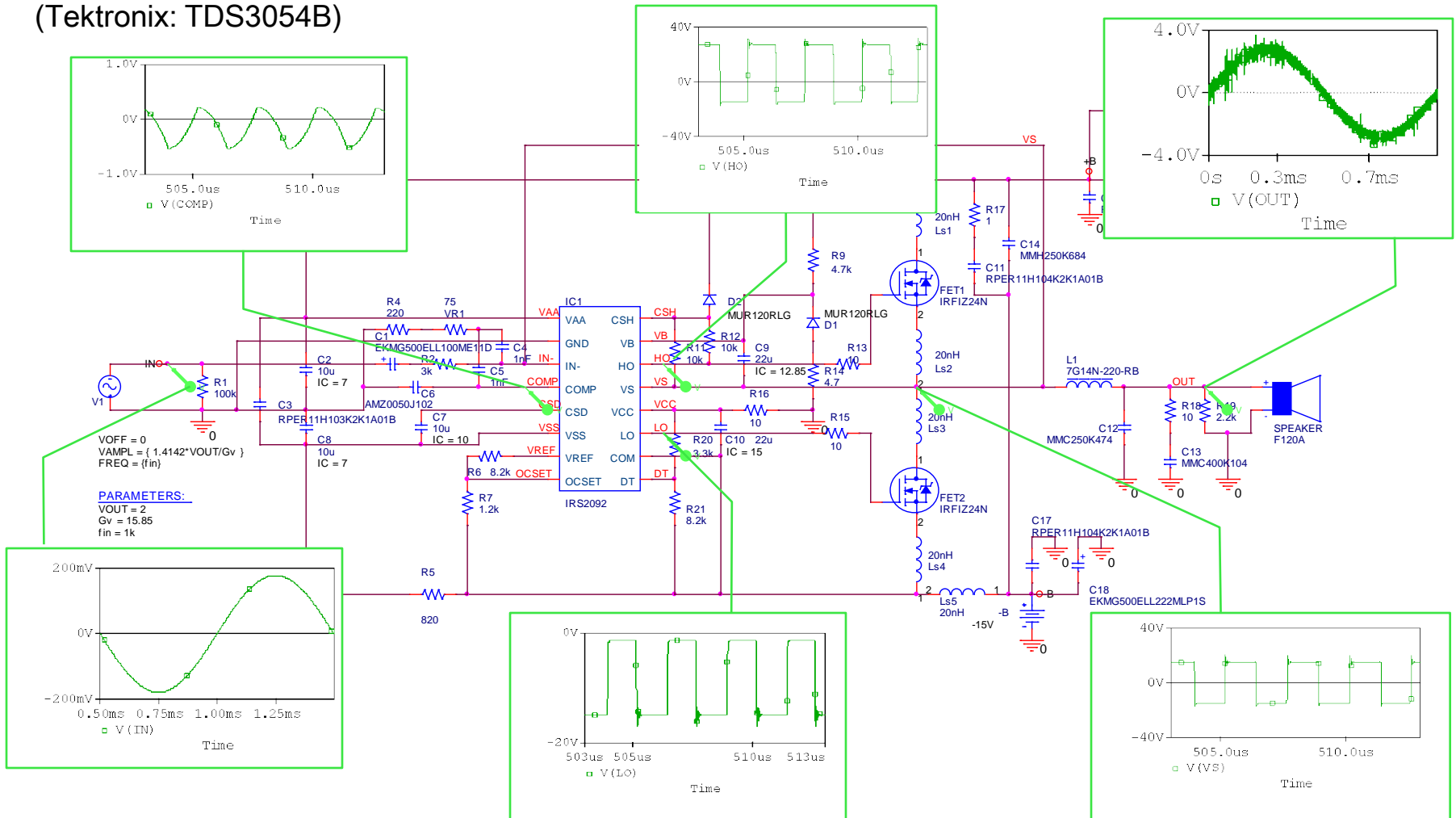
## 2. Waveforms Evaluation





Class D amplifier circuit are simulated and compared with measured waveforms from oscilloscope (Tektronix: TDS3054B)



   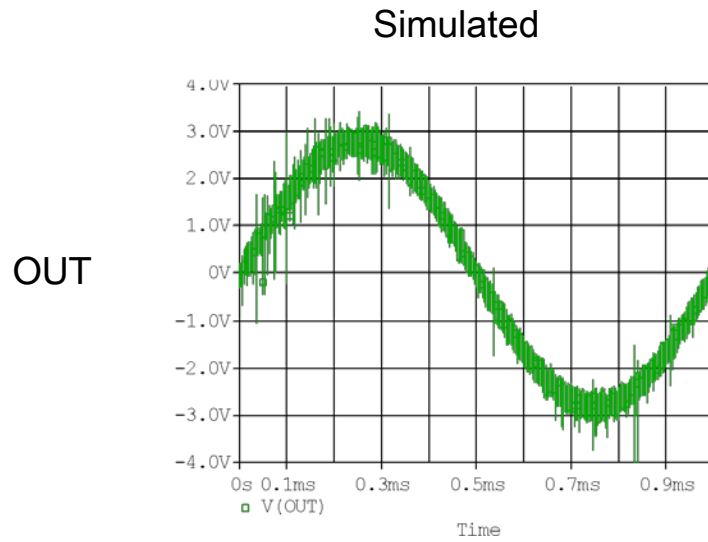
### 3. Simulated vs. Measured Waveform (1/3)


    
### 3. Simulated vs. Measured Waveform (2/3)



 
### 3. Simulated vs. Measured Waveform (3/3)



# 4. Voltage gain of the amplifier – $G_V$

$$G_V = \frac{R_{FB}}{R_{IN}}$$

 

VOFF = 0  
 VAMPL = 0.14142  
 FREQ = {Freq}

**PARAMETERS:**

Freq = 1k  
 RIN = 3k


- Analysis**  
 Time Domain (Transient)  
 Run to time: 1ms  
 Start saving data after: 100n  
 Maximum step size: 100n  
 Skip the initial transient bias point calculation (SKIPBP)
- Sweep variable  
 Global parameter: RIN  
 Value list: 2.4k, 3k

- .Options**  
 RELTOL: 0.01  
 VNTOL: 1.0u  
 ABSTOL: 1.0n  
 CHGTOL: 0.01p  
 GMIN: 1.0E-12  
 ITL1: 500  
 ITL2: 200  
 ITL4: 10



## 4. Voltage gain of the amplifier – $G_V$

---

 



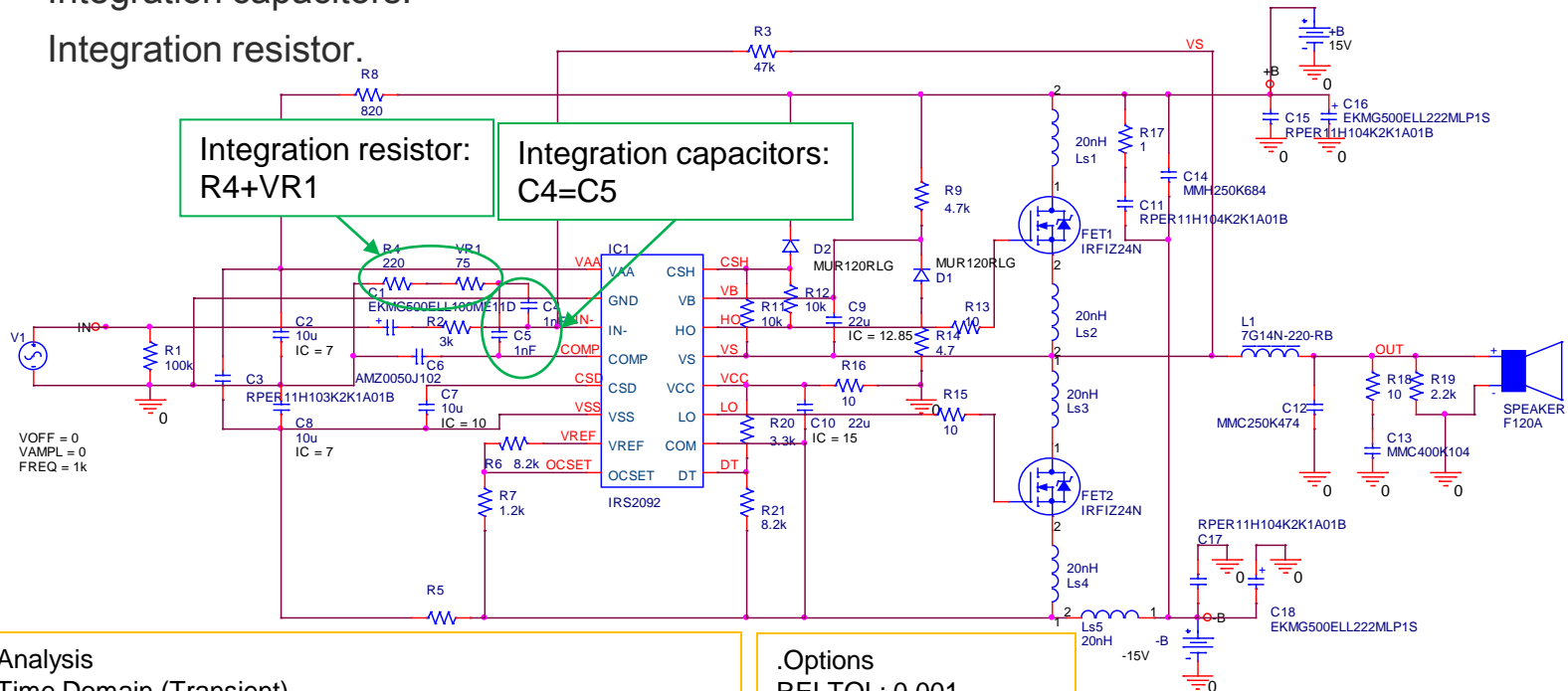
# 5. Self-Oscillating Frequency

Self oscillating frequency is design by setting the following items

- Integration capacitors.
- Integration resistor.




**Analysis**  
 Time Domain (Transient)  
 Run to time: 1ms  
 Start saving data after: 0.5m  
 Maximum step size: 40n  
 Skip the initial transient bias point calculation (SKIPBP)

**.Options**  
 RELTOL: 0.001  
 VNTOL: 1.0u  
 ABSTOL: 1.0n  
 CHGTOL: 0.01p  
 GMIN: 1.0E-12  
 ITL1: 500  
 ITL2: 200  
 ITL4: 10




# 5. Self-Oscillating Frequency

Simulated

 

Measured

 


# 6. Dead-time


Dead-time Mode	R20	R21
DT1 (25ns)	3.3k	8.2k
DT2 (40ns)	5.6k	4.7k
DT3 (65ns)	8.2k	3.3k
DT4 (105ns)	-	< 10k

Analysis  
 Time Domain (Transient)  
 Run to time: 1ms  
 Start saving data after: 0.5ms  
 Maximum step size: 40ns  
 Skip the initial transient bias point calculation (SKIPBP)

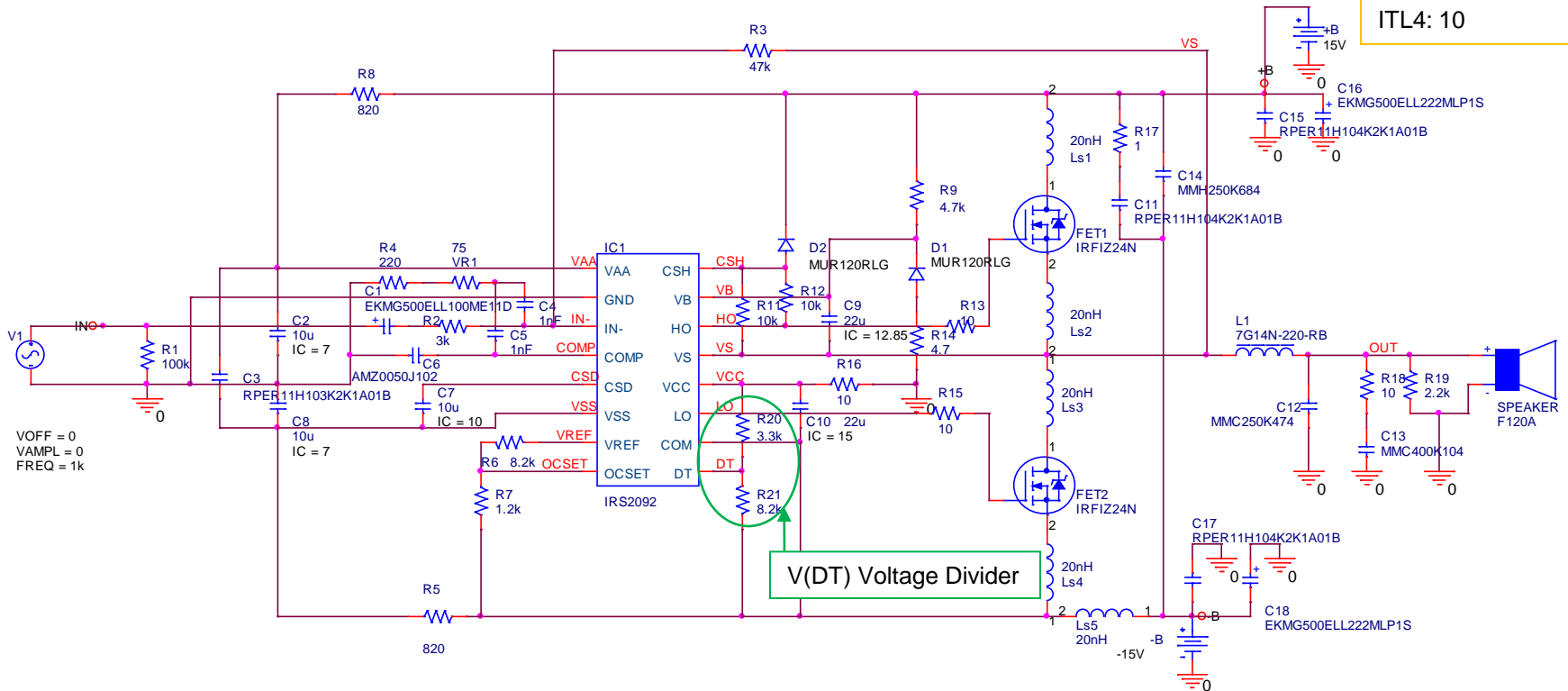
.Options  
 RELTOL: 0.001  
 VNTOL: 1.0u  
 ABSTOL: 1.0n  
 CHGTOL: 0.01p  
 GMIN: 1.0E-12  
 ITL1: 500  
 ITL2: 200  
 ITL4: 10



# Dead-time DT1(25ns)

 


# Dead-time DT3(65ns)

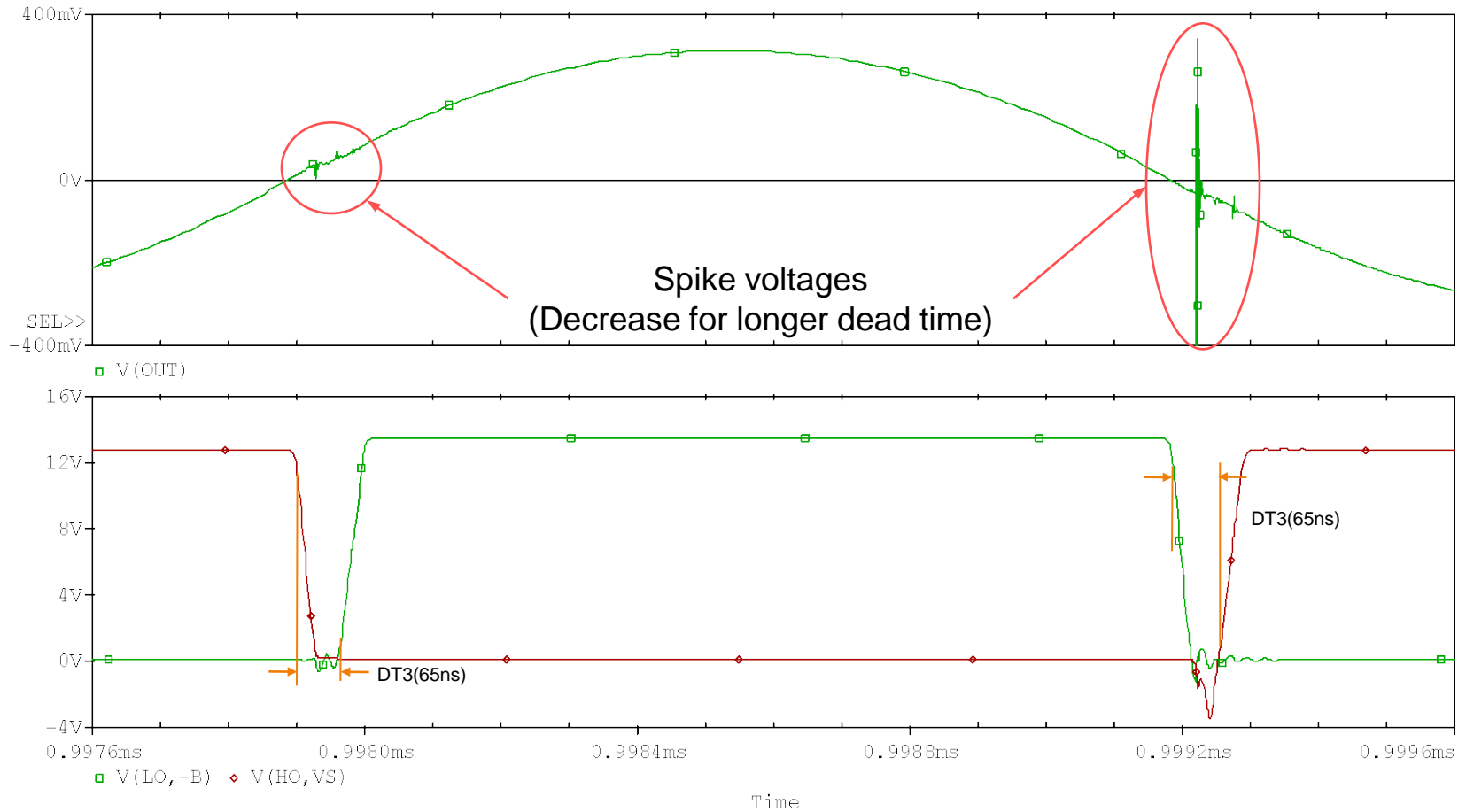
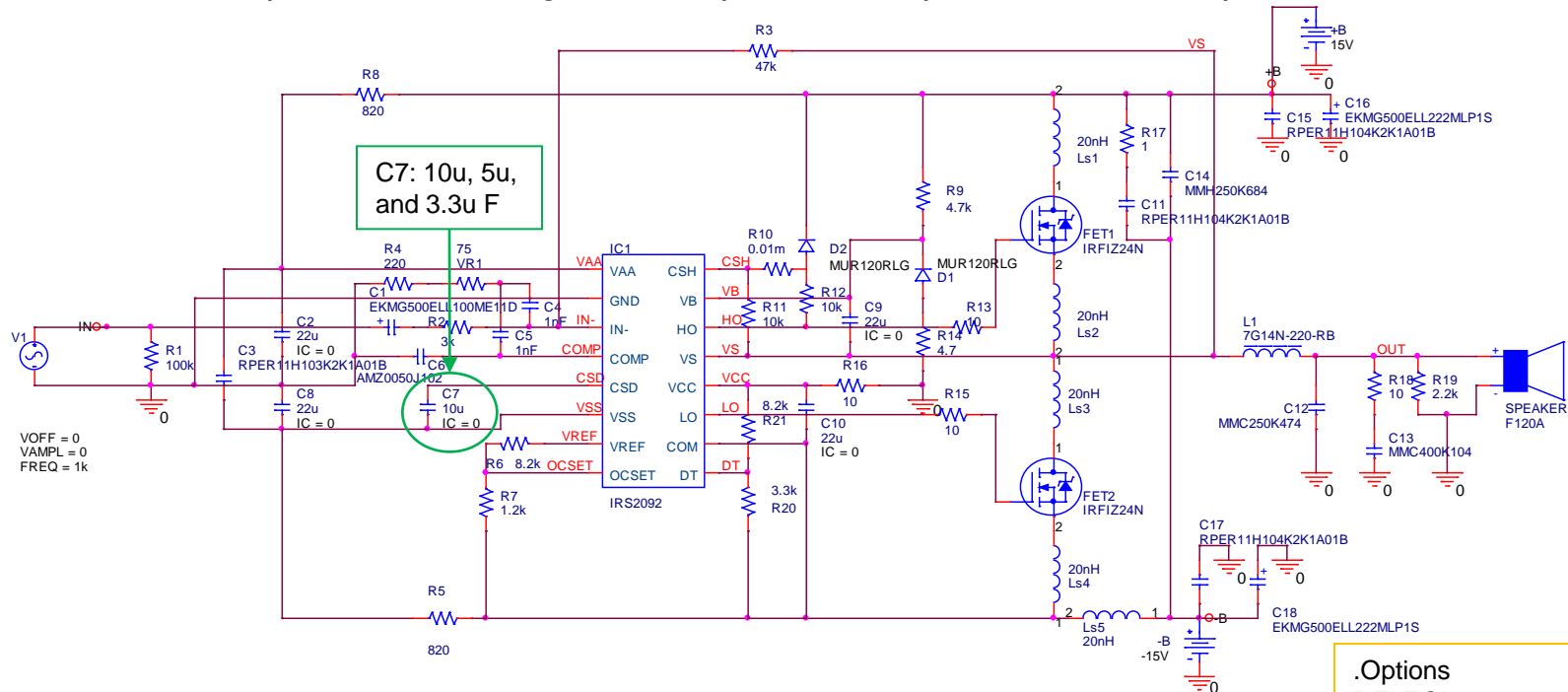
# 7. Turn-on transient

- Start-up sequencing is achieved through the charging of the CSD voltage (C7). Simulation will show how capacitors are charged to complete the sequence for each capacitance value.



## Analysis

Time Domain (Transient)

Run to time: 975ms

Start saving data after: 100n

Maximum step size: 100u

Skip the initial transient bias point calculation (SKIPBP)

## .Options

RELTOL: 0.01

VNTOL: 1.0u

ABSTOL: 1n

CHGTOL: 0.01p

GMIN: 1.0E-12


ITL1: 500

ITL2: 200


ITL4: 10



# Turn-on transient: C7 = 10uF

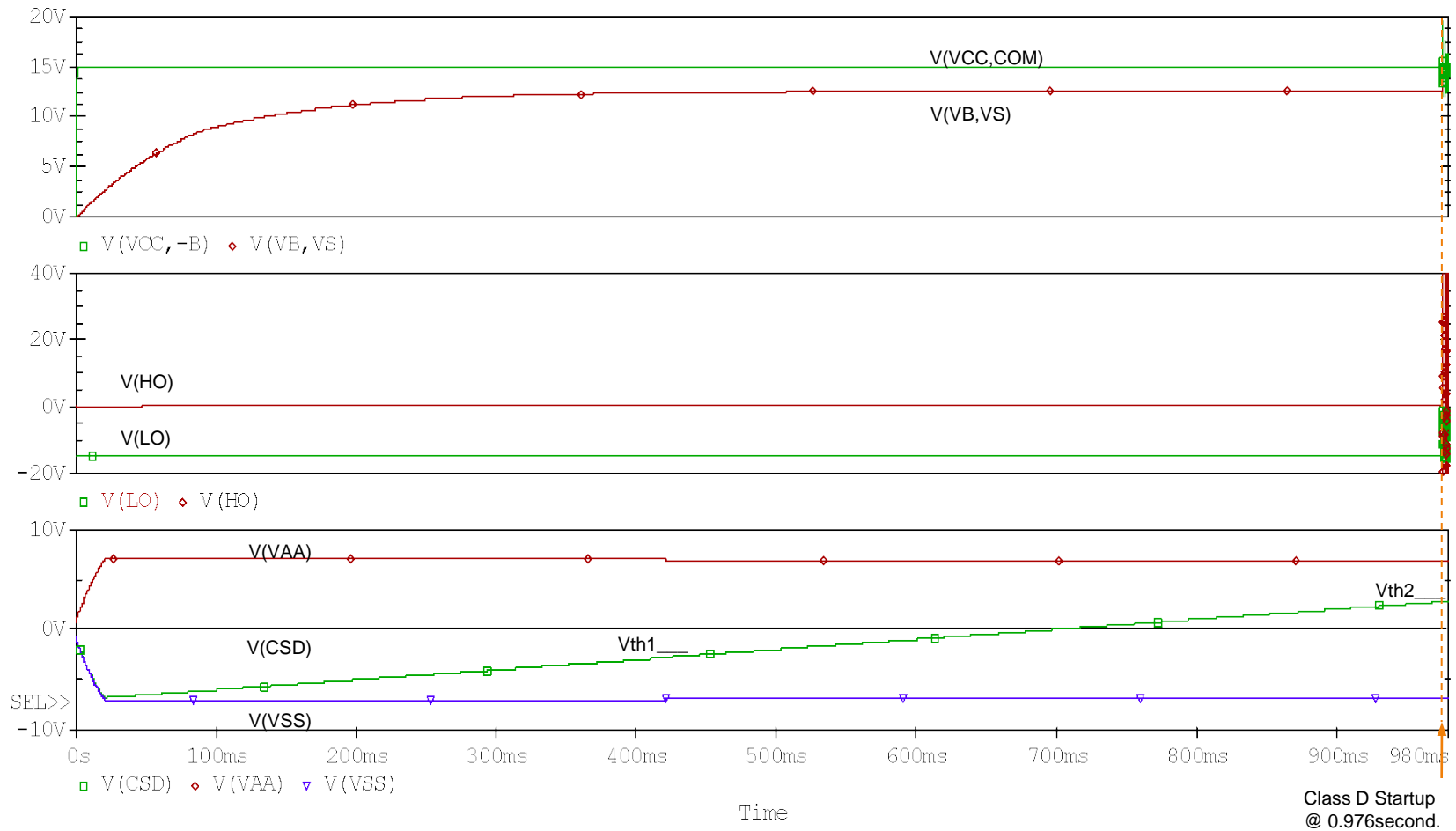


# Turn-on transient: C7 = 5uF

 




# Turn-on transient: C7 = 3.3uF

 


Class D Startup  
@ 0.320second.
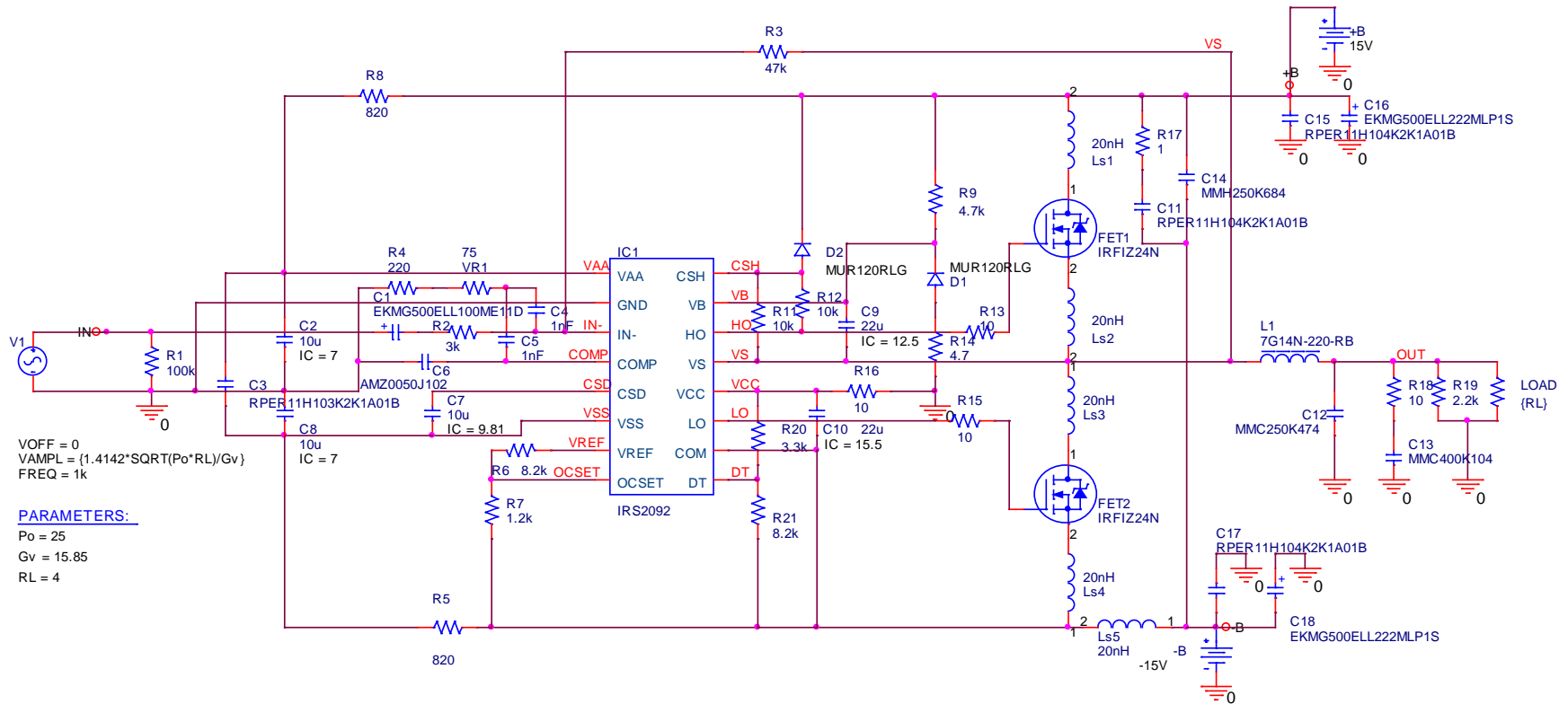
# 8. Components stress

- This simulation shows how voltage and current are applied to each components at the maximum load condition (25W,4ohm).



 
# Components Stress Simulated Result for Diodes, FETs, Inductor, and 4ΩLoad


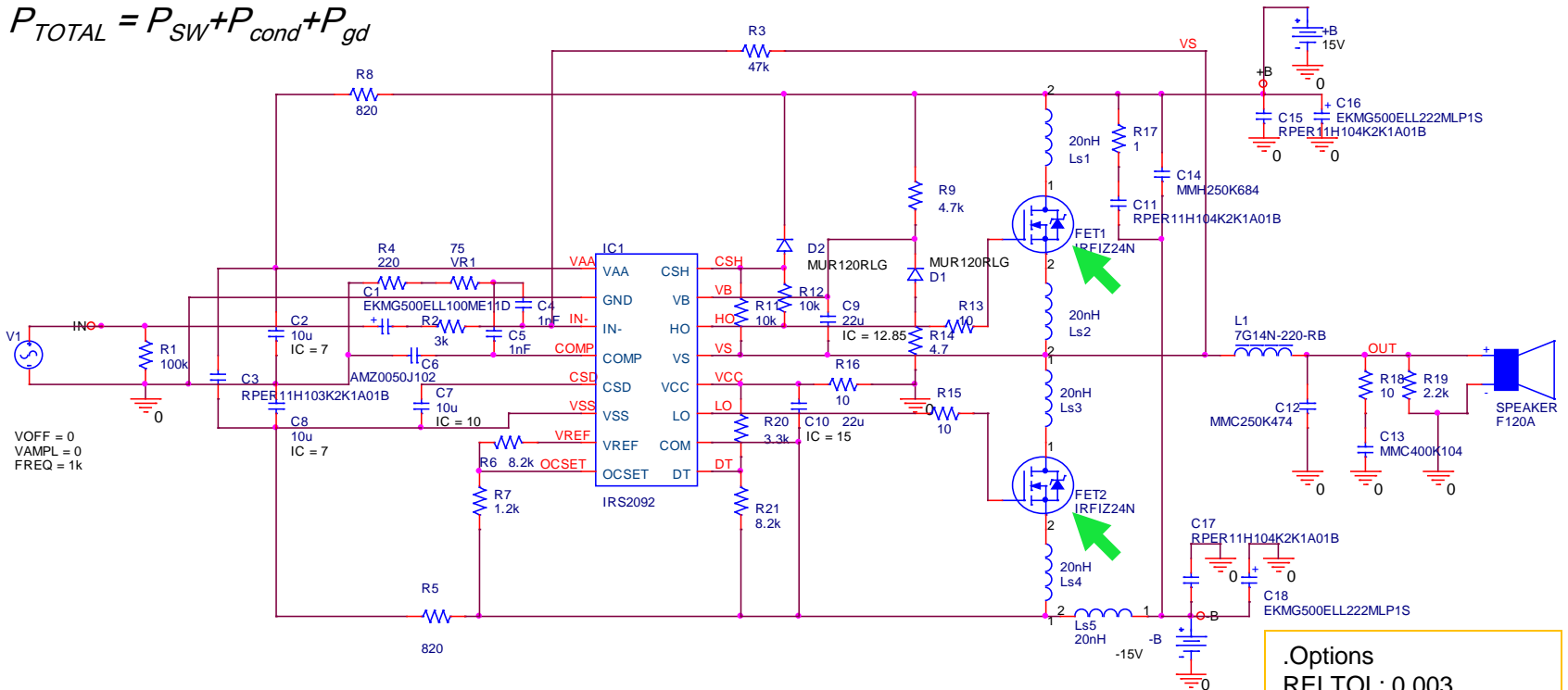
# 9. Power losses in the MOSFETs

The total power loss in MOSFET are given by:

$$P_{TOTAL} = P_{SW} + P_{cond} + P_{gd}$$



### Analysis

Time Domain (Transient)

Run to time: 500us

Start saving data after: 100n

Maximum step size: 2n

Skip the initial transient bias point calculation (SKIPBP)

### .Options

RELTOL: 0.003

VNTOL: 1.0m

ABSTOL: 100n

CHGTOL: 0.01p

GMIN: 1.0E-12

ITL1: 500



ITL2: 200

ITL4: 20
  
# Power losses FET1(Standard Model)

FET1: ID and VDS are simulated and compared with scope (Tektronix: TDS3054B) waveforms



$P_{SW}$ ,  $P_{cond}$ , and  $P_{gd}$  are calculated by PSpice.


  
# Power losses FET2(Standard Model)

FET2: ID and VDS are simulated and compared with scope (Tektronix: TDS3054B) waveforms


$P_{SW}$ ,  $P_{cond}$ , and  $P_{gd}$  are calculated by PSpice.


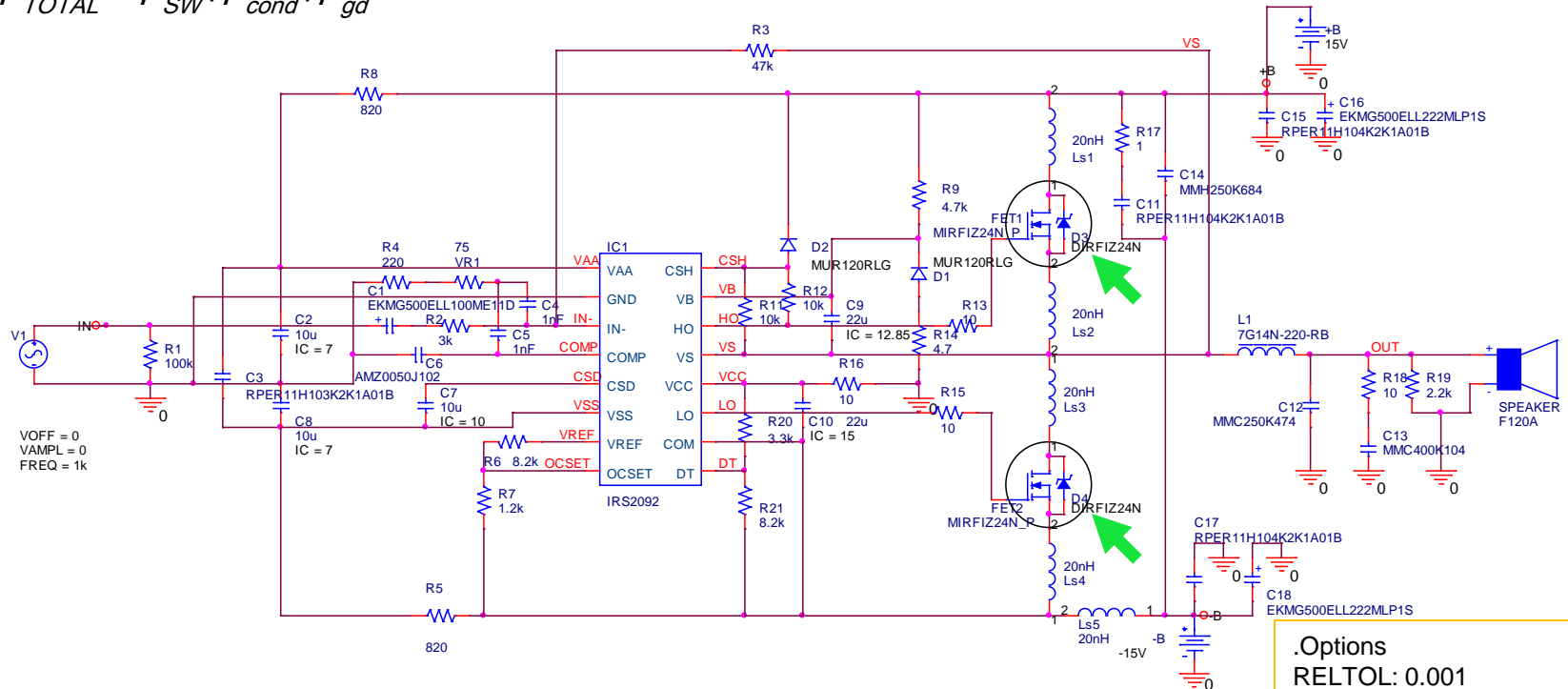
# Power losses in the MOSFETs (Professional model)

The total power loss in MOSFET are given by:

$$P_{TOTAL} = P_{SW} + P_{cond} + P_{gd}$$



## Analysis

Time Domain (Transient)

Run to time: 500us

Start saving data after: 100n

Maximum step size: 2n

Skip the initial transient bias point calculation (SKIPBP)

## .Options

RELTOL: 0.001

VNTOL: 1.0m

ABSTOL: 100n

CHGTOL: 0.01p

GMIN: 1.0E-12

ITL1: 500



ITL2: 200

ITL4: 10
 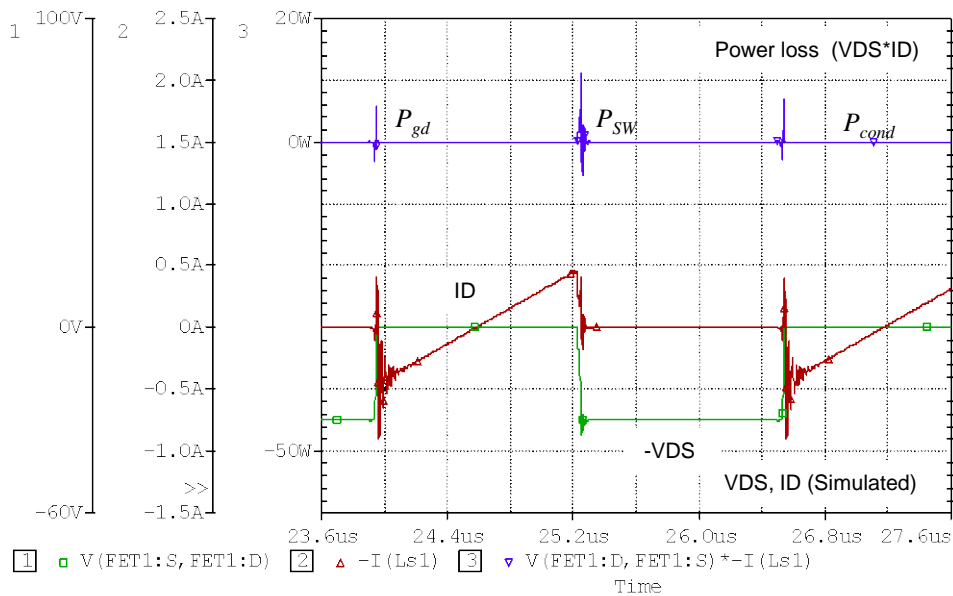
# Power losses FET1(Professional Model)

FET1: ID and VDS are simulated and compared with scope (Tektronix: TDS3054B) waveforms

$P_{SW}$ ,  $P_{cond}$ , and  $P_{gd}$  are calculated by PSpice.






 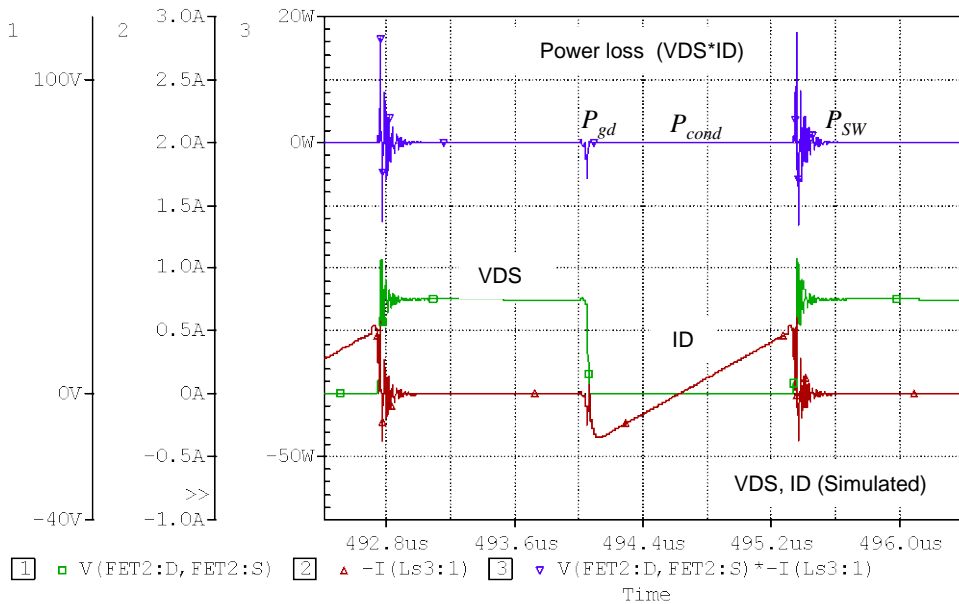
# Power losses FET2(Professional Model)



FET2: ID and VDS are simulated and compared with scope (Tektronix: TDS3054B) waveforms

$P_{SW}$ ,  $P_{cond}$ , and  $P_{gd}$  are calculated by PSpice.


  
# FET: IRFIZ24N Qg Standard vs. Professional Model



- Gate charge characteristics in Professional model has more accurate results than standard model.



$V_{DD}=44V, I_D=10A$ $, V_{GS}=10V$	Measurement	Simulation	Error (%)
Standard Model: Qg(nc)	13.400	12.543	-6.396
Professional Model: Qg(nc)	13.400	13.409	0.067
  
# FET: IRFIZ24N $P_{gd}$ Standard vs. Professional Model


- ▶ Simulated  $P_{gd}$ , Standard model compared to Professional model, shows some different result caused by different Qg characteristics of the models.



※ Professional model requires more simulation time and might cause some convergence error.
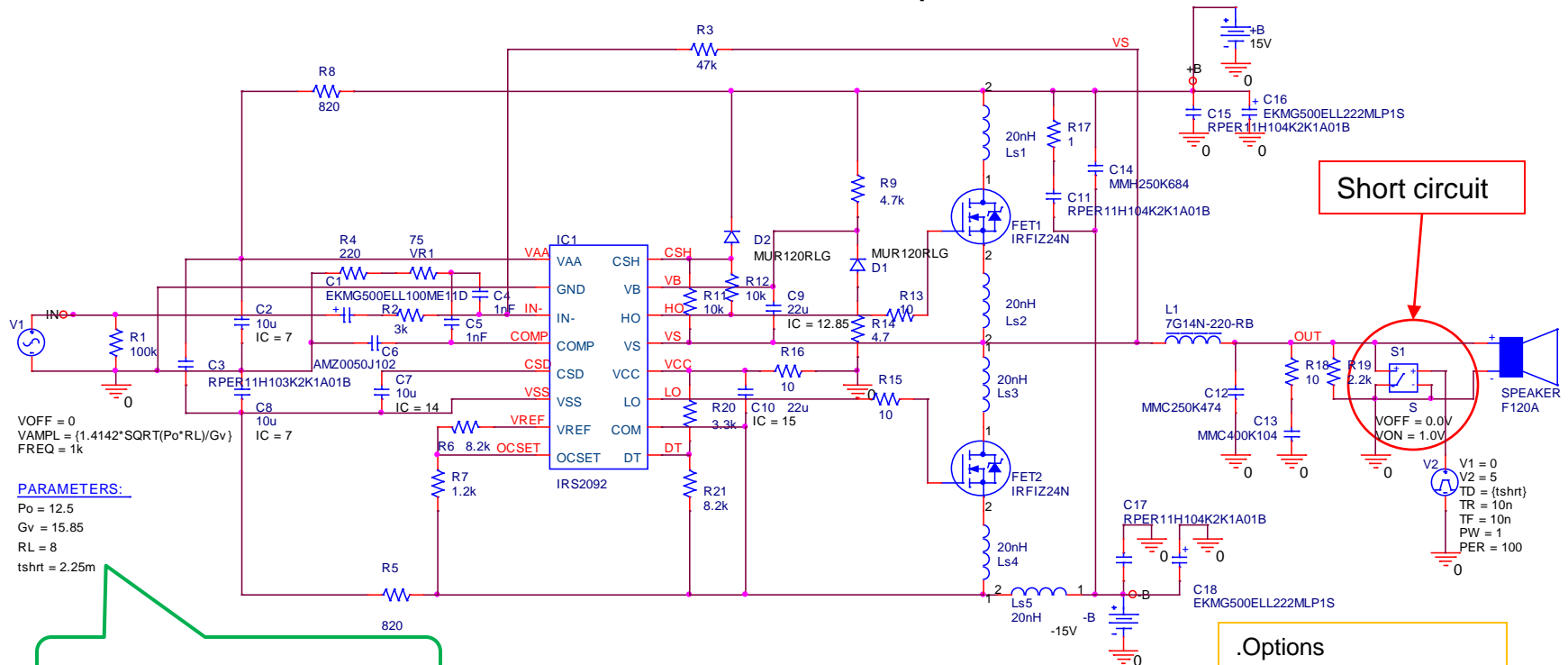
# 10. Short circuit vs. switching output shutdown

- ▶ This simulation will show how the IRS2092 responds to a short circuit condition.



VOFF = 0  
 VAMPL =  $(1.4142 \cdot \sqrt{Po \cdot RL}) / Gv$   
 FREQ = 1k


**PARAMETERS:**  
 Po = 12.5  
 Gv = 15.85  
 RL = 8  
 tshrt = 2.25m

Short circuit at 2.25ms.


**Analysis**  
 Time Domain (Transient)  
 Run to time: 4ms  
 Start saving data after: 100n  
 Maximum step size: 100n  
 Skip the initial transient bias point calculation (SKIPBP)

**.Options**  
 RELTOL: 0.01  
 VNTOL: 1.0u  
 ABSTOL: 1n  
 CHGTOL: 0.01p  
 GMIN: 1.0E-12  
 ITL1: 500  
 ITL2: 200  
 ITL4: 10
 
# Short Circuit vs. Switching Output Shutdown (Positive Side)



 
# Short Circuit vs. Switching Output Shutdown (Negative Side)


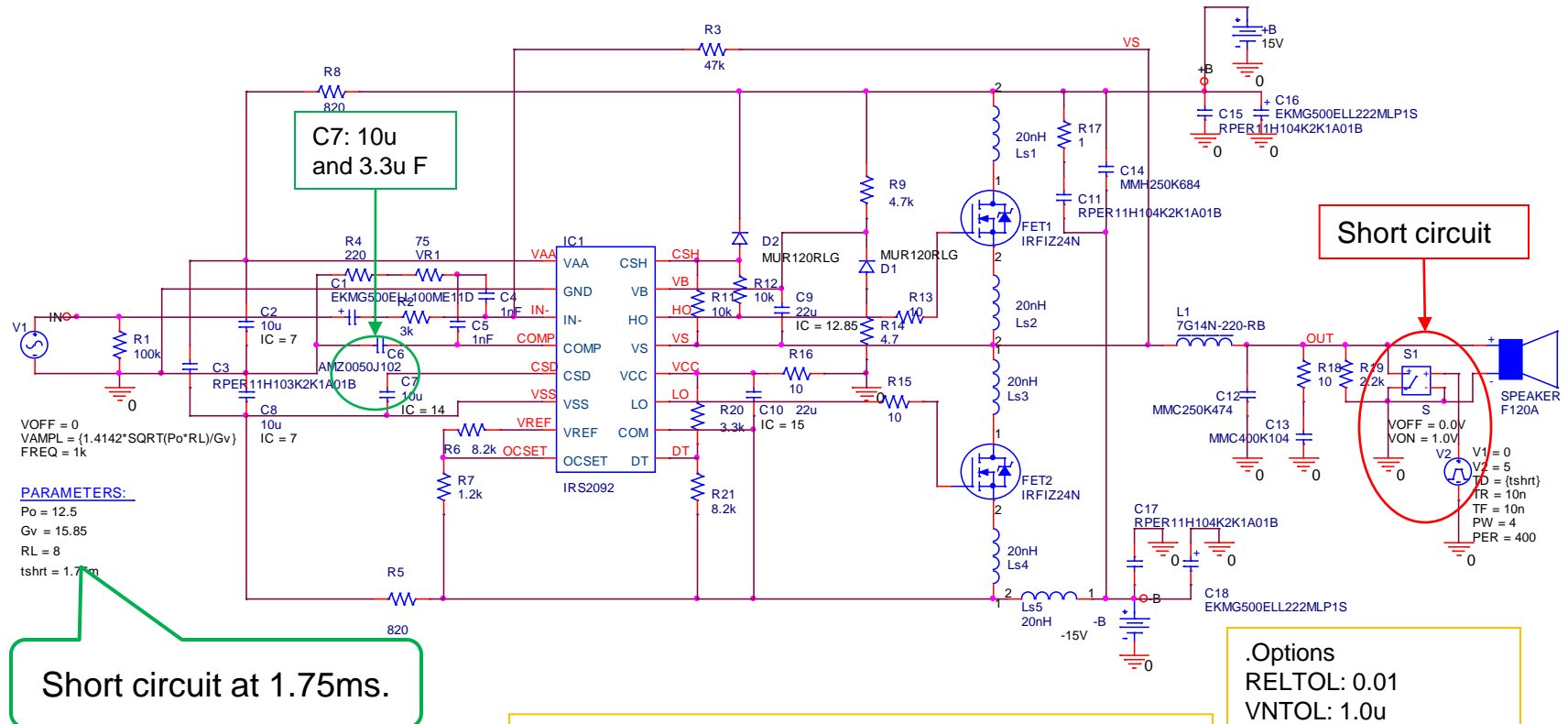
# 11. Short Circuit Response


- ▶ This simulation will show how the IRS2092 responds to a short circuit condition.



Analysis  
 Time Domain (Transient)  
 Run to time: 1.25s  
 Start saving data after: 100n  
 Maximum step size: 100u  
 Skip the initial transient bias point calculation (SKIPBP)


.Options  
 RELTOL: 0.01  
 VNTOL: 1.0u  
 ABSTOL: 1n  
 CHGTOL: 0.01p  
 GMIN: 1.0E-12  
 ITL1: 500  
 ITL2: 200  
 ITL4: 10

# Short Circuit Response: C7 = 10uF

 




# Short Circuit Response: C7 = 3.3uF

 
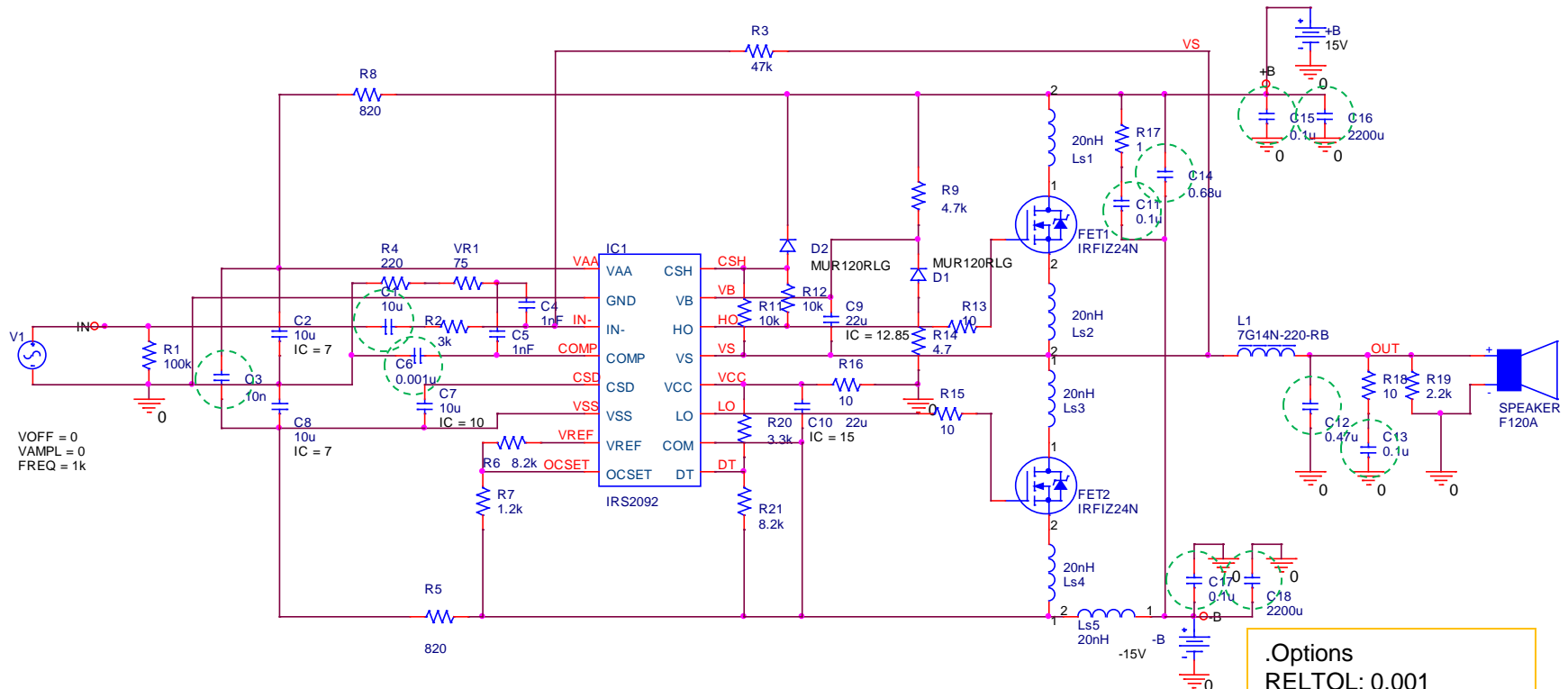
# 12. Capacitor models

- ▶ Capacitor models are needed for the simulation to include spike voltage.




VOFF = 0  
VAMPL = 0  
FREQ = 1k

Analysis  
Time Domain (Transient)  
Run to time: 1ms  
Start saving data after: 0.5m  
Maximum step size: 40n  
 Skip the initial transient bias point calculation (SKIPBP)


.Options  
RELTOL: 0.001  
VNTOL: 1.0u  
ABSTOL: 1.0n  
CHGTOL: 0.01p  
GMIN: 1.0E-12  
ITL1: 500  
ITL2: 200  
ITL4: 10
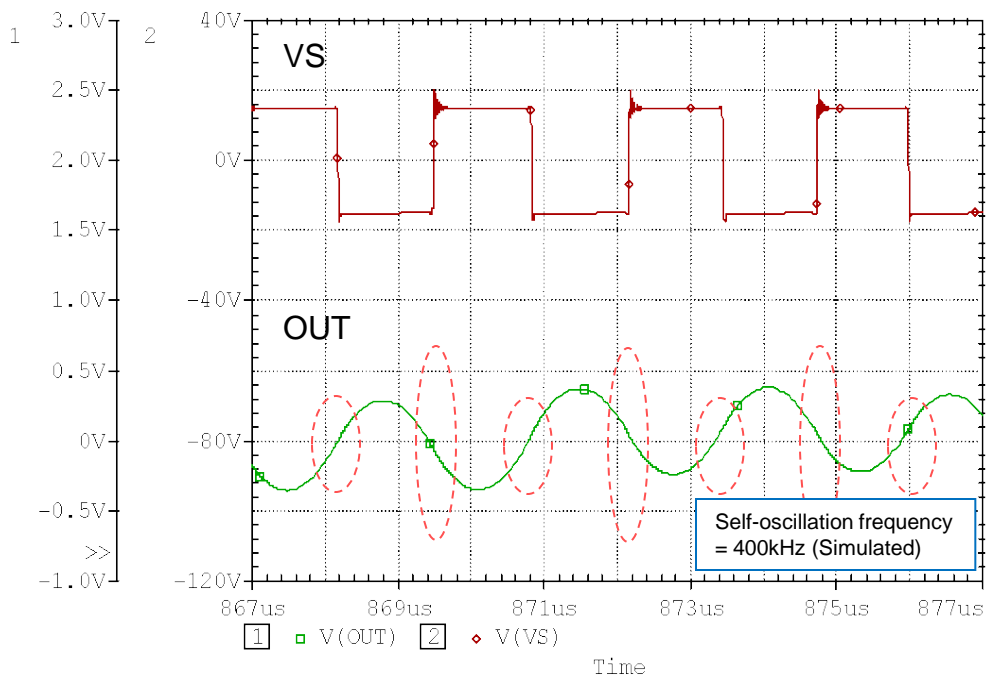
# Simulation Result (without Capacitor Model)

Simulated (without output capacitor models)




Measured

 


# Simulation Result (with Capacitor Model)

Simulated (with output capacitor models)

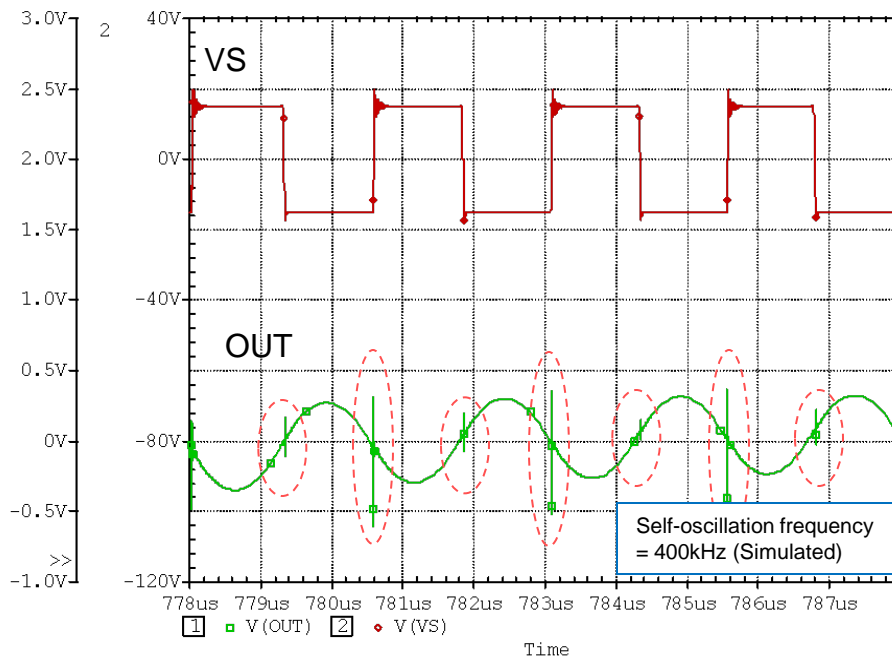

Measured

 


## 13. Simulated Performance of the circuit with different FETs

---

IRFIZ24N Key Parameters		
$V_{DS}$	55	V
$I_D$	14	A
$R_{DS(ON)}$ typ. @ 10V	70	m $\Omega$
$Q_g$ typ.	13.4	nC
$t_{ON}$ typ.	38.9	ns
$t_{OFF}$ typ.	46	ns
$Q_{rr}$ typ.	120	nC





IRFI4024H-117P Key Parameters		
$V_{DS}$	55	V
$I_D$	11	A
$R_{DS(ON)}$ typ. @ 10V	48	m $\Omega$
$Q_g$ typ.	8.9	nC
$t_{ON}$ typ.	7.9	ns
$t_{OFF}$ typ.	16.4	ns
$Q_{rr}$ typ.	11	nC
 
# Simulated Performance of the circuit with different FETs



	IRFIZ24N	IRFI4024H-117P
Efficiency (@ 25W, 4Ω)	93.505%	94.578%
Distortion (@ 1kHz, 4Ω, 10W)	0.0144 %THD	0.0201 %THD
    
# Simulated Performance of the circuit with different FETs



# Simulations Index

---

<b>Simulation</b>	<b>Folder Name</b>
1. Efficiency Evaluation.....	Efficiency
2. THD Evaluation.....	THD
3. Frequency Response Evaluation.....	FrqRsp
4. Waveforms Evaluation.....	Waveforms
5. Voltage gain of the amplifier – $G_v$ .....	Gv
6. Self-Oscillating Frequency.....	OSC
7. Dead-time Evaluation.....	DT
8. Turn-on transient.....	StartUp
9. Component stresses.....	Stress
10. Power losses in the MOSFETs (Standard model) .....	FET(STD)
11. Power loss in the MOSFETs (Professional Model) .....	FET(PRO)
12. Short Circuit vs. Switching Output Shutdown.....	Short
13. Short Circuit Response.....	ShrtRsp

