
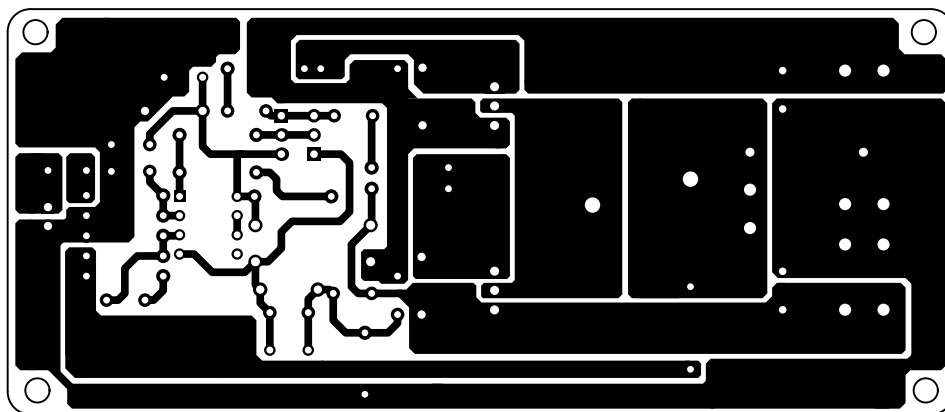


Class D 200 Watt Amplifier

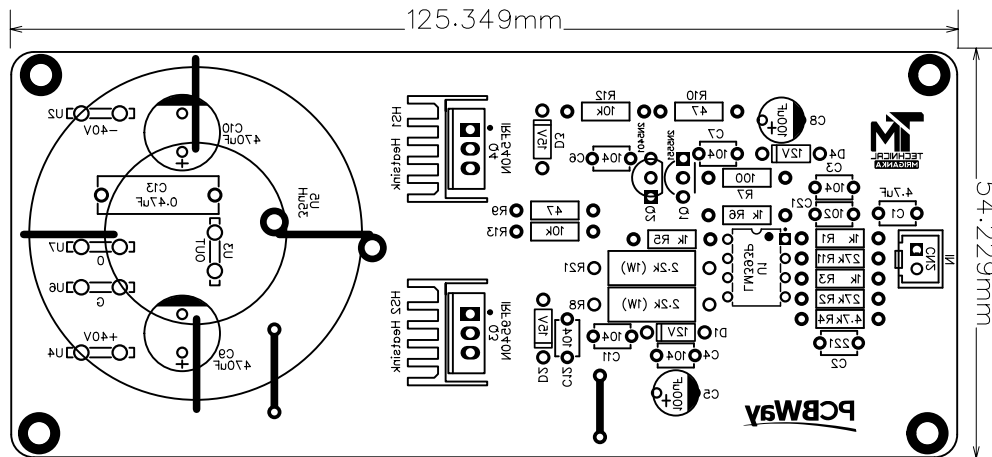

www.technicalmriganka.com


*Note - This is printout page. Don't mirror this PCB Layout. Print on A4 page by Laser Printer.

*License - ©Technical Mriganka. You can't use this PCB Layout for commercial purpose. You can use this PCB Layout only for Educational and DIY projects.

Components

1. 2×10KΩ resistor 1/4W.
2. 4×1KΩ resistor 1/4W.
3. 1×4.7KΩ resistor 1/4W.
4. 2×27KΩ resistor 1/4W.
5. 2×47Ω resistor 1/4W.
6. 1×100Ω resistor 1/4W.
7. 2×2.2KΩ resistor 1W.
8. 2×Zener diode 1N4742 (12V 1W).
9. 1×Zener diode 1N4744 (15V 1W).
10. 1×Transistor 2N5401.
11. 1×Transistor 2N5551.
12. 6×0.1uF (104) capacitor 100V.
13. 1×0.001uF (102) capacitor 100V.
14. 1×220pF (221) capacitor 100V.
15. 1×2 pin connector base 2.54 mm.
16. 1×IC LM393.
17. 1×4.7uF capacitor 25V/ 50V.
18. 2×100uF capacitor 25V/ 50V.
19. 2×470uF capacitor 50V/ 63V.
20. 5×6.3 mm vertical PCB terminal.
21. 1×Mosfet IRF540N.
22. 1×Mosfet IRF9540N.
23. 1×0.47uF (474) capacitor 250V.
24. 1×Coil 35uH.

©www.technicalmriganka.com

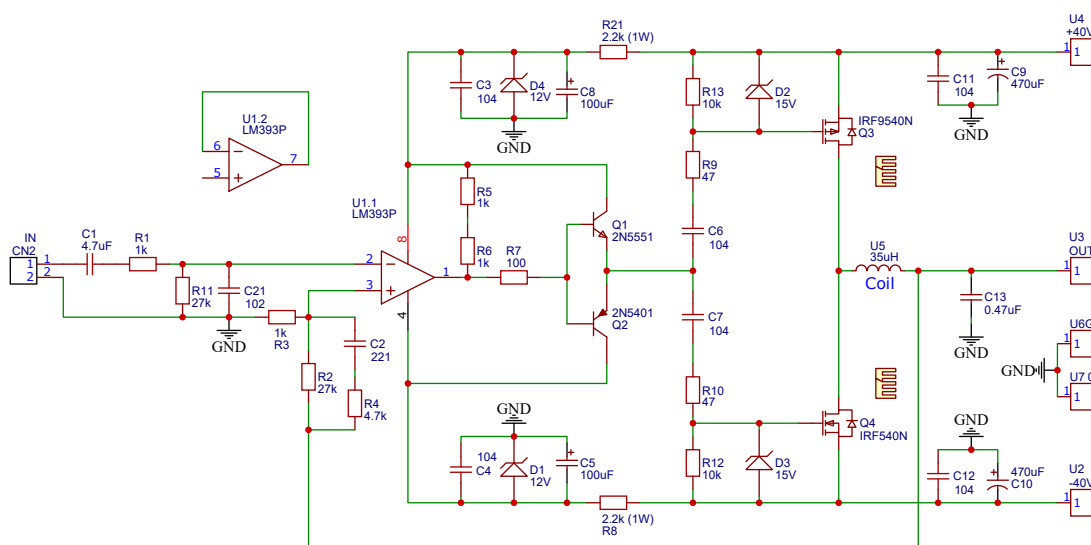

TITLE:		REV:
Company:		Sheet:
Date:	Drawn By:	