

EFY

PROJECTS

&

IDEAS

VOLUME

00

More than 90 fully tested
and ready-to-use
electronics circuits

2000

Electronics For You

issues

JANUARY 2000

CONSTRUCTION PROJECTS

- 1) MICROPROCESSOR-CONTROLLED TRANSISTOR LEAD IDENTIFIER ----- 1
- 2) CONVERSION OF AUDIO CD PLAYER TO VIDEO CD PLAYER — I----- 9

CIRCUIT IDEAS

- 1) MULTIPURPOSE CIRCUIT FOR TELEPHONES -----13
- 2) SIMPLE CODE LOCK-----13
- 3) AUTOMATIC BATHROOM LIGHT-----14
- 4) SMART FLUID LEVEL INDICATOR -----15
- 5) AUTOMATIC SCHOOL BELL SYSTEM -----16
- 6) DESIGNING AN RF PROBE -----18

FEBRUARY 2000

CONSTRUCTION PROJECTS

- 1) PC BASED SPEED MONITORING SYSTEM -----19
- 2) STEREO CASSETTE PLAYER -----24

CIRCUIT IDEAS

- 1) BASS AND TREBLE FOR STEREO SYSTEM -----29
- 2) PROTECTION FOR YOUR ELECTRICAL APPLIANCES-----29
- 3) DIGITAL WATER LEVEL METER -----30
- 4) UNIVERSAL HIGH-RESISTANCE VOLTMETER-----31
- 5) TRIAC/TRANSISTOR CHECKER -----32
- 6) A NOVEL METHOD OF FREQUENCY VARIATION USING 555 -----33

MARCH 2000

CONSTRUCTION PROJECTS

- 1) RESONANCE TYPE L-C METER-----34
- 2) ELECTROLYSIS-PROOF COMPLETE WATER-LEVEL SOLUTION -----38

CIRCUIT IDEAS

- 1) PENDULUM DISPLAY-----42
- 2) AUDIO LEVEL INDICATOR -----42
- 3) CLEVER RAIN-ALARM-----44
- 4) LASER CONTROLLED ON/OFF SWITCH -----45
- 5) TELEPHONE CONVERSATION RECORDER -----45
- 6) SIMPLE AND ECONOMIC SINGLE- PHASING PREVENTOR -----46

APRIL 2000

CONSTRUCTION PROJECTS

- 1) SMART CLAP SWITCH -----48
- 2) ELECTRONIC VOTING MACHINE -----51

CIRCUIT IDEAS

- 1) WATER-TANK LEVEL METER -----57
- 2) PHONE BROADCASTER-----58
- 3) TELEPHONE CALL METER USING CALCULATOR AND COB -----59
- 4) SIMPLE ELECTRONIC CODE LOCK -----60
- 5) LATCH-UP ALARM USING OPTO-COUPLER -----61
- 6) MINI VOICE-PROCESSOR -----61

MAY 2000

CONSTRUCTION PROJECTS

- 1) DIGITAL NUMBER SHOOTING GAME -----63
- 2) PC INTERFACED AUDIO PLAYBACK DEVICE: M-PLAYER -----66

CIRCUIT IDEAS

- 1) STEPPER MOTOR DRIVER-----73
- 2) ELECTRONIC DIGITAL TACHOMETER -----74
- 3) LIGHT-OPERATED LIGHT SWITCH -----75
- 4) PRECISION DIGITAL AC POWER CONTROLLER -----76
- 5) LUGGAGE SECURITY SYSTEM -----77

JUNE 2000

CONSTRUCTION PROJECTS

- 1) PORTABLE OZONE GENERATOR -----78
- 2) CONFERENCE TIMER -----84

CIRCUIT IDEAS

- 1) ADD-ON STEREO CHANNEL SELECTOR-----87
- 2) WATER TEMPERATURE CONTROLLER -----88
- 3) EMERGENCY LIGHT -----89
- 4) PARALLEL TELEPHONES WITH SECRECY -----90
- 5) TWO-DOOR DOORBELL -----91
- 6) POWERFUL PEST REPELLER -----91

JULY 2000

CONSTRUCTION PROJECTS

- 1) BUILD YOUR OWN C-BAND SATELLITE TV-RECEIVER -----92
- 2) EPROM-BASED PROGRAMMABLE NUMBER LOCK -----99

CIRCUIT IDEAS

- 1) POWER-SUPPLY FAILURE ALARM----- 102
- 2) STOPWATCH USING COB AND CALCULATOR----- 102
- 3) DIAL A VOLTAGE ----- 103
- 4) ELECTRONIC DANCING PEACOCK ----- 104
- 5) INVERTER OVERLOAD PROTECTOR WITH DELAYED AUTO RESET ----- 105
- 6) TELEPHONE LINE BASED AUDIO MUTING AND LIGHT-ON CIRCUIT ----- 106

AUGUST 2000

CONSTRUCTION PROJECTS

- 1) DISPLAY SCHEMES FOR INDIAN LANGUAGES—PART I (Hardware and Software) ----- 108
- 2) 8085 μ P-KIT BASED SIMPLE IC TESTER ----- 115

CIRCUIT IDEAS

- 1) LOW COST PCO BILLING METER ----- 119
- 2) AUTOMATIC MUTING CIRCUIT FOR AUDIO SYSTEMS ----- 120
- 3) 2-LINE INTERCOM-CUM-TELEPHONE LINE CHANGEOVER CIRCUIT ----- 120
- 4) GUARD FOR REFRIGERATORS AND AIR-CONDITIONERS ----- 121
- 5) RADIO BAND POSITION DISPLAY ----- 122

SEPTEMBER 2000

CONSTRUCTION PROJECTS

- 1) DISPLAY SCHEMES FOR INDIAN LANGUAGES—PART II (Hardware and Software)----- 123
- 2) DIGITAL CODE LOCK ----- 133

CIRCUIT IDEAS

- 1) BINARY TO DOTMATRIX DISPLAY DECODER/DRIVER ----- 137
- 2) AUTOMATIC SPEED-CONTROLLER FOR FANS AND COOLERS ----- 139
- 3) BLOWN FUSE INDICATOR ----- 140
- 4) OVER-/UNDER-VOLTAGE CUT-OFF WITH ON-TIME DELAY ----- 140
- 5) ONE BUTTON FOR STEP, RUN, AND HALT COMMANDS ----- 142

OCTOBER 2000

CONSTRUCTION PROJECTS

- 1) MOSFET-BASED 50Hz SINEWAVE UPS-CUM-EPS ----- 143
- 2) R-2R D/A CONVERTER-BASED FUNCTION GENERATOR USING PIC16C84 MICROCONTROLLER ---- 150

CIRCUIT IDEAS

- 1) SIMPLE SWITCH MODE POWER SUPPLY ----- 155
- 2) TOILET INDICATOR ----- 155
- 3) FEATHER-TOUCH SWITCHES FOR MAINS ----- 156
- 4) DIGITAL FAN REGULATOR ----- 157
- 5) TELEPHONE RINGER USING TIMER ICS ----- 159

NOVEMBER 2000

CONSTRUCTION PROJECTS

- 1) PC-TO-PC COMMUNICATION USING INFRARED/LASER BEAM ----- 160
- 2) MULTI-EFFECT CHASER LIGHTS USING 8051 MICROCONTROLLER ----- 166

CIRCUIT IDEAS

- 1) AUTOMATIC BATTERY CHARGER ----- 170
- 2) TEMPERATURE MEASUREMENT INSTRUMENT ----- 171
- 3) VOICE BELL ----- 172
- 4) MOVING CURTAIN DISPLAY ----- 173
- 5) PROXIMITY DETECTOR ----- 174

DECEMBER 2000

CONSTRUCTION PROJECTS

- 1) ELECTRONIC BELL SYSTEM ----- 175
- 2) SIMPLE TELEPHONE RECORDING/ANSWERING MACHINE ----- 179

CIRCUIT IDEAS

- 1) MULTICHANNEL CONTROL USING SOFT SWITCHES ----- 183
- 2) AN EXCLUSIVE SINEWAVE GENERATOR ----- 184
- 3) TTL THREE-STATE LOGIC PROBE ----- 185
- 4) AM DSB TRANSMITTER FOR HAMS ----- 185
- 5) GROUND CONDUCTIVITY MEASUREMENT ----- 186
- 6) STEPPER MOTOR CONTROL VIA PARALLEL PORT ----- 187

January

2000

MICROPROCESSOR-CONTROLLED TRANSISTOR LEAD IDENTIFIER

ARUP KUMAR SEN



Transistor lead identification is crucial in designing and servicing. A circuit designer or a serviceman must be fully conversant with the types of transistors used in a circuit. Erroneous lead identification may lead to malfunctions, and, in extreme cases, even destruction of the circuit being designed or serviced.

Though transistor manufacturers encapsulate their products in different package outlines for identification, it is impossible to memorise the outlines of innumerable transistors manufactured by the industry. Although a number of manuals are published, which provide pin details, they may not always be accessible. Besides, it is not always easy to find out the details of a desired transistor by going through the voluminous manuals. But, a handy gadget, called transistor lead identifier, makes the job easy. All one has to do is place the transistor in the gadget's socket to instantly get the desired information on its display, irrespective of the type and package-outline of the device under test.

A manually controlled version of the present project had been published in June '84 issue of *EFY*. The present model is totally microprocessor controlled, and hence all manually controlled steps are replaced by software commands. A special circuit, shown in Fig. 1, which acts as an interface to an 8085-based microprocessor kit, has been developed for the purpose.

Principle

Base and type identification. When a semiconductor junction is forward-biased, conventional current flows from the source into the p-layer and comes out of the junction through the n-layer. By applying proper logic voltages, the base-emitter (B-E) or base-collector (B-C) junction of a bipolar transistor may be forward-biased. As a result, if the device is of npn type,

current enters only through the base. But, in case of a pnp device, current flows through the collector as well as the emitter leads.

During testing, when leads of the 'transistor under test' are connected to terminals 1, 2, and 3 of the test socket (see Fig.1), each of the leads (collector, base, and emitter) comes in series with one of the current directions indicating LEDs (D2, D4, and D6) as shown in Fig. 1. Whenever the current flows toward a particular junction through a particular lead, the LED connected (in proper direction) to that lead glows up. So, in case of an npn-device, only the LED connected to the base lead glows. However, in case of a pnp-device, the other two LEDs are lit. Now, if

generated with Table I, a microprocessor can easily indicate the type (nnp or pnp) and the base of the device under test, with respect to the test socket terminals marked as 1, 2, and 3. The logic numbers, comprising logic 1 (+5V) and logic 0 (0V), applied to generate the base-Id, are three bit numbers—100, 010, and 001. These numbers are applied sequentially to the leads through the testing socket.

Collector identification. When the base-emitter junction of a transistor is forward-biased and its base-collector junction is reverse-biased, conventional current flows in the collector-emitter/emitter-collector path (referred to as C-E path in subsequent text), the magnitude of which depends upon the magnitude of the base current and the beta (current amplification factor in common-emitter configuration) of the transistor. Now, if the transistor is biased as above, but with the collector and emitter leads interchanged, a current of much reduced strength would still flow in the C-E path. So, by comparing these two currents, the collector lead can be easily identified. In practice, we can apply proper binary numbers (as in case of the base identification step mentioned earlier) to the 'device under test' to bias the junctions sequentially, in both of the aforesaid condi-

TABLE I

Orientation No.	Test socket terminal 3	Test socket terminal 2	Test socket terminal 1	Base-Id for npn	Base-Id for pnp	Collector-Id for pnp and npn
1	C	B	E	02	05	04
2	C	E	B	01	06	04
3	E	C	B	01	06	02
4	E	B	C	02	05	01
5	B	E	C	04	03	01
6	B	C	E	04	03	02

B=Base C=Collector E=Emitter Note: All bits of higher nibble are set to zero.

a glowing LED corresponds to binary 1, an LED that is off would correspond to binary 0. Thus, depending upon the orientation of the transistor leads in the test socket, we would get one of the six hexadecimal numbers (taking LED connected to terminal 1 as LSB), if we consider all higher bits of the byte to be zero. The hexadecimal numbers thus generated for an npn and pnp transistor for all possible orientations (six) are shown under columns 5 and 6 of Table I. Column 5 reflects the BCD weight of B (base) position while column 6 represents 7's complement of the column 5 number.

We may call this 8-bit hexadecimal number *base identification number* or, in short, *base-Id*. Comparing the base-Id,

TABLE II

Q2 (MSB)	Q1	Q0 (LSB)
0	0	1
0	1	0
1	0	0


TABLE III. SET 1

Q2	Q1	Q0
0	0	1
0	1	0
1	0	0

TABLE IV. SET 2

Q2	Q1	Q0
1	1	0
1	0	1
0	1	1

Fig. 1: Schematic circuit diagram of the transistor lead identifier

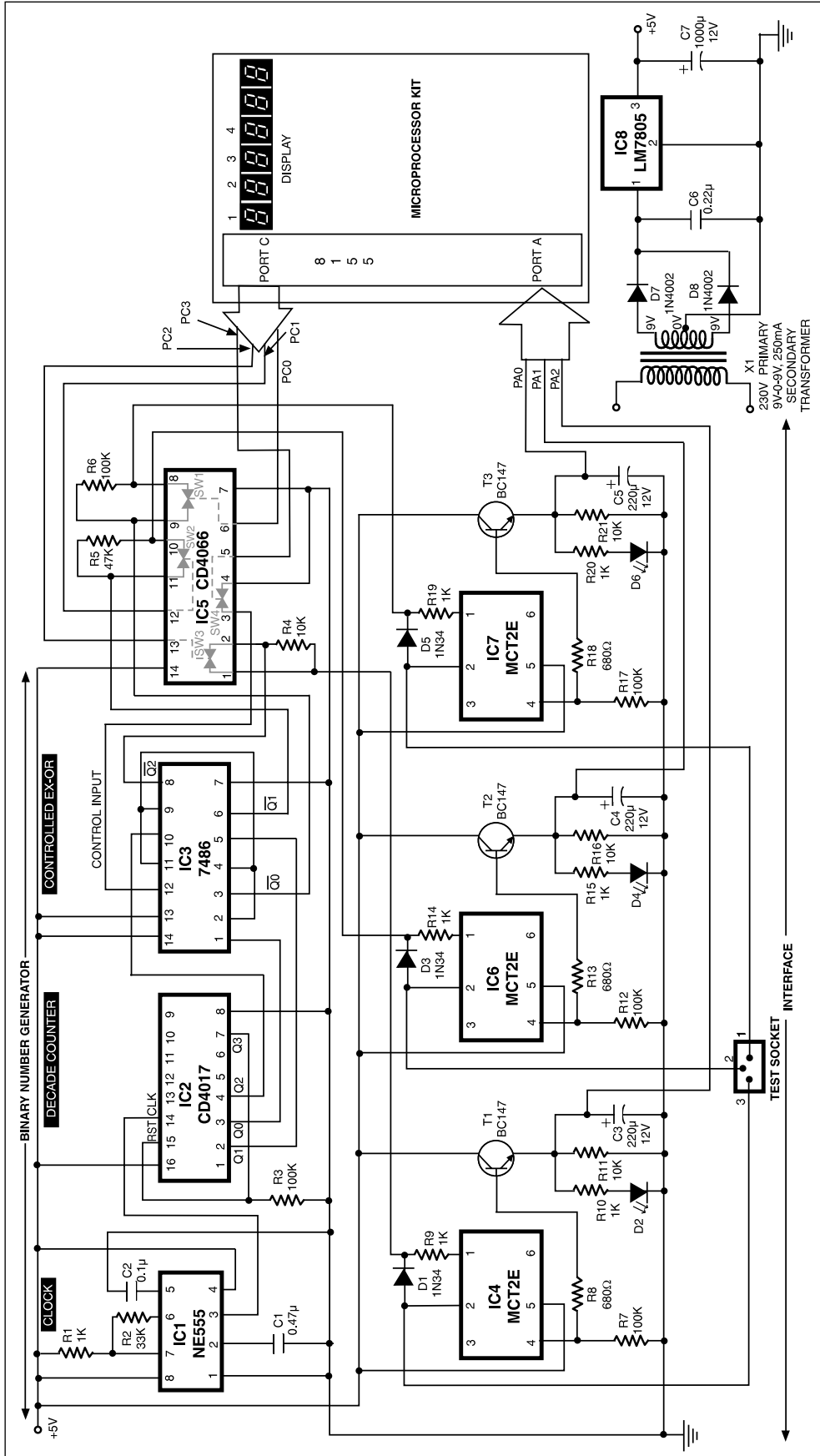

tions. As a result, the LEDs connected to the collector and emitter leads start flickering alternately with different brightness. By inserting a resistor in series with the base, the LED glowing with lower brightness can be extinguished.

In the case of an NPN device (under normal biasing condition), conventional current flows from source to the collector layer. Hence, the LED connected to the collector only would flicker brighter, if a proper resistor is inserted in series with the base. On the other hand, in case of a pnp device (under normal biasing condition), current flows from source to the emitter layer. So, only the LED connected to the emitter lead would glow brighter. As the type of device is already known by the base-Id logic, the collector lead can be easily identified. Thus, for a particular base-Id, position of the collector would be indicated by one of the two numbers (we may call it collector-Id) as shown in column 7 of Table I.

Error processing. During collector identification for a pnp- or an npn-device, if the junction voltage drop is low (viz, for germanium transistors), one of the two currents in the C-E path (explained above) cannot be reduced adequately and hence, the data may contain two logic-1s. On the other hand, if the device beta is too low (viz, for power transistors), no appreciable current flows in the C-E path, and so the data may not contain any logic-1. In both the cases, lead configuration cannot be established. The remedy is to adjust the value of the resistor in series with the base. There are three resistors (10k, 47k, and 100k) to choose from. These resistors are connected in series with the testing terminals 1, 2, and 3 respectively. The user has to rotate the transistor, orienting

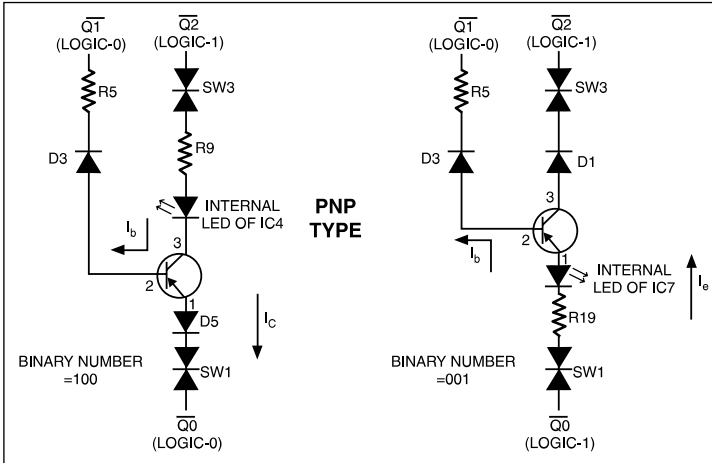


Fig. 2: Effective biasing of PNP transistors using set 1 binary numbers

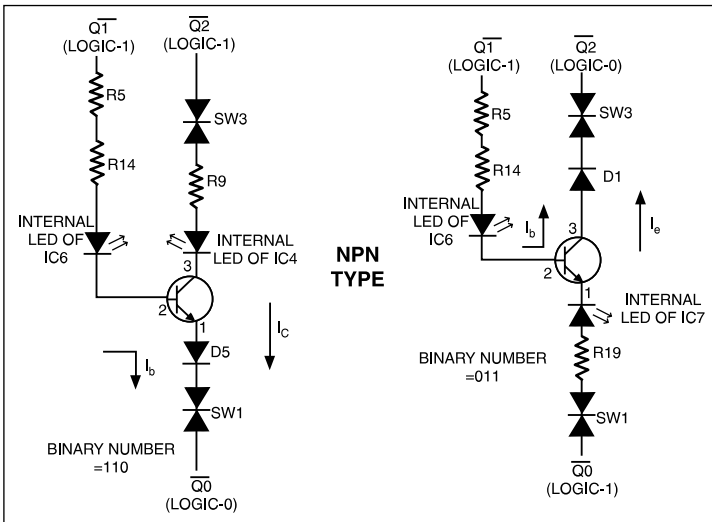


Fig. 3: Effective biasing of NPN transistors using set 2 binary numbers

the base in different terminals (1, 2, or 3) on the socket, until the desired results are obtained. To alert the user about this action, a message 'Adjust LED' blinks on the display (refer error processing routine in the software program).

The circuit

The binary number generator. In this section, IC1 (an NE555 timer) is used as a clock pulse generator, oscillating at about 45 Hz. The output of IC1 is applied to clock pin 14 of IC2 (4017-decade counter). As a result, the counter advances sequentially from decimal 0 to 3, raising outputs Q0, Q1, and Q2 to logic-1 level. On reaching the next count, pin 7 (output Q3) goes high and it resets the counter. So, the three outputs (Q0, Q1, and Q2) jointly produce three binary numbers, continuously, in a sequential manner (see Table II).

Q0 through Q2 outputs of IC2 are con-

nected to inputs of IC3 (7486, quad 2-input EX-OR gate). The outputs of IC3 are controlled by the logic level at pin 12. Thus, we obtain two sets of outputs (marked Q0, Q1, and Q2) from IC3 as given in Tables III (for pin 12 at logic 1) and IV (for pin 12 at logic 0) respectively.

One of these two sets would be chosen for the output by the software, by controlling the logical state of pin 12. Set-1 is used to identify the base and type (npn or pnp) of the 'transistor under test,' whereas set-2 is exclusively used for identification of the collector lead, if the device is of npn type.

The interface. The three data output lines, carrying the stated binary numbers (coming from pins 3, 6, and 8 of IC3), are connected separately to three bi-directional analogue switches SW1, SW2, and SW3 inside IC5 (CD4066). The other sides of the switches are connected to the terminals of the test socket through some other components shown in Fig. 1. The control line of IC3 (pin 12) is connected to the analogue switch SW4 via pin 3 of IC5. The other side of SW4 (pin 4) is grounded. If switch SW4 is closed by the software, set-1 binary numbers are applied to the device under test, and when it is open, set-2 binary numbers are applied.

To clearly understand the functioning of the circuit, let us assume that the

'transistor under test' is inserted with its collector in slot-3, the base in slot-2, and the emitter in slot-1 of the testing socket.

Initially, during identification of the base and type of the device, all the analogue switches, except SW4, are closed by the software, applying set-1 binary numbers to the device. Now, if the device is of pnp type, each time the binary number 100 is generated at the output of IC3, the BC junction is forward-biased, and hence, a conventional current flows through the junction as follows:

Q2 (logic 1) → SW3 → R9 → internal LED of IC4 → slot3 → collector lead → CB junction → base lead → slot-2 → D3 → pin 10 of IC5 → SW2 → Q1 (logic 0).

Similarly, when the binary number 001 is generated, another current would flow through the BE junction and the internal LED of IC7. The number 010 has no effect, as in this case both the BC and BE junctions become reversed biased.

From the above discussion it is apparent that in the present situation, as the internal LEDs of IC4 and that of IC7 are forward-biased, they would go on producing pulsating optical signals, which would be converted into electrical voltages by the respective internal photo-transistors. The amplified pulsating DC voltages are available across their emitter resistors R7 and R17 respectively. The emitter followers configured around transistors T1 and T3 raise the power level of the optocoupler's output, while capacitors C3 and C5 minimise the ripple levels in the outputs of emitter followers.

During initialisation, 8155 is configured with port A as an input and ports B and C as output by sending control word 0E(H) to its control register.

Taking output of transistor T1 as MSB(D2), and that of T3 as LSB(D0), the data that is formed during the base identification, is 101 (binary). The microprocessor under the software control, receives this data through port A of 8155 PPI (port number 81). Since all the bits of the higher nibble are masked by the software, the data become 0000 0101=05(H). This data is stored at location 216A in memory and termed in the software as base-Id.

Now, if the device is of npn type, the only binary number that would be effective is 010. Under the influence of this number both BC and BE junctions would be forward-biased simultaneously, and hence conventional current would flow in the following two paths:

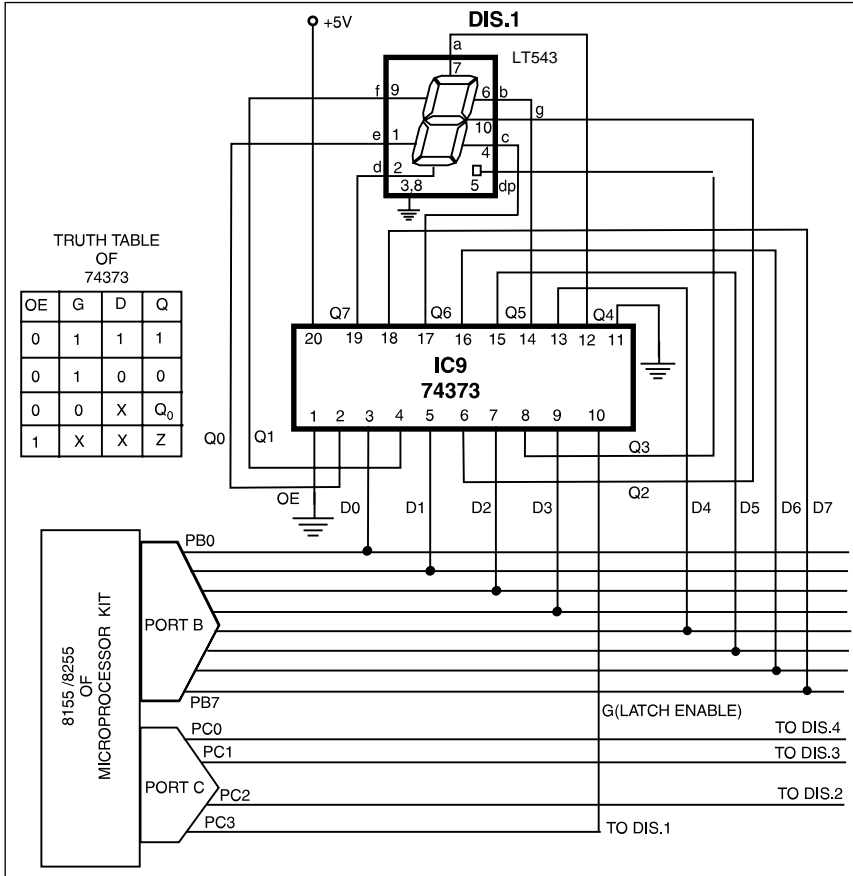


Fig. 4: Schematic circuit of special display system

1. \bar{Q}_1 (logic 1) \rightarrow SW2 \rightarrow R14 \rightarrow internal LED (IC6) \rightarrow slot-2 \rightarrow base lead \rightarrow BC junction \rightarrow collector lead \rightarrow slot-3 \rightarrow D1 \rightarrow SW3 \rightarrow Q2 (logic 0)

2. \bar{Q}_1 (logic 1) \rightarrow SW2 \rightarrow R14 \rightarrow internal LED (IC6) \rightarrow slot-2 \rightarrow base lead \rightarrow BE junction \rightarrow emitter lead \rightarrow slot 1 \rightarrow D5 \rightarrow SW1 \rightarrow Q0 (logic 0)

Thus, only the internal LED of IC6 would start flickering, and the data that would be formed at the emitters of the transistors is also 010. Accordingly, the base-Id that would be developed in this case is 0000 0010=2(H).

Since, under the same orientation of the transistor in the socket, the base-Ids are different for a pnp and an npn device, the software can decode the type of the device.

In a similar way we can justify the production of the other base-Ids, when their collector, base, and emitter are inserted in the testing socket differently.

Once the base-Id is determined, the software sends the same number for a pnp-device (here=05(H)) through port c (port number 83), with the bit format shown in Table V.

As a result, the control input of SW2 (pin 12 of IC5) gets logic 0. So the switch opens to insert resistor R5 in series with the base circuit. This action is necessary to identify the emitter (and hence the collector) lead as described earlier under 'Principle' sub-heading.

On the contrary, since an npn-de-

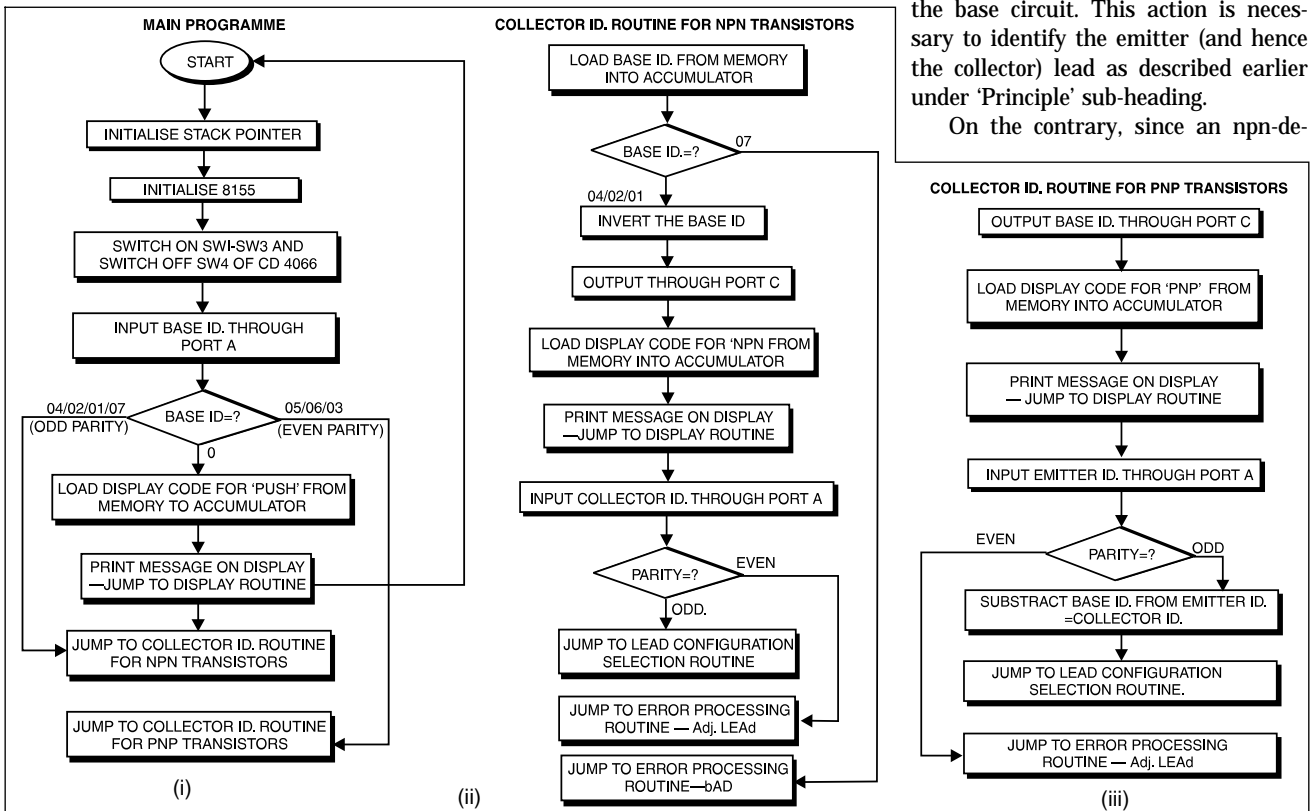


Fig. 5: Flowcharts for the main program and various subroutines

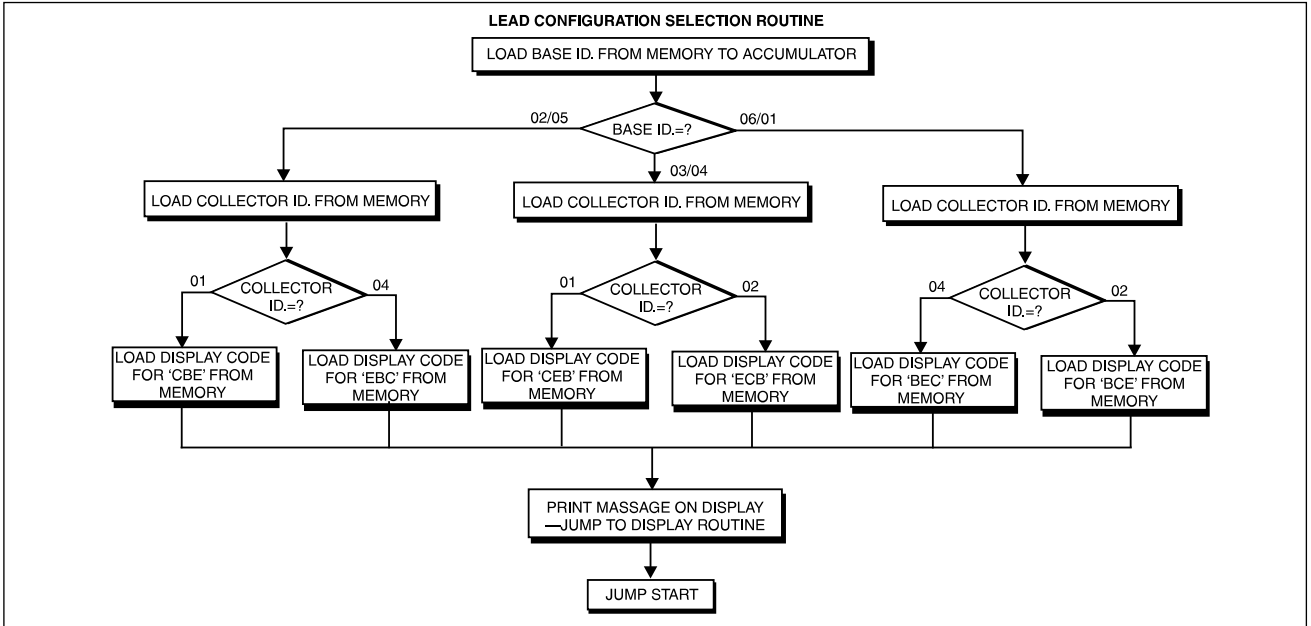


Fig. 5 (iv)

PC7	PC6	PC5	PC4	PC3	PC2	PC1	PC0
0	0	0	0	0	1	0	1

PC7	PC6	PC5	PC4	PC3	PC2	PC1	PC0
0	0	0	0	1	1	0	1

vice uses the set-2 binary numbers for identification of the collector (hence the emitter), the same number (base-Id) obtained during base identification cannot be sent through port c, if the device under test is of npn type. The base-Id found must be EX-ORED first with 0F (H). Since the base-Id found here is 02 (H), the data to be sent through port c in this case would be as shown in Table VI.

Note that PC3 becomes logic-1, which would close switch SW4 to get the set-2 binary numbers.

Once resistor R5 is inserted in the base circuit, and set-1 binary numbers are applied to the device (pnp type), it would be biased sequentially in three distinct ways, of which only two would be effective. The same are shown in Fig. 2.

In case of binary number 100, the current through the internal LED of IC4 would distinctly be very low compared to the current flowing during number 001, through the internal LED of IC7. If R5 is of sufficiently high value, the former current may be reduced to such an extent that the related LED would be off. Hence, the data that would be formed at the emit-

ters of transistors T1-T3 would be 001. It would be modified by the software to 0000 0001=01(H). This is termed in the software as emitter-Id and is stored at memory location 216B.

On the other hand, if the device is of npn type, set-2 binary numbers are to be applied to it, and the transistor would be biased as shown in Fig. 3. Here, only the internal LED of IC4 would flicker. So, the data at the output would be 100=04(H). This is termed in the software as collector-Id, and is stored in memory location 216C. (In case of pnp-device, the collector-Id is determined mathematically by subtracting the Base-Id from the emitter-Id.)

So the result could be summarised as:
 pnp type:
 Base-Id = 05(H), Collector-Id = 01(H).
 npn type:
 Base-Id = 02(H), Collector-Id = 01(H).

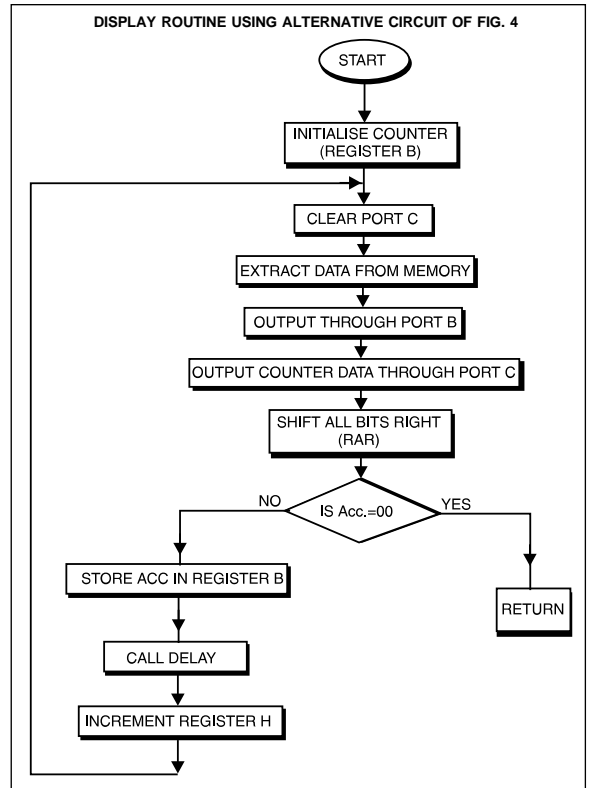


Fig. 5 (v)

With this result, the software would point to configuration CBE in the data table, and print the same on the display. By a similar analysis, lead configuration for any other orientation of the device in the test socket would be displayed by the software, after finding the related base-and collector-Id.

 


Fig. 6: Actual-size, single-sided PCB layout for the circuit in Fig. 1

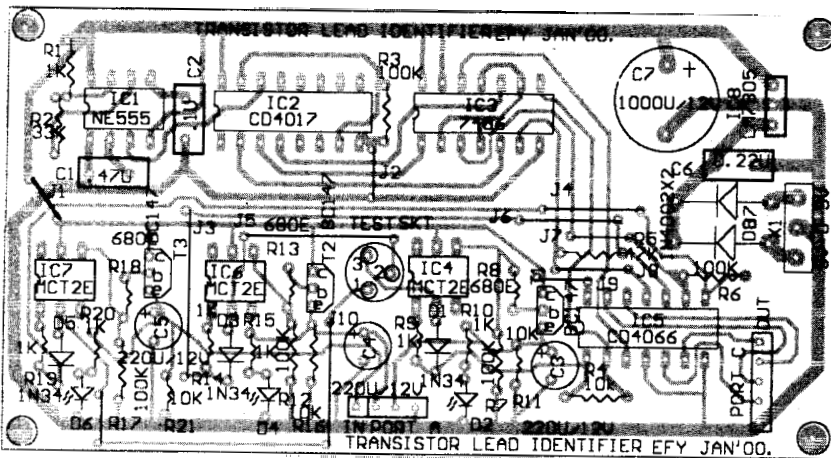


Fig. 7: Component layout for the PCB

The Display. The display procedure described in this article is based on IC 8279 (programmable keyboard/display interface) which is used in the microprocessor kit. The unique feature of the 8279-based display system is that, it can run on its own. You just have to dump the data to be displayed on its internal RAM, and your duty is over. 8279 extracts this data from its RAM and goes on displaying the same without taking any help or consuming the time of the microprocessor in the kit.

Unfortunately, not all the microprocessor kits present in the market are fitted with this IC. Instead, some of them use a soft-scan method for display purpose. Hence, the stated procedure cannot be run in those kits. Of course, if the monitor program of the kit is to be used, which may have an in-built display routine to display the content of four specific memory locations—all at a time, the same may be used in place of the present

display procedure.

Note: Display subroutine at address 20FC used at EFY, making use of the monitor program of the Vynitics 8085 kit, during program testing, is listed towards the end of the software program given by the author. To make use of the author's display subroutine, please change the code against 'CALL DISPLAY' instruction (code CDFC 20) everywhere in the program to code CD 40 21 for 8279 based display or code CD 07 21 for alternate display referred in the next paragraph.

Alternatively, one can construct a special display system using four octal D-type latches (74373) and four seven-segment LED displays (LT543). Only one latch and one display has been shown in the schematic circuit of Fig. 4 along with its interface lines from 8155 or 8255 of the kit. To drive this display, a special soft-scan method explained in the following para has to be used.

The soft scan display procedure.

PARTS LIST

<i>Semiconductors:</i>	
IC1	- NE555, timer
IC3	- CD4017, decade counter-decoder
IC3	- 7486, quad EX-OR gates
IC4,IC6,IC7	- MCT2E, optocoupler
IC5	- CD4066, quad bilateral switch
IC8	- LM7805, 3-terminal +5V regulator
T1,T2,T3	- BC147, npn transistor
D1,D3,D5	- 1N34, point contact diode
D2,D4,D6	- LED, 5mm
D7,D8	- 1N4002, rectifier diode
<i>Resistors (All 1/4 watt +/- 5% metal/carbon film unless stated otherwise)</i>	
R1,R9,R10,R14,	
R15,R19,R20	- 1 kilo-ohm
R2	- 33 kilo-ohm
R5	- 47 kilo-ohm
R4,R11,R16,R21	- 10 kilo-ohm
R3,R6,R7,R12,R17	- 100 kilo-ohm
R8,R13,R18	- 680 ohm
<i>Capacitors:</i>	
C1	- 0.5µF polyester
C2	- 0.1µF polyester
C3-C5	- 220µF/12V electrolytic
C6	- 0.22µF polyester
C7	- 1000µF/12V electrolytic
<i>Miscellaneous:</i>	
X1	- 230V/9V-0.9V, 250mA power transformer

The procedure extracts the first data to be displayed from memory. The start memory address of the data to be displayed is to be supplied by the calling program. This data (8-bit) is output from port B of 8155/8255 PPI (after proper coding for driving the seven-segment displays), used in the kit. Data lines are connected in parallel to all the octal latches. But only one of the four latches is enabled (via a specific data bit of port c of 8155/8255) to receive the data and transfer the same to its output to drive the corresponding seven-segment LED display. To enable a particular latch, a logic 1 is sent through a particular bit of port c (bit 4 here, for the first data) by the software. Subsequently, logic 0 is sent through that bit to latch the data transferred. The program then jumps to seek the second data from memory, and sends the same through port B as before. However, in this case logic 1 is sent through bit 3 of port c, to latch the data to the second seven-segment LED display, and so on.

Register B of 8085 is used as a counter, and is initially stored with the binary number 00001000 (08H). Each time a data is latched, the logic 1 is shifted right by one place. So, after the fourth data is latched, the reg. B content would be 0000 0001. Shift-

C O N S T R U C T I O N

Memory Map And Software listing in 8085 Assembly Language

RAM Locations used for program	:2000H - 21BBH
Stack pointer initialised	:2FFFFH
Monitor Program	:0000H - 0FFFFH
Display Data Table	:2160H - 219AH
Control/Status Register of 8155	:80H
Port A (Input) of 8155	:81H
Port B (Output) of 8155	:82H
Port C (Output) of 8155	:83H

Address	Op Code	Label	Mnemonic	Comments
2087	E607		ANI 07H	Checks only first three bits
2089	EAA021		JPE ERR	If 2 bits are at logic-1 jumps to 21A0
208C	326C21		STA 216CH	Store the No. (Collector-Id) into mem.
208F	C39220		JMP P4	Jumps to select lead configuration

:Lead configuration selection program

Address	Op Code	Label	Mnemonic	Comments
:Initialisation, base and type identification				
2000	31FF2F	MAIN:	LXI SP,2FFFFH	Initialisation of the ports. A as the
2003	3E0E		MVI A,0EH	input and C as the output port.
2005	D380		OUT 80H	Sends 07 through port C to make SW1,
2007	3E07		MVI A,07H	SW2, SW3 ON and SW4 OFF.
2009	D383		OUT 83H	Time delay should be allowed before
200B	CD3320		CALL DELAY	measuring the logic voltages across
200E	CD3320		CALL DELAY	capacitors C1, C2, and C3, so that
2011	CD3320		CALL DELAY	they charge to the peak values.
2014	AF		XRA A	Clears the accumulator
2015	DB81		IN 81H	Input data from interface through.
portA	2017E607		ANI 07H	Test only first 3 bits, masking others
2019	326A21		STA 216AH	Stores the number in memory.
201C	CA2A20		JZ P	If the number is zero jumps to 202A
201F	EA3D20		JPE P2	If the number has even no. of 1s,
				jumps to 203D (refer note 2)
2022	E26820		JPO P3	If the number has odd no. of 1s, jump
				to 2068 (refer note 1)
2025	00		NOP	No operation
2026	00		NOP	No operation
2027	00		NOP	No operation
2028	00		NOP	No operation
2029	00		NOP	No operation
202A	218921	P:	LXI H,2189H	Points to message "PUSH" in data
				table
202D	CDFC20		CALL DISPLAY	Displays the message
2030	C30020		JMP MAIN	Jumps to start.

:Delay sub-routine

2033	11FFFF	DELAY:	LXI D,FFFFH	Loads DE with FFFF
2036	1B		DCX D	Decrements DE
2037	7A		MOV A,D	Moves result into Acc.
2038	B3		ORA E	OR E with Acc.
2039	C23620		JNZ 2036	If not zero, jumps to 2036
203C	C9		RET	Returns to calling program

:Collector identification program for PNP transistors

203D	216A21	P2:	LXI H,216AH	Points of Base-Id in data table
2040	7E		MOV A,M	Extracts the number to the
				accumulator
2041	D383		OUT 83H	Send the number to the interface
2043	216021		LXI H,2160H	Points to message 'PnP' in data table
2046	CDFC20		CALL DISPLAY	Displays the message
2049	CD3320		CALL DELAY	Waits for few moments
204C	CD3320		CALL DELAY	Waits for few moments
204F	CD3320		CALL DELAY	Waits for few moments
2052	AF		XRA A	Clears the accumulator
2053	DB81		IN 81H	Seeks data from the interface
2055	E607		ANI 07H	Masks all bits except bits 0,1 and 2
2057	EAA021		JPE ERR	If the data contains even no. of 1s
				jumps to error processing routine
205A	326B21		STA 216BH	Stores the data (Emitter-Id) in memory
205D	47		MOV B,A	Moves the Emitter-Id. to B register
205E	3A6A21		LDA 216AH	Extracts Base-Id from memory
2061	90		SUB B	Subtracts Emitter-Id from Base-Id
2062	326C21		STA 216CH	Stores the result(Collector-Id) in mem.
2065	C39220		JMP P4	Jumps to select lead configuration

:Collector identification program for NPN transistors

2068	216A21	P3:	LXI H,216AH	Points to Base-Id in data table
206B	7E		MOV A,M	Extract the number to the accumulator
206C	FE07		CPI 07H	Refer note 1
206E	CAB621		JZ ER	Jumps to error processing routine
2071	EE0F		XRI 0FH	Refer note 2
2073	D383		OUT 83H	Send the number to the interface
2075	216421		LXI H,2164H	Points to the message "nPn"
2078	CDFC20		CALL DISPLAY	Displays the same
207B	CD3320		CALL DELAY	Waits for few moments
207E	CD3320		CALL DELAY	Waits for few moments
2081	CD3320		CALL DELAY	Waits for few moments
2084	AF		XRA A	Clears the accumulator
2085	DB81		IN 81H	Seeks data from the interface

2092	216A21	P4:	LXI H,216AH	Extracts Base-Id from memory location
2095	7E		MOV A,M	216A to the accumulator
2096	FE05		CPI 05H	If the number is 05,
2098	CABA20		JZ P4	jumps to subroutine 4A
209B	FE06		CPI 06H	If the number is 06,
209D	CAD020		JZ P4B	jumps to the subroutine 4B
20A0	FE03		CPI 03H	If the number is 03,
20A2	CAE620		JZ P4C	jumps to the subroutine 4C
20A5	FE02		CPI 02H	If the number is 02,
20A7	CABA20		JZ P4A	jumps to the subroutine 4A
20AA	FE01		CPI 01H	If the number is 06,
20AC	CAD020		JZ P4B	jumps to the subroutine 4B
20AF	FE04		CPI 04H	If the number is 04,
20B1	CAE620		JZ P4C	jumps to the subroutine 4C
20B4	CDFC20	M:	CALL DISPLAY	Jumps to display the lead configuration
				selected in P4A or P4B or P4C
20B7	C30020		JMP MAIN	Jumps back to start

:Lead configuration selection (Base Id.=05 or 02)

20BA	216C21	P4A:	LXI H,216CH	Extracts Collector-Id from memory
				location
20BD	7E		MOV A,M	216C to the accumulator
20BE	FE01		CPI 01H	If it is = 01, jumps to 20CA
20C0	CACA20		JZ E	If it is = 04, points to lead
				configuration "EbC"
20C3	217521		LXI H,2175H	in data table
20C6	C3B420		JMP M	Jumps to display the lead
				configuration pointed
20C9	00		NOP	NOP
20CA	217121	E:	LXI H,2171H	Points to lead config."CbE" and jumps
20CD	C3B420		JMP M	display the configuration

:Lead configuration selection (Base Id.= 06 or 01)

20D0	216C21	P4B:	LXI H,216CH	Extracts Collector-Id from memory
				location
20D3	7E		MOV A,M	216C to the accumulator
20D4	FE02		CPI 02H	If it is STE02, jumps to 20E0
20D6	CAE020		JZ B1	If it is =04, points to lead
20D9	217D21		LXI H,217DH	configuration "bEC" in data table
20DC	C3B420		JMP M	Jumps to display the lead
				configuration pointed
20DF	00		NOP	No operation
20E0	217921	B:	LXI H,2179H	Points to lead configuration "bCE"
20E3	C3B420		JMP M	and jumps display the configuration

:Lead configuration selection (Base Id.=03 or 04)

20E6	216C21	P4C:	LXI H,216CH	Extracts Collector-Id from memory
				location
20E9	7E		MOV A,M	216C to the accumulator
20EA	FE01		CPI 01H	If it is =01, jumps to 20F6
20EC	CAF620		JZ C	If it is =02, points to lead
20EF	218121		LXI H,2181H	configuration "ECb" in data table
20F2	C3B420		JMP M	Jumps to display the lead
20F5	00		NOP	configuration pointed; no operation
20F6	218521	C:	LXI H,2185H	Points to lead configuration "CEb"
20F9	C3B420		JMP M	and jumps to display the configuration

:Display routine using 8279 of the kit (if present)

2140	0E04		MVI C,03	Sets the counter to count 4 characters
2142	3E90		MVI A,90	Sets cont.8279 to auto-incr. mode
2144	320160		STA 6001	Address of 8279 cont. reg.=6001
2147	7E		MOV A,M	Moves 1st data character from mem.
				Loc. pointed to by calling instruction.
2148	2F		CMA	Inverts data (refer note below)
2149	320060		STA,6000	Stores data in 8279 data reg.
				(addr=6000)
214C	0D		DCR C	Decrements counter
214D	CA5421		JZ 2154	Returns to calling program if count=0
2150	23		INX H	Increments memory pointer
2151	C34721		JMP2147	Jumps to get next character from
				memory
2154	C9		RET	Returns to the calling program

Note: In the microprocessor kit used, data is inverted before feeding the 7-seg display.

:Alternative Display Subroutine to be used with interface circuit of Fig. 4

2107	0608		MVI B,08H	Store 0000 1000 in reg.B
2109	3E00		MVI A,00H	Out 00H through Port C to latch data
				in all

C O N S T R U C T I O N

Address	Op Code	Label	Mnemonic	Comments	Addr.	Data	Display	Addr.	Data	Display	Addr.	Data	Display	
210B	D383		OUT 83H	74373s. (no data would move to O/Ps)	2164	45	n	217D	C7	b	218D	C7	b	
210D	7E		MOV A,M	Moves the 1st char. Of the data pointed, to the accumulator (mem. address given by calling program)	2165	37	P	217E	97	E	218E	77	A	
210E	D382		OUT 82H		2166	45	n	217F	93	C	218F	E5	d	
2110	78		MOV A,B	By moving out reg.B data through port C	2167	00		2180	00		2190	00		
2111	D383		OUT 83H	a specific latch is enabled.	216A			2181	97	E	2191	7	a	
2113	1F		RAR	Logic 1 of counter data moves right 1 bit	216B			2182	93	C	2192	E5	d	
2114	FE00		CPI 00H	Checks to see logic 1 moves out from acc.	216C			2183	C7	b	2193	E1	J	
2116	CA2121		JZ 2121H	(All 4 data digits latched)to return to the calling program.	2171	93	C	2184	00		2194	00		
2119	47		MOV B,A	Else stores back new counter data to B reg.	2172	C7	b	2185	93	C	2196	83	L	
211A	CD3320		CALL DELAY		2173	97	E	2186	97	E	2197	97	E	
211D	23		INX H	Memory pointer incremented by 1	2174	00		2187	C7	b	2198	77	A	
211E	C30921		JMP 2109H	Jumps to the next character from the table	2175	97	E	2188	00		2199	E5	D	
2121	C9		RET	Returns to the calling program	2176	C7	b				219A	00		
;Error Sub-routine					Address of routines/labels:									
21A0	219121	ERR:	LXI H,2191H	Points to the message "Adj." in memory	MAIN	2000	P	202A	DELAY	2033	D	2036		
21A3	CDFC20		CALL DISPLAY	Calls the display routine to display the same	P2	203D	P3	2068	P4	2092	M	20B4		
21A6	CD3320		CALL DELAY	Waits	P4A	20BA	E	20CA	P4B	20D0	B	20E0		
21A9	CD3320		CALL DELAY	Waits	P4C	20E6	C	20F6	DISPLAY	20FC	ERR	21A0		
21AC	219621		LXI H,2196H	Points to the message "LEAd" in memory	BAD	21AF	ER	21B6						
21AF	CDFC20	BAD:	CALL DISPLAY	Calls the display routine to display	Notes:									
21B2	C30020		JMP MAIN	Jumps back to start	1. During Base identification, if the data found has odd parity, only then the program jumps to this routine (starting at 2068 at P3) for collector identification. A single logic-1 denotes a good transistor, whereas three logic-1 (i.e. Base-Id = 07) denote a bad transistor with shorted leads. Hence the program jumps to error processing routine to display the message "bAd".									
21B5	00		NOP	No operation	2. The purpose of sending the Base-Id number to the interface through Port-C, is to insert a resistor in series with the Base (as indicated in the principle above). The logic-1(s) of the Base-Id, set the switches connected with the collector and emitter leads to "ON", and that with the base to "OFF". The result is, the resistor already present in the base circuit (10K, 47K or 100K which one is applicable), becomes active. To achieve this result, the Base-Id found for an NPN device is to be inverted first.									
21B6	218D21	ER:	LXI H,218DH	Points to message "bAd" in the data table	;Display subroutine used by EFY using monitor program of Vinytics kit.									
21B9	C3AF21		JMP BAD	Jumps to display the message	20FC	C5		DISPLAY: PUSH B						
Data table:					20FD	3E00		MVI A,0H						
Addr.	Data	Display	Addr.	Data	Display	Addr.	Data	Display	20FF	0600		MVI B,0H		
2160	37	P	2179	C7	b	2189	37	P	2101	7E		MOV A,M		
2161	45	n	217A	93	C	218A	E3	U	2102	CDD005	CALL	05D0H		
2162	37	P	217B	97	E	218B	D6	S	2105	C1		POP B		
2163	00		217C	00		218C	67	H	2106	C9		RET		

TABLE VII				
; Modification to Collector Identification Program for pnp Transistors				
Address	Op Code	Label	Mnemonic	Comments
203D	216021	P2:	LXI H,2160H	Points to message 'PnP' in data table
2040	CDFC20		CALL DISPLAY	Displays the message
2043	216A21		LXI H,216AH	Points to Base-Id in data table
2046	7E		MOV A,M	Extract the number to the accumulator
2047	D383		OUT 83H	Send number via port C to interface

TABLE VIII				
; Modification to Collector Identification Program for npn Transistors				
Address	Op Code	Label	Mnemonic	Comments
2068	216421	P3:	LXI H,2164H	Points to the message 'nPn'
206B	CDFC20		CALL DISPLAY	Displays the same on display.
206E	216A21		LXI H,216AH	Points to Base-Id in DATA table
2071	7E		MOV A,M	Extract the number to the accumulator
2072	FE07		CPI 07H	Refer note.1 (see original program.)
2074	CAB621		JZ ER	Jumps to error processing routine
2077	EE0F		XRI 0FH	Refer note.2 (see original program.)
2079	D383		OUT 83H	Send number to interface (via port C)

ing operation is done after first moving the data from the register to the accumulator, and then storing the result back into the register once again if the zero flag is not set by the RAR operation.

Now, with the reg. B content = 0000 0001, one more shifting of the bits towards right would make the accumulator content = 0000 0000, which would set the zero flag. And hence the program would jump

back to the calling one. It would be interesting to note the same reg. B content (a binary number comprising a logic 1) is sent through port c to enable the particular latch.

Since the base Id numbers and the code to enable a specific latch are sent through the same port (port c) in the alternate display, the base Id must be sent first for displaying the message PnP/nPn. Therefore changes or modifications are required in the original program pertaining to collector identification program for pnp transistors (at locations 203D through 2048) and npn transistors (at locations 2068 through 207A) as given in Tables VII and VIII respectively.

Software flow charts. Software flow charts for main program and various sub-routines are shown in Fig. 5.

PCB and parts list are included only for the main interface diagram of Fig. 1. The actual-size, single-sided PCB for the same is given in Fig. 6 while its component layout is shown in Fig. 7. □

CONVERSION OF AUDIO CD PLAYER TO VIDEO CD PLAYER — I



PUNERJOT SINGH MANGAT

The analogue technology is giving way to the digital technology as the latter offers numerous advantages. Digital signals are not only free from distortion while being routed from one point to another (over various media), but error-correction is also possible. Digital signals can also be compressed which makes it possible to store huge amounts of data in a small space. The digital technology has also made remarkable progress in the field of audio and video signal processing.

Digital signal processing is being widely used in audio and video CDs and CD playing equipment. These compact disks have brought about a revolution in the field of audio and the video technology. In audio CDs, analogue signals are first converted into digital signals and then stored on the CD. During reproduction, the digi-

tal data, read from the CD, is reconverted into analogue signals. In case of video signals, the process used for recording and reproduction of data is the same as used for audio CDs. However, there is an additional step involved—both during recording as well as reproduction of the digital video signals on/from the compact disk. This additional step relates to the compression of data before recording on the CD and its decompression while it is being read. As video data requires very large storage space, it is first compressed using MPEG- (Motion Picture Expert Group) compatible software and then recorded on the CD. On reading the compressed video data from the CD, it is decompressed and passed to the video processor. Thus with the help of the compression technique huge amount of video data (for about an hour) can be stored in one CD.

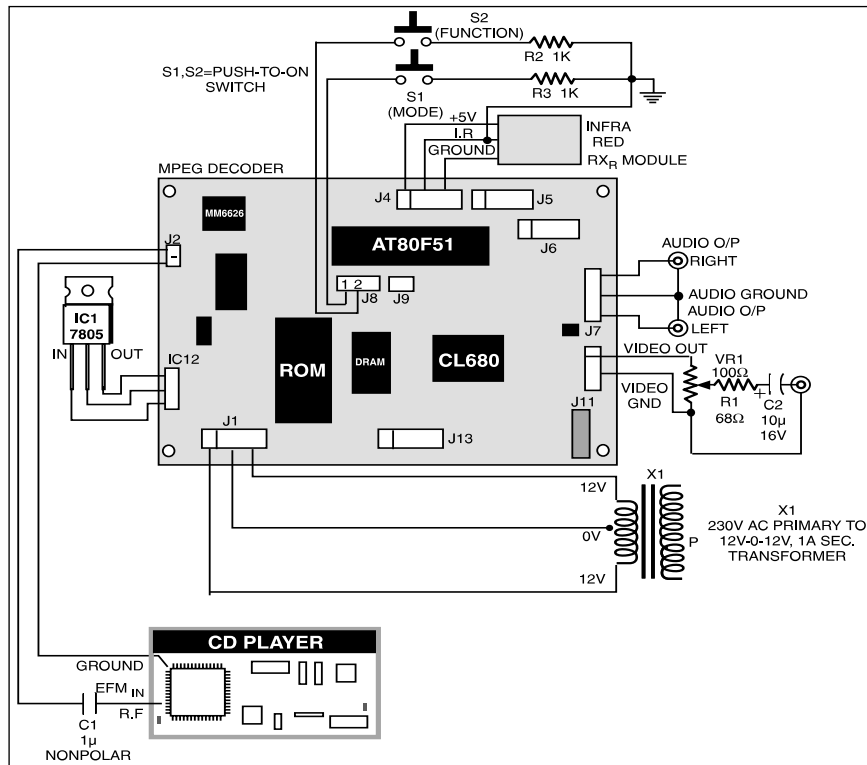


Fig. 1: Complete schematic layout and connection diagram for conversion of Audio CD to Video CD player

PARTS LIST-1

Semiconductors:

IC1 - LM7805 voltage regulator +5V

Resistors (All $\frac{1}{4}W$, $\pm 5\%$ metal/carbon film, unless stated otherwise):

R1 - 68 ohm

R2, R3 - 1 kilo-ohm

VR1 - 100 ohm cermet (variable resistor)

Capacitors:

C1 - 1 μ F paper (unipolar)

C2 - 10 μ F, 16V electrolytic

Miscellaneous:

X1 - 230V AC primary to 12V-0-12V, 1A sec. transformer

S1, S2 - Push-to-on tactile switch

- MPEG decoder card (Sony Digital Tech.)

- TV modulator (optional)

- AF plugs/jacks (with screened wire)

- Co-axial connectors, male/female

- Co-axial cable

Conversion

An audio CD player, which is used to play only audio CDs, can be converted to play the video CDs as well. Audio CD players have all the required mechanism/functions to play video CDs, except an MPEG card, which is to be added to the player. This MPEG card is readily available in the market. This MPEG card decompresses the data available from the audio CD player and converts it into proper level of video signals before feeding it to the television.

Construction

Step-by-step conversion of audio CD player to video CD player is described with reference to Fig. 1.

Step 1. Connection of MPEG card to TV and step-down power transformer to confirm proper working of the MPEG card.

- Connect IC7805, a 5-volt regulator, to the MPEG card. Please check for correct pin assignments.
- Connect audio and video outputs of the



Fig 2: Photograph of TV scene

MPEG card to the audio/video input of TV via jacks J7 and J11 respectively. Use only shielded wires for these connections.

- Check to ensure that the step-down transformer provides 12-0-12 volts at 1 ampere of load, before connecting it to the MPEG card. Connect it to the MPEG card via jack J1.
- Switch on the TV to audio/video mode of operation. Adjust the 100-ohm preset connected at the video output of MPEG card to mid position.
- Switch on the MPEG card by switching on 230 volts main supply to the 12-0-12 volt transformer.
- If everything works right, 'Sony Digital Technology' will be displayed on the television. The TV screen will display this for about 5 seconds before going blank. Adjust the 100-ohm preset for proper level of video signals.

Step 2. Connections to audio CD player after confirmation of proper functioning of MPEG card during step1.

- Open your audio CD player. Do this very carefully, avoiding any jerks to the audio CD player, as these may damage the player beyond repair.
- Look for the IC number in Table II (on page 47) that matches with any IC in your audio CD player.
- After finding the right IC, note its RF EF MIN pin number from the Table I.
- Follow the PCB track which leads away

from RF EFM in pin of the IC and find any solder joint (land) on this PCB track. Solder a wire (maximum half meter) to this solder joint carefully. Other end of this wire should be joined to RF jack J2 of the MPEG card.

Caution: *Unplug the soldering iron from the mains before soldering this wire because any leakage in the soldering iron may damage the audio CD player.*

- Another wire should be joined between the ground of the audio CD player and the ground of jack J2 of the MPEG card.
- This finishes the connection of the MPEG card to the audio CD player.

Step 3. Playing audio and video CDs.

- Switch on the power for the audio CD player and the MPEG card.
- Put a video CD in the audio CD player and press its play button to play the video CD.
- After a few seconds the video picture recorded on the CD will appear on the television.
- The play, pause, eject, rewind, forward, track numbers, etc buttons present on the audio CD can be used to control the new video CD player.

Now your audio CD player is capable of playing video CDs as well. You can connect a power amplifier to the MPEG card to get a high-quality stereo sound. The author tested this project on many audio players including Thompson Diskman and

S1 (mode switch)	S2 (function switch)
Slow	—
Discview	—
Pal/NTSC	Pal NTSC
Vol+	Volume Up
Vol-	Volume Down
Key+	Left volume down
Key-	Right volume down
L/R/CH	Left, Right, Mute, Stereo
Play/Pause	—

Note: The above mentioned functions can also be accessed using remote control.

Kenwood Diskman. A photograph of one of the scenes in black and white is included as Fig. 2. (Please see its coloured clipping on cover page.)

No special PCB is required and hence the same is not included.

The author has preferred to use Sony Digital Technology Card (against KD680 RF-35C of C-Cube Technology) because of many more functions it provides.

Additional accessibility features of this card (Sony Digital Technology), as shown in Table I can be invoked by adding two push-to-on switches between jack 8(J8) and ground via 1K resistors (Fig 1). These will enhance the already mentioned functions and facilities available on this card, even though it has not been possible to exploit the card fully due to non-availability of technical details. I hope these additions will help the readers get maximum mileage from their efforts.

CONVERSION OF AUDIO CD PLAYER TO VIDEO CD PLAYER — II

K.N. GHOSH

Want to convert your audio compact disk player into video compact disk player. Here is a simple, economical but efficient add-on circuit design that converts your audio cDplayer to video CD player.

Description

Decoder card. The add-on circuit is based on VCD decoder card, KD680 RF-35c, also known as MPEG card adopting MPEG-1 (Motion Picture Expert Group) stan-

dard, the international standard specification for compressing the moving picture and audio, comprising a DSP (digital signal processor) IC chip, CL860 from C-cube (Fig. 3). The VCD decoder card features small size, high reliability, and low power consumption (current about 300ma) and real and gay colours. This decoder card has two play modes (Ver. 1.0 and Ver. 2.0) and also the forward

and backward scan facility with 9-view pictures, slow-motion play, volume and tone control and R/L (right/left) vocal.

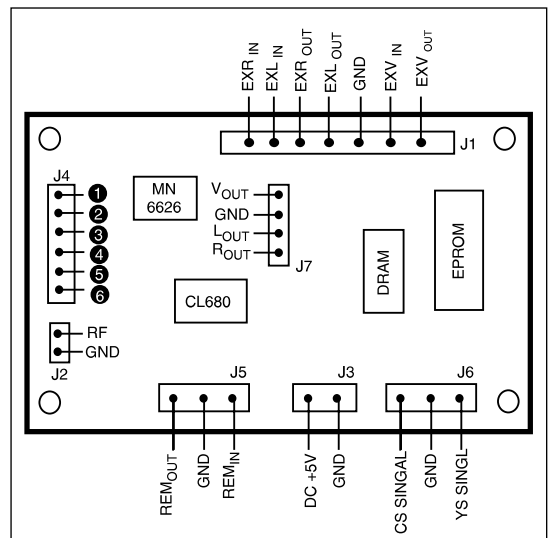


Fig. 3: Layout diagram of MPEG card from c-cube

TABLE II

DSP ICs and their EFM RF pin numbers

DSP IC	EFM /RF Pin	DSP IC	EFM /RF Pin
KS 5950	5	CXA 1372Q	32, 46
KS 5990, 5991	5	CXA 1471S	18, 27
KS 9210 B	5	CXA 1571S	18, 35
KS 9211 B E, 9212	5	AN 8370S	12, 31
KS 9282	5, 66	AN 8373S	9, 35
KS 9283	66	AN 8800SCE	12
KS 9284	66	AN 8802SEN	9
CXD 1125 QX	5	TDA 3308	3
CXD 1130 QZ	5	LA 9200	35
CXD 1135	5	LA 9200 NM	36
CXD 1163 Q	5	LA 9211 M	72
CXD 1167 R	36	HA 1215 8 NT	46, 72
CXD 1167 Q/QE	5	SAA 7210	3, 25
CXD 20109	9, 20	(40 pin)	
CXD 2500 AQ/BQ	24	SAA 7310	32
CXD 2505 AQ	24	(44 pin)	
CXD 2507 AQ	14	SAA 7341	36, 38
		SAA 7345	8
		SAA 7378	15
CXD 2508 AQ	36	TC 9200 AF	56
CXD 2508 AR	36	TC 9221 F	60
CXD 2509 AQ	34	TC 9236 AF	51, 56
CXD 2515 Q	36, 38	TC 9284	53
CXD 2518 Q	36	YM 2201/FK	76
LC 7850 K	7	YM 3805	8
LC 7860 N/K/E	7, 8	YM 7121 B	76
LC 7861 N	8	YM 7402	4, 71
LC 7862	30	HD 49215	71
LC 78620	11	HD 49233	19
LC 78620 E	11	AFS	
LC 7863	8	UPD 6374 CU	23
LC 7865	8	UPD 6375 CU	46
		M 50422 P	15
LC 7866 E	7, 8	M 50427 FP	15, 17
LC 7867 E	8	M 504239	17
LC 7868 E	8	M 515679	4
LC 7868 K	8	M 51598 FP	20
LC 78681	8	MN 35510	43
MN 6617	74	M 65820 AF	17
MN 6222	11	M 50423 FP	17
MN 6625 S	41	CX 20109	20, 9
MN 6626	3, 62	SAA7311	25
MN 6650	6	M50122P	15
MN 66240	44	M50123 FP	17
MN 66271 RA	44, 52	M50127 FP	17
MN 662720	44	UPD6374 CV	3
CXA 72S	18, 46	NM2210FK	76
CXA 1081Q	2, 27	YM2210FK	76

The decoder card converts your CD players or video games to VCD player to give almost DVD-quality pictures.

The decoder card mainly consists of sync signal separator, noise rejection circuit, digital to analogue converter, micro computer interface, video signal processor, and error detector, etc. Audio and video signals stored on a CD are in a high-density digital format. On replay, the digital information is read by a laser beam and converted into analogue signals.

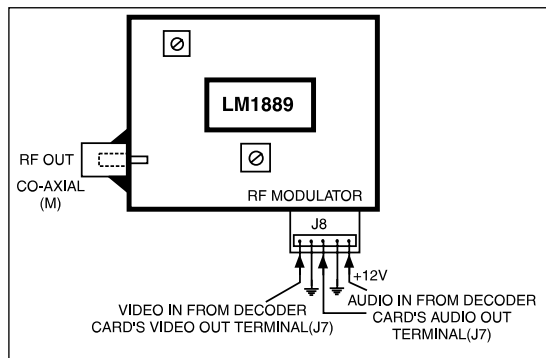


Fig. 4: Layout of TV RF modulator

PARTS LIST-2

- Semiconductors:
 IC1 - LM78L05, voltage regulator +5V
 IC2 - 78L12, voltage regulator +12V
 D1, D2 - 1N4001, rectifier diode
- Capacitors:
 C1 - 2200µF, 35V electrolytic
 C2, C3 - 100µF, 16V electrolytic
- Miscellaneous:
 - 230V AC primary to 18V-0-18V, 1A sec. transformer
 - MPEG decoder card (C-cube Digital Tech.)
 - TV modulator (optional)
 - AF plugs/jacks (with screened wire)
 - Co-axial connectors, male/female
 - Co-axial cable

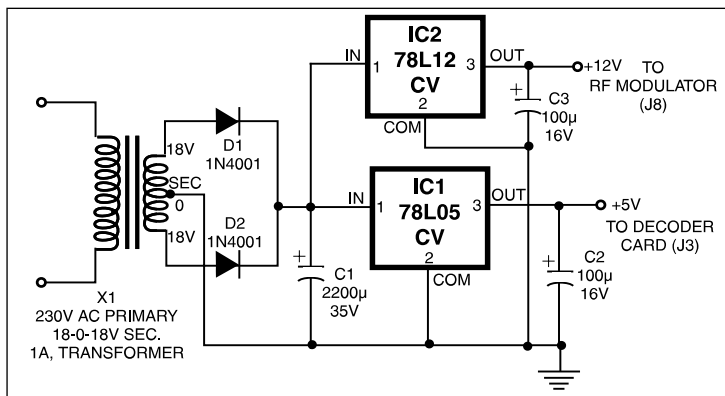


Fig. 5: Power supply to cater for MPEG card and RF modulator

 


Fig. 6: Block diagram of connections to decoder card and modulator

cuit, digital to analogue converter, micro computer interface, video signal processor, and error detector, etc. Audio and video signals stored on a CD are in a high-density digital format. On replay, the digital information is read by a laser beam and converted into analogue signals.

One can also use another VCD decoder card comprising an MPEG IC 680, from Technics, and a DSP IC chip, CXD2500, with powerful error-correction from Sony. Similarly, another card, KD2000-680RF comprising an MPEG IC chip, CL680 from Technics and a DSP IC chip, MN6627 from C-cube.

RF modulator. For those who do not have audio-video in-

put (AV in) facility in their TV, can make use of a pre-assembled audio-video to RF converter (modulator) module of 48.25MHz or 55.25 MHz (channel 2 or channel3), which is easily available in the market (refer Fig. 4). The audio and video signals from the decoder card are suitably modulated and combined at the fixed TV channel's frequency in the RF modulator. The output from the modulator can be connected to antenna connector of a colour television.

Power supply unit: The VCD decoder card and the RF modulator requires +5V and +12V regulated power supply

respectively. Supply design uses two linear regulators 7805 and 7812 (Fig. 5). The voltage regulators fitted with TO 220-type heat sink should be mounted on a CD player enclosure's rear panel. The circuit can be wired on a general-purpose PCB.

Installation steps:

1. Find suitable place in the enclosure of the audio CD player

for fixing the decoder card, RF modulator, and the power supply unit. Make appropriate diameter holes and fix them firmly.

2. Make holes of appropriate dimensions on the rear panel for fixing sockets for power supply and RF output.

3. Refer to Table II (Combined for Part-I and II) and confirm DSP chip type of the existing audio CD player for EFM (eight to fourteenth modulation)/RF Signal (from optical pick-up unit of the audio CD player) pin number, connect EFM in wire to this pin.

4. Make all the connections as per Fig. 6.

Text of articles on the above project received separately from the two authors have been reproduced above so as to make the information on the subject as exhaustive as possible. We are further

adding the following information which we have been able to gather during the practical testing of the project at EFY.

1. There may be more than one PCB used in an audio CD player (i.e additional for FM radio and tape recorder functions) and even the DSP chips referred in Table I, may not figure on it. For example, we could not find the subject IC used in AIWA audio CD player. The PCB, which is located closest under the laser system, is related to CD

player part. The DSP chip, more often than not, would be a multipin SMT device. In the AIWA system we located two such chips (LA9241M and LC78622E both from Sanyo). Their data-sheets, picked up from the Internet, revealed the former chip to be an ASP (analogue signal processor) and latter one (LA78622E) is the CD player DSP chip for which E_{FMIN} is not found in Table I. For this chip E_{FMIN} pin is pin 10 while pin 8 is the nearest digital ground pins-which we used.

 


Fig. 7: Modified 5V regulator for enhancing current capability

2. Of the two converter cards (one displaying 'Sony Digital Technology' and the other displaying 'C-cube Technology' on the CTV screen), the latter card's resolution and colour quality was found to be very good when tested by us. The C-cube card needs a single 5V DC supply for its operation.

3. During testing it was ob-

served that frequently, the picture/frames froze on the CTV screen and the power to the MPEG converter card had to be switched off and on again. This fault was attributed to inability of 7805 regulator to deliver the required current (about 300 mA) to the MPEG card. The regulator circuit was therefore modified as shown in Fig. 7 to provide a bypass path for current above 110 mA (approximately). A step-down transformer of 9V-0-9V, 500mA is adequate if the modulator has its own power supply arrangement (refer paragraph 4 below).

4. RF modulator for TV channels E2 and E3 are available in the market complete with step-down transformer, hence there may not be any need to wire up a 12V regulator circuit of part II.

5. Apart from the facilities (available in the MPEG decoder card KD680RF-3SC from C-cube) as explained by the author, there are other facilities such as IR remote control of the card functions (via Jack J5) and realisation of change-over between NTSC and PAL modes (via jack J4-no connections means PAL mode). Similarly, Jack J1 is meant for external audio and video input from exchange and connection of audio and video outputs to CTV. The foregoing information is available on document accompanying the MPEG decoder card. However, the detailed application/information is not provided and as such we have not tested these facilities.

6. EFM is a technique used for encoding digital samples of audio signals into series of pits and lands into the disc surface. During playback these are decoded into digital representation of audio signal and converted to analogue form using digital-to-analogue converter for eventual feeding to the loud speakers.

7. For those enthusiasts who wish to rig-up their own video modulator, an application circuit from National Semiconductor Ltd, making use of IC LM2889, which is pin for pin compatible with LM1889 (RF section), is given in Fig 8.

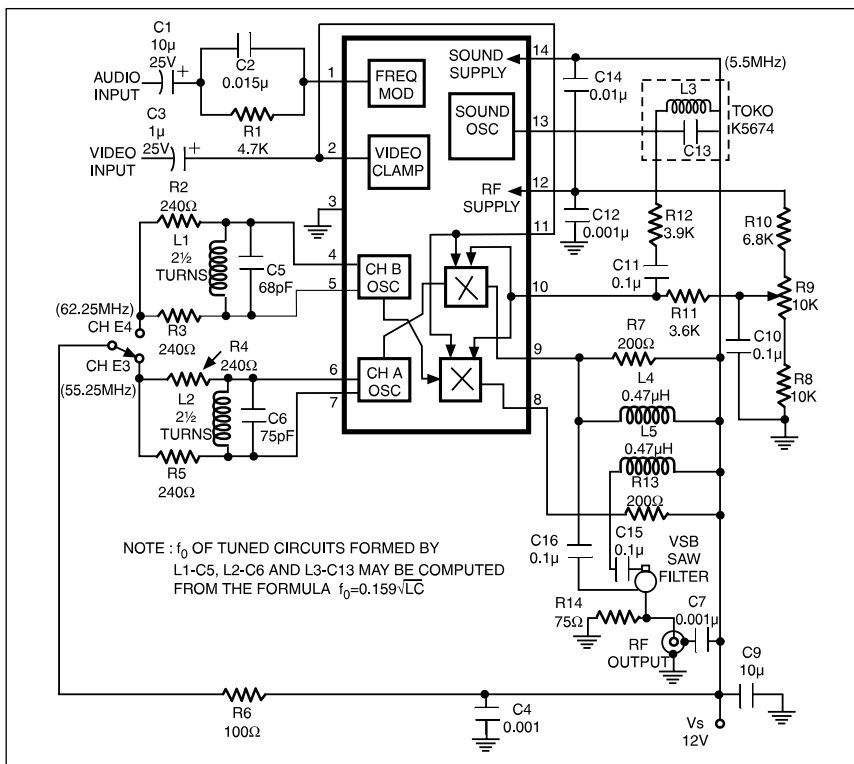


Fig. 8: Two channel video modulator with FM sound

—Tech Editor

MULTIPURPOSE CIRCUIT FOR TELEPHONES

RANJITH G. PODUVAL



This add-on device for telephones can be connected in parallel to the telephone instrument. The circuit provides audio-visual indication of on-hook, off-hook, and ringing modes. It can also be used to connect the telephone to a CID (caller identification device) through a relay and also to indicate tapping or misuse of telephone lines by sounding a buzzer.

In on-hook mode, 48V DC supply is maintained across the telephone lines. In this case, the bi-colour LED glows in green, indicating the idle state of the telephone. The value of resistor R1 can be changed somewhat to adjust the LED glow, without loading the telephone lines (by trial and error).

In on-hook mode of the hand-set, potentiometer VR1 is so adjusted that base of T1 (BC547) is forward biased, which, in turn, cuts off transistor T2 (BC108). While adjusting potmeter VR1, ensure that the LED glows only in green and not in red.


When the hand-set is lifted, the voltage drops to around 12V DC. When this

happens, the voltage across transistor T1's base-emitter junction falls below its conduction level to cut it off. As a result tran-

the telephone ring.

A CID can be connected using a relay. The relay driver transistor can be connected via point A as shown in the circuit. To use the circuit for warning against misuse, switch S1 can be left in on position to activate the piezo-buzzer when anyone tries to tap the telephone line. (When the telephone line is tapped, it's like the off-hook mode of the telephone hand-set.)

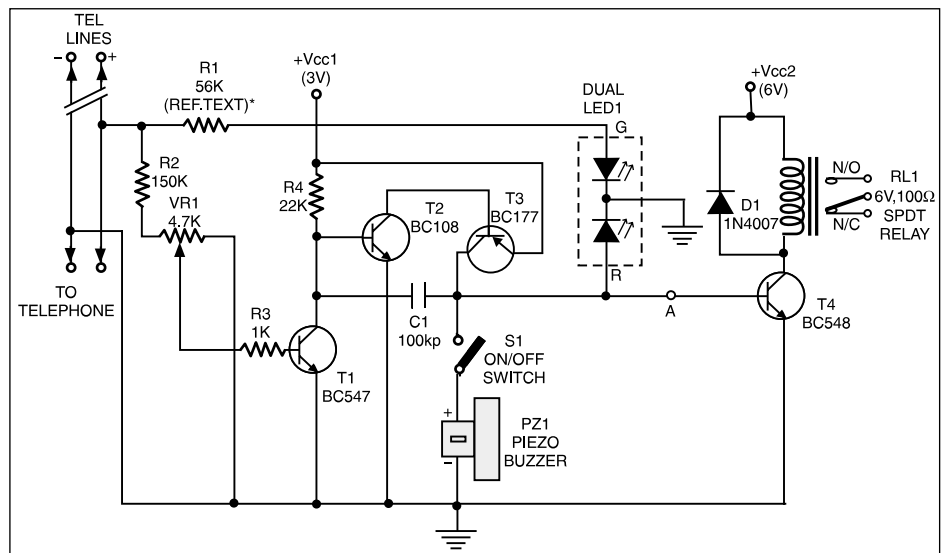Two 1.5V pencil cells can provide Vcc1 power supply, while a separate power sup-



sistor pair T2-T3 starts oscillating and the piezo-buzzer starts beeping (with switch S1 in on position). At the same time, the bi-colour LED glows in red.

In ringing mode, the bi-colour LED flashes in green in synchronisation with

ply for Vcc2 is recommended to avoid draining the battery. However, a single 6-volt supply source can be used in conjunction with a 3.3V zener diode to cater to both Vcc2 and Vcc1 supplies.

SIMPLE CODE LOCK

YASH D. DOSHI



The circuit described here is of an electronic combination lock for daily use. It responds only to the right sequence of four digits that are keyed in remotely. If a wrong key is touched, it resets the lock. The lock code can be set by connecting the line wires to the pads A, B, C, and D in the figure. For


example, if the code is 1756, connect line 1 to A, line 7 to B, line 5 to C, line 6 to D and rest of the lines—2, 3, 4, 8, and 9—to the reset pad as shown by dotted lines in the figure.

The circuit is built around two CD4013 dual-D flip-flop ICs. The clock pins of the four flip-flops are connected to A, B, C,

and D pads. The correct code sequence for energisation of relay RL1 is realised by clocking points A, B, C, and D in that order. The five remaining switches are connected to reset pad which resets all the flip-flops. Touching the key pad switch A/B/C/D briefly pulls the clock input pin high and the state of flip-flop is altered. The Q output pin of each flip-flop is wired to D input pin of the next flip-flop while D pin of the first flip-flop is grounded. Thus, if correct clocking sequence is followed then low level appears at Q2 output of IC2 which energises the relay through relay driver

transistor T1. The reset keys are wired to set pins 6 and 8 of each IC. (Power-on-reset capacitor C1 has been added at EBY during testing as the state of Q output is indeterminate during switching on operation.)

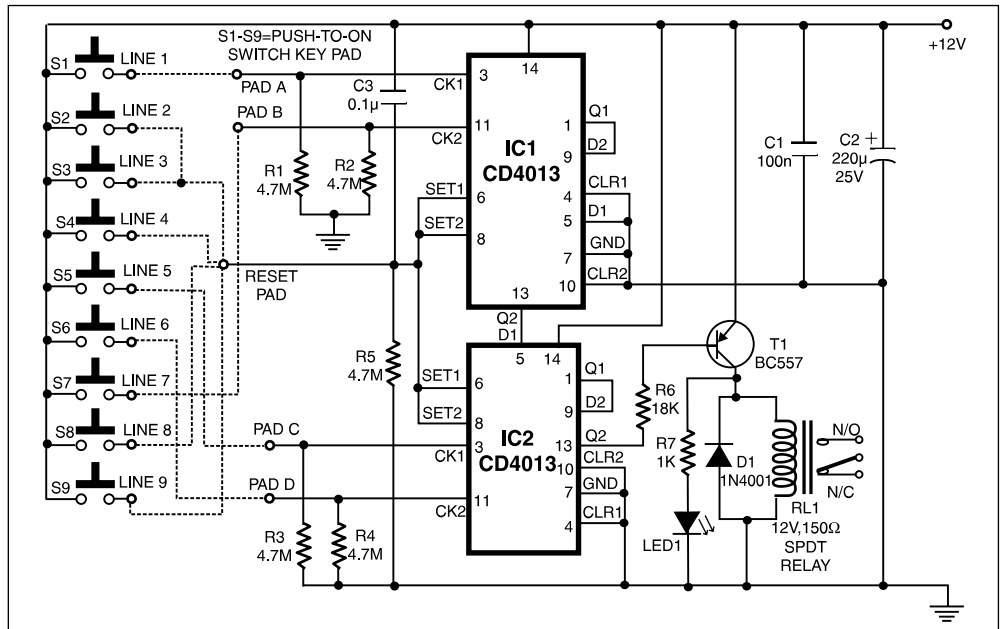This circuit can be usefully employed in cars so that the car can start only when the correct code sequence is keyed in via the key pad. The circuit can also be used in various other applications.



AUTOMATIC BATHROOM LIGHT

JAYAN A.R.



This circuit is used to automate the working of a bathroom light. It is designed for a bathroom fitted with an automatic door-closer, where the manual verification of light status is difficult. The circuit also indicates whether the bathroom is occupied or not. The circuit uses only two ICs and can be operated from a 5V supply. As it does not use any mechanical contacts it gives a reliable performance.

One infrared LED (D1) and one infrared detector diode (D2) form the sensor part of the circuit. Both the infrared LED and the detector diode are fitted on the frame of

the door with a small separation between them as shown in Fig. 1. The radiation from IR LED is blocked by a small opaque strip (fitted on the door) when the door is closed. Detector diode D2 has a resistance in the range of meg-ohms when it is not activated by IR rays. When the door is opened, the strip moves along with it. Radiation from the IR LED turns on the IR detector diode and the voltage across

a reference potential set by preset VR1. The preset is so adjusted as to provide an optimum threshold voltage so that output of IC2(a) is high when the door is closed and low when the door is open. Capacitor C1 is connected at the output to filter out unwanted transitions in out-

 


Fig. 1

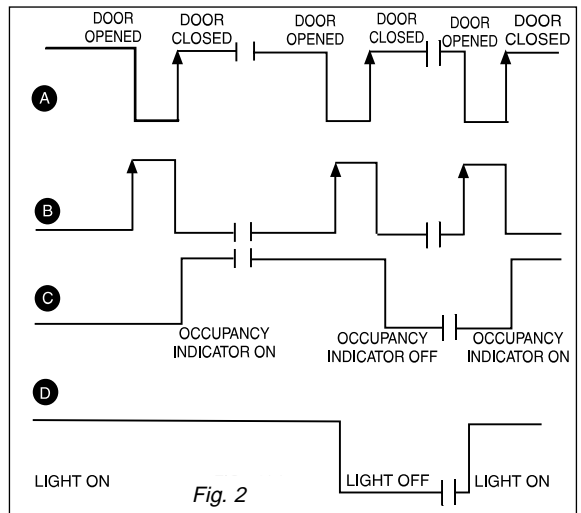


Fig. 2

it drops to a low level.

Comparator LM358 IC2(a) compares the photodetector against

put voltage generated at the time of opening or closing of the door. Thus, at point A, a low-to-high going voltage transition is available for every closing of the door after opening it. (See waveform A in Fig. 2.)

The second comparator IC2(b) does the reverse of IC2(a), as the input terminals are reversed. At point B, a low level is available when the door is closed and it

switches to a high level when the door is opened. (See waveform B in Fig. 2.) Thus, a low-to-high going voltage transition is available at point B for every opening of the door, from the closed position. Capacitor C2 is connected at the output to filter out unwanted transitions in the output voltage generated at the time of closing or opening of the door.

IC 7474, a rising-edge-sensitive dual-D flip-flop, is used in the circuit to memorise the occupancy status of the bathroom. IC1(a) memorises the state of the door and acts as an occupancy indicator while IC2(b) is used to control the relay to turn on and turn off the bathroom light. Q output pin 5 of IC1(a) is tied to D input pin 12 of IC1(b).

At the time of switching on power for the first time, the resistor-capacitor combination R3-C3 clears the two flip-flops. As a result Q outputs of both IC1(a) and IC1(b) are low, and the low level at the output of IC1(b) activates a relay to turn on the bathroom light. This operation is independent of the door status (open/closed).

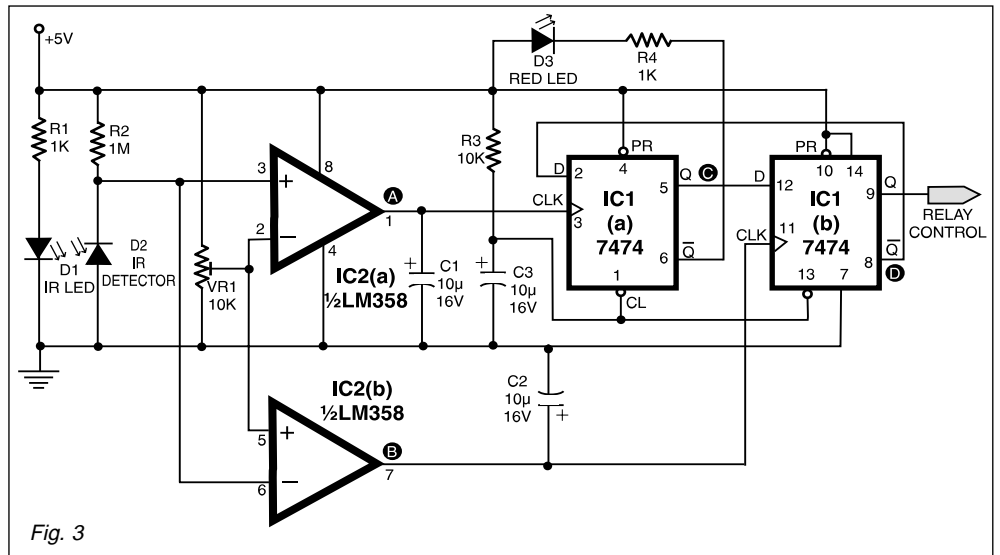


Fig. 3

The occupancy indicator red LED (D3) is off at this point of time, indicating that the room is vacant.

When a person enters the bathroom, the door is opened and closed, which provides clock signals for IC1(b) (first) and IC1(a). The low level at point c (pin 5) is clocked in by IC1(b), at the time of opening the door, keeping the light status unchanged.

The high level point d (pin 8) is clocked in by IC1(a), turning on the occupancy indicator LED (D3) on at the time of

closing of the door. (See waveform c in Fig. 2.)

When the person exits the bathroom, the door is opened again. The output of IC1(b) switches to high level, turning off the bathroom light. (See waveform d in Fig. 2.) The closing of the door by the door-closer produces a low-to-high transition at the clock input (pin 3) of IC1(a). This clocks in the low level at Q output of IC1(b) point d to Q output of IC1(a) point c, thereby turning off the occupancy indicator.

SMART FLUID LEVEL INDICATOR

THOMMACHAN THOMAS



Most of the fluid level indicator circuits use a bar graph or a seven-segment display to indicate the fluid level. Such a display using LEDs or digits may not make much sense to an ordinary person. The circuit presented here overcomes this flaw and displays the level using a seven-segment display—but with a difference. It shows each level in meaningful English letters. It displays the letter E for empty, L for low, H for half, A for above average, and F for full tank.

The circuit is built using CMOS ICs. CD4001 is a quad. NOR gate and CD4055 is a BCD to seven-segment decoder and display


driver IC. This decoder IC is capable of producing some English alphabets besides the usual digits 0 through 9. The BCD codes for various displays are given in Table I. The BCD codes are generated by NOR gates because of their interconnections as the sensing probes get immersed in water. Their operation being self-explanatory is not included here.

Note that there is no display pattern like E or F available from the IC. Therefore to obtain the pattern for letters E and F, transistors T1 and T2 are used. These transistors blank out the unnecessary segments from the seven-segment display. It can be seen that letter E is

generated by blanking 'b' and 'c' segments of the seven-segment display while it decodes digit 8. Letter F is obtained by blanking segment 'b' while it decodes letter p.

As CMOS ICs are used, the current con-

D	C	B	A	DISPLAY
L	L	L	L	0
L	L	L	H	1
—	—	—	—	2
—	—	—	—	3
—	—	—	—	4
—	—	—	—	5
—	—	—	—	6
—	—	—	—	7
H	L	L	L	8
H	L	L	H	9
H	L	H	L	L
H	L	H	H	H
H	H	L	L	P
H	H	L	H	A
H	H	H	L	—
H	H	H	H	BLANK

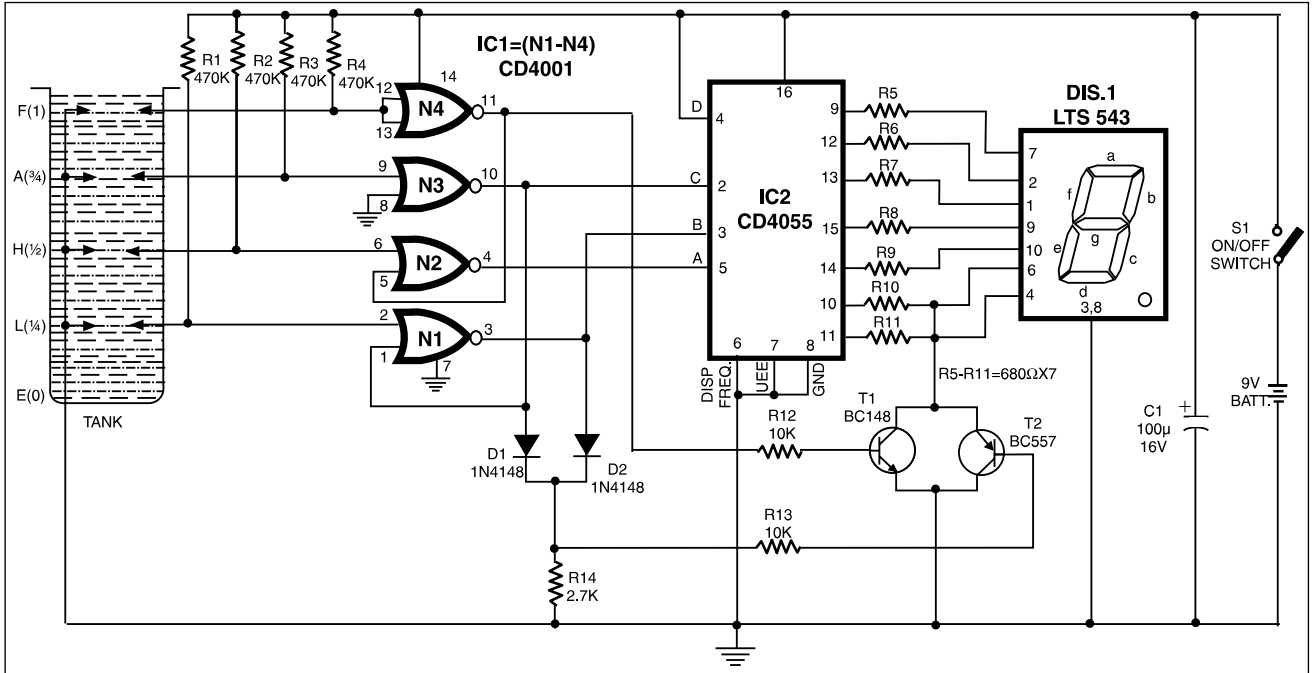

sumption is extremely low. This makes it possible to power the circuit from a battery. The input sensing current through the fluid (with all the four probes im-

mersed in water) is of the order of 70 μ A, which results in low rate of probe deterioration due to oxidation as also low levels of electrolysis in the fluid.

Note: This circuit should not be used with inflammable or highly reactive fluids.

AUTOMATIC SCHOOL BELL SYSTEM



Dr D.K. KAUSHIK


This is an effective and useful project for educational institutions. In most schools and colleges, the peon rings the bell after every period (usually of a 40-minute duration). The peon has to depend on his wrist watch or clock, and sometimes he can forget to ring the bell in time. In the present system, the human error has been eliminated. Every morning, when the school starts, someone has to just switch on the system and it thereafter work automatically.

The automatic microprocessor controlled school bell system presented here

has been tested by the author on a Vynitics' microprocessor-8085 kit (VMC-8506). The kit displays the period number on two most significant digits of address field and minutes of the period elapsed on the next two digits of the address field. The data field of the kit displays seconds continuously.

The idea used here is very simple.

The programmable peripheral interfacing (PP) Intel-8255-1 chip present in the microprocessor kit has been used. It has three 8-bit wide input/output ports (port A, port B, and port C). Control word 80 (hex) is used to initialise all ports of 8255-1 as output ports. Bit 0 of port A (PA_0) is connected to the base of transistor BC107 through a 10-kilo-ohm resistor as shown in the figure. It is used to energise the relay when PA_0 pin of 8255-1 is high. A siren, hooter, or any bell sound system with an audio amplifier of proper wattage (along with 2 or 3 loudspeakers) may be installed in the school campus. The relay would get energised after every 40 minutes for a

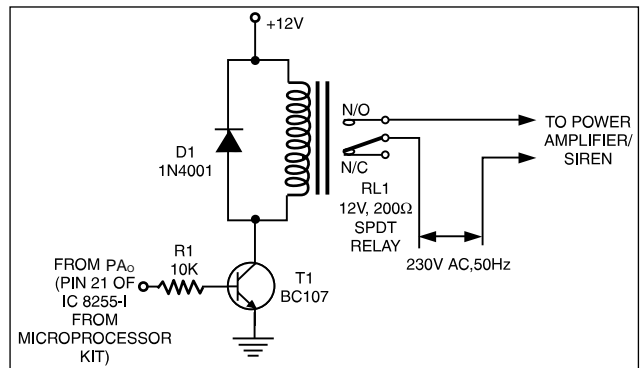

few seconds. The program (software) and data used for the purpose are given below in mnemonic and machine code forms. The program is self-explanatory.

The program and data have been entered at specific memory locations. However, the readers are at liberty to use any other memory area in their kits, depending on their convenience. Two monitor programs (stored in kit's ROM/EPROM) at locations 0347H (for clearing the display) and 05D0H (for displaying contents of memory locations 2050H through 2055 in the address and data fields respectively)

have been used in the program. Please note that before calling the display routine, registers A and B are required to be initialised with either 00 or 01 to indicate to the monitor program as to where the contents of above-mentioned memory locations are to be displayed (e.g. address field or data field), and whether a dot is to be displayed at the end of address field or not. (Readers should refer to their kit's documentation before using the display routine.) In Vinytics' kit, if register A contents are 00, the address field is used for display, and if it is 01, the

data field is used for display. Similarly, if register B contains 00 then no dot is displayed at the end of address field, else if B contents are 01, a dot is displayed.

When the program is executed on the microprocessor kit, a bell sound would be heard for a few seconds. The address and data fields would initially display :

01 00 00

01 indicates start of first period with 00 as elapsed minutes and 00 seconds in the data field. The data field (seconds) are continuously incremented.

Address	Op-code	Label	Mnemonic	Comments	Address	Op-code	Label	Mnemonic	Comments
20 FC	3E 80		MVI A, 80H	Initialise 8255-1 as output port	21 66	3E 04	SS	MVI A, 04	Put A=4
20 FE	DE 03		OUT 03 H		21 68	77		MOV M, A	
2100	31 FF 27		LXI SP, 27FFH	Initialise the stack pointer	21 69	AF	TT	XRA A	A=0
2103	CD 47 03		CALL 0347H	Clears the display	21 6A	47		MOV B,A	B=0
2106	C3 69 21		JMP TT	Jump to ring the bell	21 6B	21 50 20		LXI H, 2050H	
2109	AF	AA	XRA A	Put A=0	21 6E	CD D0 05		CALL 05D0H	Display the period no. and minutes in address field
210 A	47		MOV B, A	Put B=0	21 71	3E 01		MVI A, 01H	A=1
210 B	21 50 20		LXI H, 2050 H	Starting address of display	21 73	06 00		MVI B, 00H	B=0
210 E	CD D0 05		CALL 05D0H	Call output routine to display period no. & minutes to address field	21 75	21 54 20		LXI H, 2054 H	
21 11	3E 01		MVI A, 01H	A=01	21 78	CD D0 05		CALL 05D0 H	Display the seconds in data field
21 13	06 00		MVI B, 00H	B=00	21 7B	3E 01		MVI A, 01H	
21 15	21 54 20		LXI H, 2054H	Current sec.	21 7D	D3 00		OUT 00H	Exite the 8255:1 for engergising the relay (rings the bell)
21 18	CD D0 05		CALL 05D0H	Address of LSD of current sec.	21 7F	21 55 20		LXI H, 2055H	
21 1B	21 55 20		LXI H, 2055H		21 82	3E 00		MVI A, 00H	Stores 00 to memory location
21 1E	7E		MOV A, M	Move the LSD of current sec. to acc.	21 84	77		MOV M, A	2055 to
21 1F	C6 01		ADI 01 H	Add 01 to acc.	21 85	2B		DCX H	2052 H
21 21	FE 0A		CPI 0AH	Compare LSD of sec. with 0AH (10 decimal)	21 86	77		MOVM, A	
21 23	CA 36 21		JZ RR	If LSD completes 09 jump to RR	21 87	2B		DCX H	
21 26	77		MOV M, A	Move the acc. content to 20 55 H location	21 88	77		MOV M, A	
21 27	06 02	DD	MVI B, 02H	Delay	21 89	2B		DCX H	
21 29	11 00 FA	YY	LXI D, FA00H	Sub-	21 8A	77		MOV M,A	
21 2C	CD 00 25		CALL 2500H	Routine	21 8B	2B		DCXH	
21 2F	05		DCR B	For	21 8C	7E		MOV A, M	Brings the LSD current period no. to acc
21 30	C2 29 21		JNZ YY	1 second	21 8D	C6 01		ADI 01	Add 1 to it compare with OA
21 33	C3 09 21		JMP AA	After delay of 1 sec. Jump to AA for display the time	21 8F	FE 0A		CPI 0A	
21 36	3E 00	RR	MVI A, 00H	A=0	21 91	CA 98 21		JZ XX	If LSD of period no. complete 09 then jump to XX
21 38	77		MOV M, A	Store Acc. To memory location	21 94	77		MOVM, A	Else store it to memory location
21 39	2B		DCX H	Decrement HL pair content	21 95	C3 A0 21		JMP XY	Jump to XY
21 3A	7E		MOV A, M	Move the MSD of sec to acc.	21 98	3E 00	XX	MVI A, 00H	A=0
21 3B	C6 01		ADI 01H	Add 01 to Acc.	21 9A	77		MOV M,A	Store it to main location
21 3D	FE 06		CPI 06H	Compare MSD of sec with 06H	21 9B	2B		DCX H	
21 3F	CA 46 21		JZ UU	If sec. complete 59 move to UU	21 9C	7E		MOV A, M	Store MSD of period no. to acc
21 42	77		MOV M, A	Store acc. content to memory location	21 9D	C6 01		ADI 01H	Add 1 to it
21 43	C3 27 21		JMP DD	Jump for delay of 1 sec.	21 9F	77	XXX	MOV M,A	Store it memory location
21 46	3E 00	UU	MVI A, 00	Put A=00 after completing 59 seconds	21 A0	06 02	XY	MVI B, 02	
21 48	77		MOV M,A		21 A2	11 00 FA	XYZ	LXI D, FA 00H	Program 1 sec display
21 49	2B		DCX H		21 A5	CD 00 25		CALL 2500 H	
21 4A	7E		MOV A,M	Move current LSD of minutes to acc.	21 A8	05		DCR B	
21 4B	C6 01		ADI 01H	Add 01 to acc.	21 A9	C2 A2 21		JNZ XYZ	
21 4D	FE 0A		CPI 0A	Compares acc. to 0A H	21 AC	AF		XRA	A=0
21 4F	CA 56 21		JZ VV	Jump to VV if LSD of minutes completes 09	21 AD	47		MOV B,A	B=0
21 52	77		MOV M,A	Move acc. to memory location	21 AE	21 50 20		LXI H, 2050H	
21 53	C3 27 21		JMP DD	Jump for delay of 1 sec.	21 B1	CD D0 05		CALL 05D0H	
21 56	3E 00	VV	MVI A,00H		21 B4	3E 01		MVI A, 01H	
21 58	77		MOV M,A		21 B6	06 00		MVI B, 00H	Program to display
21 59	2B		DCX H	Decrement H-L pair content	21 B8	21 54 20		LXI H, 2054 H	The period no.
21 5A	7E		MOV A,M	Move MSD of minutes to acc.	21 BB	CD D0 05		CALL 05 D0 H	Minutes and second
21 5B	C6 01		ADI 01H	Add 01 to acc.	21 BE	21 55 20		LXI H, 2055H	
21 5D	FE 04		CPI 04H	Compare acc. content with 04 H	21 C1	7E		MOV A, M	LSD of stored current second to acc
21 5F	CA 66 21		JZ SS	If minutes 40 then jump to SS	21 C2	C6 01		ADI 01H	Add 1 to it
21 62	77		MOV M,A		21 C4	FE 06		CPI 06H	Compare with 06
21 63	C3 27 21		JMP DD	Jump for delay of 1 sec	21 C6	C2 9F 21		JNZ XXX	If not 06 jump to XXX
					21 C9	3E 00		MVIA, 00H	A=0
					21 CB	D3 00		OUT 00H	Output to 8255 to de-energise the relay

Address	OP CODE	LABEL	Mnemonic	Comments
21 CD	C3 09 21		JMP AA	Repeat for next period
DELAY SUBROUTINE				
25 00	1B	NEXT	DCX D	
25 01	7A		MOV A, D	
25 02	B3		ORA E	
25 03	C2 00 25		JNZ NEXT	
25 06	C9		RET	

Address	OPCODE	LABEL	Mnemonic	Comments
DATA				
20 50	00			MSD of period no.
20 51	00			LSD of period no.
20 52	00			MSD of minutes
20 53	00			LSD of minutes
20 54	00			MSD of seconds
20 55	00			LSD of seconds

DESIGNING AN RF PROBE



N.S. HARISANKAR, VU3NSH

Radio frequency probe is used to directly measure the level of RF RMS voltage present across two points. It is one of the most useful test instruments for home brewers as well as for communication equipment service/design labs.

RF voltage level being measured provides useful information only when the probe has been designed for use with a specific multimeter. The design of RF probe is a function of the meter we intend to use it with. If a meter with a different input resistance is used with the probe, the reading will be incorrect. The value of R_x (refer figure) is so chosen that when this resistor is connected in parallel with input resistance of the multimeter, the peak value is about 1.414 times the RMS voltage. Resistor R_x has to drop this excess voltage so that meter indication is accurate. If we know the input resistance of the meter, we can calculate the value of R_x with the help of the following relationship:

Let meter DC input resistance

$$X \cdot 1.414 = R_y$$

Then $R_x = R_y - \text{meter DC input resistance}$

For example, if meter input resistance is 20 meg-ohm, $R_y = 28.28$ meg-ohm and $R_x = 8.28$ meg-ohm.

We can convert the RF voltage level

TABLE I
Voltage to Watts Conversion for 50 ohms Termination

RMS (V)	RF Power (W)
2.24	0.1
3.88	0.3
5.0	0.5
7.08	1
12.25	3
15.90	5
20.0	8
22.4	10
38.75	25
41.85	35
50.0	50

In other words, for 5-watt power in a 50-ohm load, the voltage across the load is 15.85 volts.

The rectified DC voltage at the cathode of diode D1 is at about the peak level of the RF voltage at the tip of the probe. Use shielded cable in between the probe output and meter. It will act as feed-through capacitance and thus avoid RF interference. The maximum RF input voltage level depends on the peak inverse voltage (PIV) of diode D1. The shielded lead length is too large to give accurate results at UHF. Please refer Tables I and II


Table II

Meter DC Impedance	R_x
20 Meg-ohm	8.25 Meg-ohm
10 Meg-ohm	4.14 Meg-ohm
1 Meg-ohm	41.4 kilo-ohm
20 kilo-ohm	8.28 kilo-ohm

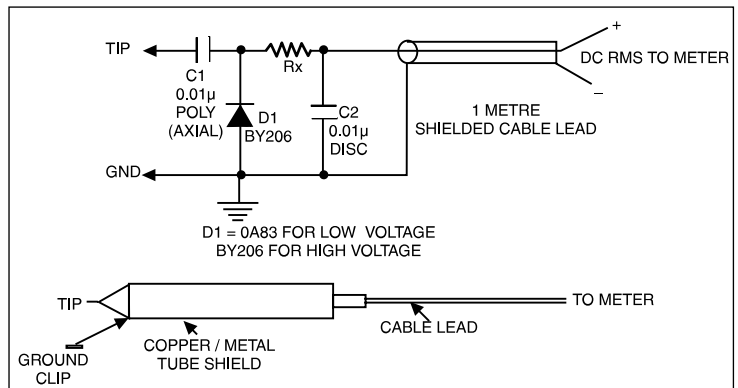(E) so measured across a given load resistance (R) to RF watts (W) using the following relationship:
Power P = E^2 / R watts (W)

For example, if RF probe voltage reading across a load resistance of 50 ohms is found to be, say, 15.85 volts, the power in the load = $15.85 \times 15.85 / 50 = 5W$ approx.

for ready conversion of RF voltage level (RMS) to equivalent power across a 50-ohm load and deduction of R_x value for a given meter's DC input resistance respectively.



February

2000

PC BASED SPEED MONITORING SYSTEM

SANTHOSH JAYARAJAN

This project describes the software and hardware necessary to monitor and capture in real time the speed of any rotating object. The speed may be defined/stored/displayed in any of the three units: RPM (rev./minute), RPS (rev./second), or RPH (rev./hour). The system uses a sampling time of two seconds and can store up to 16 minutes of data per file. The x and y axes can be scaled to read any speed and the x-axis can be 'stretched' to observe clustered points.

The hardware mainly comprises a proximity switch whose output is connected to the printer (LPT1) port of the computer through an optocoupler. The proximity switch is used as a speed-sensor. The program is written in C++ and has effective error handling capability and a help facility. This system can be used to monitor the speed of rotating parts in the industry or to read and record wind speeds.

The hardware interface

The hardware interface circuit is given in Fig. 1. A 230V AC primary to 0-9V, 250mA secondary transformer followed by IC 7805 is used for catering to the power supply requirement for proximity switch and the opto-coupler. The proximity switch, as shown in Fig. 2, is a 3-wire switch (e.g. PG Electronics' EDP101) which operates at 6V to 24V DC.

The inductive type proximity switch senses any metal surface from a distance of about 5 mm to 8 mm. Thus, a gear or fan blade is ideal for counting the number of revolutions. The number of teeth that trigger (switch-on) the proximity switch during every revolution are to be known for the software to calculate the speed of

the machinery. The output of the circuit, available across resistor R2, is fed to the PC via 25-pin 'D' connector of parallel port LPT1. Pin 11 pertains to data bit D7 of the input port 379(hex) of the LPT1 port having base address 378(hex), and pin 25 is connected to PC ground. (In fact, pins 18 through 25 of the parallel port are strapped together and connected to ground.)

The proximity switch is mounted on a stationary part, such as a bolt or stud, in such a way that it senses each tooth of the rotating part as shown in Fig. 3. Two fixing nuts are provided on the threaded

As interface circuit can easily be wired on any general-purpose PCB, no PCB layout is included for it. The two wires to be extended to 25-pin parallel port may be connected using a 25-pin male 'D' connector.

Lab Note: Magnetic proximity switches, from various manufacturers, are available in the market. The important specifications include operating DC voltage range, operating current and its sensitivity, i.e. the maximum distance from a metallic object such that the switch operates. These specifications are normally mentioned on the proximity switch itself or in the accompanying literature.

The software

The structural block diagram of the software is shown in Fig. 4. The software has the following four main modules, which are activated from the main menu using four of the function keys, F1 through F4.

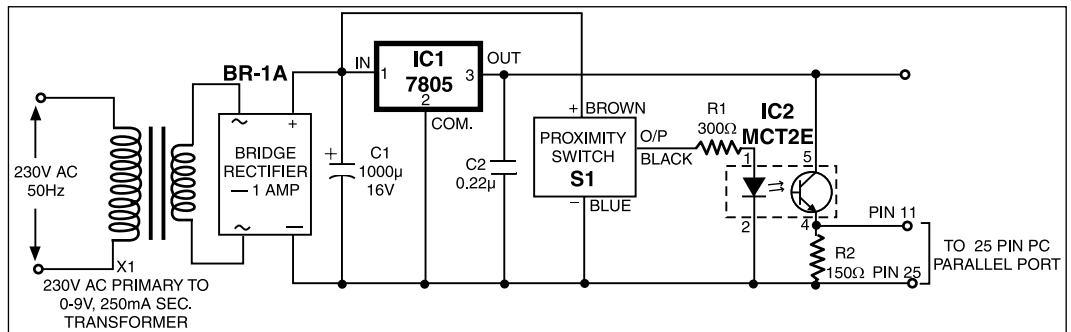


Fig. 1: Interface circuit for PC based speed monitoring system

body of the proximity switch for securing it firmly onto a fixed part of the machinery.

The software prompts the operator to enter the number of teeth (being sensed during every revolution), which is used by the program for calculation of RPM, RPS, or RPH, as the case may be. In any specific application, where non-metallic rotating parts are present and inductive proximity switch cannot be used, one may use photoelectric switch to do the counting for 2-second sampling period.

 


Fig. 2: Proximity switch

 


Fig. 3: Mounting of proximity switch

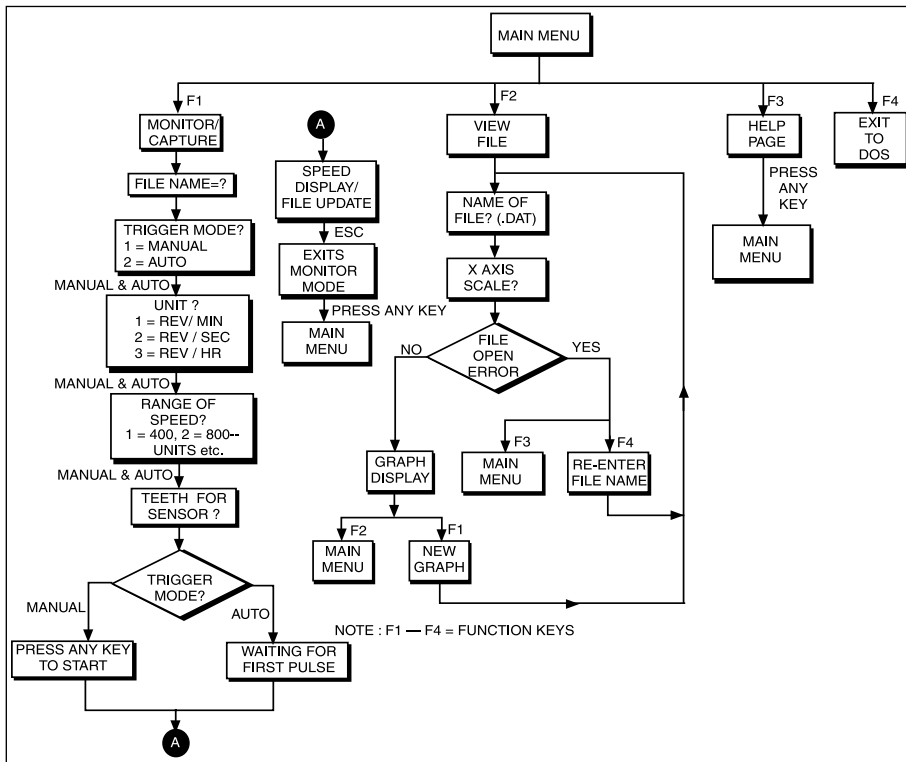


Fig. 4: Structural block diagram of software

PARTS LIST	
<i>Semiconductors:</i>	
IC1	- 7805 regulator 5V
IC2	- MCT2E opto-coupler
<i>Resistors (all 1/4 watt, ± 5% metal/carbon film, unless stated otherwise)</i>	
R1	- 300-ohm
R2	- 150-ohm
<i>Capacitors:</i>	
C1	- 1000µF, 16V electrolytic
C2	- 0.22µF polyester
<i>Miscellaneous:</i>	
X1	- 230V AC primary to 0-9, 250mA sec. transformer
BR-1A	- Bridge rectifier, 1-amp.
S1	- Proximity switch (refer text)

the system waits for the first pulse from the proximity switch to start monitoring and capturing of data.

(c) The next entry relates to 'units', which has the following further options:

- 1 = Revolutions/min.
- 2 = Revolutions/sec.
- 3 = Revolutions/hr

(d) The next entry pertains to the 'range of speed,' which must be more than the maximum speed that is expected. The options are:

- 1 = 400 units
- 2 = 800 units, etc

(e) The next entry concerns the 'number of teeth' and represents the number of pulses from the proximity switch per revolution.

After making the above entries, the following message is displayed on the monitor screen:

"Trigger mode: Auto (or Manual) Waiting for first pulse (or Press any key to start)" depending on the trigger mode. If manual mode has been selected, then hit any key to start. If auto mode is selected, the software waits for the first pulse from the proximity sensor to proceed. The display then shows the speed in the units selected and the capture file name. Pressing ESC exits the monitor mode after closing the capture file. Pressing any other key returns to main menu.

2. Viewing a graph file. This module is used to view an existing data file. Sequential contents of a DEMO.DAT file are shown in a box (using eight columns). If a non-existent filename is entered, the software detects the opening error and prompts the user for re-entering the filename. The various prompts for entering the required data are:

(a) File name - Enter the full filename

HELPS.PG1 file contents

+++SPEED MASTER HELP PAGE+++

This software can be used to capture and monitor the speed of any rotating part for a maximum of eight minutes with a total sampling time of two seconds. The software has four menu levels which can be selected from the Main Menu.

In Capture/Monitor mode the software has two trigger modes, viz, Manual, which waits for a key press and Auto, which waits for the first pulse from the sensor.

The captured file can be viewed in any X-axis scale. However, all points coming out of the view page are clipped off.

When using the gear teeth for speed calculation, please enter the teeth per revolution to enable internal calculation of speed to be made.

Enter the filename where the data is to be stored, when prompted. The same file can be viewed in the view page option. If an invalid file name is entered, or the file cannot be opened, an error is displayed and the user can exit to Main.

...Press Any Key to Return to Main...

1. Speed monitor and capture module. This module is used to monitor the speed and store the data in a user-defined file.

(a) The module first prompts for the filename. The file name is entered with an extension .DAT.

(b) The next entry is called 'trigger mode'. It specifies how the software should start monitoring and capturing data. The options are: 1 = manual and 2 = auto. If option 1 is selected, the system waits for a key press to start the monitoring and capturing operation.

If option 2 (auto mode) is selected,

FILE Contents of DEMO.DAT Showing Rev./min.							
1	0	0	0	0	0	0	0
15	0	0	0	0	0	0	0
0	0	0	15	0	0	0	0
0	0	0	30	0	0	0	0
0	0	0	0	0	15	0	0
0	15	0	90	0	15	0	0
0	15	0	0	0	0	0	0
0	120	0	0	0	0	0	15
30	30	0	0	30	0	0	0
0	150	0	0	0	0	0	0
30	0	0	0	0	0	0	15
0	30	0	0	0	0	0	0
0	0	0	0	0	0	0	0
0	15	60	0	0	15	0	0
30	150	0	0	0	0	0	0
0	0	0	0	0	15	0	0

with extension.

(b) Enter the x-axis scale factor to enable the graph to be 'stretched' on the x-axis to observe cramped points properly. After entering the x-axis scale, the graph appears along with all relevant data, like scale factors for x and y axis, file name,

and units, etc.

(c) While still in the graph mode, you may view a new graph after pressing F1. For returning to the main menu, press F2.

3. Help. This module provides one page of help and reads from a file called

HELPS.PG1. If this file cannot be opened, or is not available, the software prompts with "Help file not found or cannot be opened." Pressing any key from the help page returns one to main menu. The contents of HELPS.PG1 are given in the box (on previous page).

Program Listing for SPEEDM.CPP

```
#include<conio.h>
#include<iostream.h>
#include<graphics.h>
#include<dos.h>
#include<stdio.h>
#include<time.h>
#include<fstream.h>
#include<process.h>
#include<stdlib.h>
void startgraphics();//start graphics system//
void openingmenu();//opening menu//
void monitor();//monitor and save to file//
float readspeed(int unit,int teeth);//read the speed//
void display(int unit);//display the speed//
void view();//View a Speed vs Time Graph//
void grid();//Draw the graph grid//
void displayhelp(char helpfilename[10]);
void exiit();
void help();
int roundoff(float number);
//Global Variables//
int unit;int teeth;
float speed;
char monitorfile[8];
int gdriver;int gmode;
int mid;
//Program main menu//
void main()
{
startgraphics();
openingmenu();
}
//Graphics initialisation//
void startgraphics()
{
registerbgidriver(EGAVGA_driver);
registerbgiFont(small_font);
registerbgiFont(triplex_font);
int gdriver = DETECT, gmode;
initgraph(&gdriver, &gmode, "");
}
//Opening menu//
void openingmenu()
{
setfillstyle(LTSLASH_FILL,5);
bar(10, 10, 635, 470);
setlinestyle(SOLID_LINE,0,2);
rectangle(10,10,635,470);
setlinestyle(SOLID_LINE,0,2);
rectangle(200,40,400,90);
setcolor(BLUE);
line(200,91,400,91);
line(200,92,400,92);
line(401,90,401,40);
settextstyle(2,HORIZ_DIR,8);
setcolor(YELLOW);
outtextxy(220,50,"SPEED TRACK");
setcolor(LIGHTBLUE);
outtextxy(150,120,"1.SPEED MONITOR & CAPTURE - F1");
setcolor(LIGHTRED);
outtextxy(150,180,"2.VIEW SPEED vs TIME GRAPH - F2");
setcolor(LIGHTMAGENTA);
```

```
outtextxy(150,240,"3.SPEED TRACK HELP - F3");
setcolor(LIGHTCYAN);
outtextxy(150,300,"4.EXIT TO SHELL - F4");
setcolor(LIGHTGREEN);
outtextxy(180,360,"Enter your choice ");
outtextxy(200,383,“(F1 TO F4) ”);
USERCHOICE:
while(!kbhit())
{
char userchoice=getch();
switch(userchoice)
{
case (char(59)):monitor();break;
case (char(60)):view();break;
case (char(61)):help();break;
case (char(62)):exiit();break;
default:goto USERCHOICE;
}
}
//Monitoring the speed online and storing the data//
void monitor()
{
int s;int t;
int trigger;
int yrange;
char unitf[8];
int speedf;
restorcrtmode();
clrscr();
window(1,1,80,25);
clrscr();
textcolor(YELLOW);
textbackground(LIGHTBLUE);
gotoxy(25,3);
printf(" - S P E E D T R A C K -");
gotoxy(25,4);
printf("=====");
gotoxy(25,6);
printf("MONITOR & CAPTURE PAGE");
window(10,8,75,8);
textcolor(YELLOW);
clrscr();
printf("Enter file name to store Speed data (*****) - ");
scanf("%8s", &monitorfile);
GETTRIGGER:
textcolor(YELLOW);
clrscr();
printf("Enter trigger mode(1=Manual,2=First pulse) - ");
scanf("%d", &trigger);
if(trigger<1 || trigger>2)
{
clrscr();
textcolor(YELLOW+BLINK);
printf(".....Value out of range,Enter 1 or 2.....");
delay(2000);
goto GETTRIGGER;
}
GETUNIT:
textcolor(YELLOW);
```

```
clrscr();
printf("Enter Unit for Speed(1=Rev/min,2=Revs/sec,3=Revs/Hr) - ");
scanf("%d", &unit);
if(unit<1 || unit>3)
{
textcolor(YELLOW+BLINK);
clrscr();
printf(".....Value out of range..... ");
delay(2000);
goto GETUNIT;
}
GETRANGE:
textcolor(YELLOW);
clrscr();
printf("Enter Range for Speed(1=400 units, 2=800 units.etc) - ");
scanf("%d", &yrange);
if(yrange<1 || yrange>100)
{
textcolor(YELLOW+BLINK);
clrscr();
printf(".....Value out of range..... ");
delay(2000);
goto GETRANGE;
}
GETTEETH:
textcolor(YELLOW);
clrscr();
printf(" Enter Number of teeth for Sensor - ");
scanf("%d", &teeth);
if(teeth<1 || teeth>100)
{
textcolor(YELLOW+BLINK);
clrscr();
printf(".....Value out of range..... ");
delay(2000);
goto GETTEETH;
}
//Open the file for data storage
fstream infile;
infile.open(monitorfile,ios::out);
//Store the units
char *unitf1 = "Rev/min";
char *unitf2 = "Rev/sec";
char *unitf3 = "Rev/hr";
switch(unit)
{
case 1:infile<<unitf1<<endl;break;
case 2:infile<<unitf2<<endl;break;
case 3:infile<<unitf3<<endl;break;
}
//Entering the units and y scale to capture file//
//fstream infile;
//infile.open(monitorfile,ios::out);
infile<<yrange<<endl;
clrscr();
//Setting the trigger mode//
switch(trigger)
{
case 1:textcolor(YELLOW+BLINK);printf("Trigger mode: Manual ..Press any key to Start");getch();break;
case 2:textcolor(YELLOW+BLINK);printf("Trigger mode: Auto..Waiting for first pulse..");
```

```

s=inp(0x379);t=s;while(s==t)s=inp(0x379);break;
default:texcolor(YELLOW+BLINK);cprintf
("Trigger mode: Manual ..Press any key to
Start"); getch();break;
}
startgraphics();
for(int pointno=1;pointno<481;++pointno)
{
char in;
display(unit);
speedf=roundoff(speed);
infile<<speedf<<endl;
if (kbhit())
{
if ((in = getch()) == '\x1B')break;
}
infile.close();//Close the file,clean up and return
to main//
restorecrtmode();
window(10,8,75,8);
textcolor(YELLOW+BLINK);
cprintf("Data Capture Interrupted or File full(960
sec)..Press any key..");
getch();
startgraphics();
openingmenu();
}
//Read the speed and convert into the asked
units//
float readspeed(int unit,int teeth)
{
int sett=255;int tes=255;mid=0;
clock_t start, end=0;
sett=inp(0x379);
tes=sett;
for(start=clock();(end-start)/CLK_TCK<2.0;
end=clock())
{
sett=inp(0x379);
if(sett!=tes)++mid;
tes=sett;
}
//Calculation of the speed depending on unit
selected//
switch(unit)
{
case 1:return(mid*15.0/(teeth));
case 2:return(mid/(4.0*teeth));
case 3:return(mid*900.0/teeth);
default:return(mid/(4.0*teeth));
}
}
//Display the speed on the screen update every 2
secs//
void display(int unit)
{
char msgd[80];
char msgf[80];
fstream infile;
setcolor(LIGHTRED);
setbkcolor(LIGHTGREEN);
settextstyle(1,HORIZ_DIR,4);
rectangle(5,5,630,470);
outtextxy(175,30,"SPEED MASTER");
moveto(150,400);
outtext("Press ESC to exit....");
outtextxy(150,300,"Capture file =");
sprintf(msgf, "%s", monitorfile);
outtextxy(400,300,msgf);
moveto(150,100);
outtext("Speed ");
switch(unit)
{
case 1:outtextxy(250,100,"in Revs/Min");break;
case 2:outtextxy(250,100,"in Revs/Sec");break;
case 3:outtextxy(250,100,"in Revs/Hr");break;
}
}
speed=readspeed(unit,teeth);
cleardevice();
sprintf(msgd, "%f", speed);
outtextxy(250,200,msgd);
}
void view()//View a speed vs time graph//
{
VIEWSTART:
closegraph();
int xscale=1;int yscale;
char msgx[2];char msgmaxy[5];char msgmaxx
[5];char msgy[2];char msgun[8];char gunits[8];
char msgfile[10];
char filename[8];
char msgpoint[5];
int coordinate[10000];
int errorcode;
fstream infile;
window(1,1,80,25);
clrscr();
textcolor(RED);
textbackground(BLUE);
gotoxy(25,3);
cprintf(" - S P E E D M A S T E R - ");
gotoxy(25,5);
cprintf(" VIEW FILE PAGE ");
window(10,8,50,8);
textcolor(YELLOW);
clrscr();
cprintf(" Enter name of file to view - ");
scanf("%8s", &filename);
scalefactor:
int i=0;int pointcount=0;
XAXIS:
clrscr();
cprintf(" Enter X axis scale factor - ");
scanf("%d", &xscale);
if(xscale<0 | xscale>9) goto XAXIS;
infile.open(filename,ios::in);
if(infile.fail())
{
window(10,8,70,9);
textcolor(YELLOW+BLINK);
clrscr();
cprintf("..Error opening file or file does not
exist..\n\r Press F3 to exit,F4 to re-enter ");
ERRORGRAPH:
while (!kbhit())
{
char choicegraph;
choicegraph=getch();
switch(choicegraph)
{
case (char(62)):goto VIEWSTART;
case (char (61)):main();break;
default:goto ERRORGRAPH;
}
}
infile>>gunits>>yscale;
while(!infile.eof())
{
infile>>coordinate[i];
++;
++pointcount;
}
infile.close();
startgraphics();
cleardevice();
setcolor(CYAN);
setbkcolor(DARKGRAY);
rectangle(10,40,490,440);
settextstyle(2,HORIZ_DIR,6);
outtextxy(140,15,"Speed Master..GRAPH VIEW
PAGE..");
setcolor(GREEN);
outtextxy(492,40,"Graph Variables");
}
outtextxy(492,60,"X scale =");
outtextxy(492,75,"Y scale =");
outtextxy(492,90,"Units = ");
outtextxy(492,105,"File = " );
outtextxy(492,120,"Points = " );
setcolor(GREEN);
outtextxy(492,150,"Options:");
outtextxy(492,165,"F1= New Graph");
outtextxy(492,180,"F2= Main Menu");
outtextxy(492,210,"NOTE:");
outtextxy(492,225,"X axis=960sec");
outtextxy(492,240,"Y axis=400units");
outtextxy(492,255,"For Xscale=1");
outtextxy(492,270,"and Yscale=1");
setcolor(YELLOW);
sprintf(msgx, "%d", xscale);
outtextxy(580,60, msgx);
sprintf(msgy, "%d", yscale);
outtextxy(580,75, msgy);
sprintf(msgun, "%s", gunits);
outtextxy(580,90, msgun);
sprintf(msgfile, "%5s", filename);
outtextxy(565,105, msgfile);
sprintf(msgpoint, "%d", pointcount);
outtextxy(567,120, msgpoint);
sprintf(msgmaxx, "%d", (960/xscale));
outtextxy(480,450,msgmaxx);
sprintf(msgmaxy, "%d", (400*yscale));
outtextxy(10,20,msgmaxy);
outtextxy(60,20,msgun);
outtextxy(480,460,"Seconds");
grid();
setviewport(10,40,490,440,1);
setcolor(GREEN);
int x1=0;int y1=0;
int j;
for (j=0;j<pointcount-1;++j)
{
line(x1*xscale,400-y1/yscale,(j+1)*xscale,400-
coordinate[j]/yscale);
x1=j+1;
y1=coordinate[j];
}
GRAPHMENU:
while (!kbhit())
{
char choiceg;
choicég=getch();
switch(choicég)
{
case (char(59)):goto VIEWSTART;
case (char (60)):closegraph();main();break;
default:goto GRAPHMENU;
}
}
//To draw the graph grid//
void grid()
{
int i;
setcolor(RED);
for(i=140;i<440;i=i+100)
line(10,i,490,i);
setcolor(BLUE);
for (i=70;i<490;i=i+60)
line(i,40,i,440);
}
//Main help call function//
void help()
{
closegraph();
clrscr();
displayhelp("HELPS.PG1");
getch();
}
//Exit to shell with graphics clean up//
void exiti()
{
}

```

C O N S T R U C T I O N

```
cleardevice();
setbkcolor(LIGHTGREEN);
setcolor(RED);
moveto(150,200);
outtext("Exiting to DOS.");
delay(2000);
closegraph();
exit(1);
}
//Display the helpfile if resident or else indicate
  error//
void displayhelp(char helpfilename[10])
{
fstream infile;
textbackground(BLACK);
window(1,1,80,25);
textcolor(LIGHTRED);
const int max=80;
char buffer[max];
clrscr();
```

```
infile.open(helpfilename,ios::in);
if(infile.fail())
{
window(10,8,70,9);
textcolor(YELLOW+BLINK);
clrscr;
cprintf(".....HELP NOT AVAlABLE OR ERROR
OPENING FILE.....\n\r ....Press any KEY TO
RETURN TO MAIN....");
getch();
main();
}
while(!infile.eof())
{
infile.getline(buffer,max);
cout<<buffer;
cout<<endl;
}
infile.close();
getch();
```

```
main();
}
//Function to round off the float number to the
nearest integer//
int roundoff(float number)
{
int quotient;
float result;
quotient=int(number);
result=number-quotient;
if(result>0.5)
{
return(quotient+1);
}
else
{
return(quotient);
}
}
```

□

STEREO CASSETTE PLAYER



REJO G. PAREKKATTU

An electronics hobbyist always finds pleasure in listening to a song from a cassette player assembled with his own hands. Here are the details of a stereo cassette player with the following features, which many electronics enthusiasts would love to assemble and enjoy:

1. Digital 4-function selector (radio, tape, line input, and transmit).
2. Four sound modes (normal, low boost, hi-fi, and x-bas).
3. Bass and treble controls.
4. Function and output level displays.
5. Built-in FM transmitter for cordless head-phones.

Description

The functional block diagram of the stereo

cassette player is shown in Fig. 1. The circuit may be divided into three functional sections as shown in the block diagram.

Section I (Fig. 2). It comprises a stereo

head preamplifier, a function selector, and an FM transmitter. The preamplifier is built around IC LA3161. The outputs from 200-ohm stereo R/P (record/play) head are connected to the left and right input pins 1 and 8 of LA3161 preamplifier. A 9V regulated power supply, obtained from the voltage regulator built around transistor T1, is used for the preamplifier. The outputs of this preamplifier are routed to the function selector configured around two CD4066 (quad bipolar analogue switches) and an HEF4017 (decade counter).

When any control input pin (5, 6, 12,

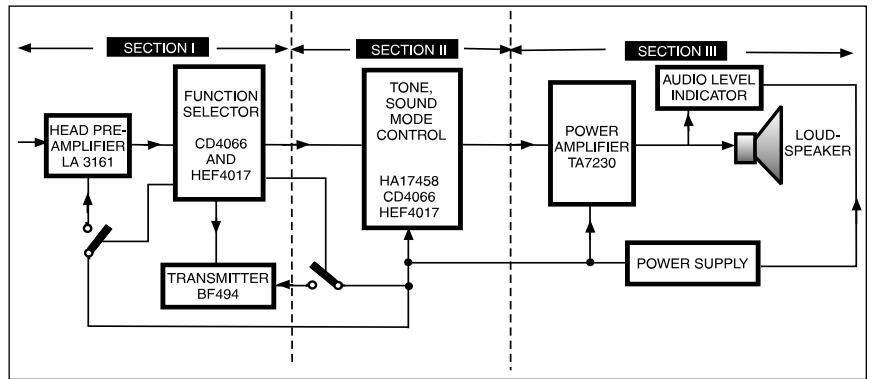


Fig. 1: Functional block diagram of stereo cassette player

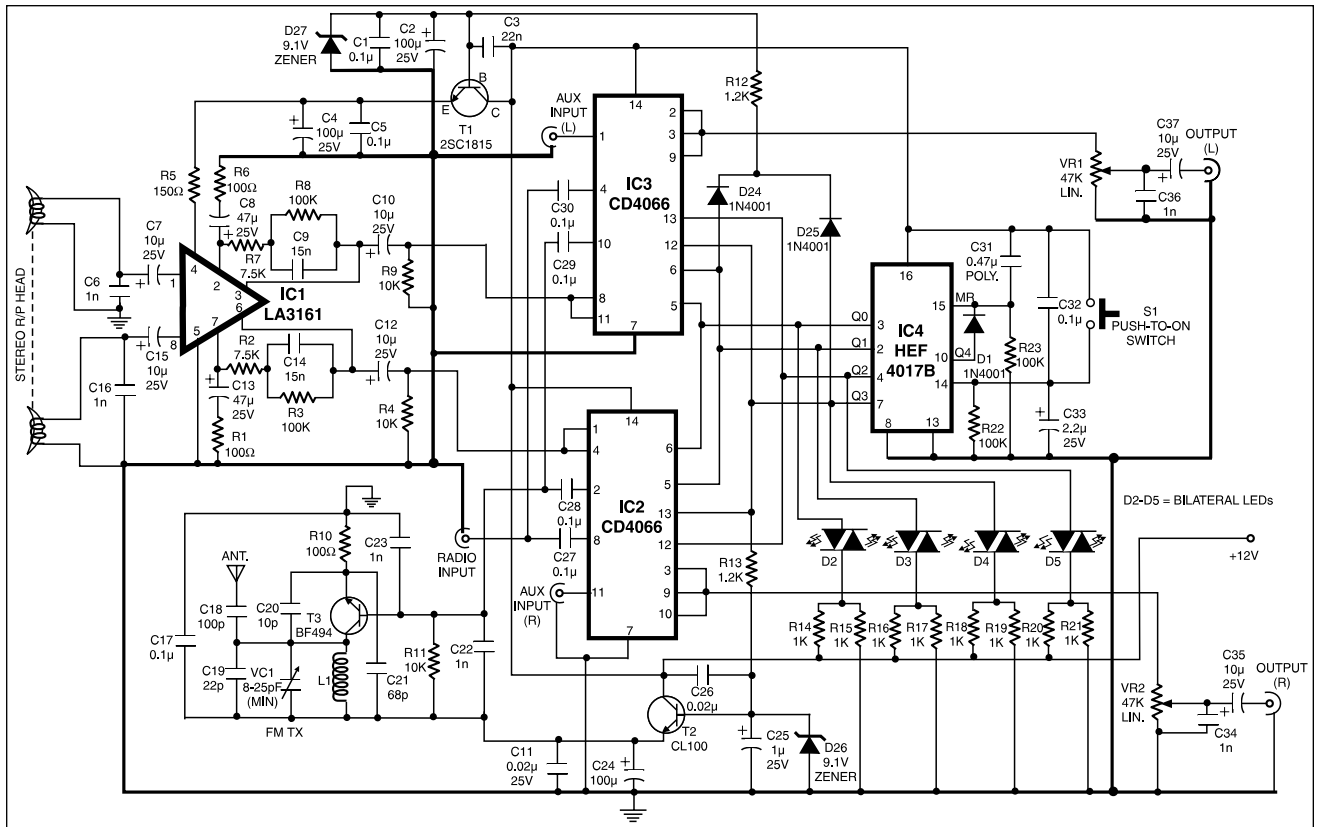


Fig. 2: Preamplifier and function selector and FM TX (Section I)

 


Fig. 3: Internal schematic diagram of CD4066 switcher IC

and 13) of CD4066, as shown in Fig. 3, is made high, it can switch AC and/or DC signals between its corresponding output pins (3-4, 8-9, 10-11, and 1-2 respectively) in both direc-

tions. In other words, it acts like an analogue switch which can be turned on or off by making its input control pin high or low. A single IC contains four such switches/sections (A, B, C, and D). The control inputs of the two ICS (CD4066) are derived from the decade counter IC (HEF4017). Only four outputs of this IC (Q0 through Q3) are used and the fifth output Q4 (pin 10) is connected to the reset pin (pin 15) via diode D1.

When power is turned on, the output Q0 (pin 3) of this IC will be high. In this condition any audio signal fed to the 'radio I/P' terminal reaches the output. If desired, the audio output from a radio

receiver can be connected to this input terminal. Circuit diagram and details of such radio receivers have appeared in earlier issues of EFY. With each depression of switch S1, the outputs of IC4 (Q0-Q3) go high sequentially to control different modes of operation. When Q1 (pin 2) of IC4 goes high, the audio sig-

nals from the output of the preamplifier reach the output terminals of the circuit. At the same time, a 9V regulated power supply to the preamplifier is switched on through transistor T1. When Q2 (pin 4) goes high, any audio signals applied to the auxiliary I/P terminals (Aux. I/P (L) and Aux. I/P(R)) reach the output terminals. When Q3 (pin 7) goes high, the power to both the FM transmitter and preamplifier is switched on and the signals from the preamplifier appear at the base of transistor T3 (BF494) which, in association with some passive components, forms an FM transmitter. The details of coil L1 are included in the parts list. The frequency of this transmitter falls between 88 and 108 MHz.

The frequency can be slightly varied by adjusting trimmer capacitor VC1. The transmitted signals can be received on any FM receiver working in 88-108 MHz range. LEDs D2 through D5 are bilateral LEDs which are used to display the selected function.

Section II. This section employs a JFET dual operational amplifier LF353 whose gain for different audio frequencies is controlled by the corresponding potentiometer settings (VR3 and VR6 for bass, VR4 and VR5 for treble for left and right channels respectively) and, additionally, by sound mode selector switch S2. The simplified circuit diagram for left channel is shown in Fig. 4, while the complete schematic circuit diagram is shown in Fig. 5.

In the simplified diagram, the function of decade counter IC (HEF 4017) and bipolar analogue switcher ICs (CD4066) are replaced by a simple switch, SW. The output of preamplifier (section I) is applied as input to the inverting terminal of op-amp IC8 and at the output we obtain a 180° phase shifted amplified signal. Potentiometers VR3 and VR4 are used to control low frequencies (bass) and high frequencies (treble) respectively.

In the normal mode (Q0 output of IC7 high), pole-P of switch SW is in contact with terminals 1 and 2 simultaneously. In this condition, normal gain is achieved for both high and low frequencies as per settings of

 


Fig. 4: Simplified schematic diagram of tone and sound mode control (left channel)

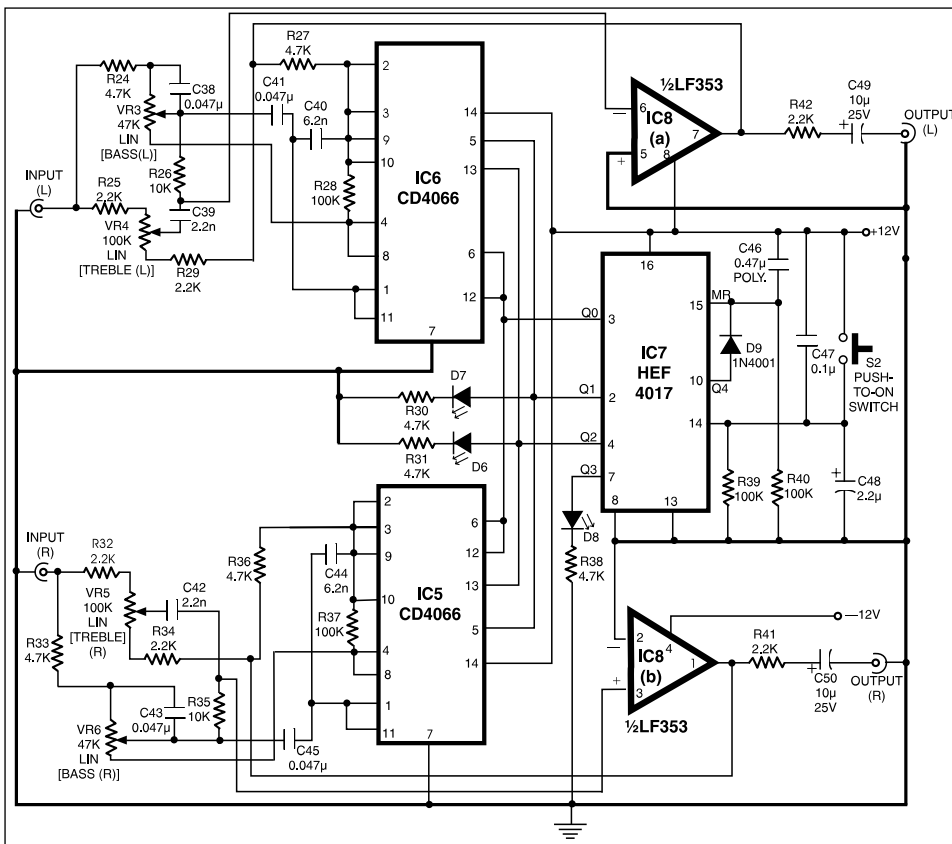


Fig. 5: Tone and sound mode control (Section II)

VR3 and VR4. But the mid-range frequency components get attenuated due to capacitor C41 (0.047µF).

In the hi-fi mode (Q1 output of IC7 high), pole-P of the switch is in contact with terminal 1. In this position, normal gain is achieved for entire audio frequency range (since capacitor C41 is disconnected from the feedback path).

When pole-P of switch sw is in position 2 (Q2 output of IC7 high), the attenuation of mid-range frequency components is re-established and also the gain of the amplifier for very low frequencies increases (since an additional feedback resistance of 100k (R25) is introduced in the feedback loop). This is the low-frequency boost mode.

When pole-P is in con-

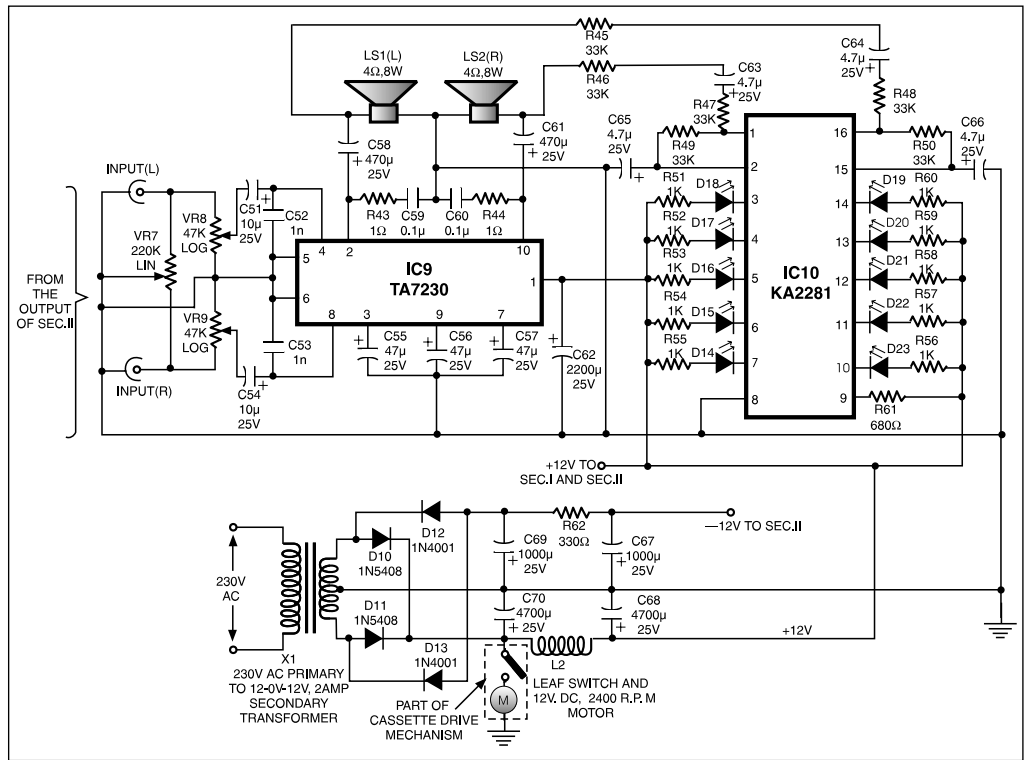


Fig. 6: Preamplifier, audio level indicator, and power supply (Section III)

PARTS LIST

<i>Semiconductors:</i>		
IC1	- LA3161 stereo preamplifier	
IC2,IC3,IC5,IC6	- CD4066B quad bilateral analogue switch	
IC7,IC4	- HEF4017B decade counter	
IC8	- LF353 JFET input dual op-amp	
IC9	- TA7230 stereo power amplifier	
IC10	- KA2281 stereo level indicator	
T1	- 2SC1815 npn transistor	
T2	- CL100 npn transistor	
T3	- BF494 npn transistor	
D1,D12,D13, D24 D25,D9	- 1N4001 rectifier diode	
D2,D3,D4,D5	- Bilateral coloured LEDs	
D6-D8,D14-D23	- Coloured LED	
D10,D11	- 1N5408 rectifier diode	
D26,D27	- 9.1V zener	
<i>Resistors (all ¼W, ±5% metal carbon film, unless stated otherwise)</i>		
R1,R6,R10	- 100-ohm	
R2,R7	- 7.5-kilo-ohm	
R3,R8,R22,R23, R28,R37,R39,R40	- 100-kilo-ohm	
R4,R9,R11, R26,R35	- 10-kilo-ohm	
R5	- 150-ohm	
R12,R13	- 1.2-kilo-ohm	
R14-R21,R51-R60	- 1-kilo-ohm	
R24,R27,R33,R30	- 1-kilo-ohm	
R31,R36,R38	- 4.7-kilo-ohm	
R25,R32,R29, R34 R41,R42	- 2.2-kilo-ohm	
R43,R44	- 1-ohm	
R45-R50	- 33-kilo-ohm	
R61	- 680-ohm	
R62	- 330-ohm,0.5W	
VR1-VR3,VR6	- 47-kilo-ohm linear potmeter	
VR4,VR5	- 100-kilo-ohm linear potmeter	
VR7	- 220-kilo-ohm linear potmeter	
VR8,VR9	- 47-kilo-ohm log potmeter	
<i>Capacitors:</i>		
C1,C5,C17,C27-C30, C32,C47,C59,C60	- 0.1µF ceramic disc	
C2,C4,C24	- 100µF, 25V electrolytic	
C3,C11,C26	- 22nF ceramic disc	
C6,C16,C22,C23 C34,C36,C22, C23,C52,C53	- 1nF ceramic disc	
C7,C15,C35,C37 C49,C50,C10, C12,C51,C54	- 10µF, 25V electrolytic	
C8,C13,C55, C56,C57	- 47µF, 25V	
C9,C14	- 15nF polyester	
C18	- 100pF ceramic disc	
C19	- 22pF ceramic disc	
C20	- 10pF ceramic disc	
C21	- 68pF ceramic disc	
C25	- 1µF, 25V electrolytic	
C31,C33,C46,C48	- 2.2µF, 25V electrolytic	
C38,C41,C43,C45	- 0.047µF polyester	
C39,C42	- 2.2nF polyester	
C40,C44	- 6.2nF polyester	
C58,C61	- 470µF, 25V electrolytic	
C62	- 2200µF electrolytic	
C63-C66	- 4.7µF, 25V electrolytic	
C67,C69	- 1000µF, 25V electrolytic	
C68,C70	- 4700µF, 25V electrolytic	
VC1	- 8-25pF trimmer	
<i>Miscellaneous:</i>		
L1	- 5T, 22 SWG, 5mm dia air core	
L2	- 250T, 18 SWG over a ferrite rod	
X1	- 230V AC primary to 12-0-12V, 2A sec. transformer	
S1,S2	- Push-to-on tactile switch	
	- Tape drive mechanism complete with 200-ohm R/P stereo head, leaf switch, and 12V DC, 2400 rpm motor	
LS1,LS2	- Telescopic antenna	
	- 4-ohm, 8W, 9cm diameter woofers with piezoelectric tweeter	
	- Readymade FM/AM radio receiver kit	
	- Cabinet	
	- Shielded cable	
	- Heat sink and other hardware items	

 


Fig. 7. Actual-size, single-sided PCB for stereo cassette player

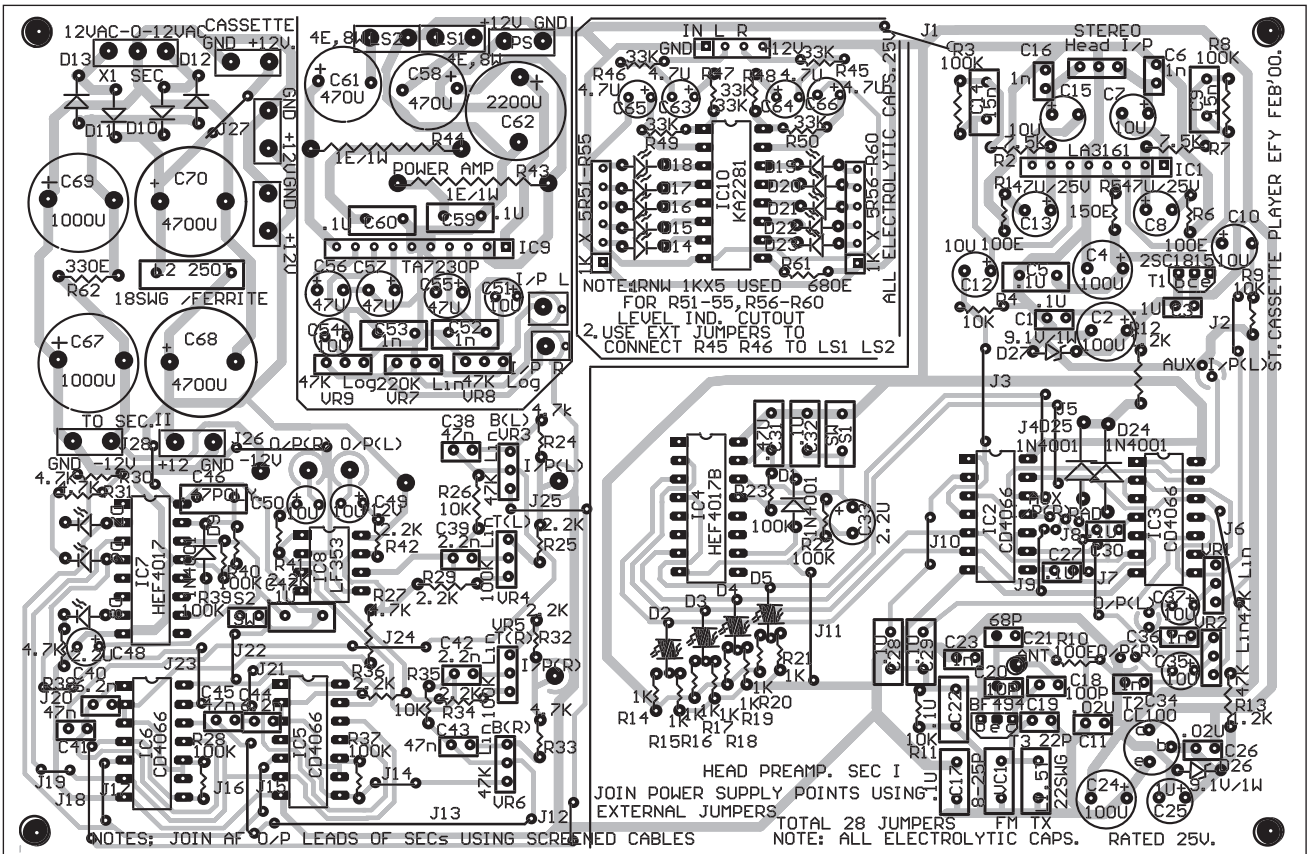


Fig. 8. Component layout for the PCB

tact with terminal 3 (Q3 output of IC7 high), normal gain is provided for the high-frequency components (treble) and higher gain is available for a wide range of low frequencies (including some mid-range frequencies). This is termed as the X-BAS mode. The gain of the amplifier for different frequencies, in each of the above-mentioned modes, is also dependent on VR3 and VR4 potmeter settings.

In the actual circuit diagram, the bipolar analogue switcher (CD4066) replaces switch SW. The LEDs D6, D7, and D8 are used to represent the sound modes—low-boost, hi-fi, and X-BAS respectively. Switch S2 is used to select various sound modes. At power on, Q0 (pin 3) of IC7 is high and therefore normal sound mode is on.

Section III (Fig. 6). This section comprises an audio power amplifier, a 12V dual power supply, and an audio level indicator. The power amplifier used is the popular IC-TA7230, which delivers up to 7-watt (RMS) power per channel into a 4-ohm load. This IC has in-built short circuit protection and over-temperature cut-off. A suitable heat sink must be connected

to the IC to prevent thermal run-away. Potmeters VR8 and VR9 are volume controls for left and right channels respectively, while VR7 is the balance control.

A dual power supply is used for the circuit. The +12V section uses a π filter with capacitors in the parallel arms and an inductor in the series arm. However, for the -12V supply, the inductor of the series arm (as used for +12V supply) is replaced by a resistor. Filters are provided to reduce the ripple factor and thereby reduce hum (noise). Please refer inductor details in parts list.

The audio level indicator is built around IC KA2281. LEDs D14 through D23 are connected at its outputs to show the audio level of each channel in five steps. The input to this audio level indicator is derived from the output of the power amplifier. The gain of this level indicator can be varied by changing the values of resistors R49 and R50.

Assembly

The complete circuit, with the exception of the audio level indicator, can be as-

sembled on a single PCB. A separate PCB is used for the audio level indicator and for mounting LEDs (D2 through D8). Single-sided, actual-size PCB for the complete circuit is given in Fig. 7. The component layout for the PCB is shown in Fig. 8.

Use sockets for all ICs except IC1 and IC9. Shielded wires must be used for connections to stereo head and all potentiometers. The PCB must be mounted away from power transformer and DC motor.

Inductor L2 should also be placed away from the power transformer. If inductor L2 is difficult to procure or fabricate, it may be substituted with a 5-ohm, 5W wire-wound resistor.

A suitable cassette drive mechanism and cabinet may be used to assemble the stereo cassette player. Readymade cabinets and cassette mechanisms are available in the market.

Adjust potmeters VR1 and VR2 for minimum distortion at higher volume level. Use separate aeriels for FM transmitter and FM receiver. □

BASS AND TREBLE FOR STEREO SYSTEM

VIVEK SHUKLA

Modern audio frequency amplifiers provide flat frequency response over the whole audio range from 16 Hz to 20 kHz. To get faithful reproduction of sound we need depth of sound, which is provided by bass (low notes). Hence low-frequency notes should be amplified more than the high-frequency notes (treble). To cater to the individual taste, and also to offset the effect of noise present with the signal, provision of bass and treble controls is made. The combined control is referred to as tone control.

The circuit for bass and treble control shown in the figure is quite simple and cost-effective. This circuit is designed to be adopted for any stereo system. Here, the power supply is 12-volt DC, which may be tapped from the power supply of stereo system itself. For the sake of clarity, the figure here shows only one channel (the circuit for the other channel being identical). The input for the circuit is taken from the output of preamplifier stage for the left as well as right channel of the stereo system

Potentiometer VR1 (10-kilo-ohm) in series with capacitor C4 forms the treble

control. When the slider of potentiometer VR1 is at the lower end, minimum treble signal develops across the load. The lowest point is referred to as treble cut. As the slider is moved upward, more and more treble signal is picked up. The highest point is referred to as treble boost.


Bass would be cut if capacitive reac-

Hence, bass has nil attenuation, and it is called bass boost. When the slider is at the lowest end, capacitor C1 is effectively in parallel with potentiometer VR2. In this position, bass will have maximum attenuation, producing bass cut.

Bass boost and bass cut are effective by ± 15 dB at 16 Hz, compared to the output at 1 kHz. Treble boost and treble cut are also effective by the same amount at 20 kHz, compared to the value at 10 kHz.

After assembling the circuit, we may check the performance of the bass and treble sections as follows:

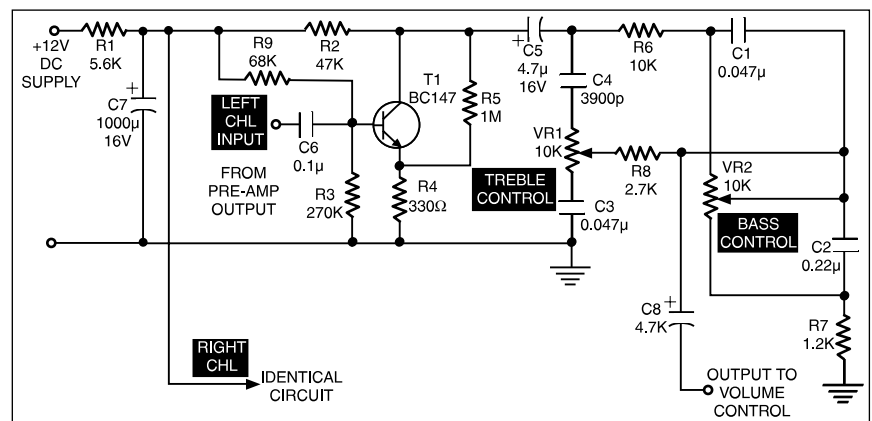1. Set the slider of the potentiometers at their mid-positions.
2. Turn-on the stereo system.
3. Set the volume control of stereo



tance in series with the signal increases. Thus, when the slider of potentiometer VR2 is at the upper end, capacitor C1 is shorted and the signal goes directly to the next stage, bypassing capacitor C1.

system at mid-level.

4. Set the slider at the position of optimum sound effect.

This circuit can be easily assembled using a general-purpose PCB.

PROTECTION FOR YOUR ELECTRICAL APPLIANCES

MALAY BANERJEE

Here is a very low-cost circuit to save your electrically operated appliances, such as TV, tape recorder, refrigerator, and other instruments during sudden tripping and resumption of mains supply. Appliances like refrigerators and air-conditioners are more prone

to damage due to such conditions.

The simple circuit given here switches off the mains supply to the load as soon as the power trips. The supply can be resumed only by manual intervention. Thus, the supply may be switched on only after it has stabilised.


The circuit comprises a step-down transformer followed by a full-wave rectifier and smoothing capacitor C1 which acts as a supply source for relay RL1. Initially, when the circuit is switched on, the power supply path to the step-down transformer X1 as well as the load is incomplete, as the relay is in de-energised state. To energise the relay, press switch S1 for a short duration. This completes the path for the supply to transformer X1 as also the load via closed contacts of switch S1. Meanwhile, the supply to relay becomes available and it gets energised to provide a parallel path for the supply to the transformer as well as the load.

If there is any interruption in the



power supply, the supply to the transformer is not available and the relay de-energises. Thus, once the supply is interrupted even for a brief period, the relay is de-energised and you have to press switch S1 momentarily (when the supply resumes) to make it available to the load.

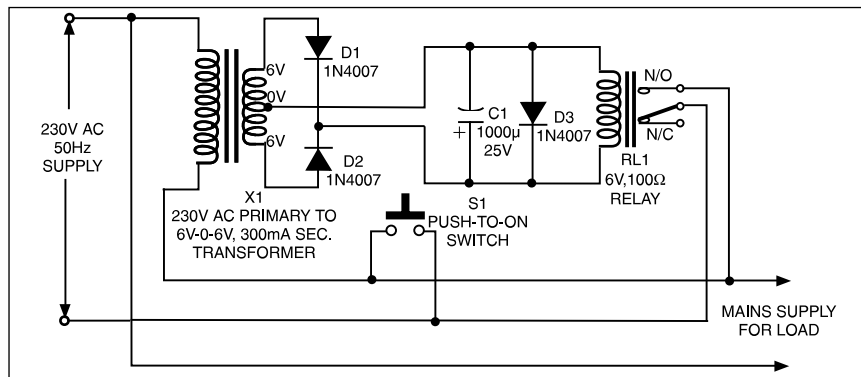Very-short-duration (say, 1 to 5 milliseconds) interruptions or fluctuations will not affect the circuit because of presence of large-value capacitor which has to discharge via the relay coil. Thus the circuit provides suitable safety against erratic power supply conditions.



DIGITAL WATER LEVEL METER

K. UDHAYA KUMARAN, VU3GTH



This digital water level meter shows up to 65 discrete water levels in the overhead tank (OHT). This helps to know the quantity of water in the OHT quite precisely. The circuit is specially suited for use in apartments, hostels, hotels, etc, where many taps are connected to one OHT. In such cases, if someone forgets to close the tap, this circuit would alert the operator well in time.

Normally, for multi water level readings, one has to use complicated circuits employing multi-core wires from the OHT to the circuit. This circuit does away with such an arrangement and uses just a 2-core cable to monitor various water levels. Fig. 2 shows various water levels and the corresponding readings on 7-segment displays.


IC1 and IC2 shown in Fig. 1 are CD4033 (decade up counter cum 7-segment decoder) which form a two-digit frequency counter. The CK pin 1 and CE pin 2 of IC1 are used in such a way that the counter advances when pin 1 is held high and pin 2 undergoes a high-to-low transition.

For water level reading,

this frequency counter needs two types of inputs. One of these is a continuous 30Hz clock (approx.), which is applied to pin 2 of IC1. The other is a timing pulse,

which is applied to pin 1 of IC1. It comprises a positive pulse of variable duration (0.5 second to 3 seconds, depending upon the water level in the tank) followed by 4-second low level.

Thus, during positive duration of timing pulse at pin 1 of IC1, the frequency counter is allowed to count the number of negative going pulses which are continuously available at its pin 2. At the same time the pnp transistor T1 remains cut-off due to the positive voltage at its base, and

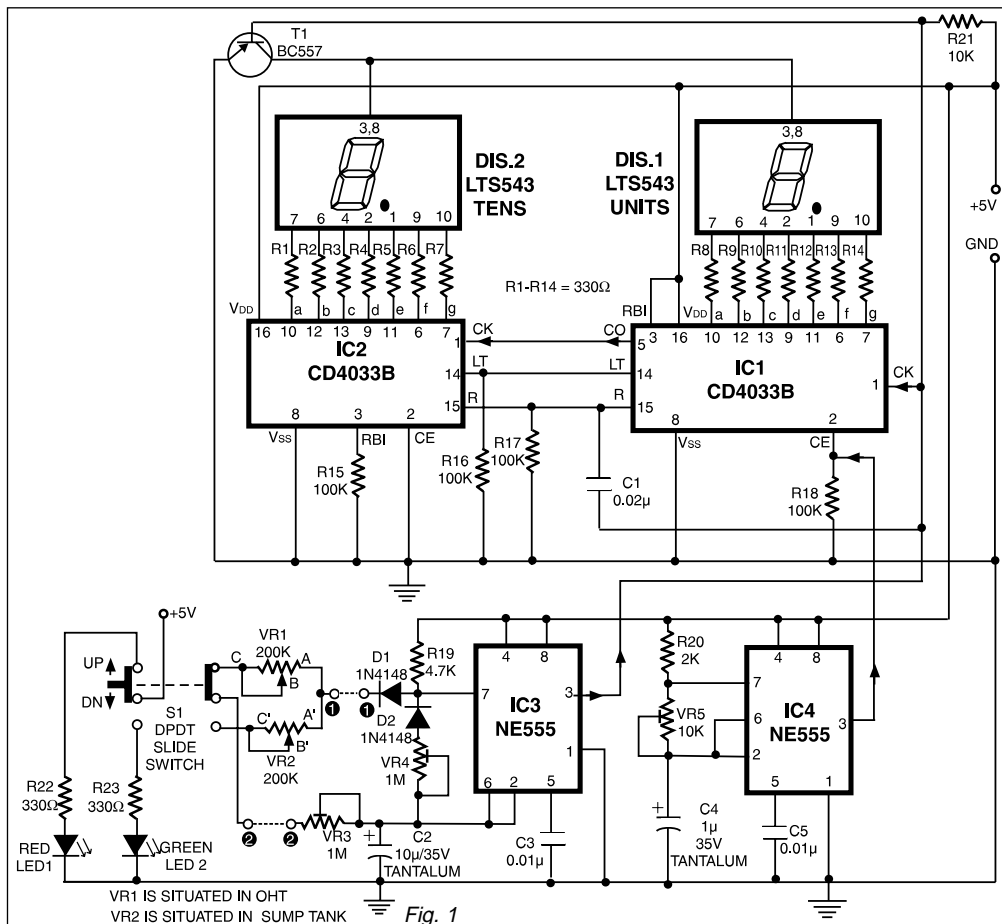

 


Fig. 2

 


Fig. 3

so the displays (DIS.1 and DIS.2) remain off. However, at the end of positive pulse at pin 1 of IC1 (and base of transistor T1), the frequency counter is latched. During the following 4-second low level period, transistor T1 conducts and displays DIS.1 and DIS.2 show the current count. At beginning of the next positive timing pulse the frequency counter resets (as the reset pin 15 of IC1 and IC2 receives a differentiated positive going pulse via capacitor C1) and starts counting afresh.

Thus, this digital water level meter shows water level reading for four-second duration and then goes off for a variable period of 0.5 second to 3 seconds. Thereafter the cycle repeats. This type of display technique is very useful, because if there is ripple in water, we shall otherwise observe rapid fluctuations in level readings, and shall not get a correct idea of the

actual level.

Timer IC4 is used as a free-running astable multivibrator which generates continuous 30Hz clock pulses with 52 per cent duty cycle. The output of IC4 is available at its pin 3, which is connected to pin 2 of IC1.

The other timer, IC3, is used as timing pulse generator wherein we have independent control over high and low duration (duty cycle) of

the timing pulses available at its output pin 3. The different duration of high and low periods of the timing pulses are achieved because the charging and discharging paths for the timing capacitor C2 differ. The charging path of capacitor C2 consists of resistor R19, diode D1, and potentiometers VR1 for OHT (or VR2 for sump tank, depending upon the position of slide switch S1) and VR3. However, the discharge path of capacitor C2 is via diode D2 and variable resistor VR4.

By adjusting preset VR4, the low-duration pulse period (4 seconds) can be set. The low-pulse duration should invariably be greater than 3 seconds.

Potmeter VR1 (or VR2), a linear wirewound pot, is fitted in such a way in the overhead tank (or sump tank) that when water level is minimum, the value of VR1 = 2 kilo-ohm. When water level in the tank is maximum, the in-circuit value of potmeter VR1 increases to 340-kilo-ohm (approximately). This is achieved by one-third movement of pot shaft. The change in resistance of VR1 results in the change in charging period of capacitor C2. Thus,

depending upon the level of water in the tank, the in-circuit value of VR1 (or VR2) resistance changes the charging time of capacitor C2 and so also the duration of positive pulse period of IC3 from 0.5 second to 3 seconds.

Adjustment of presets for achieving the desired accuracy of count can be accomplished, without using any frequency counter, by using the following procedure (which was adopted by the author during calibration of his prototype):

1. First adjust the values: VR1 (or VR2) = 2 kilo-ohm, VR3 = 64 kilo-ohm, VR4 = 90 kilo-ohm, VR5 = 23.5 kilo-ohm.

2. Now switch on the circuit. The 7-segment DIS.1 and DIS.2 blink. If necessary, adjust VR3 such that the display goes 'on' for 4-second period.

3. If display readout is 15, increase value of pot VR1 from 2-kilo-ohm to 340-kilo-ohm. Now, the display should show 90. If there is a difference in the displayed count, slightly adjust presets VR5 and VR3 in such a way that when VR1 is 2-kilo-ohm the display readout is 15, and when VR1 is 340-kilo-ohm the display readout is 90.

4. If 15- to 90-count display is achieved with less than one-third movement of pot shaft, increase the value of VR5 slightly. If 15- to 90-count display is not achieved with one-third movement of pot shaft, decrease value of VR5.

If you need this digital water level meter to monitor the levels of water in the overhead as well as the sump tanks, it can be done by moving DPDT slide switch to down (DN) position. The indication of the position selected is provided by different colour LEDs (refer Figs 1 and 2) or by using a single bi-colour LED. To monitor water level in more than two tanks, one may use a similar arrangement in conjunction with a rotary switch.

For timing capacitors C2 and C4 use tantalum capacitors for better stability.

UNIVERSAL HIGH-RESISTANCE VOLTMETER

YOGESH KATARIA




The full-scale deflection of the universal high-input-resistance voltmeter circuit shown in the figure

depends on the function switch position as follows:

- (a) 5V DC on position 1

- (b) 5V AC rms in position 2
 - (c) 5V peak AC in position 3
 - (d) 5V AC peak-to-peak in position 4
- The circuit is basically a voltage-to-

E_{dc} input	Meter Current
5.00V	44 μ A
4.00V	34 μ A
3.00V	24 μ A
2.00V	14 μ A
1.00V	4 μ A

 

current converter. The design procedure is as follows:

- Calculate R_I according to the application from one of the following equations:
 - (a) DC voltmeter: $R_{IA} = \text{full-scale } E_{DC} / I_{FS}$
 - (b) RMS AC voltmeter (sine wave only): $R_{IB} = 0.9 \text{ full-scale } E_{RMS} / I_{FS}$
 - (c) Peak reading voltmeter (sine wave only): $R_{IC} = 0.636 \text{ full-scale } E_{PK} / I_{FS}$

(d) Peak-to-peak AC voltmeter (sine wave only): $R_{ID} = 0.318 \text{ full-scale } E_{PK-TO-PK} / I_{FS}$

The term I_{FS} in the above equations refers to meter's full-scale deflection current rating in amperes.

It must be noted that neither meter resistance nor diode voltage drops affects meter current.

Note: The results obtained during practical testing of the circuit in EFY lab are tabulated in Tables I through IV.

A high-input-resistance op-amp, a bridge rectifier, a microammeter, and a few other discrete components are all that are required to realise this versatile circuit. This circuit can be used for measurement of DC, AC RMS, AC peak, or AC peak-to-peak voltage by simply changing the value of the resistor connected between the inverting input terminal of the op-amp and ground. The voltage to be measured is connected to non-invert-

E_{rms} input	Meter Current
5V	46 μ A
4V	36 μ A
3V	26 μ A
2V	18 μ A
1V	10 μ A

E_{pk} input	Meter Current
5V peak	46 μ A
4V peak	36 μ A
3V peak	26 μ A
2V peak	16 μ A
1V peak	6 μ A

$E_{pk-To-Pk}$	Meter Current
5V peak to peak	46 μ A
4V peak to peak	36 μ A
3V peak to peak	26 μ A
2V peak to peak	16 μ A
1V peak to peak	7 μ A

ing input of the op-amp.

TRIAC/TRANSISTOR CHECKER

PRAVEEN SHANKER



Here is a very simple circuit which can be used for testing of SCRs as well as triacs. The circuit could even be used for checking of pnp and npn transistors.

The circuit works on 3V DC, derived using a zener diode in conjunction with a step-down transformer and rectifier arrangement, as shown in the figure. Alternatively, one may power the circuit using two pencil cells.

For testing an SCR, insert it in the socket with terminals inserted in proper slots. Slide switch S3 to 'on' position (towards 'a') and press switch S1 momentarily. The LED would glow and keep glowing until switch S2 is pressed or mains supply to step-down transformer is interrupted for a short duration using switch S4. This would indicate that the SCR under test is serviceable.

With switch S3 in 'off' position (towards 'b'), you may connect a

milliammeter or a multimeter to monitor the current flowing through the SCR. If the SCR is 'no good,' the LED would never glow. If the SCR is faulty (leaky), the LED would glow by itself. In other words, if the LED glows only on pressing switch S1 momentarily and goes off on pressing

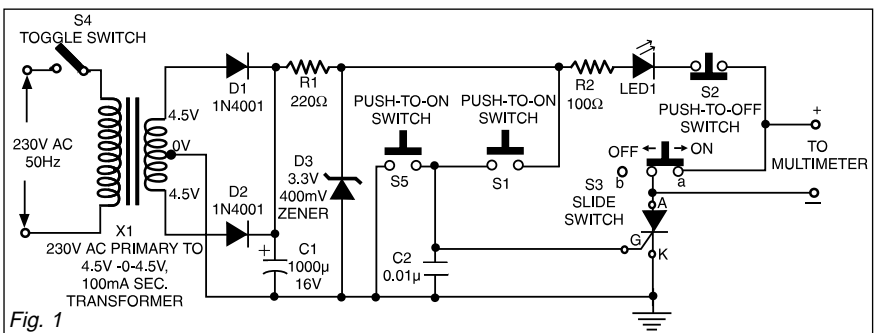


Fig. 1

 


Fig. 2

switch S2, the SCR is good.

For testing a triac, initially connect its MT1 terminal to point A (positive), MT2 to point K (negative), and its gate to point G. Now, on pressing switch S1 momentarily, the LED would glow. On pressing switch S2 momentarily, the LED would go off. Next, on pressing switch S5, the LED will not glow.

Now reverse connections of MT1 and

MT2, i.e. connect MT1 to the negative and MT2 to the positive side. For a good working triac, S2 would not initiate conduction in the triac and the LED would remain off. On the other hand, momentary depression of S5 would initiate conduction of the triac and LED1 would glow.

The indication of a leaky triac is similar to that of an SCR. If, during both the above-mentioned tests, the LED lights up, only then the triac is good.

Before connecting any SCR/triac in the circuit, please check its anode/MT1's connection with the case. (**Note:** A triac is

actually two SCRs connected back to back. The first accepts positive pulse for conduction while the second accepts negative pulse for conduction.)

You can also check transistors with this circuit by introducing a resistor (about 1 kilo-ohm) between the junction of switches S1 and S5 and point G. The collector of npn or emitter of pnp transistor is to be connected to positive (point A), while emitter of an npn and collector of a pnp transistor is to be connected to negative (point K). The base in both cases is to be connected to point G.

Fig. 2 indicates the conventional current direction and forward biasing condition for pnp and npn transistors. If the transistor under test is of npn type, on pressing S1, the LED glows, and on releasing or lifting the finger, it goes off, indicating that the transistor is good. For pnp transistor, the LED glows on pressing switch S5 and goes off when it is released. This indicates that the transistor under test is good. A leaky or short-circuited SCR or transistor would be indicated by a permanent glow of the LED by itself, i.e. without pressing switch S1 or S5.

A NOVEL METHOD OF FREQUENCY VARIATION USING 555

VYJESH M.V.




Electronics For You readers are very much familiar with the functioning of timer 555 in astable mode of operation. Traditionally, if at all there was a need to keep the duty factor constant and change the frequency continuously, the method was to use a variable capacitor, rated in picofarads. But in that case, changing the frequency in tens of hertz range would become tedious. On the other hand, sacrificing duty factor, change of frequency can be done by changing the values of R1 or R2.

Both of the above-mentioned problems can be overcome simply by using a variable resistor, as shown in the circuit diagram. Surprisingly, increase of resistance

VR1 (Ω)	Frequency (Hz) (C1=0.1μ)	Frequency (Hz) (C1=1μ)
10	453	46
33	455	46.5
68	459	47
100	462	48
220	467	50
500	478	52
1000	506	55
2000	585	63
3300	780	81
4700	1300	140
5600	2200	244
	Duty Cycle =66%	Duty Cycle =68%

 Note: Using higher values of capacitors (e.g., 10μ) or higher values of resistors (e.g., 6.8k), the results were found to be erratic.



results in increase of frequency, instead of decrease. When the value of variable resistor is zero, frequency is given by

$$f = \frac{1.44}{(R1+2R2)C1}$$

Now, when the value of variable resistor VR1 is increased, the frequency increases from the value of 'f' as determined from above formula (with VR1=0).

Lab note: The circuit has been practically verified with two different values of timing capacitor C1 and the results obtained are tabulated in Table I.

March


2000

RESONANCE TYPE L-C METER

ARUP KUMAR SEN



The voltage developed across a capacitor or an inductor in a series-resonant LCR circuit reaches its maximum value at resonance. This fact can be used to find the value of an unknown inductance or a capacitance. The present circuit is based on this very principle and it may be used to measure an inductance of even less than 1 μH, or a capacitance of the order of a few pico Farads. The quality factor 'Q' of the circuit can be measured if the applied RF voltage and the resonant voltage, developed across an inductor or a capacitor, are measured with the help of a sensitive RF volt-

 

Author's prototype

meter, by comparing a known value of inductance (called work-coil) and a standard variable calibrated capacitor. The resonance condition is detected by a peak detector which detects the peak voltage developed across

varying the value of the standard calibrated capacitor. Since frequency of the RF source is the same in both the cases (say f MHz), the unknown value of inductance of the coil under test, L_x (in micro henries), can be calculated using the following relation:

$$L_x = \frac{(C_A - C_B) \times 10^6}{(2\pi f)^2 C_A C_B} \mu\text{H} \quad (1)$$

When inductance L_w (in micro Henries) of the work-coil is known, the value of unknown inductor, L_x , can also be calculated using the relation:

$$L_x = \frac{L_w \times (C_A - C_B)}{C_B} \mu\text{H} \quad (2)$$

Alternatively, the coil under test can be connected directly to the circuit, without any work-coil in series. In this case the inductance is given by the relation:

$$L_x = \frac{10^6}{(2\pi f)^2 C} \mu\text{H} \quad (3)$$

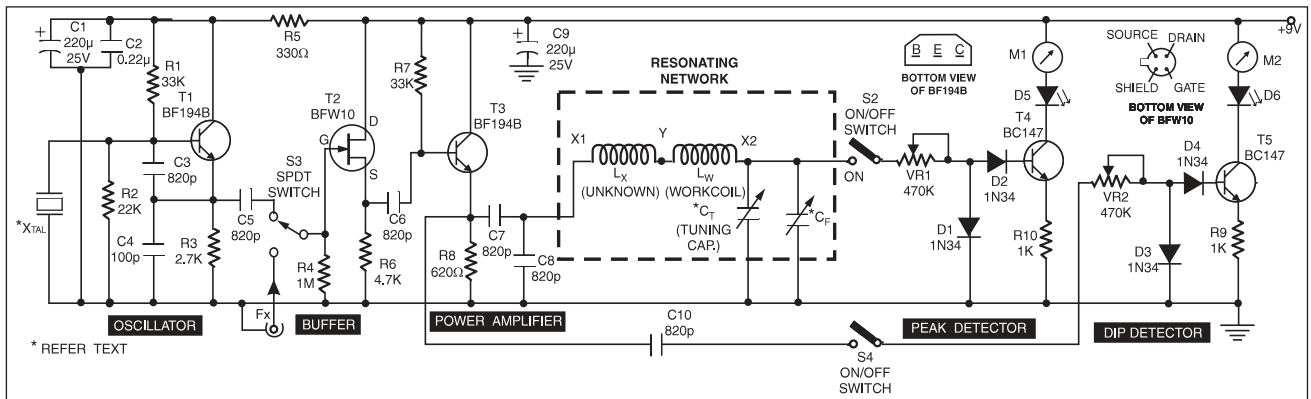


Fig. 1: Schematic diagram of the resonance L-C meter

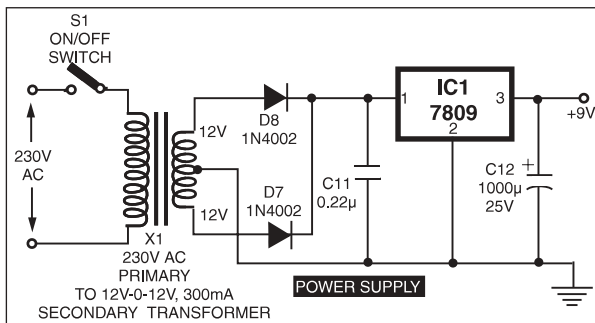


Fig. 2: 9V power supply

meter, since Q is simply the ratio of these two voltages.

Methodology

Signal from a variable-frequency RF source is applied to the coil under test, which is in series with a resonating network com-

prising a known value of inductance (called work-coil) and a standard variable calibrated capacitor. The resonance condition is detected by a peak detector which detects the peak voltage developed across the capacitor at resonance and gives a visual indication of the same. An unknown inductance is measured in two steps as follows:

1. The circuit is tuned to resonance, using calibrated tuning capacitor, with the work-coil in the circuit. The in-circuit value of calibrated capacitor is noted. Let this value

be C_A in pico Farads.

2. The unknown inductance is brought in series with the work-coil, and the circuit is returned to resonance using the calibrated capacitor. Let the new in-circuit value of the calibrated capacitor be C_B pico Farads.

In both the cases tuning is done by

where f is in MHz and C is in pF.

The value of a small unknown capacitor, C_x , can also be measured similarly in the following two steps:

1. A resonant condition is achieved by varying the standard capacitor against a particular combination of a work-coil and a crystal (forming part of crystal oscillator). Let the in-circuit value of tuning capacitor be C_A pF.

2. The unknown capacitor is connected in parallel to the standard capacitor, and decreasing the value of the standard tuning capacitor brings the resonant condition back. Let this new in-circuit value of the tuning capacitor be C_B pF.

The value of the unknown capacitor C_x would be the difference of these two values of the standard variable capacitor, i.e.

$$C_x = (C_A - C_B) \text{ pF} \quad (4)$$

 


Fig. 3: Single-layer coil

The formulae (1) to (3) are based on the assumption that there would be no mutual inductive coupling between the work-coil and the coil under test, and no stray capacitance exists to affect the resonating network. The stray capacitance, if any, is to be determined and added to both C_A and C_B to get better accuracy. The stray capacitance would have no effect upon the results obtained using the method pertaining to formula (4) above, as it would be cancelled out by the subtraction procedure.

Description

In the present circuit shown in Fig. 1, the RF signal source is formed using a crystal-controlled Colpitt's oscillator, a buffer amplifier, and a power amplifier.

 


Fig. 4: Actual-size, single-sided PCB layout for the circuit

The frequency of the RF source may be varied from 1.8 MHz to 14.3 MHz by connecting different crystals of known resonant frequencies. (Refer parts list.)

Transistor T1, along with capacitors C3 and C4, and crystal Xtal, forms the Colpitts oscillator. The crystal operates near its parallel resonant frequency. Necessary positive feedback is obtained via capacitors C3 and C4 with a feedback factor $\beta = (C3+C4)/C3$. Since the voltage gain A of a common-collector stage is less than unity, β is made slightly greater than unity to sustain oscillation. (Loop gain $A\beta$ becomes 1 in steady-state condition.) The output of the oscillator is taken from emitter of transistor T1 and is fed to the power amplifier transistor T3, through a buffer stage. Field-effect transistor T2, configured as a common drain amplifier, serves as a buffer amplifier. Due to the high input impedance of the source follower, loading on the oscillator is very low. Moreover, any variation in the output load impedance has no pulling effect on the oscillator frequency. The use of common collector configuration for the oscillator and the power amplifier stages provides a better high-frequency response.

The peak voltage at resonance is indicated by the intensity of LED D5 connected to the collector terminal of transistor T4. A milliammeter (M1) may also be used in series with the LED to get sharper tuning. The base of transistor T4 is driven by the average DC voltage developed over a complete cycle, at the output of a half-bridge rectifier. The rectifier is formed with two

PARTS LIST

Semiconductors:	
IC1	- 7809, 3-terminal +9V regulator
T1, T3	- BF194B npn transistor
T2	- BFW10 field-effect transistor
T4, T5	- BC147 npn transistor
D1-D4	- 1N34/OA79 point-contact signal diode
D5, D6	- LED, 5mm
D7, D8	- 1N4002 rectifier diode
<i>Resistors (all 1/4W, ±5% metal carbon film, unless stated otherwise)</i>	
R1, R7	- 33-kilo-ohm
R2	- 22-kilo-ohm
R3	- 2.7-kilo-ohm
R4	- 330-ohm
R5	- 1-meg-ohm
R6	- 4.7-kilo-ohm
R8	- 620-ohm
R9, R10	- 1-kilo-ohm
VR1, VR2	- 470-kilo-ohm, variable (linear)
Capacitors:	
C1, C9	- 220µF, 25V electrolytic
C2, C11	- 0.2µF ceramic disc
C3	- 100pF polyester
C4 - C8, C10	- 820pF polyester
C12	- 1000µF, 25V electrolytic
C _T	- 10pF - 280pF 2J type
C _F	- 0pF - 10pF trimmer
Miscellaneous:	
X1	- 230V AC primary to 12V-0-12V, 250mA secondary transformer
LW	- Work-coil (refer Table I)
M1, M2	- DC mA meter, 1 mA F.S.D.
Xtal	- 1.8, 3.5, 6, 10, 12, 14.3 MHz quartz crystal
SW1, SW2,	
SW4	- ON/OFF switch
SW3	- SPDT switch
	- BNC and SIP connectors
	- Snap connectors for coils (male/female)

point-contact RF signal diodes (1N34), D1 and D2. The input signal to the bridge is the voltage developed across the parallel combination of variable capacitors C_T (calibrated tuning capacitor, such as the one used in radio work with $C_{max} \approx 280$ pF for 2J) and C_F (calibrated fine tuning capacitor 0-10 pF). Diode D1 conducts only during positive half cycle of the input signal and causes a base current proportional to the average value of the signal voltage to flow through the B-E (base-emitter) junction of transistor T4. On the other hand, diode D2 conducts heavily during negative half cycle and ensures that no reverse-bias leakage current flows through diode D1 via B-E junction. (The leakage current reduces the average voltage developed over a complete cycle, and hence, reduces the intensity of the LED.) If a second identical detector stage, built around transistor T5, is connected to the power amplifier output (emitter of tran-

TABLE I

Work-coil Specifications for Different Crystal Frequencies

Crystal frequency (MHz)	SWG enameled copper wire	Turns /inch	Coil diameter (in inch)	No. of turns closely wound	Inductance (µH)
1.8	36	120	0.4	88	45
3.5	36	120	0.3*	42	15
6.0	36	120	0.3*	30	10
10.0	28	63	10/16	10	2.3
12.0	28	63	10/16	10	2.3
14.3	28	63	10/16	10	2.3

***Note.** The coils are to be wound on standard ebonite coil formers (ferrite cored) that are used in radio work. The listed inductance values are with the core almost completely dipped in the hole of the former. The values, without a core, would be approximately half of the listed values.

TABLE II

Construction Details of the Coils

Coil	Radius(r) (inch)	Length(l) (inch)	Turns(N)	L* (μH)
L ₁	10.4/16	5/16	20	7
L ₂	10.4/16	3/16	10	2.2
L ₃	0.25	1.25	77	25
L ₄	0.25	13/16	50	15
L ₅	10.4/16	2/16	4	0.4

* $L_x = \frac{(r \times N)^2}{9r + 10l} \mu H$

TABLE III

Determination of the Unknown Inductances by Two-frequency Method

Coil	Peak response obtained at f _{osc} (MHz)	C(pF)	Results L(μH)
L ₁	3.5	265.2	7.16
	6	74.8	
L ₂	10	81.6	2.1
	14.3	20.4	
L ₃	1.8	265.2	25.2
	3.5	37.8	

sistor T3), it would show a dip in the intensity of the LED, as the resonant circuit is tuned to a peak.

Positive 9V supply, for the meter circuit, is derived using a conventional three-terminal fixed-voltage regulator IC 7809. AC mains voltage is stepped down by power transformer X1 from 230V AC to 12V AC, which is then rectified to deliver the unregulated DC input to the regulator IC. (Refer Fig. 2.)

Construction

During construction, special care is to be exercised towards lead dressing. Any stray coupling from output to input through a stray capacitance, or an unwanted mutual inductance, may produce unwanted oscillations, which would hamper the reliability of the meter. Since stray capacitances play a very adverting role in a measurement, the same should be minimised by keeping the length of the connecting wires as short as possible.

The voltage developed across tuning capacitors (C_T and C_F) gradually increases as the frequency of oscillation is lowered. Hence, the input to the peak detector must be controlled accordingly for its safe operation. On the other hand, a reduction in the applied voltage to the peak detector reduces the current through the LED, which again enhances the sharp-

 


Fig. 5: Component layout for the PCB

ness in tuning. The peak detector input should not have any direct coupling with the power amplifier via a stray resistance or capacitance, as it would cause hindrance during the search for a peak.

To get better results, different work-coils are to be used with different crystal frequencies. The details of these coils are given in Table I.

If a continuously variable RF source is desired, one may substitute the crystal in the oscillator circuit with a suitable combination of an inductance and a variable condenser. The approximate frequency of oscillation of the circuit can be determined with the help of a radio receiver—by bringing it close to the meter circuit. The frequency on the dial at which maximum reception would be heard is the desired frequency.

The required inductance for a particular frequency range can be calculated from the following relation:

$$L = \frac{\lambda_{max} - \lambda_{min}}{(1885)^2 \cdot C_{max}} \mu H \quad (5)$$

Here, C is in μF and C_{max} ≈ 280 pF for 2J. λ is the wavelength in metres corre-

sponding to a particular frequency, and is given by the relation:

$$\lambda = \frac{300}{f} \text{ metres,}$$

where f is the frequency in MHz.

To wind a coil of required inductance, we may use the following equation:

$$L = \frac{(r.l.n)^2}{9r + 10l} \mu H \quad (6)$$

Here, r is the mean radius, l is the length of the coil in inches, and n is the number of turns per inch of the selected SWG (as per

wire tables). Initially, a table of l-vs-L is to be generated for a particular SWG, by putting various values of winding length l in equation (6) and finding the resultant L. The winding length, and consequently the number of turns required for the inductance calculated above, may then be found from this table. However, it is to be noted that formula (6) above could only help us to get close to the target inductance. The desired value is then achieved by adjusting its core, after connecting the coil in the circuit.

In equation (6) we may substitute N (total number of turns) for product l.n, if desired.

Methods

Some methods to find the value of inductance are given below:

1. Direct connection. Most of the unknown inductances may be measured by connecting them directly to the circuit and using the relation:

$$L = \frac{10^8}{(2\pi f)^2 \cdot C} \mu H \quad (7)$$

Here, f is in MHz and C is in pF. The steps to be followed are given below:

1. Switch on the RF generator (switch S1) with the coil under test connected to the circuit across points X1-X2.
2. Switch on S2 to apply RF power to the resonating network.
3. Rotate LED-intensity-control potentiometer VR1 to obtain the maximum intensity of LED D5.
4. Tune calibrated tuning capacitor C_T (and/or fine-tuning calibrated capacitor C_F) for maximum intensity

TABLE IV
Determination of Unknown Inductances by Series Connection Method

Coil	Peak response obtained at f _{osc} (MHz)	C(pF)	Results (μH)
L ₁ (L _w)	6	65	L ₂ =2.3
L ₁ (L _w)+L ₂ (L _x)	6	40.8	
L ₃ (L _w)	1.8	265.2	L ₄ =13.6
L ₃ (L _w)+L ₄ (L _x)	1.8	156.4	
L ₂ (L _w)	14.3	20.4	L ₅ =0.43
L ₂ (L _w)+L ₅ (L _x)	14.3	10.3	

of LED D5, or peak on the meter. The intensity of LED D5, or the deflection of the meter pointer, would be the maximum at resonance. If no peak is found, it might be due to low signal input to the peak detector. Gradually decrease the in-circuit resistance value of potmeter VR1. If still no peak is found, it would mean that crystal frequency is not appropriate. Try with another crystal.

5. Note down the capacitance values from the dials of C_T and C_F . The total value of capacitance C is given by $C = C_T + C_F + C_{\text{Stray}}$.

The value of C_{Stray} may be in the range of 10-30 pF. If C_T is sufficiently high, C_{Stray} may be dropped from the calculation.

6. Calculate the value of L_x using equation (7).

2. Series connection. This includes following steps:

1. Insert a crystal in the crystal socket. Connect the coil under test across terminals X1-Y and a suitable work-coil across X2-Y (Table I). Initially short X1-Y terminals using a small wire. Tune C_T and C_F to get a peak on LED D5 (or meter). Note the capacitance values from the dials of tuning capacitors C_T and C_F . Let this value be C_A . If no peak is obtained, try with another crystal and work-coil combination.

2. Remove the short across X1-Y and retune the circuit by rotating C_T (and/or C_F) towards lower capacitance value to establish the peak once again. Make a fine adjustment using C_F . Note the new positions on the dials. Let the new sum of C_T and C_F be C_B .

3. Calculate the value of the unknown inductance from Eqs (1) or (2) given above.

3. Two-frequency method. If a coil of inductance L_x gives peak responses on two different frequencies— f_A at C_A and f_B at C_B on tuning the dial—then L_x can be calculated from the formula given below:

$$L_x = \frac{1}{C_A \cdot C_B} \left(\frac{1}{(2\pi f_A)^2} - \frac{1}{(2\pi f_B)^2} \right) \quad (8)$$

Method to find the value of capacitance. Follow the steps given below:

1. Tune the circuit to resonance

against a particular crystal and work-coil combination.

2. Read the capacitance values from the dials. Let the sum be C_A pF.

3. Connect the capacitor under test in parallel with C_T .

4. Retune the circuit to get the peak back.

5. Note the new values of capacitance from the dials. Let the sum be C_B pF.

6. Calculate the unknown capacitance from the relation:

$$C_x = (C_A - C_B) \text{ pF}$$

Method to determine an unknown frequency. Frequency of an unknown RF sinewave signal may be measured by following the steps given below:

1. Connect a suitable work-coil in the circuit.

2. Connect the RF signal source (with unknown frequency F_x) to the gate of buffer transistor T2, after disconnecting the crystal oscillator from it, with the help of switch S3.

3. Apply power to the meter by turning switch S1 'on'.

4. Apply RF power to the resonant circuit after turning switch S2 'on'.

5. Tune the resonant circuit to get a peak. If no peak is obtained, try with another work-coil.

6. Note the capacitance value from the dials of the tuning capacitors. Let the sum be C .

7. Calculate the frequency of the incoming RF signal using the following relation:

$$f = \frac{1000}{2\pi \sqrt{L_w \cdot C}} \text{ MHz}$$

Here, L_w is in μH and C in pF.

Calibration

If a standard variable capacitor is not available, we may use, after proper calibration, a 2J type variable capacitor which is generally used for radio work. To calibrate the same, follow the steps given below:

1. Switch on the RF source with a 3.5

MHz crystal, 17 μH work-coil, and a 2J capacitor for C_T .

2. Rotate the tuning capacitor towards its maximum capacity (approx. 280 pF).

3. Tune by varying the slug of the coil to get a peak on the meter or LED.

4. If you require a resolution of 10 pF, connect a standard low-tolerance 10 pF capacitor in parallel with C_T . Instantly the circuit would be out of tune.

5. Rotate capacitor C_T to get back the peak again. Mark the new position of C_T . It would be $C_{\text{max}} = 10$ pF.

6. Redo steps 4 and 5 to cover the entire angular span ($\approx 180^\circ$). Each time the new position of C_T would be 10pF less than its previous value.

Limitations

While tuning with C_T to get a resonance, the LCR circuit may produce a peak voltage at the harmonic frequency of the crystal used, which would give misleading results. To avoid this situation, the positions of those harmonic frequencies on the dial of C_T for a particular crystal and work-coil combination, should be spotted first, by rotating the capacitor over its full swing.

During tuning, if a conductive body is brought near the resonant network of the variable capacitor, interference would be produced.

Results

Coils practically wound, using the formulae given in the article, and inductance practically determined, using two-frequency method and series connection method, are tabulated in Tables II, III, and IV respectively.

Power supply may be assembled separately on the PCB, which may be cut out from the main PCB. Variable tuning capacitors (C_T and C_F), snap connectors for coils (L_w and L_x), switches, LEDs, potmeters, etc may be mounted on front panel. □

ELECTROLYSIS-PROOF COMPLETE WATER-LEVEL SOLUTION

LOKESH KUMATH



comprises a step-down transformer (with secondary voltage and current rating of 15V-0-15V, 1A respectively), followed by a bridge rectifier, filter, and 12-volt regulators [LM7812 for +12V (V_{CC}) and LM7912 for -12V (V_{EE})]. Capacitors C1-C4, across rectifier diodes, and C8 and C10, across regulator output, function as noise eliminators. Diodes D5 and D6 are

One major problem in using water as a conducting medium arises due to the process of electrolysis, since the sensor probes used for level detection are in contact with water and they get deteriorated over a period of time. This degradation occurs due to the deposition of ions on the probes, which are liberated during the process of electrolysis. Thereby, the conductivity of the probes decreases gradually and results in the malfunctioning of the system. This can be avoided by energising the probes using an AC source instead of a DC source.

The circuit presented here incorporates the following features:

1. It monitors the reservoir (sump tank) on the ground floor and controls the pump motor by switching it 'on' when the sump tank level is sufficient and turning it 'off' when the water in the sump tank reaches a minimum level.
2. Emergency switching on/off of the pump motor manually is feasible.
3. The pump motor is operated only if the mains voltage is within safe limits. This increases the life of the motor.
4. It keeps track of the level in the overhead tank (OHT) and switches on/off the motor accordingly automatically.
5. It checks the proper working of the motor by sensing the water flow into the tank. The motor is switched 'on' and 'off' three times, with a delay of about 10 seconds, and if water is not flowing into the overhead tank due to any reason, such as air-lock inside the pipe, it warns the user by audio-visual means.
6. It gives visual and audio indications of all the events listed above.
7. An audio indication is given while the motor is running.
8. The system is electrolysis-proof.

Description

The power supply section (Fig. 1). It

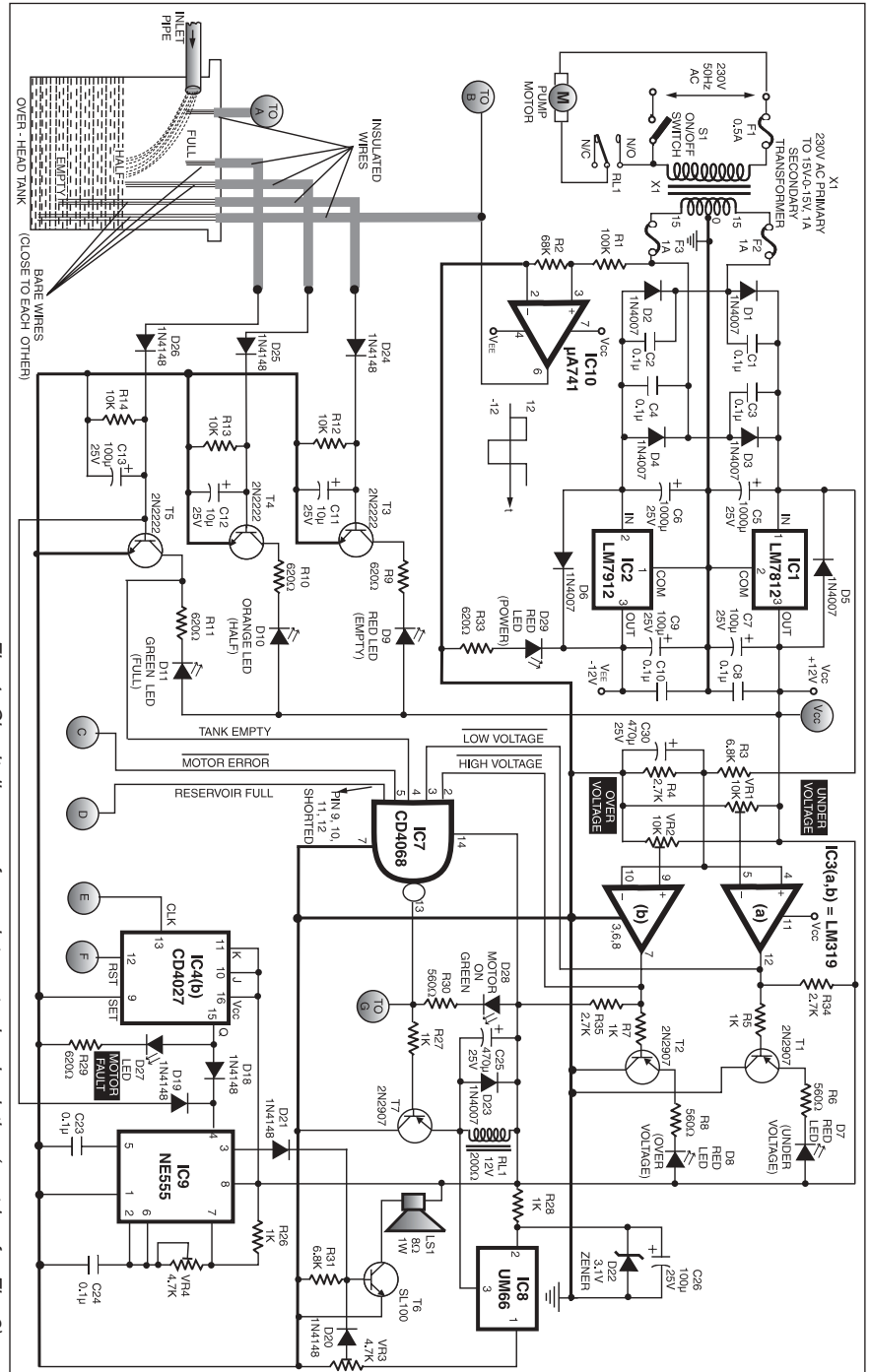


Fig. 1: Circuit diagram of complete water level solution (contd. refer Fig. 2)

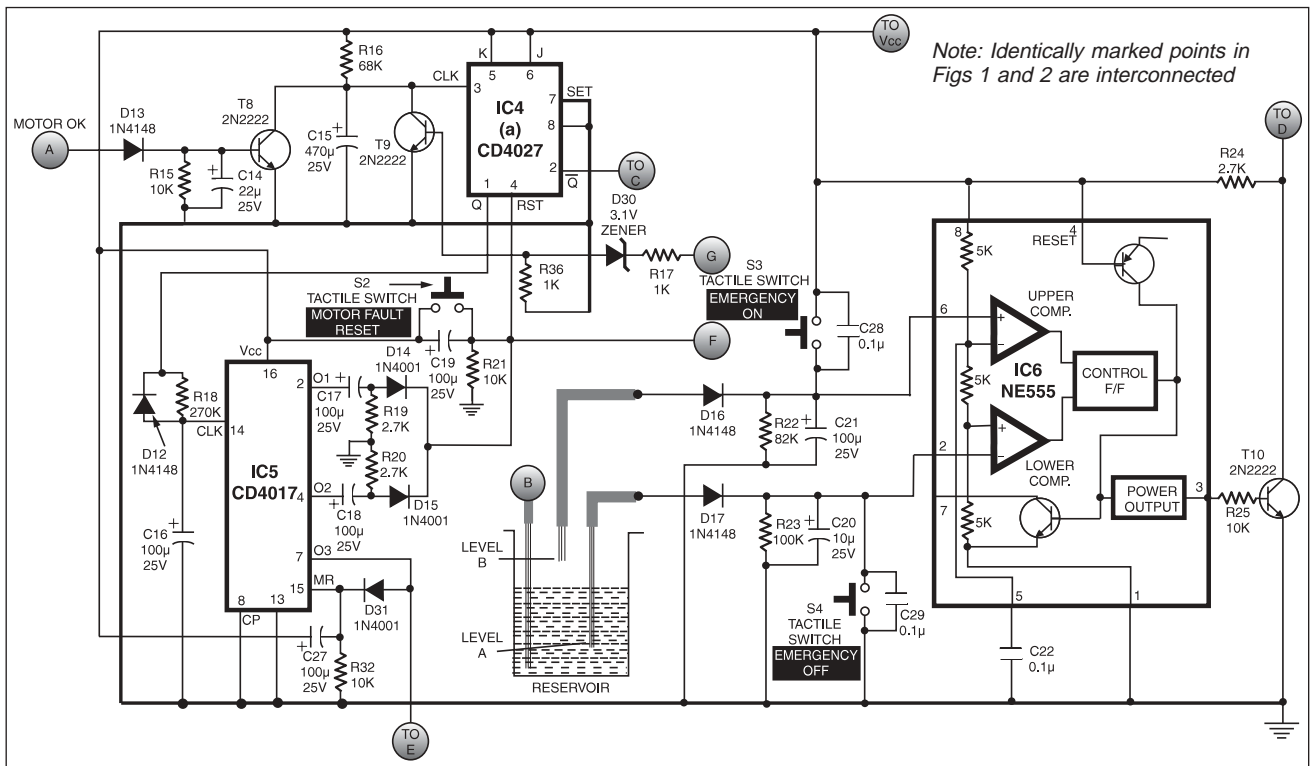


Fig. 2: Part circuit of complete water level solution (contd. from Fig. 1)

used as protection diodes.

The under- and over-voltage cut-off section (Fig. 1). It comprises a dual comparator, two pnp transistors, and a few other discrete components. This part of the circuit is meant to stop the motor in case of a low mains voltage (typically 180V to 190V) or a voltage higher than a specified level (say 260V to 270V). The unregulated DC is sampled by means of a potential divider network comprising resistors R3 and R4. The sampled voltage is given to two comparators inside IC LM319. The reference voltages for these two comparators are set by presets VR1 and VR2. The outputs of both the comparators are active-low (normally high, until the low or high voltage limits are exceeded). That is, when the AC mains goes below (or rises above) the preset levels, the outputs of the comparators change to logic zero. The output of either comparator, when low, results in lighting up of the respective LED—D7 (for lower limit) and D8 (for upper limit) via transistors T1 and T2 (2N2907), which are switching transistors.

The outputs from the comparators also go to 8-input NAND gate IC7 (CD4068) to control the motor via transistor T7. All inputs to IC7 are high when all conditions required for running of the pump motor are fulfilled. When one or more conditions

are not met, the output of IC7 goes high to de-energise relay RL1 via transistor T7.

Bipolar squarewave generation (Fig. 1). One side of the secondary of transformer X1 is also connected to op-amp IC10 (μ A 741), which is used here as a comparator to provide bipolar square wave (having positive and negative halves). It is not advised to directly connect the secondary output to the probe in the tanks because, if due to any reason the primary and secondary get shorted, there is a risk of shock, as the secondary would be directly connected to the probes immersed in water inside the tank. But if we use a comparator in between the secondary and probes, the IC would get open in case primary and secondary windings are short-circuited. For additional safety, fuses F2 and F3, both of 1A capacity, are connected to the output of secondary windings.

Pump motor fault-detection circuit (Figs 1 and 2). A sensor probe detects the flow of water. It is fixed just at the mouth of the inlet pipe, inside the overhead tank. When the motor is off (output 'G' of NAND gate IC7 is high), transistor T9 (2N2222) is 'on' (saturated) and, therefore, capacitor C15 is short-circuited. It also pulls the clock input pin 3 of IC4(a) flip-flop to ground. Zener D30 ensures that

transistor T9 does not conduct with logic 0 voltage (1 to 2V) at its base.

When the motor is running (all the inputs to NAND gate IC7 are high), transistor T9 base is pulled to ground and thus capacitor C15 starts charging via resistor R16. The RC combination is selected [using the well-known charging formula $V(t) = V_{final} (1 - e^{-t/RC})$] such that it takes about 15 seconds for the capacitor to reach $1/3 V_{cc}$, i.e. about 4 volts to clock flip-flop IC4(a) to toggle, taking its \bar{Q} pin low to stop the motor (via IC7, transistor T7, and relay RL1). However, if water starts flowing within 15 seconds after the starting of motor, transistor T8 would start conducting and discharge capacitor C15, not allowing it to charge, irrespective of the state of transistor T9. Thus capacitor C15 remains discharged.

But if water does not flow due to any reason, such as air lock or pump motor failure, IC4(a) toggles after about 15 seconds, which makes its \bar{Q} pin 2 low. As a result, the output of IC7 goes high and the motor stops. Simultaneously, capacitor C15 is discharged. At the instant \bar{Q} goes low, Q (pin 1) goes high and so a clock is applied to IC5 via resistor-capacitor combination of R18-C16, so that clock input pin 14 of IC5 goes high after about 10 seconds. As a result, pin 2 of IC5 goes

 


Fig. 3: Actual-size, single-sided PCB layout for the circuit shown in Figs 1 and 2

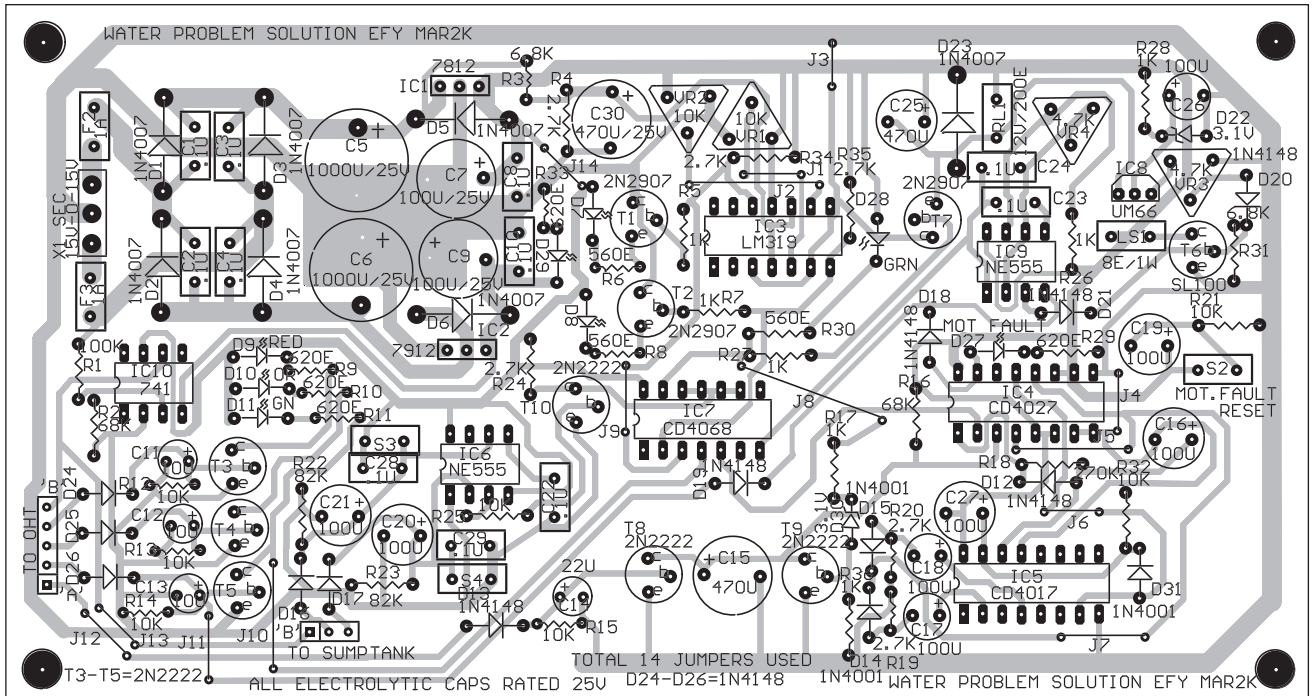


Fig. 4: Component layout for the PCB

high and resets IC4(a) to make \bar{Q} high again. This starts the motor.

But if water still does not flow into the OHT this time, \bar{Q} of IC4(a) becomes low again to switch off the motor. Simultaneously, IC5 gets another clock pulse and IC4(a) is reset once again after 10

seconds to restart the motor. If this condition repeats for the third time, pin 7 of IC5 goes high, to reset it. The same output from pin 7 of IC5 functions as a clock pulse for IC4(b), to give a logic high signal to $\overline{\text{RESET}}$ pin 4 of IC9 (NE555), configured as astable multivibrator.

The output of IC9 is used to switch 'on' the speaker at the set frequency. The frequency (tone) can be set using preset VR4. The Q output of IC4(b) is also used to light up the 'Motor Fault' LED D27. This fault condition can be reset by pressing switch S2 to reset IC4(a) and IC4(b),

 


Fig. 5: Proposed front-panel layout

after taking appropriate remedial action such as filling the foot-valve of the motor with water or by removing the air-lock inside the pipe.

Reservoir/sump tank level detection (Fig. 2). To start the motor when the water level in the reservoir is sufficient (level B), and to stop the motor when the level falls below a particular level (level A), are the two functions performed by this section. IC6 (timer NE555) is configured here to function in the bistable mode of operation. When the water level is below the minimum level A, both pins 2 and 6 of IC6 are low. In this state, the output is high, as the internal R-S flip-flop is in the set condition.

When water rises up to level A and above, but below level B, pin 2 is at high level. But in this state no change occurs at the output because both the inputs to the flip-flop are at logic zero, and so the initial condition remains at the output.

When water touches level B probe, pin 6 goes high and the output low. As a result, collector of transistor T10 goes high and the motor starts, if all other inputs of IC7 are also high. Thus, water level in the reservoir starts decreasing, and when it goes below level A, the output of IC6 goes high and the motor stops.

Capacitors C20 and C21 act as filter capacitors. The value of C21 is selected such that it takes about 10 seconds to reach $2/3 V_{cc}$ potential at pin 6, thereby avoiding any erroneous start of the motor due to random fluctuations in the water level of the reservoir due to any reason. Resistors R22 and R23 are bleeder resistors for discharging these capacitors. Switches S3 and S4 are used to switch 'on' and switch 'off' the motor respectively, in case of any emergency.

Miscellaneous functions (Figs 1 and 2). Transistors T3 through T5 are used to drive LEDs D9 through D11, which indicate the level of water inside the overhead tank. The base of transistor T5 is also connected to RESET pin 4 of IC9 to sound an alarm (similar to that in case of

motor fault), indicating that the overhead tank has been filled completely. At this instant LED D11 is lit to indicate this condition, while during motor fault condition motor fault LED D27 is lit. Thus, by using the same alarm facility and two different LEDs, two different conditions are indicated. The collector of the

same transistor T5 is connected to NAND gate IC7 to switch off the motor when the tank is filled up to its maximum level.

The ground pin of melody generator UM66 (IC8) is connected to the emitter of transistor T7. Thus, the melody IC is 'on' when the motor is running. The volume of this melody can be controlled by preset VR3.

Diode D23 connected across the relay is the 'snubber' diode to protect emitter junction of T7. Capacitor C25 is added to avoid chattering of the relay.

LS1 can be any 0.25W-1W, 8-ohm speaker. RL1 should be a good-quality 12V, 200-ohm relay, with a contact rating of at least 10A. The combinations of capacitor-resistor C19-R21 and C27-R32 form power-on reset circuits. Since the CMOS ICs are used here, the noise margin is quite high. The front-panel layout for the system is given in Fig. 5.

Precautions

1. The probes should be made of a material which is rust-proof, such as aluminium or brass.
2. Adjust presets VR1 and VR2 using an auto-transformer.
3. IC1 and IC2 should be provided with heat-sinks.
4. Level A of the reservoir should be such that the foot-valve is just under water.
5. The probes energised with AC (connected to output of IC10) should run up to the bottom of the OHT and sump tanks.
6. The water-flow-sensing probe should be installed well above the 'tank-full' level.
7. Remember that the 'low level' LED indicates that water is between the 'low level' and 'half level'. When both 'low level' and 'half level' LEDs are on, the water level is between 'half' and 'full level'.
8. The probes inserted deep, down to the bottom, should be completely uncovered up to the top position of the tank, and the different probes should be as close

PARTS LIST

Semiconductors:

IC1	- 7812, +12V regulator
IC2	- 7912, -12V regulator
IC3	- LM319 dual comparator
IC4	- CD4027 dual JK flip-flop
IC5	- CD4017 Johnson ring counter
IC6, IC9	- NE555 timer
IC7	- CD4068, 8-input NAND gate
IC10	- μ A741 op-amp
IC8	- UM66 melody generator
T1, T2, T7	- 2N2907 pnp switching transistor
T3-T5, T8-T10	- 2N2222 npn switching transistor
T6	- SL100 npn transistor
D1-D6, D23	- 1N4007 rectifier diode
D7-D11, D27-D29	- LED, coloured
D12, D13, D16-D21	-
D24-D26	- 1N4148 switching diode
D14, D15, D31	- 1N4001 rectifier diode
D22, D30	- 3.1V zener diode

Resistors (all $1/4$ watt, $\pm 5\%$ carbon film, unless stated otherwise):

R1, R23	- 100-kilo-ohm
R2, R16	- 68-kilo-ohm
R3, R31	- 6.8-kilo-ohm
R4, R19, R20, R24, R34, R35	- 2.7-kilo-ohm
R5, R7, R17, R26-R28, R36	- 1-kilo-ohm
R6, R8, R30	- 560-ohm
R9-R11, R29, R33	- 620-ohm
R12-R15, R21, R25, R32	- 10-kilo-ohm
R18	- 270-kilo-ohm
R22	- 82-kilo-ohm
VR1-VR2	- 10-kilo-ohm, preset
VR3, VR4	- 4.7-kilo-ohm, preset

Capacitors:

C1-C4, C8, C10	-
C22-C24, C28, C29	- 0.1 μ F ceramic disc
C5, C6	- 1000 μ F, 25V electrolytic
C7, C9, C13, C16-C19, C21, C26, C27	- 100 μ F, 25V electrolytic
C11, C12, C20	- 10 μ F, 25V electrolytic
C14	- 22 μ F, 25V electrolytic
C15, C25, C30	- 470 μ F, 25V electrolytic

Miscellaneous:

X1	- 230V AC to 15V-0-15V, 1A sec. transformer
RL1	- Relay 12V, 200-ohm with contact rating \geq 10A
LS1	- IC bases
S1	- Speaker, 8-ohm, 1W
S2-S4	- Heat-sinks for IC1 and IC2
F1	- Mains on/off switch
F2-F3	- Single-pole tactile switches
	- 0.5A fuse
	- 1A fuse
	- Sensing probes

as possible (but not too close to avoid any water droplets sticking across them) to have minimum water resistance.

A single-sided, actual-size PCB for the complete circuit of the project is given in Fig. 3, and a component layout for the same is given in Fig. 4. □

PENDULUM DISPLAY



K.P. VISWANATHAN

The circuit presented here can be used for producing eye-catching effects like 'pendulum' and 'dashing light'. To and fro motion of a pendulum can be simulated by arranging ten bulbs in a curved fashion and lighting them up sequentially, first in one direction and then in the other, using this circuit. For pendulum effect, the frequency of oscillator should be quite low.


Similarly, one may create a dashing light effect by using 19 bulbs and connecting them in such a way that bulb number 1 and 19, 2 and 18, 3 and 17, so on are in parallel. For achieving the dashing light effect, the oscillator frequency should be comparatively high.

In this circuit NOR gates N1 and N2 form an oscillator whose period can be adjusted through potmeter VR1. Oscillator output is fed to clock pin 15 of IC2 (CD4029), which is a binary/BCD up/down counter. As long as pin 10 of IC2 is at logic 1, it counts up; when it changes to logic 0, it counts down. This changeover is explained below.

The BCD outputs of IC2 are connected to IC3 (CD4028), which is a 1-of-10 decoder. As per sequential BCD in-

through Triac10) via corresponding transistors (T1 through T10) to light up the bulbs connected to them.

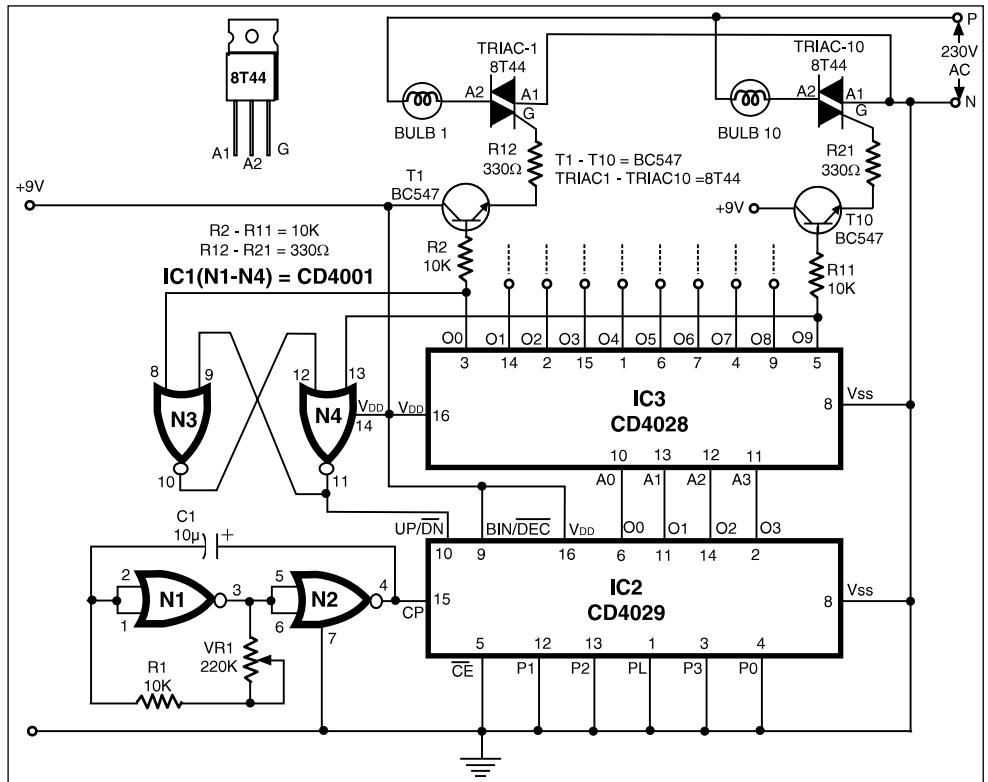Initially, when output O0 of IC3 goes high, the output of flip-flop formed by NOR gates N3 and N4 goes high, thus keeping pin 10 of IC2 at logic 1, and the counter counts up. Subsequently, when output O9 become high, the flip-flop is toggled and pin 10 of IC2 is pulled to



puts (up or down), outputs of IC3 go high and trigger the triacs (Triac1

logic 0, and the counter starts counting down. The cycle repeats endlessly.

AUDIO LEVEL INDICATOR



LOKESH KUMATH

The audio level indicator described here is quite simple and utilises readily available ICs. The function of the circuit can be understood with reference to Fig. 2 which shows two concentric circles formed by red and green LEDs respectively.

When the audio level increases, the speed of the roulette (moving light ef-

fect in the circles) also increases. The lighting LEDs of one of the two circles would appear to move in clockwise direction, while the other circle's LEDs appear to move in anticlockwise direction. When no audio is available, the speed of these two roulettes appears to be constant.

Although the LEDs here are ar-

ranged in circular form and only two colours are used, a number of different combinations are possible. For example, one may have red and green LEDs arranged in two rows, one over the other. LEDs of one row may be made to appear moving from left to right and of the other in the opposite direction, i.e from right to left.

In the circuit shown in Fig. 1, IC 555 is wired to operate in an astable mode as a voltage controlled oscillator (VCO). The only difference here is that pin 5 (which is a frequency controlling

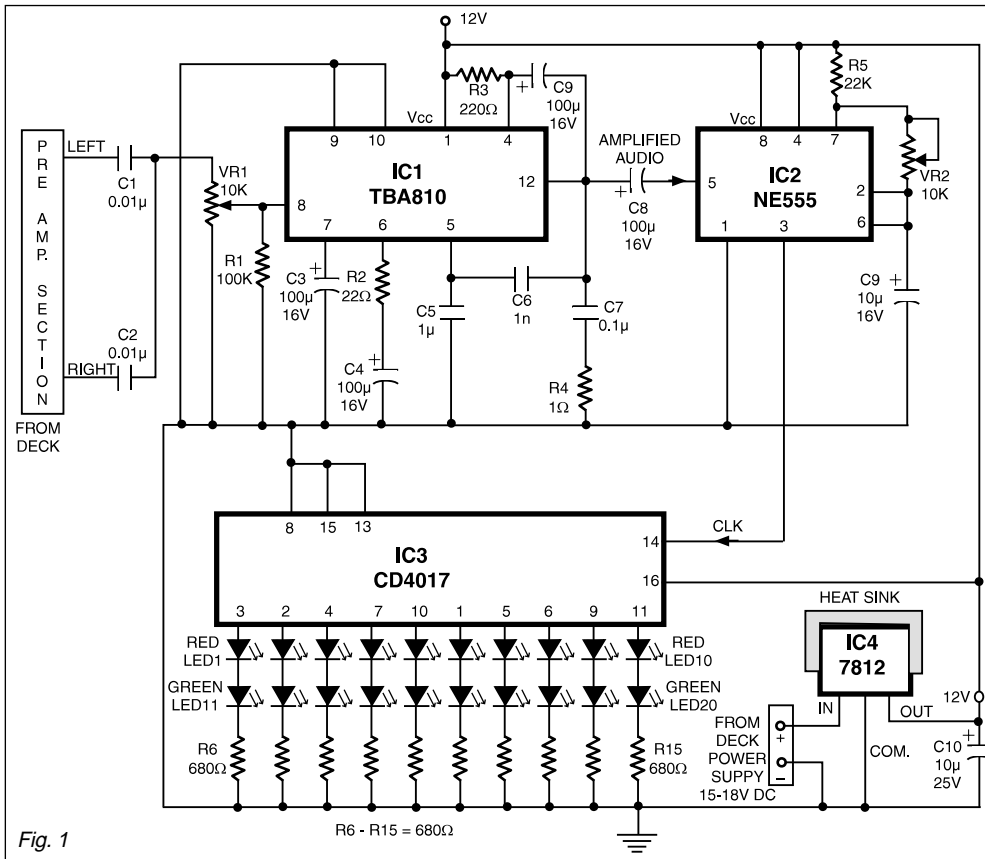


Fig. 1

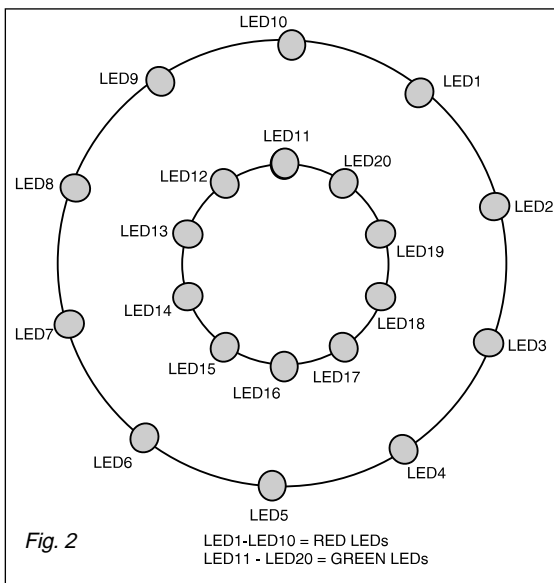


Fig. 2

LED1-LED10 = RED LEDs
LED11 - LED20 = GREEN LEDs

The audio output is not taken directly from the output of the deck (across speaker terminals) because the output across speaker terminals depends upon the setting of the volume control and would vary from one model to the other. Here, the left and the right outputs (in case of a stereo deck) are fed to the input of an audio amplifier IC TBA810, via capacitors C1 and C2 (0.01µF). These low-value capacitors help to maintain the required separation between left and right channels. Otherwise, at high frequencies the separation may fall tremendously, thereby short-circuiting L and R channels.

The 10k preset VR1 before IC TBA810 is used to control the output level so that at maximum output the potential at pin 5 of 555 is such that the frequency of 555 is between 1

and 15 Hz (approximately). Otherwise, all the LEDs at the output of IC3 will appear flickering. The other 10k preset VR2 is used to set the normal speed of the roulette, between 2 and 3 Hz. One point to be noted here is, that the audio signals should be taken from the output of preamplifier IC of the deck just before the volume control. The output will depend on the setting of volume control (which we do not want) if the taken after the volume control. The power supply for the circuit may be tapped from the power supply of the deck, as shown in Fig. 1. The power supply voltage in a deck is not exactly 12V DC, but is around 15 to 18V. It is preferable to connect a 7812 regulator IC for 12V regulation.

pin connected to the inverting terminal of a comparator inside the IC) is not grounded via a capacitor, but the potential at this pin is made to change in accordance with the audio level. This causes the internal flip-flop of timer NE555 to set and reset according to the audio level, and hence the output frequency varies correspondingly. This output is fed to the clock input pin of ring counter IC CD4017 whose output advances at a rate proportional to the clock input or the audio level present at pin 5 of IC2.

and 15 Hz (approximately). Otherwise, all the LEDs at the output of IC3 will appear flickering.

The other 10k preset VR2 is used to set the normal speed of the roulette, between 2 and 3 Hz. One point to be noted here is, that the audio signals should be taken from the output of preamplifier IC of the deck just before the volume control. The output will depend on the setting of volume control (which we do not want) if the taken after the volume control.

The power supply for the circuit may be tapped from the power supply of the deck, as shown in Fig. 1. The power supply voltage in a deck is not exactly 12V DC, but is around 15 to 18V. It is preferable to connect a 7812 regulator IC for 12V regulation.

CLEVER RAIN-ALARM

M.K. CHANDRA MOULEESWARAN



Usually rain-alarms employ a single sensor. A serious drawback of this type of sensor is that even if a single drop of water falls on the sensor, the alarm would sound. There is a probability that the alarm may be false. To overcome this drawback, here we make use of four sensors, each placed well away from the other at suitable spots on the roof. The rain alarm would sound only if all the four sensors get wet. This reduces the probability of false alarm to a very great extent.

The four rain-sensors SR1 to SR4, along with pull-up resistors R1 to R4 (connected to positive rails) and inverters N1 to N4, form the rain-sensor-monitor stage. The sensor wires are brought to the PCB input points E1 to E5 using a 5-core cable. The four outputs of Schmitt inverter gates N1 to N4 go to the four inputs of Schmitt NAND gate N7, that makes the alarm driver stage.

When all four sensors sense the rain, all four inputs to gates N1 through N4 go low and their outputs go high. Thus all



put of gate N7 is high if any one or more of the rain-sensor plates SR1 through SR4 remain dry. The output of gate N7 is coupled to inverter gates N5 and N6. The output from gate N5 (logic 1 when rain is sensed) is brought to 'EXT' output connector, which may be used to control other external devices. The output from the other inverter gate N6 is used as enable input for NAND gate N8, which is configured as a low-frequency oscillator to drive/modulate the piezo buzzer via transistor T1. The frequency of the oscillator/modulator stage is variable between 10 Hz and 200 Hz with the help of preset VR1. The buzzer is of piezo-electric type having a continuous tone that is interrupted by the low-frequency output of N8. The buzzer will sound whenever rain is sensed (by all four sensors).

6V power supply (100mA) is used here to enable proper interfacing of the CMOS and TTL ICs used in the circuit. The power supply requirement is quite low and a 6-volt battery pack can be easily used. During quiescent-state, only a negligible current is consumed by the circuit. Even during active state, not more than 20mA current is needed for driving a good-quality piezo-buzzer. Please note that IC2, being of TTL type, needs a 5V regulated supply. Therefore zener D1, along with capacitor C2 and resistor R5, are used for this purpose.

A parallel-track, general-purpose PCB or a veroboard is enough to hold all the components. The rain-sensors SR1 to SR4 can be fabricated as shown in the construction guide in Fig. 2. They can be made simply by connecting alternate parallel tracks using jumpers on the component side. Use some epoxy cement on and around the wire joints at A and B to avoid corrosion. Also, the sensors can be cemented in place with epoxy cement.

If the number of sensors is to be increased, just add another set of four inputs to NAND gate N7 along with the associated discrete components.

 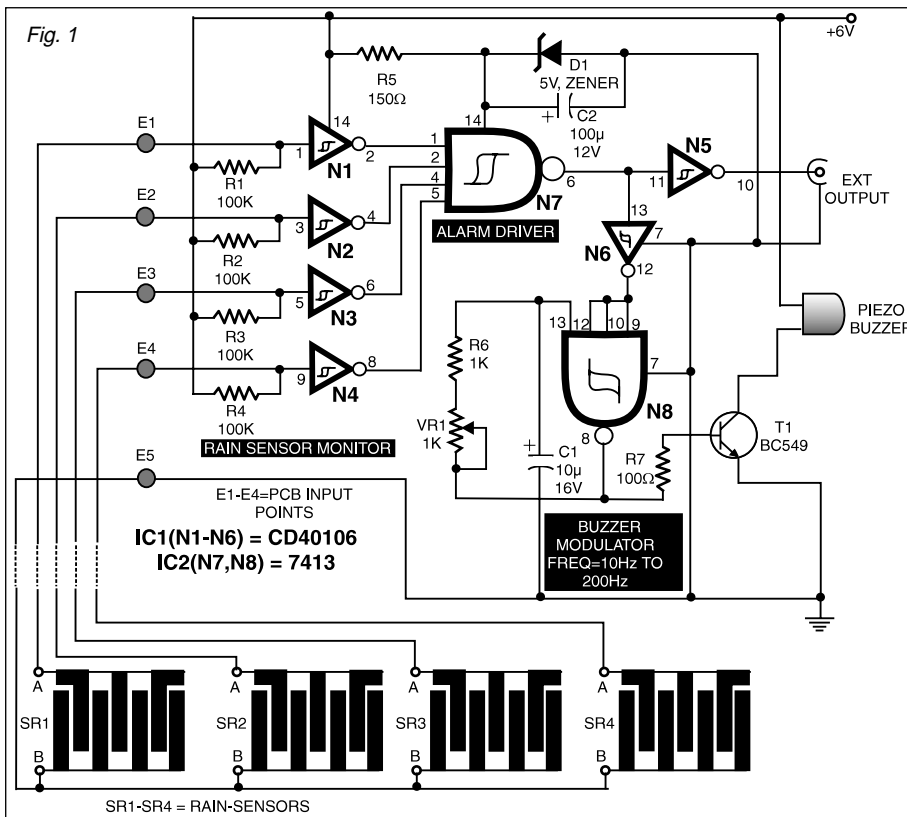Another good utility of the rain-alarm is in agriculture. When drip-irrigation is employed, fix the four sensors at four corners of the tree-pits, at a suitable height from the ground. Then, as soon as the water rises to the sensor's level, the circuit can be used to switch off the water pump.



LASER CONTROLLED ON/OFF SWITCH

Dr K.P. RAO




This circuit is built around a 555 timer using very few components. Since the circuit is very simple, even a novice can easily build it and use it as a controlling device. A laser

is factorily, though it can be controlled from still longer distances. Aiming (aligning) the laser beam exactly on to the LDR is a practical problem.

The circuit is very useful in switch-

only in dark or dull-lit environments.

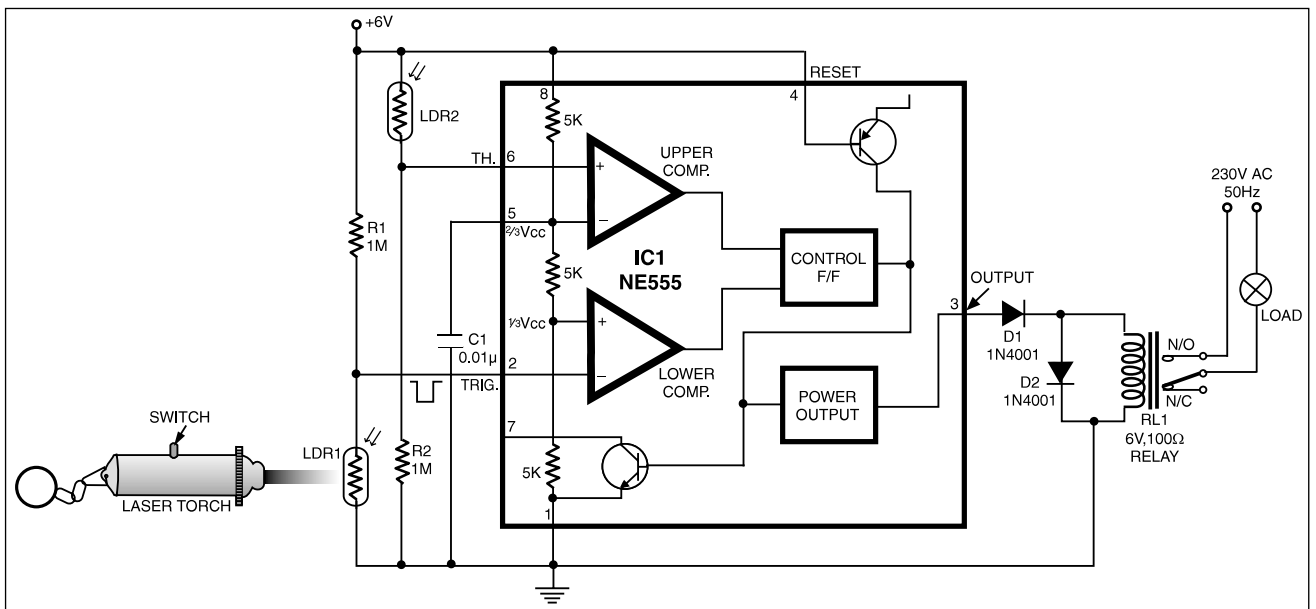By focussing the laser beam on LDR1 the connected gadget can be activated through the relay, whereas by focussing laser beam on LDR2 we can



pointer, now easily available in the market, can be used to operate this device.

This circuit has been tested in operational conditions from a distance of 500 metres and was found to work sat-

ing on/off a fan at night without getting off the bed. It can also be used for controlling a variety of other devices like radio or music system. The limitation is that the circuit is operational

switch off the gadget. The timer is configured to operate in bistable mode.

The laser pointers are available for less than Rs 150 in the market. The cost of the actual circuit is less than Rs 50.

TELEPHONE CONVERSATION RECORDER

PRADEEP VASUDEVA



This circuit enables automatic switching-on of the tape recorder when the handset is lifted. The tape recorder gets switched off when the handset is replaced. The signals are suitably attenuated to a level at which they can be recorded using the 'MIC-IN' socket of the tape recorder.

Points X and Y in the circuit are

connected to the telephone lines. Resistors R1 and R2 act as a voltage divider. The voltage appearing across R2 is fed to the 'MIC-IN' socket of the tape recorder. The values of R1 and R2 may be changed depending on the input impedance of the tape recorder's 'MIC-IN' terminals. Capacitor C1 is used for blocking the flow of DC.


The second part of the circuit controls relay RL1, which is used to switch on/off the tape recorder. A voltage of 48 volts appears across the telephone lines in on-hook condition. This voltage drops to about 9 volts when the handset is lifted. Diodes D1 through D4 constitute a bridge rectifier/polarity guard. This ensures that transistor T1 gets voltage of proper polarity, irrespective of the polarity of the telephone lines.

During on-hook condition, the output from the bridge (48V DC) passes through 12V zener D5 and is applied to the base of transistor T1 via the voltage divider comprising resistors R3 and R4. This switches on transistor T1 and its collector is pulled low. This, in turn,

causes transistor T2 to cut off and relay RL1 is not energised.

When the telephone handset is lifted, the voltage across points X and Y falls below 12 volts and so zener diode D5 does not conduct. As a result, base of transistor T1 is pulled to ground potential via resistor R4 and thus is cut off. Thus, base of transistor T2 gets forward biased via resistor R5, which results in the energisation of relay RL1. The tape recorder is switched 'on' and recording begins.

The tape recorder should be kept

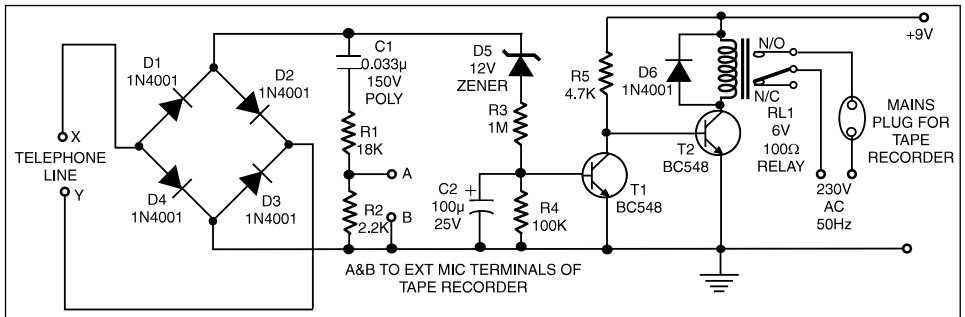

loaded with a cassette and the record button of the tape recorder should remain pressed to enable it to record the conversation as soon as the handset is

lifted. Capacitor C2 ensures that the relay is not switched on-and-off repeatedly when a number is being dialled in pulse dialing mode.

SIMPLE AND ECONOMIC SINGLE-PHASING PREVENTOR



PRAVINCHANDRA B. MEHTA

Three-phase motors and other appliances are widely used in all sectors of industry. These appliances are prone to damage due to single phasing. Apart from damage to the costly apparatus, it may also cause a production loss. Many circuits of single phasing preventor (SPP) are available but the circuit suggested here is very simple and economical.


Easily-available mains step-down transformers X1, X2, and X3 (230V AC primary to 0-12V, 500mA secondary rating) are used with their primaries connected in star mode and secondaries in open delta mode. The characteristic of this type of connection is that when three-phase balanced input is applied to the primaries, no output across open delta secondaries will be available. But in case of major unbalance or single-phasing, some voltage, called residual voltage, is induced in the secondaries across points 1 and 6 shown in

the circuit diagram. Three-phase supply is given to apparatus (load) through contactor C. While the primaries of transformers X1, X2, and X3 are connected ahead of the contactor. The contactor can be energised via N/C (normally closed) contacts of relay RL1 by pressing

switch S1.

As soon as single-phasing or major unbalance occurs, 8 to 12 volts are induced across point P1-P2, which after rectification operates relay RL1. As a result, the supply to contactor coil is cut off and it de-energises, thereby protecting the apparatus. Lamp L(d) is also lit up (unless B phase has failed), indicating that SPP has operated. Lamps L(a), L(b), and L(c) indicate the healthiness of three phases R, Y, and B. After resumption of the balanced 3-phase supply, the contactor will automatically energise (with S1 closed) and supply to the appliance will be resumed.

Notes: 1. In the actual circuit for-

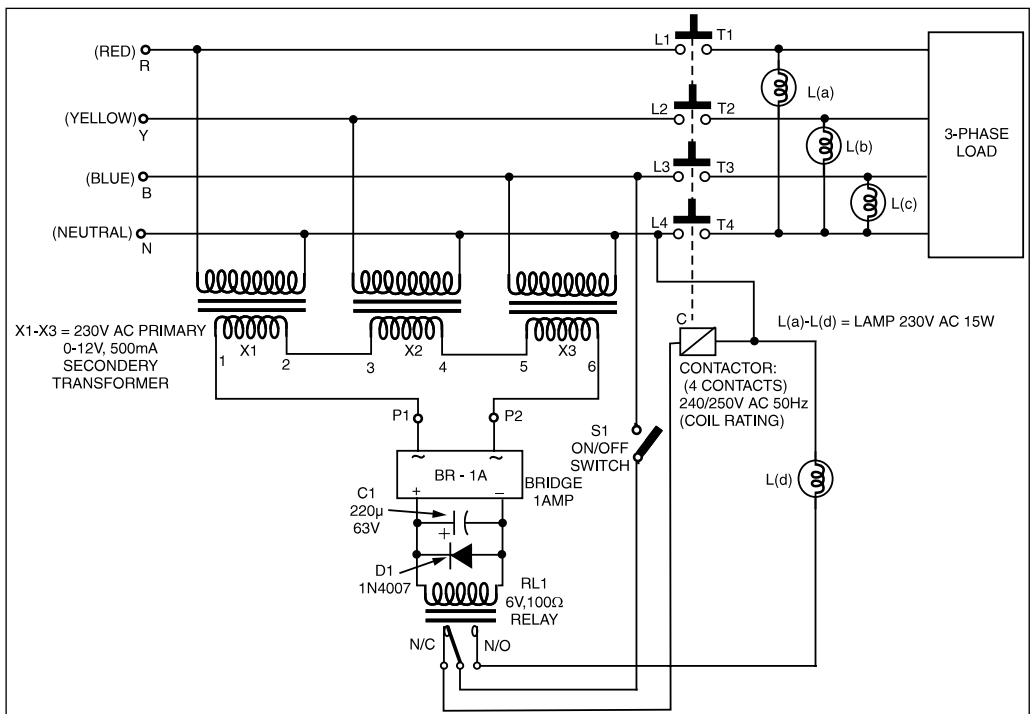

warded by the author, the transformers X1, X2, and X3 primaries as well as switch S1 were connected after the contacts of contactor. As a result energisation of contactor was not feasible. Even when switch S1 was shifted to a 'live' phase, relay RL1 (as well as contactor C) was energising/de-energising in quick succession during single-phasing and causing sparking—for obvious reasons. Hence the circuit was suitably modified at EFY (as presented).

2. The relay was also changed from 12V to 6V rating, as 12V relay was not

energising properly with single-phasing.

3. Proper polarity of the transformer connections has to be ensured in the above circuit. To determine proper polarity, connect the primary ends which are eventually to be connected to three phases, to any single phase (the other ends are connected to neutral). Now proceed to connect secondaries of two of the three transformers in series and measure the AC output across the unconnected ends. This should be double (24V AC) of the individual secondary output (12V AC). If it is not so, reverse one of

the two secondary connections to get the required output. Similarly, connect the third transformer secondary in series with the other two secondaries. The output across the unconnected ends should now be treble (36V AC). If it is not so, reverse the connections of the third secondary. Now shift the primary ends (connected to single phase) to each of the three phases, as shown in the figure. The voltage across points P1-P2 will be nearly zero if all three phases are present.

—Technical Editor

April

2000

SMART CLAP SWITCH

LOKESH KUMATH

Circuit of a smart clap switch, incorporating certain unique features, is presented here. It overcomes the shortcomings observed in normal clap switches. The following two special features, which you would not have observed in other clap switches, are included in its design:

(a) It comprises a 4x4 clap switch, i.e. it operates only when you clap four times to switch 'on' a device. Similarly, for switching 'off' the device, you are required to again clap four times.

(b) The clapping should occur within an interval of about 3.5 seconds, otherwise the clap switch status will remain unchanged.

In a simple clap switch, the connected device is switched 'on' by a single clap and is switched 'off' in a similar manner by a single clap. Since the transducer used in a clap switch is normally a condenser mic, it is unable to detect difference between a clap and a sound produced when a metallic object falls to the ground or simply the sound of a shouting person. This is a common problem in clap switches.

In the circuit of the smart clap switch, this problem is completely eliminated. Thus, it will not be affected by any spurious sound, including the one produced when a door is strongly banged. This can be well understood from the working of the circuit explained below.

The circuit

230V AC is converted into 12V regulated DC supply using 15-0-15,1A secondary, step-down transformer and other related components. Since CMOS ICs are used in the circuit, its power consumption is quite low and the noise immunity of the circuit is high (about 5.4V).

Resistor R1 biases the condenser microphone and the electrical signals (converted from sound waves) are fed to buffer stage N1 with high input impedance. The high-frequency noise signals are bypassed to ground by shunting the microphone with capacitor C1. The mic output is fed to a preamplifier stage built

around op-amp N2. The gain of preamplifier stage is 6.6.

The next stage comprising capacitor C4 and resistor R6 constitutes a high-pass filter with a cut-off frequency of about 3 kHz. This filter avoids false activation of the switch by spurious low-frequency sounds such as those produced by a fan, a motorcycle, and other gadgets. Although this precaution may not be absolutely essential because we are using a coded sound, it provides additional safety.

The high-pass filter stage is followed by an amplifier stage around op-amp N3 with a gain of 23. Thus, the overall gain of the op-amps N2 and N3 is about 150, which is quite adequate.

The next stage formed using op-amp N4 is a comparator. The reference voltage connected to the inverting terminal of the comparator can be varied, from about 0.2V to about 8V, by adjusting preset VR1. Thus, the sensitivity to clap sound can be set by preset VR1. The red LED D1 gives an indication that the clap signal has been detected.

[Note: IC6 (NE555), configured as a monostable, with a pulse width of 250 ms, has been added at EFY lab during the course of testing, to eliminate the effect of multiple pulses generated at the output of comparator N4, even with a single clap.]

The main control section is formed around IC5 (74C192 or CD40192), which is a 4-bit up/down presettable decade counter. 74C192/CD40192 is a CMOS version of 74192. Here, one can even use 74C193/CD40193, a 4-bit up/down binary counter, since counting up to decimal digit 8 only is involved. The above-mentioned

TABLE I				
Q _D	Q _C	Q _B	Q _A	Switch/Device status
0	0	0	0	Device remains 'off' in this region as Q _C remains at logic low
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	Device remains 'on' in this region as Q _C remains at logic high
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	Device is reset to off state (unstable state)



ICs are pin-to-pin compatible.

The other ICs used in the control section are IC3 (dual JK flip-flop) and IC4 (NE555 timer, configured as monostable flip-flop). When power is applied to the circuit, IC3, IC4, and IC5 are reset by power-on reset circuits comprising capacitor-resistor combinations of C14-R19, C11-R16, and C15-R21 respectively. Thus, all outputs of IC5 (Q_A to Q_D) are at logic zero. Hence, all the parallel load inputs (A through D) of IC5 are also at logic zero. The Q outputs of IC3 are 'low' while its \bar{Q} outputs are 'high'. The CLK2 input of IC3 is initially 'high' because transistor T1 is in conduction state.

Now, when a clap sound is produced, IC5 gets a low-to-high going clock pulse. Its count goes up from 0000 to 0001, i.e. it is incremented by one digit. Since Q_A

PARTS LIST

Semiconductors:

IC1	- LM324 quad op-amp
IC2	- 7812 +12V regulator
IC3	- CD4027 dual JK flip-flop
IC4, IC6	- NE555 timer
IC5	- 74C192 up/down decade counter
D1, D9	- Colour LED
D2-D4, D8	- 1N4007 rectifier diode
D5-D7	- 1N4148 switching diode
T1, T2	- 2N2907 pnp transistor
T3	- 2N2222 npn transistor

Resistors (all 1/4W, ±5% metal carbon film, unless stated otherwise)

R1, R15, R26	- 10-kilo-ohm
R2, R3, R18,	
R19, R21	- 100-kilo-ohm
R4, R7, R9,	
R13, R14, R16	
R20, R22, R23	- 1-kilo-ohm
R5, R6	- 5.6-kilo-ohm
R8, R24	- 22-kilo-ohm
R10	- 220-ohm
R11	- 4.7-kilo-ohm
R12	- 680-ohm
R17	- 33-kilo-ohm
R25	- 470-ohm
VR1	- 10-kilo-ohm preset

Capacitors:

C1	- 47nF ceramic disk
C2, C3	- 4.7µF, 25V electrolytic
C4, C6-C8, C12,	
C18	- 0.01µF ceramic disk
C5, C10, C13	- 100µF, 25V electrolytic
C9	- 2200µF, 25V electrolytic
C11, C17	- 10µF, 25V electrolytic
C14, C15, C16	- 0.1µF ceramic disk

Miscellaneous:

RL1	- 12V, 200-ohm relay
MIC1	- Condenser microphone
X1	- 230V AC primary to 15V-0-15V, 1A secondary transformer
	- Heat-sink
F1, F2	- 1A fuse

goes from 'low' to 'high', it acts as a clock (CLK1) for first section of IC3. As a result Q1 of the IC3 goes 'low' to trigger IC4, which produces a pulse of about 3.5-second duration at its output pin 3. The output of IC4 is inverted by transistor T1, which toggles the second JK flip-flop inside IC3. As a consequence, its Q2 output goes 'low' and the count present at the parallel load inputs are loaded. The parallel count loaded depends on the number of clock pulses arriving at IC5 within these 3.5-seconds, which again depends on the number of claps produced within the same period. Table I shows the status at parallel inputs of IC5 and the status of relay RL1 or the device connected via the normally-open contacts of the relay to the supply.

The first clap activates the monostable flip-flop IC4. It is clear from Table I that if no further claps occur within 3.5 seconds of the first clap, the parallel inputs to IC5 become 0000 be-

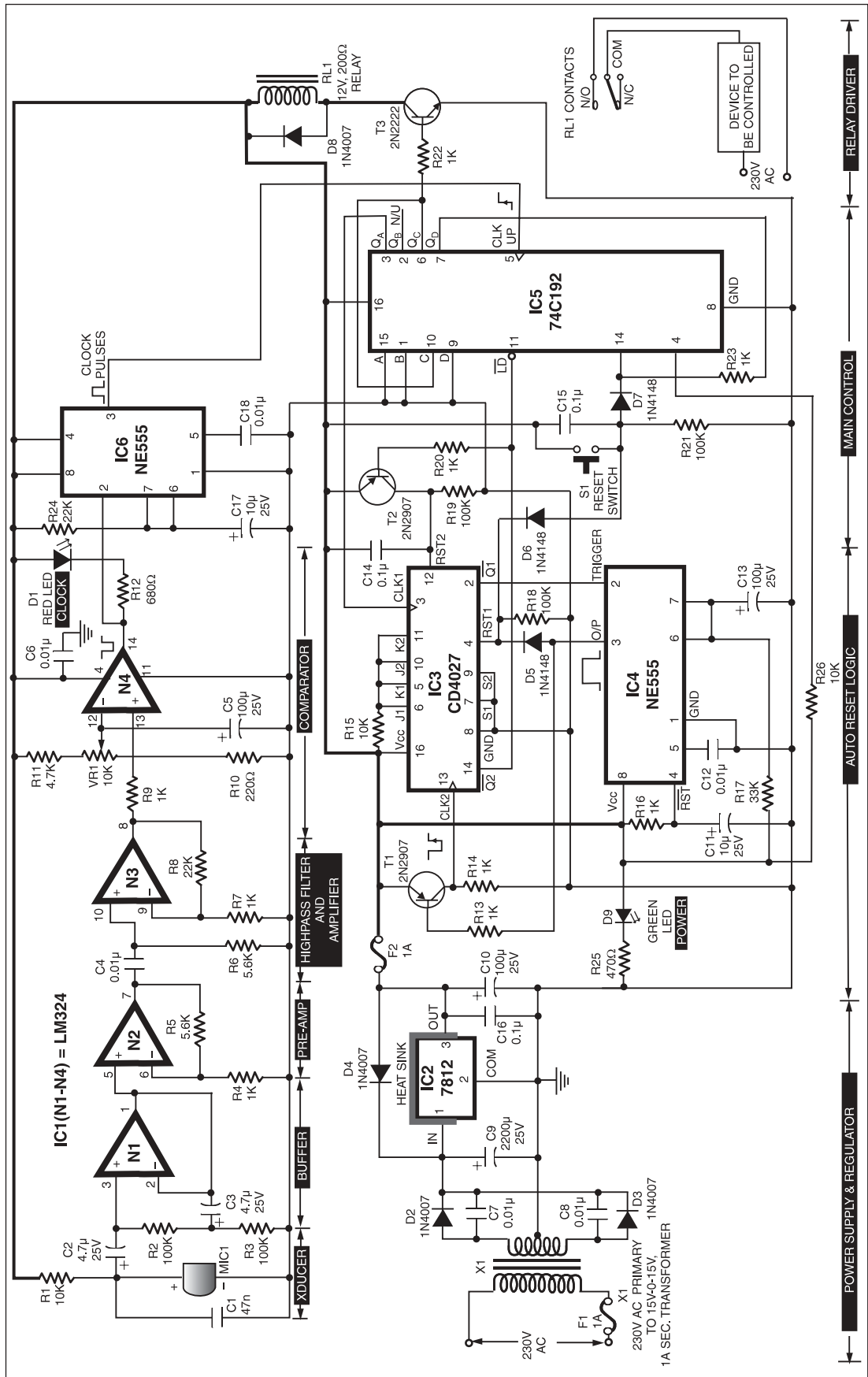


Fig. 1: Schematic diagram of smart clap switch

 


Fig. 2: Actual-size, single-sided PCB layout for the circuit

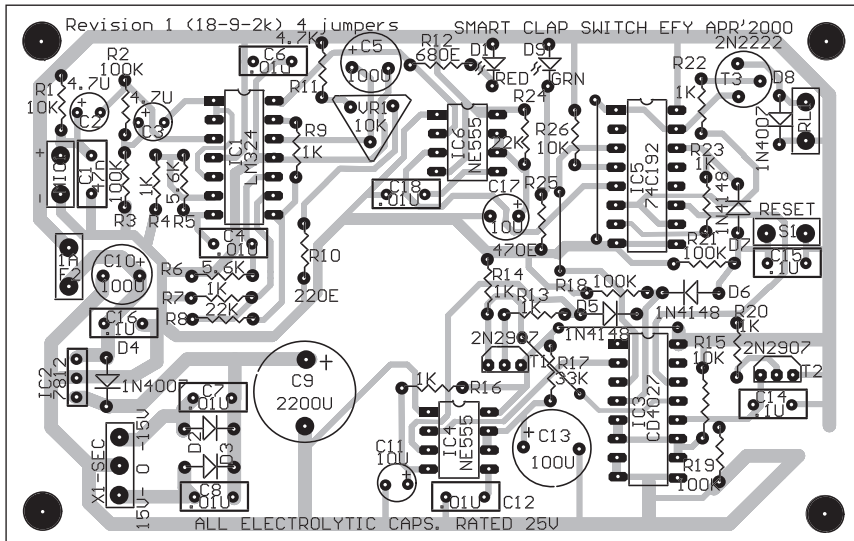


Fig. 3: Component layout for the PCB

cause Q_C output (connected to C input) would still be 'low' when load input becomes active low, at the end of 3.5-second period. Thus 0000 is loaded into IC5, thereby keeping the relay or the device connected

to the switch in its previous state.

This happens up to a total of three claps occurring within the allotted time duration of 3.5-seconds. But if three more claps occur after the first clap, within the

allotted 3.5-second time, the output of IC5 becomes 0100 and the connected device turns 'on'. At this stage, the parallel input is 0100 and therefore, on parallel loading, the output of IC5 keeps the device in the 'on' state.

Even if a total of seven claps occur (i.e. three more claps after the device is 'on'), the counter remains loaded with 0100, thereby resetting the device to its previous state. Thus, once the device is 'on', it requires a total of four claps within 3.5 seconds to turn 'off' the device. This happens because at the fourth clap count, the output reaches 1000 (from its previous output of 0100). As a result, Q_D becomes 'high', and IC3 and IC5 are reset to their initial state.

Diode D5 is used to reset flip-flop 1 of IC3, once IC4 has been triggered. Transistor T2 is used to reset flip-flop 2 of IC3 when a \overline{LD} pulse has been applied to IC5. Manual reset switch S1 (tactile type) is used to switch off the connected device, at any instant. It thus serves as an 'emergency off' switch.

Precautions. The microphone should be soldered as close to the PCB as feasible, using shielded wire. Heat-sink should be provided for the regulator IC2. If you desire to change the timings within which claps should occur, use the formula given below to calculate the values of timing resistor R and capacitor C for the pulse width of a monostable flip-flop using timer IC NE555.

$$t = 1.1 RC \text{ seconds}$$

where t is the time for which output goes 'high', R is the value of R17 in ohms, and C is the value of C13 in farads.

Finally, a switch across 'common' and 'N/O' contacts of the relay may be used to bypass the smart clap switch, if desired.

Actual-size, single-sided PCB for the circuit shown in Fig. 1 is given in Fig. 2. Component layout for the PCB is given in Fig. 3. □

ELECTRONIC VOTING MACHINE

JUNOMON ABRAHAM



Now-a-days electronic voting machines are being used effectively. The confidence of the voter in its flawless working is gradually building up and these machines are thus becoming quite popular throughout the country. (Please note that the design being presented here is not intended to resemble that of electronic voting machines used by the Election Commission. If any resemblance is noticed between the two, it is totally unintended.) Features of the electronic voting machines include avoidance of invalid votes and reduction of counting time and the consequent expenditure incurred on manpower deployment.

Hardware description

The voting machine circuit being described here is designed around Intel's basic 8085 microprocessor. It has two main units:

- (i) control and processing unit, and
- (ii) keyboard and display unit.

Keyboard and display are interfaced through a general-purpose programmable peripheral interface (PPI) IC 8255. The system monitor programs are stored in 2732 EPROM. RAM 6116 is used for storing counts and a portion of it is also used as stack. IC 74LS373 (octal D-type latch) is used for segregating the lower order address bits from multiplexed address/data bus of 8085. Two of the higher order bits are decoded by 74LS138 to generate chip select signals for IC4 through IC6. The address/address range for each device is shown in Table I. Please note that during I/O read/write instructions in μP

TABLE I
Address Map of Devices Used

Address (Hex)	Device
0000-01FF	EPROM
8000-80FF	RAM
C0	Port A
C1	Port B
C2	Port C
C3	Control port

} of 8255

Here we have used ports B and A as output ports and port C as input port.

8085, the 8-bit address used is duplicated on lower (AD0-AD7) as well as higher (A8-A15) address bus.

The system runs with a clock frequency of 1.79 MHz (i.e. half the crystal oscillator frequency of 3.58 MHz). Auto reset facility is incorporated in this system for avoiding corruption of count during interruption in power supply. This is achieved by using the latching property of SCR. A battery backup (3x1.5V UM3 type) is provided for RAM chip to retain the latest counts.

The control and processing unit comprises the 8085 microprocessor, memory (EPROM and RAM), and some function switches. To get an overview of the voting machine, we shall start with the explanation of the functional switches.

Start switch (S48). When the circuit is initially powered on, it is in reset state due to the auto reset facility. If you want to activate the system, press the 'start' button. This causes the SCR to conduct and take $\overline{\text{RS}}$ pin 36 of 8085 to logic 'high'. As a result 8085 microprocessor becomes active. In this state, the microprocessor will execute the booting program (starting at location/address 0000H).

Clear switch (S52). This switch is used for clearing the previous count in memory. When pressed, the RST 5.5 interrupt starting at location 002CH is activated. Here the vector (0100H) pointing to the sub-routine for clearing the memory contents is stored.

Display switch (S50). This switch activates RST 7.5 interrupt (location 003CH) containing vector for executing 'display routine' used for displaying the count of the votes polled by any candidate. If one wants to see the count of a specific candidate, 'display' switch is pressed first, followed by the depression of the switch on the keyboard allocated to the specific candidate.

Count switch (S51). This switch activates RST 6.5 interrupt (location 0034H, containing the jump address 00B6 for count subroutine) for activating the microprocessor to accept only one vote for a

candidate, by depressing the keyboard switch allocated to that candidate.

Reset switch (S49). If any malfunctioning is observed during the operation of the voting machine, the RESET switch can be used to shut down the system.

This voting machine has the capability to handle up to 48 candidates. Each switch on the keyboard represents one specific candidate. If one does not need all the 48 switches, only the required number of switches need to be wired. The remaining keyboard switches can be done away with. In this unit, LED D4 is used to indicate that the system is ready for accepting the next (one) vote.

Operating Procedure

1. Switch 'on' the power, using switch S53.
2. Press 'start' button.
3. A software-based security feature has been added in this system which requires one to enter the password digits via the keyboard for getting access to the machine for its operation. (The maximum length of password is seven digits, but it

PARTS LIST

Semiconductors:

IC1	- 8085A microprocessor
IC2	- 74LS373 octal latch
IC3	- 74LS138 decoder/demultiplexer
IC4	- 27C32 EEPROM
IC5	- 6116A RAM
IC6	- 82C55 programmable peripheral interface
IC7	- 74LS47, BCD to 7-segment decoder/driver
IC8	- 7805, +5V regulator
T1-T4	- BC547 npn transistor
D1, D3	- 1N4001 rectifier diode
D2, D4	- Colour LED
SCR1	- BT169

Resistors (all $\frac{1}{4}W$, $\pm 5\%$ metal carbon film, unless stated otherwise)

R1-R3	- 330-ohm
R4-R11	- 3.3-kilo-ohm
R12	- 47-ohm
R13, R22, R23	- 2.2-kilo-ohm
R14	- 680-ohm
R15-R21	- 68-ohm

Capacitors:

C1	- 10pF ceramic disc
C2	- 0.1 μF ceramic disc

Miscellaneous:

Xtal	- 3.58MHz crystal
S53	- On/off switch
S0-S52	- Tactile switch
P21	- Piezo buzzer
DIS1-DIS4	- LT542 common-anode display
	- 4.5V battery

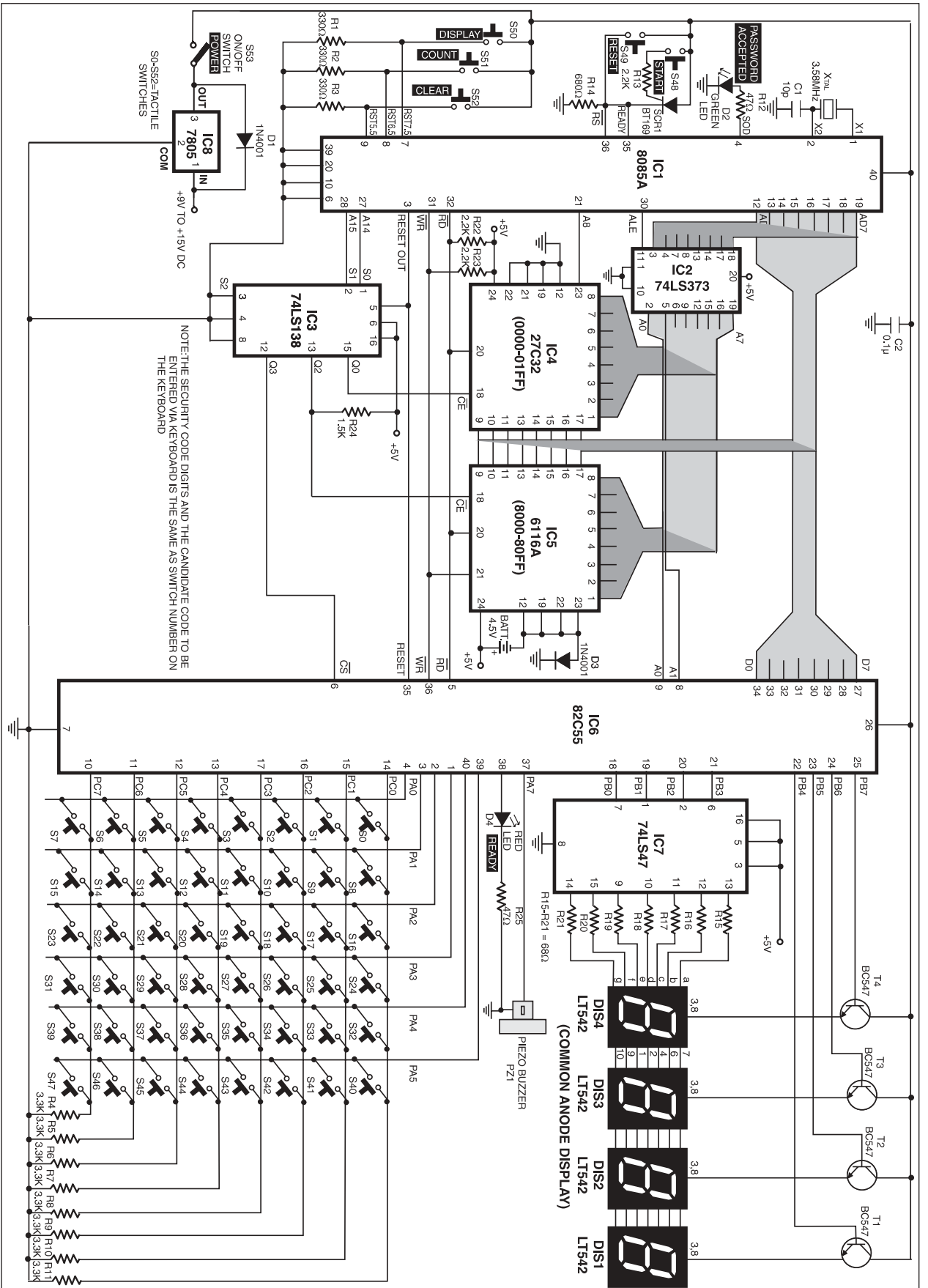


Fig. 1: Schematic diagram of the electronic voting machine.

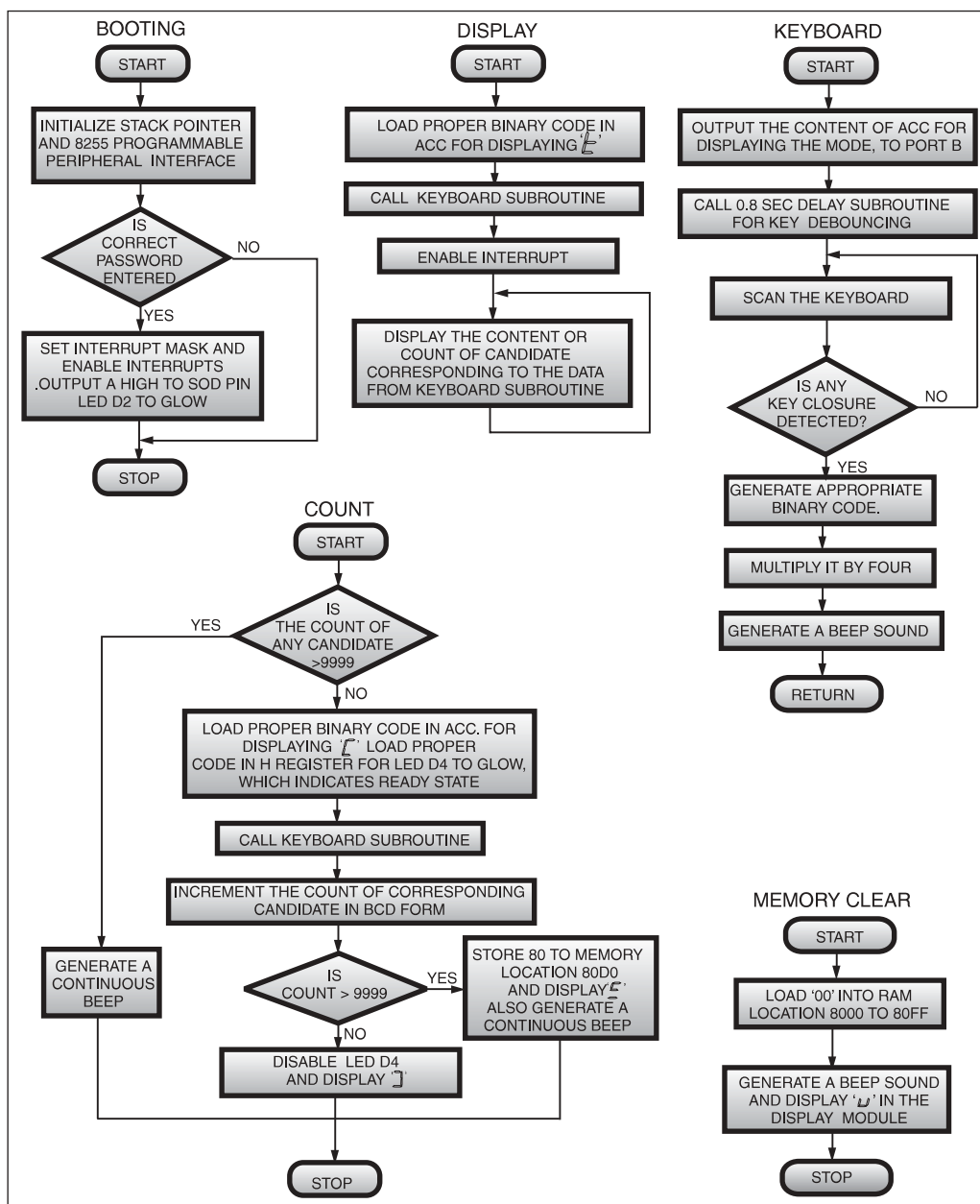


Fig. 2: Flow chart for the various software programs

can be changed by adjusting some values in the system software.) At present, only three-digit password is used. If the password digits entered via keyboard equal the password stored in the EPROM, LED D2 glows to give access for operation of the machine.

4. If the entered password is incorrect, press RESET button (S49) and proceed again from the first step.

5. Clear the previous content of count memory by pressing 'clear' button (S52). Clearance of memory is indicated by symbol 'E' in the display.

6. Now press 'count' switch S51. The

display of symbol 'E' and the glowing of LED D4 would mean that the system is ready for accepting one vote. (Please note that the 'count' switch is placed under the control of electoral staff so that it is satisfied with the identity of the voter before allowing him/her to cast his/

Address (hex)	Interrupt
0024	TRAP
002C	RST 5.5
0034	RST 6.5
003C	RST 7.5

her vote.)

7. Now, the voter can cast his/her vote by pressing the appropriate keyboard switch allocated to the candidate of his/her choice. The acceptance of the vote by the system is acknowledged by a beep sound as well as the display of the 'E' symbol in the display and 'off' condition of LED D4.

8. Steps 6 and 7 have to be repeated for casting a fresh vote.

9. If the count of any particular candidate's votes (count) is needed to be displayed, press 'display' switch and then the switch corresponding to the specific candidate on the keyboard.

10. Reset the system.

11. Switch 'off' the system.

Software description

The system programs are stored in the EPROM. The entire software is divided into five modules, namely, booting, display, clearing memory, counting, and keyboard.

The operation of each module can easily be understood with reference to the flowcharts.

Booting. This module initialises the stack pointer 8255 PPI, verifies the password entered via the

keyboard, and initialises the interrupts.

Display. This module uses the interrupt service subroutine at RST 7.5. This is used for displaying the count (votes) polled by each of the candidates.

Clearing memory. This module is invoked via interrupt service subroutine RST 5.5. It is used to clear the count memory.

Counting. This module uses the interrupt service subroutine RST 6.5. It activates the microprocessor to accept only one vote. If the count of any candidate exceeds '9999', it will produce a continuous beep sound and display 'E', and then onwards the system will not be ready for

 


Fig. 3: Actual-size, single-sided PCB layout for the circuit

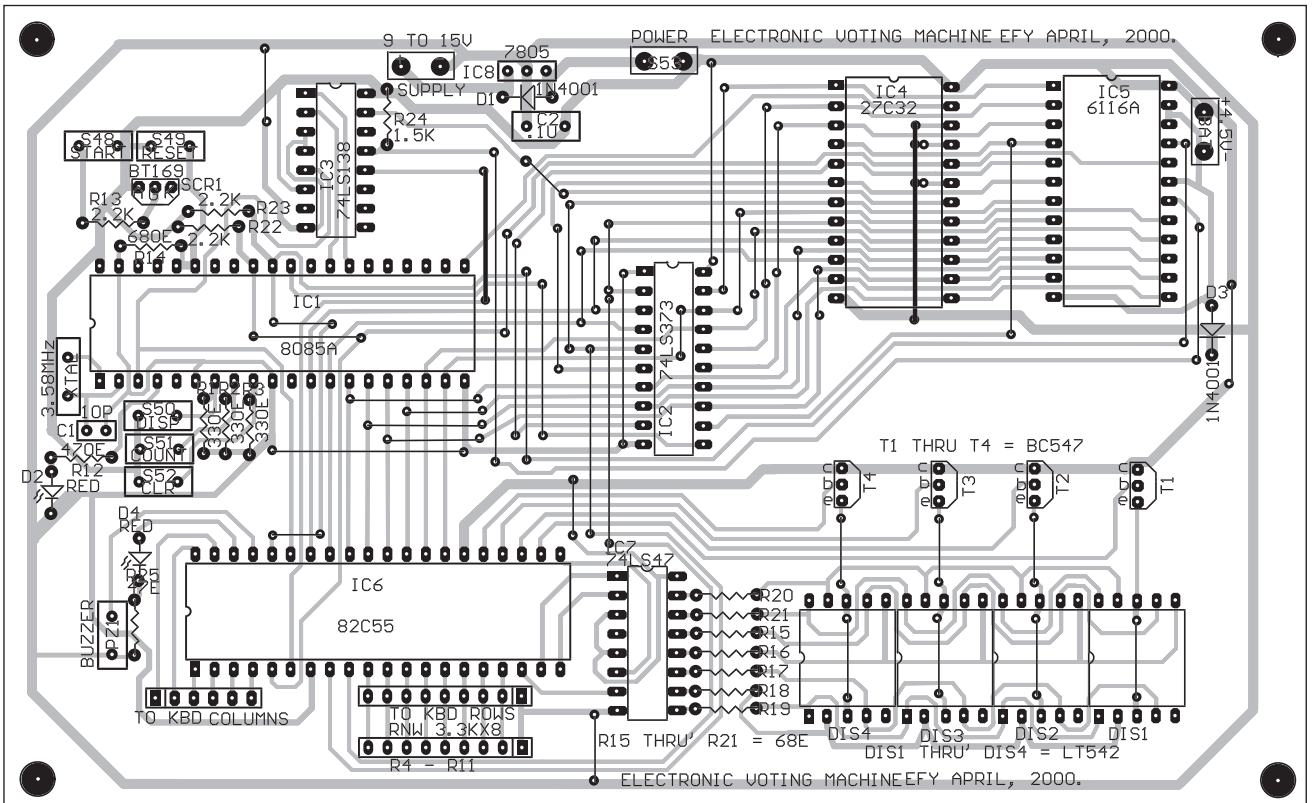


Fig. 4: Component layout for the PCB

accepting any further vote. Thus, the maximum number of votes that can be registered against any one candidate should not exceed 9999. This is the limitation in the present design.

Keyboard. This module is used for checking key closure and generating the binary value corresponding to the closed switch.

Password security

This voting machine has a password option. The length of the password is limited

to a maximum of seven digits. The password should be decided before burning the program in the EPROM. Password checking is performed during execution of booting program. For entering the password, the same keyboard switches are used that otherwise represent specific candidates.

For the setting of password (PW), the length of PW is chosen first and then it is loaded into register C using instruction 'MVI A, length' in the booting program. The digits of the password are stored in memory locations 00F9H to 00FFH. Each of the PW digits chosen has to be multi-

plied by 4 and converted into hex format, and then stored in consecutive memory locations starting from 00F9H. For example, if the PW is 1, 4, 8, the length is loaded as 03 in register C and the data is as follows:

EPROM location	Hex data	Conversion	PW digit
00F9	← 04	← 04H ← 04 ← 4x1	1
00FA	← 10	← 10H ← 16 ← 4x4	4
00FB	← 20	← 20H ← 32 ← 4x8	8

An actual-size, single-sided PCB for the circuit shown in Fig. 1 is given in Fig. 3, while its component layout is given in Fig. 4.

Software Listings

Address Opcode Mnemonics Comments

Booting Program

0000	31 FF 80	LXI SP, 80FF	Initialise SP
0003	3E 89	MVI A, 89	Initialise 8255
0005	D3 C3	OUT, C3	Port A, B = input, Port C = output
0007	11 F9 00	LXI D, 00F9	Load Stored Password (PW)
000A	0E 03	MVI C, 03	Password length = 3 digits
000C	C5	PUSH B	
000D	D5	PUSH D	
000E	AF	XRA A	Makes contents of Acc. zero
000F	67	MOV H, A	Make H reg contents zero
0010	CD 70 00	CALL KEYBOARD	
0013	D1	POP D	
0014	C1	POP B	
0015	1A	LDAX D	Load Acc. from mem loc pointed by DE
0016	BD	CMPL	
0017	C2 23 00	JNZ 0023	If PW is incorrect, stop execution
001A	13	INX D	
001B	0D	DCR C	
001C	C2 0C 00	JNZ, 000C	
001F	3E C8	MVI A, C8	If PW is right, enable the interrupts and glow the LED (D2) to indicate that the system is energised
0021	30	SIM	
0022	FB	EI	
0023	76	HLT	

RST 5.5 (contains vector for memory clearing subroutine)

002C	00	NOP	
002D	C3 00 01	JMP	Jump to Interrupt Service Subroutine MEMCLEAR

RST 6.5 (contains vector for count subroutine)

0034	00	NOP	
0035	C3 B6 00	JMP COUNT	Jump to Interrupt Service Subroutine COUNT

RST 7.5 Display subroutine

003C	00	NOP	
003D	00	NOP	
003E	31 FF 80	LXI SP, 80FF	Initialise SP
0041	3E 1E	MVI A, 1E	Load data byte for displaying
0043	26 00	MVI H, 00	display mode indicator 'E'
0045	CD 70 00	CALL KEYBOARD	Check key closure
0048	FB	EI	
0049	E5	PUSH H	
004A	06 10	MVI B, 10	Scan the display
004C	7E	MOV A, M	
004D	B0	ORA B	

Address Opcode Mnemonics Comments

004E	DE C1	OUT C1	
0050	11 7F 01	LXID 017F	
0053	1B	DCX D	
0054	7A	MOV A, D	
0055	B3	ORA E	
0056	C2 53 00	JNZ 0053	
0059	23	INX H	
005A	78	MOV A, B	
005B	07	RLC	
005C	47	MOV B, A	
005D	D2 4C 00	JNC 004C	
0060	E1	POP H	
0061	C3 49 00	JMP 0049	

Keyboard subroutine

0070	D3 C1	OUT C1	Display the mode
0072	CD 20 01	CALL DELAY(O/P contents of Acc. thro Port B)	
0075	FB	EI	
0076	1E 00	MVI E, 00	Scan the keyboard
0078	3E 80	MVI A, 80	
007A	06 06	MVI B, 06	
007C	07	RLC	
007D	6F	MOV L, A	
007E	B4	ORA H	
007F	D3 C0	OUT C0	
0081	DB C2	IN C2	
0083	0E 08	MVI C, 08	
0085	0F	RRC	
0086	DA 9C 00	JC 009C	
0089	1C	INR E	
008A	16 7F	MVI D, 7F	
008C	15	DCR D	
008D	C2 8C 00	JNZ 008C	
0090	0D	DCR C	
0091	C2 85 00	JNZ 0085	
0094	7D	MOV A, L	
0095	05	DCR B	
0096	C2 7C 00	JNZ 007C	
0099	C3 76 00	JMP 0076	
009C	F3	DI	
009D	7B	MOV A, E	If closed key is sensed, multiply the key number by 4
009E	07	RLC	
009F	07	RLC	
00A0	6F	MOV L, A	
00A1	3E 80	MVI A, 80	
00A3	67	MOV H, A	
00A4	D3 C0	OUT C0	Generate a beep
00A6	CD 20 01	CALL DELAY	
00A9	AF	XRA A	
00AA	D3 C0	OUT C0	
00AC	C9	RET	

Address	Opcode	Mnemonics	Comments
Count subroutine			
00B6	31 FF 80	LXI SP, 80FF	
00B9	3A D0 80	LDA 80D0	Load contents of mem loc 80D0
00BC	FE 80	CPI 80	If overflow occurs, generate
00BE	C2 C4 00	JNZ 00C4	continuous beep
00C1	D3 C0	JNZ 00C4	
00C3	76	HLT	
00C4	3E 1A	MVI A, 1A	If there is no overflow,
00C6	26 40	MIV H, 40	load data byte for displaying count
00C8	CD 70 00	CALL	count mode indicator '□' and
		KEYBOARD	glowing LED D4
00CB	0E 04	MIV C, 04	Increment the count of the key
00CD	7E	MOV A, M	number (candidate code) pressed
00CE	3C	INR A	Increment Acc
00CF	77	MOV M, A	Move mem (HL) to Acc.
00D0	FE 0A	CPI 0A	
00D2	C2 EB 00	JNZ 00EB	
00D5	36 00	MVI M, 0	If it becomes 10, make mem (HL)=0
00D7	23	INX H	
00D8	0D	DCR C	
00D9	C2 CD 00	JNZ 00CD	
00DC	2B	DCX H	
00DD	36 0D	MVI M, 0D	
00DF	3E 80	MVI A, 80	If overflow occurs, store 80 to
00E1	D3 C0	OUT C0	memory locatio 80D0 and display
00E3	32 D0 80	STA 80D0	'□'. Also generate a
00E6	3E 1D	MVI A, 1D	continuous beep
00E8	D3 C1	OUT C1	
00EA	76	HLT	
00ED	D3 C1	OUT C1	Success display '□'
00EF	FB	EI	

Address	Opcode	Mnemonics	Comments
00F0	76	HLT	
Password data			
00F9	04		See text
00FA	10		
00FB	20		
Memory clear subroutine			
0100	21 00 80	LXIH 8000	
0103	36 00	MVI M, 00	Load '00' to RAM areas
0105	2C	INR L	
0106	C2 03 01	JNZ 0103	
0109	3E 80	MVI A, 80	After clearing, generate
010B	D3 C0	OUT C0	a beep and display '□'
010D	CD 20 01	CALL DELAY	
0110	3E 1C	MVI A, 1C	
0112	D3 C1	OUT C1	
0114	AF	XRA A	
0115	D3 C0	OUT C0	
0117	FB	EI	
0118	76	HLT	
0.8 sec Delay Subroutine			
0120	F5	PUSH PSW	
0121	C5	PUSH B	
0122	01 FF FF	LXI B, FFFF	
0125	0B	DCX B	
0126	78	MOV A, B	
0127	B1	ORA C	
0128	C2 25 01	JNZ 0125	
012B	C1	POP B	
012C	F1	POP PSW	
012D	C9	RET	

www.electronicsforu.com

a portal dedicated to electronics enthusiasts

WATER-TANK LEVEL METER



M.K. CHANDRA MOULEESWARAN

The water-tank level meter described here is very simple and useful for monitoring the water level in an overhead tank (OHT). The water level at 30cm intervals is monitored and continuously indicated by LEDs arranged in a meter-format. When all the LEDs are 'off', it indicates that the OHT is empty. When the water level reaches the top limit, the whole LED-meter begins to flash.

The height at which the level-sensing electrodes are fitted is adjustable. Thus, the minimum and maximum level settings may be varied as desired. The range of the meter can also be enlarged to cater to any level.

No special or critical components are used. CMOS ICs are used to limit the idle current to a minimum level.

Even when all the LEDs are 'on', i.e. water reaches the top level, the demand on the power supply is reasonably low. Further, the extremely high input resistance of the Schmitt inverter gates reduces the input current and thus minimises the erosion of electrodes.

The principal part of the device is its water-level sensor assembly. By using easily


available material, it can be fabricated to meet one's own specific requirements.

The common ground reference electrode 'X' is an aluminium conduit of 15mm outer diameter and 3-metre length, to cater to a 3-metre deep overhead tank. Insulating spacer rings 'Y' (10mm length, 15mm dia.) are fabricated from electrical wiring conduits of 15mm inner diameter. These are pushed tightly over the aluminium conduit at preferred places, say 30cm apart. If the pieces are too tight, they can be heated in boiling water for softening and then pushed over 'X'.

The sensor electrodes 'Z' are made out

of copper or brass strips (6mm wide and 1mm thick) which are shaped into rings that can tightly slip over the 'Y' pieces. The ends of these strips are folded firmly and formed into solder tags S1 to S10 and SG. The wall-mounting brackets, made of aluminium die-cast, are screwed directly on 'X' at two suitable places. The sensor cable 'WC' wires are soldered to solder tags, and some epoxy cement is applied around the joints and tags to avoid corrosion by water. The common ground reference wire 'SG' is taken from tag 'T'. The cable's individual wires from S1 to S10 and SG are cut and matched in length for a neat layout. The other ends of the cable are connected to the PCB terminal points S1 to S10 and SG respectively. No separate ground is needed.

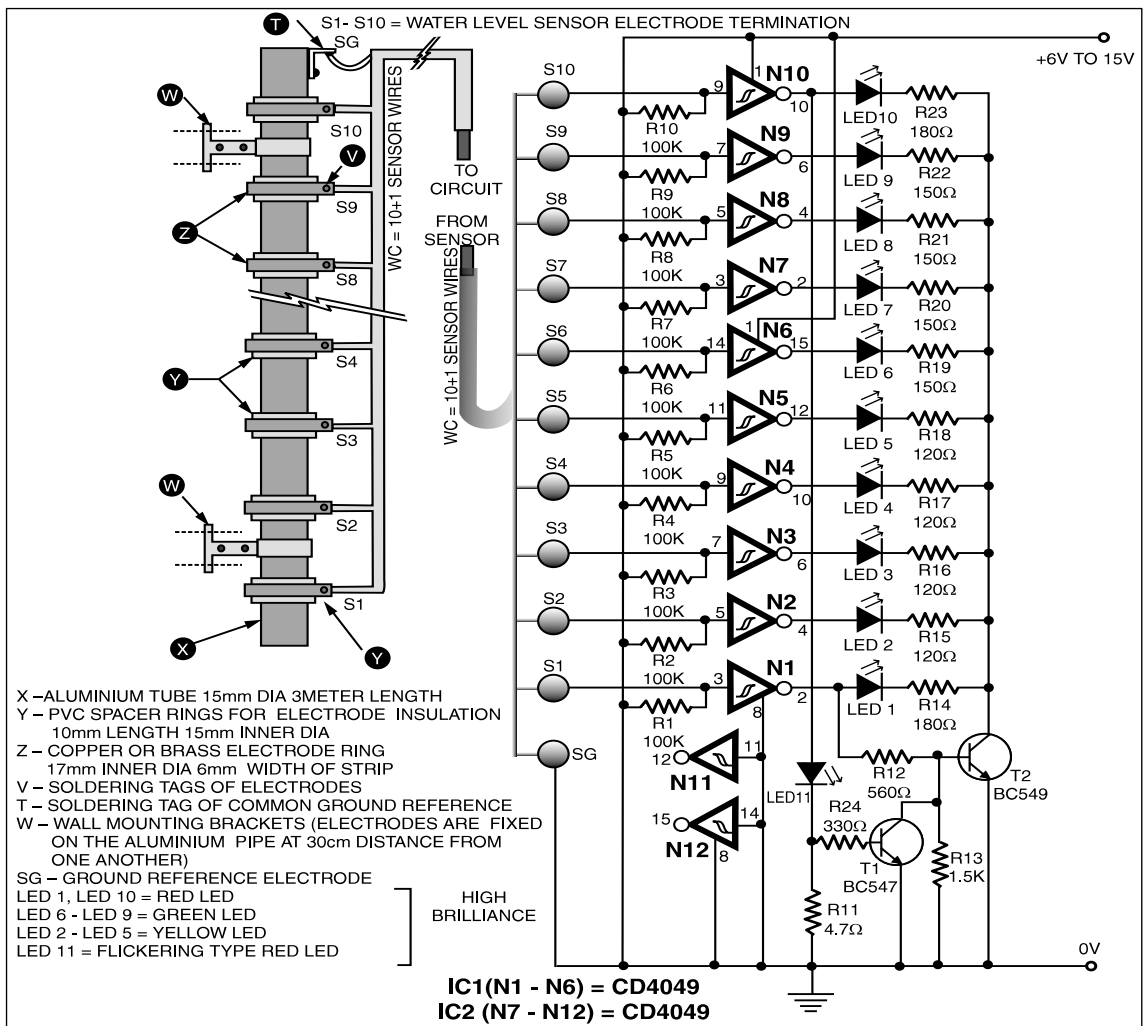The electronics portion is simple and straightforward. A long piece of veroboard can hold all the parts including the power supply section. For easy installation, the LEDs can be set at the track side of the



board, in a single line, so that they may be pushed through the cutouts in the front panel of the enclosure from inside.

The water level at 30cm intervals is monitored by corresponding sensors, causing the input to the concerned inverters (normally pulled 'high' via resistors R1 through R10) to go 'low', as soon as water reaches the respective sensors.

On initial switching 'on' of the power supply, when the tank is empty, all the electrodes are open. As a result, all the inverter inputs are 'high' (via the pull-up resistors R1 to R10) and their outputs are all 'low'. Thus, all the LEDs are 'off'. As soon as the water starts filling the tank, the rising water level grounds the first sensor. The logic 1 output of first inverter gate N1 causes conduction of transistor T2 to extend ground to one side of resis-

tors R14 through R23 via emitter-collector path of transistor T2. The LED D1 is thus lit up.

Similarly, other LEDs turn 'on' successively as the water level rises. As soon as the water in OHT reaches the top level, the output of gate N10 goes to logic 1 and causes flashing-type LED D11 to start flashing. At the same time, transistor T1 conducts and cuts off alternately, in synchronism with LED D11's flash rate, to ground the base of transistor T2 during conduction of transistor T1. As a result, transistor T2 also starts cutting 'off' during conduction of transistor T1, to make the LED meter (comprising LEDs D1 through D10) flash and thus warn that the water has reached the top level. When the water level goes down, the reverse happens and each LED is turned 'off' suc-

cessively.

The novel feature of this circuit is that whenever the water level is below the first sensor, all the LEDs are 'off' and the quiescent current is very low. Thus, a power 'on/off' switch is not so essential. Even when the LED-meter is fully on, the current drawn from the power supply is not more than 120 mA. A heat-sink may, however, be used for transistor T2, if the tank is expected to remain full most of the time. A power supply unit providing unregulated 6V DC to 15V DC at 300mA current is adequate.

Caution. A point to be noted is that water tends to stick to the narrow space at the sensor-spacer junction and can cause a false reading on the LED-meter. This can be avoided if the spacers are made wider than 10 mm.

PHONE BROADCASTER

ANJAN NANDI



Here is a simple yet very useful circuit which can be used to eavesdrop on a telephone conversation. The circuit can also be used as a wireless telephone amplifier.

One important feature of this circuit is that the circuit derives its power directly from the active telephone lines, and thus avoids use of any external battery or other power supplies. This not only saves a lot of space but also money. It consumes very low current from telephone lines without disturbing its performance. The circuit is very tiny and can be built using a single-IC type veroboard that can be easily fitted inside a telephone connection box of 3.75 cm x 5 cm.

The circuit consists of two sections, namely, automatic switching section and FM transmitter section.


Automatic switching section comprises resistors R1 to R3, preset VR1, transistors T1 and T2, zener D2, and diode D1. Resistor R1, along with preset VR1, works as a voltage divider. When voltage across the telephone lines is 48V DC, the voltage available at wiper of preset VR1 ranges from 0 to 32V (adjustable).

The switching voltage of the circuit depends on zener breakdown voltage (here 24V) and switching voltage of the transistor T1 (0.7V). Thus, if we adjust preset VR1 to get over 24.7 volts, it will cause the zener to breakdown and transistor T1 to conduct. As a result collector of transistor T1 will get pulled towards negative supply, to cut off transistor T2. At this

mitter section.

The low-power FM transmitter section comprises oscillator transistor T3, coil L1, and a few other components. Transistor T3 works as a common-emitter RF oscillator, with transistor T2 serving as an electronic 'on/off' switch. The audio signal available across the telephone lines automatically modulates oscillator frequency via transistor T2 along with its series biasing resistor R3. The modulated RF signal is fed to the antenna. The telephone conversation can be heard on an FM receiver remotely when it is tuned to FM transmitter frequency.

Lab Note: During testing of the cir-

 

stage, if you lift the handset of the telephone, the line voltage drops to about 11V and transistor T1 is cut off. As a result, transistor T2 gets forward biased through resistor R2, to provide a DC path for transistor T3 used in the following FM trans-

mitter section. The low-power FM transmitter section comprises oscillator transistor T3, coil L1, and a few other components. Transistor T3 works as a common-emitter RF oscillator, with transistor T2 serving as an electronic 'on/off' switch. The audio signal available across the telephone lines automatically modulates oscillator frequency via transistor T2 along with its series biasing resistor R3. The modulated RF signal is fed to the antenna. The telephone conversation can be heard on an FM receiver remotely when it is tuned to FM transmitter frequency.

TELEPHONE CALL METER USING CALCULATOR AND COB



K. UDHAYA KUMARAN, VU3GTH

In this circuit, a simple calculator, in conjunction with a COB (chip-on-board) from an analogue quartz clock, is used to make a telephone call meter. The calculator enables conversion of STD/ISD calls to local call equivalents and always displays current local call-meter reading.

The circuit is simple and presents an elegant look, with feather-touch operation. It consumes very low current and is fully battery operated. The batteries used last more than a year.


Another advantage of using this circuit is that it is compatible with any type of pulse rate format, i.e. pulse rate in whole number, or whole number with decimal value. Recently, the telephone department announced changes in pulse rate format, which included pulse rate in whole number plus decimal value. In such a case, this circuit proves very handy.

To convert STD/ISD calls to local calls, this circuit needs accurate 1Hz clock pulses, generated by clock COB. This COB is found inside analogue quartz wall clocks or time-piece mechanisms. It consists of IC, chip capacitors, and crystal that one can retrieve from scrap quartz clock mechanisms. These can be purchased from watch-repairing shops for less than Rs 20.

Normally, the COB inside clock mechanism will be in good condition. However, before using the COB, please check its serviceability by applying 1.5V DC across terminals C and D, as shown in the figure. Then check DC voltage across terminals A and B; these terminals in a clock are connected to a coil. If the COB is in good condition, the multimeter needle would deflect forward and backward once every second. In fact, 0.5Hz clock is available at terminals A and B, with a phase difference of 90°. The advantage of using this COB is that it works on a 1.5V DC source.

The clock pulses available from ter-

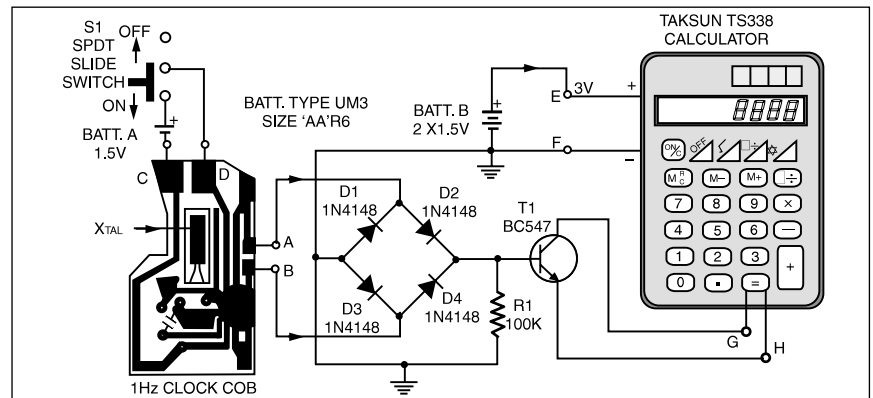минаl A and B are combined using a bridge, comprising diodes D1 to D4, to obtain 1Hz clock pulses. These clock pulses are applied to the base of transistor T1. The collector and emitter of transistor T1 are connected across calculator's '=' terminals.



The number of pulses forming an equivalent call may be determined from the latest telephone directory. However, the pulse rate (PR) found in the directory cannot be used directly in this circuit. For compatibility with this circuit, the pulse rate applicable for a particular place/distance, based on time of the day/holidays, is converted to pulse rate equivalent (PRE) using the formula $PRE = 1/PR$.

You may prepare a look-up table for various pulse rates and their equivalents (see Table). Suppose you are going to make an STD call in pulse rate 4. Note down from the table the pulse rate equivalent for pulse rate 4, which is 0.25. Please note that on maturity of a call in the telephone exchange, the exchange call meter immediately advances to one call and it

will be further incremented according to pulse rate. So one call should always be included before counting the calls.

For making call in pulse rate 4, slide switch S1 to 'off' (pulse set position) and press calculator buttons in the following order: 1, '+', 0.25, '='. Here, 1 is initial count, and 0.25 is PRE. Now calculator displays 1.025. This call meter is now ready to count. Now make the call, and as soon as the call matures, immediately slide switch S1 to 'on' (start/standby position). The COB starts generating clock pulses of 1 Hz. Transistor T1 conducts once every second, and thus '=' button in calculator is activated electronically once every second. The calculator display starts from 1.25, advancing every second as follows:

1.25, 1.5, 1.75, 2.00, 2.25, 2.50, and so on.

After finishing the call, immediately slide switch S1 to 'off' position (pulse set position) and note down the local call meter reading from the calculator display. If decimal value is more than or equal to 0.9, add another call to the whole number value. If decimal value is less than 0.9, neglect decimal value and note down only whole numbers.

To store this local call meter reading into calculator memory, press 'M+' button. Now local call meter reading is stored in memory and is added to the previous local call meter reading. For continuous display of current local call meter reading, press 'MRC' button and slide switch S1 to 'on' (start/standby position). The cur-

LOOKUP TABLE

Pulse rate (PR)	2	2.5	3	4	6	8	12	16	24	32	36	48
Pulse rate eqlt. (PRE)	0.500	0.400	0.333	0.250	0.166	0.125	0.083	0.062	0.041	0.031	0.027	0.020

Note: Here PRE is shown up to three decimal places. In practice, one may use up to five or six decimal places.

rent local call meter reading will blink once every second.

In prototype circuit, the author used TAKSUN calculator that costs around Rs 80. The display height was 1 cm. In this calculator, he substituted the two button-type batteries with two externally connected 1.5V R6 type batteries to run the calculator for more than a year.

The power 'off' button terminals were made dummy by affixing cellotape on contacts to avoid erasing of memory, should someone accidentally press the power 'off' button. This calculator has auto 'off' facility. Therefore, some button needs to be pressed frequently to keep the calculator

'on'. So, in the idle condition, the '=' button is activated electronically once every second by transistor T1, to keep the calculator continuously 'on'.

Useful hints. Solder the '=' button terminals by drilling small holes in its vicinity on PCB pattern using thin copper wire and solder it neatly, such that the '=' button could get activated electronically as well as manually. Take the copper wire through a hole to the backside of the PCB, from where it is taken out of the calculator as terminals G and H.

At calculator's battery terminals, solder two wires to '+' and '-' terminals. These wires are also taken out from cal-

culator as terminals E and F. Affix COB on a general-purpose PCB and solder the remaining components neatly. For giving the unit an elegant look, purchase a jewellery plastic box with flip-type cover (size 15cm x 15cm). Now fix the board, calculator, and batteries, along with holder inside the jewellery box. Then mount the box on the wall and paste the look-up table inside the box cover in such a way that on opening the box, it is visible on left side of the box.

Caution. The negative terminals of battery A and battery B are to be kept isolated from each other for proper operation of this circuit.

SIMPLE ELECTRONIC CODE LOCK

REJO G. PAREKKATTU



The circuit diagram of a simple electronic code lock is shown in figure. A 9-digit code number is used to operate the code lock.

When power supply to the circuit is turned on, a positive pulse is applied to the RESET pin (pin 15) through capacitor C1. Thus, the first output terminal Q1 (pin 3) of the decade counter IC (CD 4017) will be high and all other outputs (Q2 to Q10) will be low. To shift the high state from Q1 to Q2, a positive pulse must be applied at the clock input terminal (pin 14) of IC1. This is possible only by pressing the push-to-on switch S1 momentarily. On pressing switch S1, the high state shifts from Q1 to Q2.


Now, to change the high state from Q2 to Q3, apply another positive pulse at pin 14, which is possible only by pressing switch S2. Similarly, the high state can be shifted up to the tenth output (Q10) by pressing the switches S1 through S9 sequentially in that order. When Q10 (pin 11) is high, transistor T1 conducts and energises relay RL1. The relay can be used to switch 'on' power to any electrical appliance.

Diodes D1 through D9 are provided to prevent damage/malfunctioning of the IC when two switches corresponding to 'high' and 'low' output terminals are

pressed simultaneously. Capacitor C2 and resistor R3 are provided to prevent noise

number or letter can be used to mark them. Switch S10 is also placed together with other switches so that any stranger trying to operate the lock frequently presses the switch S10, thereby resetting the circuit many times. Thus, he is never able to turn the relay 'on'. If necessary, two or three switches can be connected in parallel with S10 and placed on the keyboard panel for more safety.

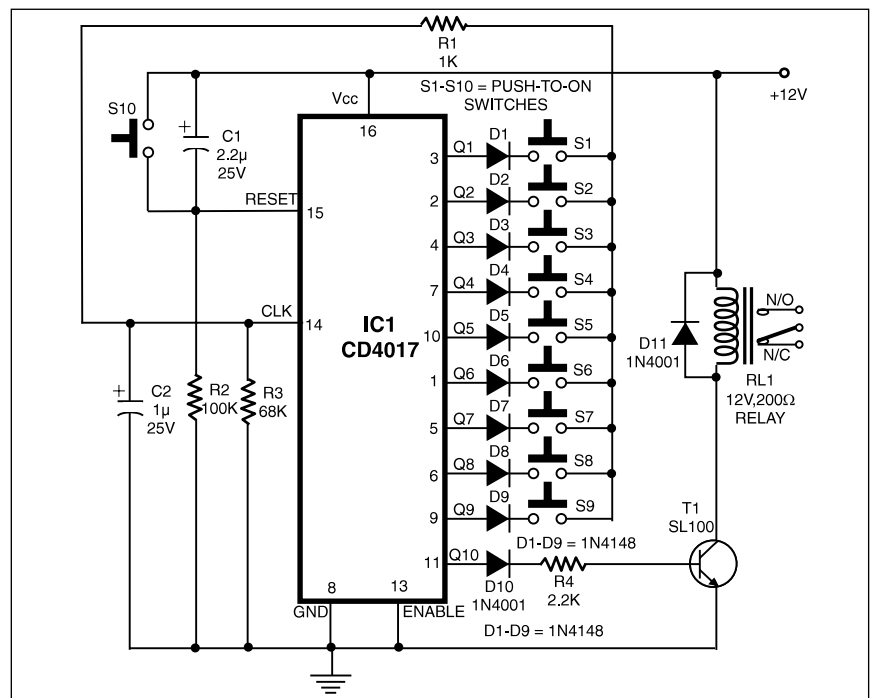A 12V power supply is used for the circuit. The circuit is very simple and can be easily assembled on a general-purpose PCB. The code number can be easily changed by changing the



during switching action.

Switch S10 is used to reset the circuit manually. Switches S1 to S10 can be mounted on a keyboard panel, and any


connections to switches (S1 to S9).

LATCH-UP ALARM USING OPTO-COUPLER

PRADEEP G.

The latch-up alarm described here is based on single IC NE555, configured as an astable multivibrator. The timing components are selected such that the oscillation frequency of the multivibrator lies within the audio range. Instead of a flip-flop stage, an opto-coupler (MCT2E) is used for latching of the alarm.

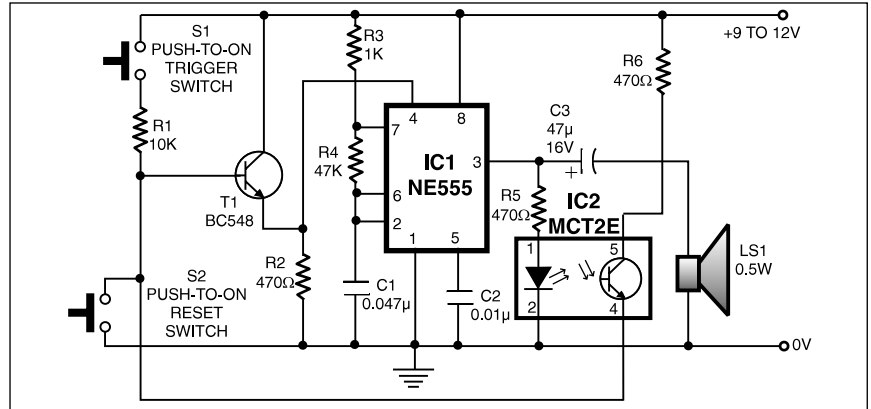Under normal condition, pin 4 of IC1 is pulled to ground via resistor R2, and its output at pin 3 is held 'low'. When switch S1 is pressed momentarily, transistor T1 conducts to bring reset pin 4 of 555 to logic 'high'. As a result, IC1 is activated and the alarm starts to sound.



Simultaneously, the LED inside opto-coupler glows and the phototransistor conducts. As a result, trigger transistor T1 gets base bias via phototransistor and resistor R6. The alarm sounds continuously until reset switch S2 is pressed. When switch S2 is pressed, transistor T1 is switched 'off' to bring pin 4 of IC1 to logic 'low' and the alarm is disabled.

MINI VOICE-PROCESSOR

(BASED ON UMC APPLICATION NOTE AND DATA SHEET FOR IC UM5506B)

The UM5506B is a highly integrated voice processor CMOS IC with in-built ADM (adaptive delta modulation) capability. The chip integrates an analogue comparator, a 10-bit D/A converter, a low-pass filter, an op-amp, and a 96-kilobit static RAM. It has an on-chip amplifier for sound recording and direct speaker driving capability.

Although 28 pins/pads are shown in the figure, its COB version mounted on a PCB, as tested at EFY Lab, had only 16 lines coming out of the COB. These lines, after proper identification, have been indicated with asterisk (*) marks in Fig. 2. Very few external components are needed for its use in applications such as greeting cards or toys. The tested PCB measured 3 cm x 5.25 cm and required only 3-volt supply for operation.

The IC, along with external components, as shown in Fig. 2, can be used for recording of sound for a recording length of 6 seconds. During record mode, the

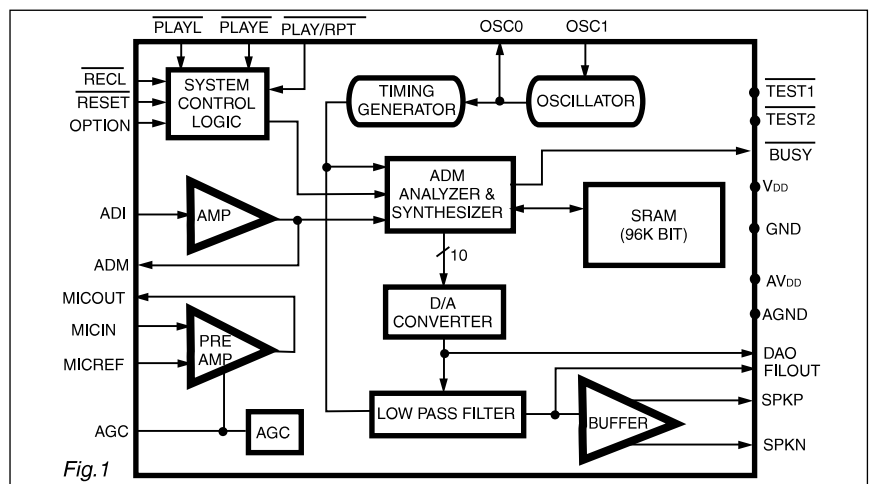


Fig. 1

voice signals picked up by the condenser mic are converted into digital signals using ADM algorithm and stored in its internal SRAM. During play mode, the digital data is converted back into analogue signals and played back through the


speaker. For understanding the operation, the functions of switches S1 through S4 and their corresponding pins is described below.

S1(RECL). Pressing (grounding) this

S2 (PLAYL). Pressing (grounding) this pin ends the power-down mode and initiates the play cycle. The stored/recorded message is played until finished or this pin is taken 'high'.

S3(PLAYE). Pressing (grounding) this pin momentarily ends the power-down mode and enters the play mode. Subsequent taking of this pin 'high' has no effect. However, pressing this pin once more finishes the play mode and the chip enters the power-down mode. The action is analogous to the falling-edge trigger mode.

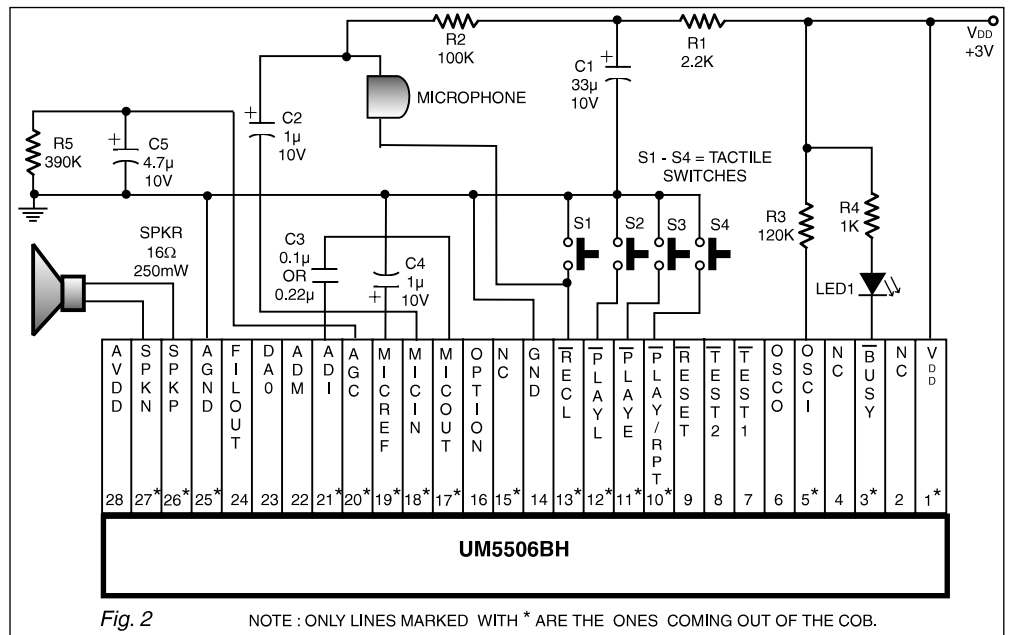S4 (PLAY/RPT). Pressing (grounding) this pin ends the power-down mode and enters the play mode. The chip will complete the recorded message and then keep repeating the message as long as it is kept pressed. When released, it will en-



ter the power-down mode.

LED1 connected to BUSY pin lights up to indicate end of power-down mode and remains 'on' during record

and play-mode active period. A beep is produced in the speaker to indicate start of record cycle and also that the memory is full. □

May

2000

DIGITAL NUMBER SHOOTING GAME

A. JEYABAL

Many electronic video games are available in the market. But for those who may prefer to assemble the game themselves, a digital number shooting game circuit is described here.

A train of single-digit random numbers appears on a 7-segment display, and the player has to shoot a number by pressing a switch corresponding to that number before it vanishes. If he shoots the number, he scores ten points which are displayed on the scoreboard. Successful shooting is accompanied by a beep sound.

The circuit

Fig. 1 shows the block diagram of the whole circuit. Blocks 1, 2, and 3 constitute the random number generator. Block 4 controls the ten triggering switches and block 5 checks for any foul play. The scoreboard is constituted by blocks 6 and 7, while block 8 is meant for audio indication.

Block 9 controls the speed of the number displayed, the digital counter, the switch controller, and the foul play checker.

Clock pulse generator. The sche-

matic diagram of digital number shooting game is shown in Fig. 2. The Schmitt trigger input NAND gates N1 and N2 of IC CD4093 (IC1) are used for producing clock pulses for random number generation. NAND gate N2, in combination with capacitor C2 and resistor R2, forms an oscillator to produce pulses. NAND gate N1 and its associated components comprising capacitor C1 and resistor R1 form another oscillator, whose frequency is ten times less than of the former oscillator.

The pulses from the two oscillators are ANDed by NAND gate N2 to get random clock pulses. The output frequency from gate N2 (pin 4) varies due to phase difference between the two oscillator frequencies and the period of 'on' state of output from gate N3 (pin 10).

The prototype was carefully watched for consecutive 150 random numbers generated by IC2 (and displayed on DIS.1). No repetition in the order of the numbers was witnessed but, interestingly, at times, the same number was repeated thrice.

Random number generator and switch controller. The output of gate N2 (pin 4) is connected to pin 1 of decade counter/decoder/7-segment LED driver

CD4033 (IC2). This IC counts and drives the 7-segment display DIS.1. The control pulse produced by gate N3 activates this display.

The clock pulses also go to decade counter/decoder IC CD4017 (IC3, pin 14). This IC controls the

trigger switches. Ten push-to-on switches designated 'S0' through 'S9' are connected to the ten Q outputs (pins 3, 2, 4, 7, 10, 1, 5, 6, 9, and 11 respectively) of this IC.

These Q outputs become 'high' one by one sequentially with every clock pulse. IC2 and IC3 must count in unison, i.e. for the number shown in the display the corresponding Q output of IC3 should be 'high'. For the numbers 0 through 9, the Q0 through Q9 outputs of IC3 respectively must become 'high'. For this purpose, the 'carry out' (pin 5) of IC2 is connected to the reset pin 15 of IC3 through a differentiator circuit comprising resistor R4 and capacitor C3.

During the transition from 9 to 0, the state of 'CO' pin 5 changes from 'low' to 'high' and the differentiator circuit produces a sharp pulse to reset IC3. Thus, in every ten pulses, any timing difference, if present, is corrected. Resistor R3 (470k) quickly discharges it during the low state of 'CO' pin 5 of IC2.

Control pulse generator. NAND gate N3, along with its external components, forms another oscillator of very low

PARTS LIST

Semiconductors:

IC1	: CD4093 Schmitt trigger quad two-input NAND gate
IC2, IC5, IC6	: CD4033 decade counter/decoder/7-segment LED display driver
IC3	: CD4017 decade counter/decoder
IC4	: CD4027 dual JK flip-flop
T1, T2	: BC547 npn silicon transistor
DIS.1-DIS.4	: LT543 common-cathode, 7-segment LED display

Resistors (all $\frac{1}{4}$ watt, $\pm 5\%$ carbon film, unless stated otherwise)

R1, R2, R4, R6-R9	: 100-kilo-ohm
R3	: 470-kilo-ohm
R5	: 1-mega-ohm
R10-R12	: 1-kilo-ohm
VR1	: 1-mega-ohm pot

Capacitors:

C1	: 0.1 μ F ceramic disk
C2	: 0.01 μ F ceramic disk
C3	: 0.001 μ F ceramic disk
C4	: 0.22 μ F ceramic disk
C5	: 100 μ F, 16V electrolytic

Miscellaneous:

PZ1	: Piezo buzzer, continuous type
S0-S10	: Push-to-on switch
S11	: On/Off switch
	: DC IN socket


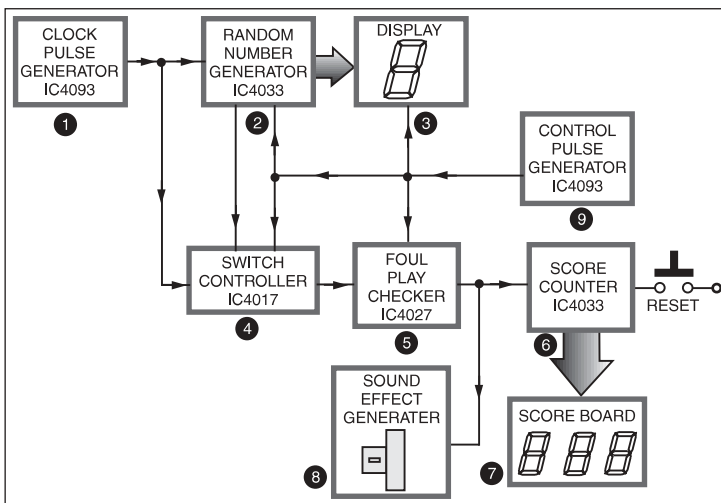


Fig. 1: Block diagram of the digital number shooting game

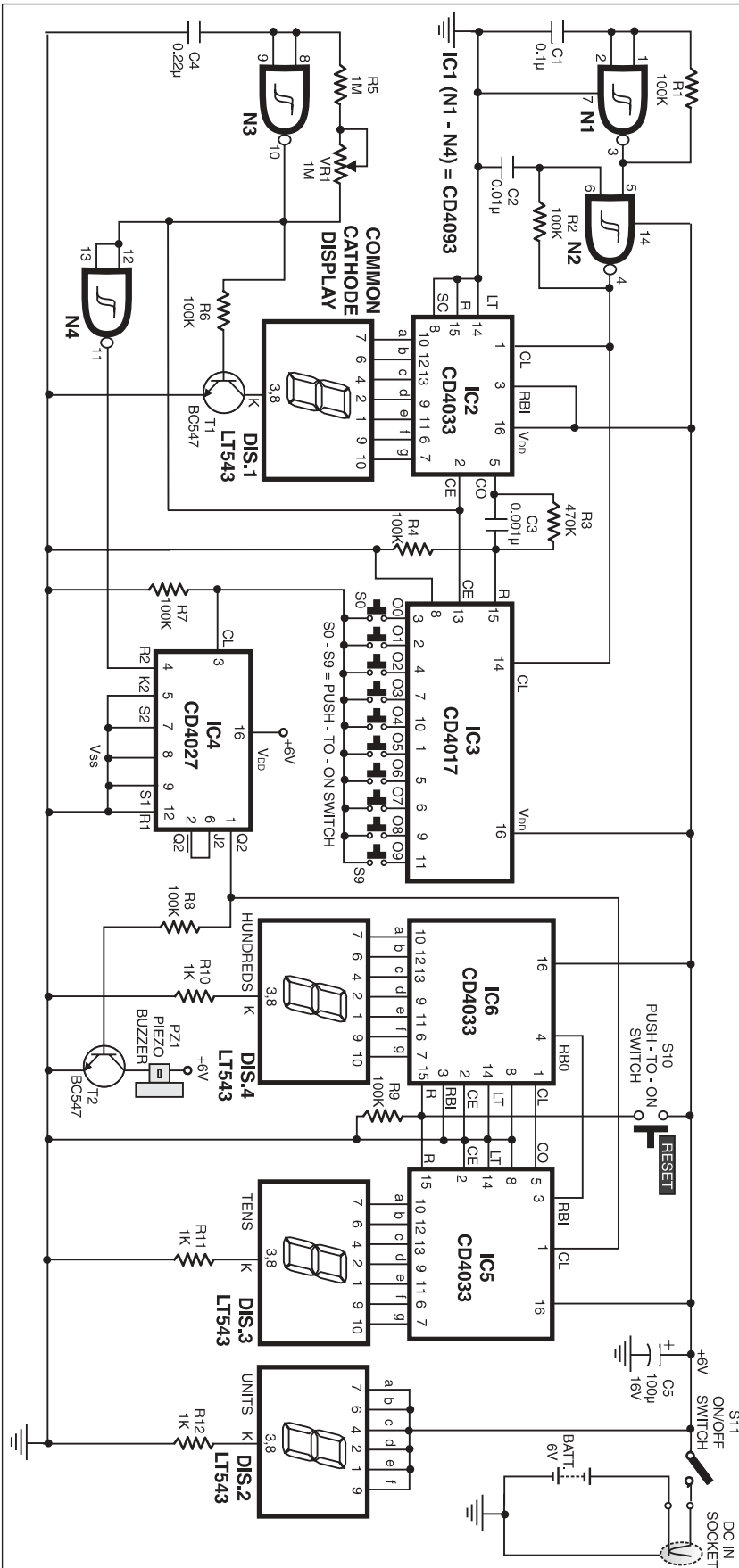

Fig. 2: Circuit diagram of the digital number shooting game



frequency (of the order of 1 Hz to 4 Hz). Its frequency can be varied with the help of potentiometer VR1.

For proper functioning of CD4033 and CD4017, their clock-enable (CE) pins 2 and 13 respectively must be held 'low'. These pins are connected to the output of gate N3 (pin 10). If these pins are in logic high state, the ICs are disabled from receiving clock pulses, and the Q outputs of IC3 and segment drive outputs of IC2 retain their last state before the CE pins go 'high'.

The control clock pulses from gate N3 also go to the base of transistor BC547B (T1). This transistor pulls down the common cathode of 7-segment LED display DIS.1 to ground during the high level of control clock pulses, to display the number.

The control pulse also performs one more function. After being inverted by NAND gate N4, it resets JK flip-flop IC CD4027 (IC4), which serves as the foul play checker.

In nutshell, during the low state of output of gate N3, both IC2 and IC3 are enabled and the pulses are counted by IC2, but the number cannot be seen in the display because transistor T1 is reverse biased and cut-off.

When the output of gate N3 changes to high state, IC2 and IC3 are disabled. T1 gets its base voltage and pulls down the cathode of display DIS.1, and the display shows the number (which is a random number). At the same time, the Q output of IC3 corresponding to the displayed number goes 'high'.

Now, if one presses the correct key corresponding to the number shown in the display, before it vanishes, a high-going pulse is applied to clock input pin 3 of IC4. Its Q output (pin 1) becomes 'high', which advances the tens counter (IC5 of the scoreboard). It also biases transistor T2, to drive the piezo buzzer PZ1 for confirmation of the number shot.

Foul play checker/debouncer. Due to bouncing, the switches produce spurious pulses and lead to erratic operation. The player may press a switch more than once to score more, and may keep pressing a switch before the respective number is displayed. This is where the foul play checker/debouncer circuit comes into play.

For faithful operation, the circuit requirements are as follows:

 


Fig. 3: Actual-size, single-sided PCB layout

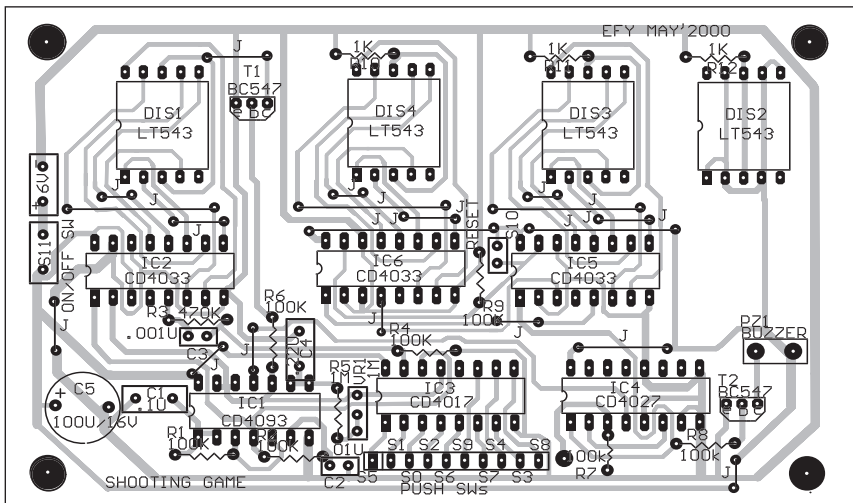


Fig. 4: Component layout for the PCB

1. The spurious pulses must be ignored.
2. The counter must advance only on the first pressing of the switch for a number and further pressing must be ignored.
3. The pressing of the switch should be effected only after the corresponding number is displayed.

To fulfil all these conditions, the dual JK flip-flop IC CD4027 (IC4) is employed and only one of the two flip-flops is used. The flip-flop is inhibited when both J and K inputs are low (requirements 1 and 2). The data on the J input is transferred to the Q output for a positive-going clock pulse only (requirement 3). The K input (pin 5) of IC CD4027 is grounded and J input (pin 6) is connected to Q output (pin 2). One terminal of all the ten switches is connected to clock input (pin 3) of IC4. Control pulses from gate N3 (pin 10) are inverted by gate N4 before it goes to

reset pin 4.

During the low-level period of gate N3, output of gate N4 is 'high' and the flip-flop (IC4) is in the reset state. If any one of the ten switches is pressed, even though clock pulses are present at clock input (pin 3) of IC4, the Q output will not change, as this IC is in the reset state.

When the output of gate N3 is 'high', the output of gate N4 is 'low', which clears IC4 from the reset state. If the player presses the correct switch, a clock pulse is applied to the clock input (pin 3) of IC CD4027. The 'high' level data from J input is transferred to Q output (pin 1) of this IC and IC5 advances by one count, which means ten points (DIS.2 is always zero). Now Q output (pin 2) of IC4, which is connected to J input, goes 'low'. As both J and K inputs are at low level, IC4 is inhibited and further clock pulses to pin 3 of IC4 have no effect.

Score counter and scoreboard.

This block comprises two decade counter/decoder/7-segment display driver ICs CD4033 (IC5, IC6), and three common cathode 7-segment LED displays (DIS.2 through DIS.4). The 'a' through 'f' segments of DIS.1, meant for units, are directly connected to positive supply rail and its cathode is connected to negative supply rail through a 1k (R12) current-limiting resistor. Thus it always shows zero.

The Q output (pin 1) of IC4 is connected to clock input (pin 1) of IC5, the tens counter. The carry-out (pin 5) of IC5 is connected to the clock input (pin 1) of IC6 for cascading hundreds counter. The CE (pin 2) and Lamp Test (pin 14) of both IC5 and IC6 are grounded, for proper functioning. Both resets (pin 15) are grounded through a 100k (R9) resistor and connected to positive supply, through reset switch S10.

Ripple blanking input (pin 3) of IC6 is grounded, so the leading zero to be displayed in DIS.4 will be blanked out. The ripple blanking output (pin 4) will be low while the number to be displayed is zero. Likewise, zero will be blanked out in display DIS.3, because RB0 of IC6 is connected to RB1 of IC5. So when reset switch S10 is depressed, the unit counter display shows only zero and the other two displays are blanked out.

The maximum score which can be displayed is 1000, after which it automatically resets to zero.

Sound-effect generator. For simplicity and compactness, a piezo buzzer (continuous type) is employed. When the Q output of IC4 goes high, after the correct switch is pressed, it forward biases transistor BC547B (T2) and drives the piezo buzzer. This produces a beep sound for confirmation of successful shooting of that number.

Construction

This circuit can be assembled on a readymade PCB or strip board. However, a proper single-sided PCB for the circuit of Fig. 2 is shown in Fig. 3 and its component layout is shown in Fig. 4. For switches, push-to-on tactile or membrane switches can be used. For power supply, four pen-torch cells (AA3) can be used with a battery holder. DC IN socket is provided for connecting a battery eliminator for operating it on mains supply. □

PC INTERFACED AUDIO PLAYBACK DEVICE: M-PLAYER



N.V. VENKATARAYALU AND M. SOMASUNDARAM

Sounds of various kinds have always fascinated human beings. Many devices have been invented for recording and playing back the sounds—from magnetic tapes to DVD (digital versatile disc), from Adlib cards to high-performance sound cards with ‘surround sound’ capability. For personal computers (PCs), there is a wide variety of such devices. A modern PC, generally, has a ‘Sound Blaster’ card installed in it. If your PC does not have a sound card, here is a low-cost audio playback circuit with bass, treble, and volume controls to create your own music player.

The playback device ‘M-player’ (i.e. media player) described here uses minimal hardware to achieve a moderately good-quality audio playback device. The software that accompanies the hardware is meant for a PC running under MS-DOS or a compatible operating system. This device can play a simple 8-bit PCM (pulse code modulation) wave file with some special effects. The PC is connected to the device through the PC parallel port.

Hardware

The circuit functions as an 8-bit mono player, i.e. the sound files (with .WAV extension) with sound quantised to eight bits or 256 levels can be played. In case of files with 16-bit quantisation, these are re-quantised as discussed under ‘Software’ subheading. Thus, only eight bits are sent to the card through the printer port.

Since there is no duplex communication necessary between the player card and the PC, it is sufficient to use the eight output data lines of the port 378H (pins 2 through 9 of 25-pin D-connector). This 8-bit digital output is converted into an analogue signal using DAC 0808 (IC1) from National Semiconductor.

The output current from the DAC varies with the input digital level (represented by bits D0 through D7), the reference voltage (V_{ref}), and the value of series resistor R1 connected to V_{ref} pin 14 of DAC0808 IC. The output current I_o (in mA) is given by the relation:

$$I_o = \frac{V_{ref}}{R1} \left[\frac{D7}{2} + \frac{D6}{4} + \frac{D5}{8} + \frac{D4}{16} + \frac{D3}{32} + \frac{D2}{64} + \frac{D1}{128} + \frac{D0}{256} \right]$$

where V_{ref} is the reference voltage in volts and R1 is the resistance in kilo-ohms.

The output current from the DAC is converted into its corresponding voltage using a simple current-to-voltage converter wired around one part of the dual wideband JFET op-amp LF353. The output from IC2(a) is the required audio signal that has to be processed and amplified to feed the speaker. The part following the I-V converter is the bass- and treble-control circuit employing RC-type variable low-pass and high-pass filters connected to the input of audio amplifier built around the second op-amp inside LF353 [IC2(b)].

The frequency response of the filters can be varied using potentiometers VR1 and VR2. The low frequencies or bass can be cut or boosted with the help of potentiometer VR1. Similarly, high frequencies or treble can be cut or boosted with the help of potentiometer VR2. At low frequencies, capacitors C2, C3, and C4 act as open circuits and the effective feedback is through 10k resistors (R4, R5, and R6) and potentiometer VR1.

The audio amplifier IC2(b) acts as an inverting amplifier and the amplification (or attenuation) of the low-frequency bass signals depends on the value of potentiometer VR1. The frequency $f1$ at which $C = C2 = C3$ becomes effective is given by the equation:

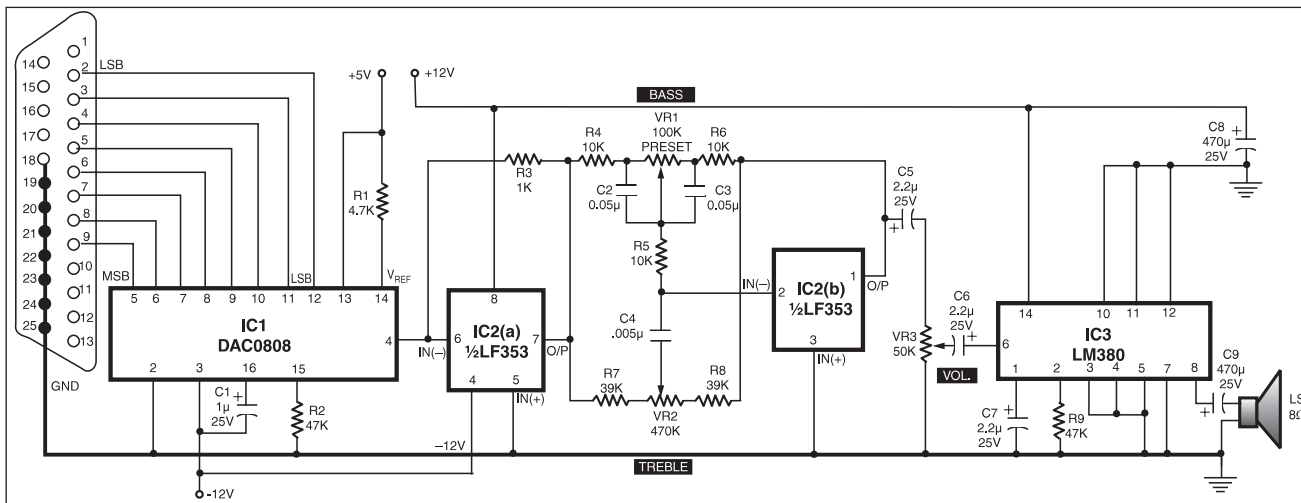


Fig. 1: Circuit of M-player audio playback device

$$f_1 = \frac{1}{2\pi \times VR_1 \times C} \text{ Hz}$$

At frequencies higher than f_2 ($f > f_2$, high end of audio range), capacitors C2 and C3 overcome the effect of potentiometer VR1. As C2 and C3 behave as short, potentiometer VR1 has no effect on the output response. Now, the gain is controlled by treble potentiometer VR2. The frequency f_2 , below which treble potentiometer VR2 has no effect on the response, is given by the equation:

$$f_2 = \frac{1}{2\pi \times VR_2 \times C_4} \text{ Hz}$$

The output of this module is sent to the final 2-watt audio power amplifier (LM380) stage through potentiometer VR3 which is used as the volume control. The power output of this module is fed to an 8-

ohm speaker. The output-end audio power amplifier is designed to give a gain of around 50.

One can also use LM380 in various other configurations as per one's requirements. Another popular configuration is the 'bridge configuration'—in which two LM380s can be used to obtain larger power output with a gain of 300.

Parallel port

The output of the parallel port is TTL compatible. So, logic level 1 is indicated by +5V and logic level 0 by 0V. The current that one can sink and source varies from port to port. Most parallel ports can sink and source around 12 mA.

The software assumes 0x378 (378H) to be the base address of the parallel port to which the device is connected. Another possible base address is 0x278 (278H). It is advised to modify this address of the parallel port in the software program, after checking the device profile.

Actual-size PCB layout for audio playback circuit of Fig. 1 is given in Fig. 2 and its component layout in Fig. 3.

Software

The software accompanying this construction project is written in Turbo C/C++ for DOS. It can be used to play simple 8-bit PCM wave files. 16-bit wave files are converted into 8-bit PCM data before proceeding.

Even stereo wave files can be played; but not the stereo way. Only one channel is chosen. Up to six-channel PCM data can be read and con-

verted into mono 8-bit PCM data. This software is accompanied with a C_TUI-based interface.

The wave file format is probably the least undocumented sound format since there are different schemes with different number of chunks of related information in the file. Even the chunks can be of variable size. Therefore it is difficult to get documentation on all available chunks.

This software can be used only on PCM data with data chunk. Every wave file has some minimum chunks (see Table II). These chunks will be present in every wave file. Then there are other chunks which are actually non-standard. In PCM itself, the above chunk may be followed either by DATA chunk or by LIST chunk which, in turn, has lots of sub-chunks. (Any information obtained on these chunks by the readers may please be shared with the authors.)

During playback, the speed with which the processor in the PC can execute the main loop is first studied using a dummy loop and thus the delay is adaptively varied with respect to the speed

 


Fig. 2: Actual-size PCB layout for M-player

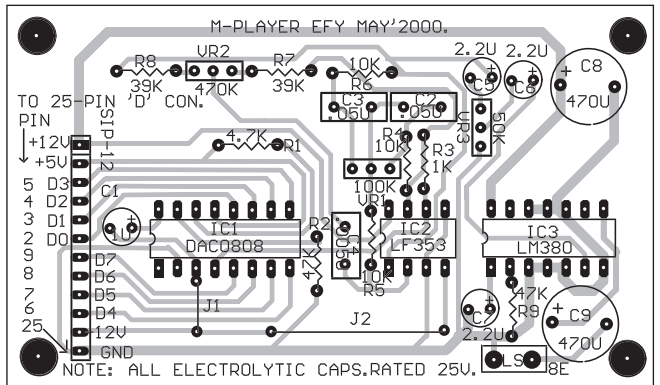


Fig. 3: Component layout for the PCB

PARTS LIST

Semiconductors:

- IC1 - DAC0808 8-bit D/A converter
- IC2 - LF353 JFET input wide-band op-amp
- IC3 - LM380, 2-watt audio amplifier

Resistors (all 1/4 watt, ±5% carbon film, unless stated otherwise)

- R1 - 4.7-kilo-ohm
- R2, R9 - 47-kilo-ohm
- R3 - 1-kilo-ohm
- R4-R6 - 10-kilo-ohm
- R7, R8 - 39-kilo-ohm
- VR1 - 100-kilo-ohm potmeter
- VR2 - 470-kilo-ohm potmeter
- VR3 - 50-kilo-ohm potmeter

Capacitors:

- C1 - 1µF, 25V electrolytic
- C2, C3 - 0.05µF ceramic disk
- C4 - 0.005µF ceramic disk
- C5-C7 - 2.2µF, 25V electrolytic
- C8, C9 - 470µF, 25V electrolytic

Miscellaneous:

- 25-pin D connector (male)
- Loudspeaker 8-ohm, 2W
- Power supply: (a) +12V, 500mA
- (b) -12V, 100mA
- (c) +5V, 100mA

TABLE I
Relevant Details of Parallel Port

Pin No. (D-type 25)	Pin No. (centronics)	SPP signal	Direction in/out	Register
2	2	Data 0	Out	Data
3	3	Data 1	Out	Data
4	4	Data 2	Out	Data
5	5	Data 3	Out	Data
6	6	Data 4	Out	Data
7	7	Data 5	Out	Data
8	8	Data 6	Out	Data
9	9	Data 7	Out	Data
18 - 25	19-30	Ground	Gnd	

TABLE II
Wave File Format

From byte	Number of bytes	Information
RIFF chunk:		
0	4	Contains the characters 'RIFF'
4	4	Size of the RIFF chunk
WAVE chunk:		
0	4	Contains the characters 'WAVE'
4	Variable	The FORMAT chunk
The normal FORMAT chunk:		
0	4	Contains the characters 'fmt'
4	4	Size of the FORMAT chunk
8	2	Value specifying the scheme 1-PCM, 85-MPEG layer III
10	2	Number of channels 1-mono, 2-stereo, etc.
12	4	Number of samples per second. This gives us the playback rate.
16	4	Average number of bytes per second. This field is used to allocate buffers, etc.
20	2	Contains block alignment information.
22	Variable	This field contains format-specific data. For PCM files, this field is 2 bytes long

of target processor. This is one of the methods to achieve invariance of the playback speed over a wide range of processor speeds available.

bass, treble, and volume for the wave file that is played. Thus, the hardware and software complement each other to provide a good music player. The software

The software can be used to play with the following effects:

- Play normally
- Play with a different playback rate, i.e. play it fast or slow
- Fade-in or fade-out the volume levels either linearly or exponentially
- Reverse the wave file and then play

The menu items can be selected using keyboard keys Alt+F for file, Alt+E for effects, and Alt+O for operation. Apart from the software, the hardware

does not include mouse support.

Conclusion

We have presented a simple sound card to playback .wav files with bass and treble controls. Though the current design plays only mono files (stereo files are converted to mono), a stereo file player can be designed in a similar manner. The software can be modified to play audio files other than .wav files without any change in the hardware circuit. The encoding format of the other audio file types (like .ra, .mp3) is only to be known. With that, those files can be decoded and raw digital 8-bit data can finally be sent to the hardware device. The hardware device can even be permanently mounted inside the PC with all the power supplies (+12V, +5V, and -12V) tapped from the system's SMPS.

Note: The complete source code consisting of Mplayer.cpp, Sounds.h, Globals.h, the executable file Mplayer.exe, and a sample wave file are likely to be included in next month's CD (optional) accompanying EFY.

Program Listing

```

MPLAYER.CPP
#include "Sounds.h"
void DisplayTip(char *string)
{
text_info tinf;
if(strlen(string)<75)
{
gettextinfo(&tinf);
textbackground(LIGHTGRAY);textcolor(RED);
gotoxy(2,25);
for(int i=0;i<75;i++) printf(" ");
gotoxy(2,25);
printf(string);
textattr(tinf.attribute);
gotoxy(tinf.curx,tinf.cury);
}
return;
}
void Window(int x1,int y1,int x2,int y2,char
*caption,int BackCol,int TextCol)
{
text_info tinfo;
int i,j;
gettextinfo(&tinfo);
textbackground(BackCol);textcolor(TextCol);
for(j=y1;j<=y2;j++){
gotoxy(x1,j);
for(i=x1;i<=x2;i++)
printf(" ");
}
gotoxy(x1+1,y1);
for(i=x1+1;i<=x2-1;i++)
printf("%c",205);
gotoxy(x1+1,y2);
for(i=x1+1;i<=x2-1;i++)

```

```

printf("%c",205);
for(j=y1+1;j<=y2-1;j++){
gotoxy(x1,j);
printf("%c",186);
gotoxy(x2,j);
printf("%c",186);
}
gotoxy(x1,y1);printf("%c",201);
gotoxy(x2,y1);printf("%c",187);
gotoxy(x1,y2);printf("%c",200);
gotoxy(x2,y2);printf("%c",188);
if(caption!=NULL){
textcolor(WHITE);
gotoxy(x1+2,y1);
printf("%s",caption);
}
textattr(tinfo.attribute);
return;
}
void DrawScreen(void)
{
textbackground(LIGHTGRAY);textcolor(BLACK);
clrscr();
Window(1,2,80,24,NULL,BLUE,WHITE);
gotoxy(1,1);printf(" File Effects Operation");
textcolor(RED);
gotoxy(3,1);printf("F");
gotoxy(12,1);printf("E");
gotoxy(24,1);printf("O");
textbackground(BLUE);textcolor(LIGHTBLUE);
gotoxy(3,10);printf(" ");
delay(75);
gotoxy(3,11);printf(" ");
delay(75);
gotoxy(3,12);printf(" ");

```

```

delay(75);
gotoxy(3,13);printf(" ");
delay(75);
gotoxy(3,14);printf(" ");
delay(75);
gotoxy(3,15);printf(" ");
delay(75);
gotoxy(3,16);printf(" ");
delay(75);
gotoxy(3,17);printf(" ");
return;
}
void MenuInitialise(void)
{
int i;
// The FILE menu option
Menu[MNU_FILE].nextMenu=MNU_EFFECT;
Menu[MNU_FILE].prevMenu=MNU_OPERATION;
Menu[MNU_FILE].Child=FALSE;
Menu[MNU_FILE].num_items=4;
for(i=0;i<4;i++)
{
Menu[MNU_FILE].Enabled[i]=TRUE;
Menu[MNU_FILE].subMenu[i]=NONE;
Menu[MNU_FILE].String[i]=(char *)malloc(15);
Menu[MNU_FILE].Tip[i]=(char *)malloc(50);
Menu[MNU_FILE].OptionID[i]=1+i;
}
Menu[MNU_FILE].Enabled[1]=FALSE;
strcpy(&(Menu[MNU_FILE].String[0][0]),"Open");
strcpy(&(Menu[MNU_FILE].String[1][0]),"Save");
strcpy(&(Menu[MNU_FILE].String[2][0]),".");
strcpy(&(Menu[MNU_FILE].String[3][0]),"Exit");
strcpy(&(Menu[MNU_FILE].Tip[0][0]),"Open the
*.wav file");

```

```

strcpy(&(Menu[MNU_FILE].Tip[1][0]),"Save as a
      *wav file");
strcpy(&(Menu[MNU_FILE].Tip[2][0])," ");
strcpy(&(Menu[MNU_FILE].Tip[3][0]),"Quit the
program");
Menu[MNU_FILE].AtX=2;Menu[MNU_FILE].AtY=2;
// The EFFECT menu option
Menu[MNU_EFFECT].nextMenu=MNU_OPERATION;
Menu[MNU_EFFECT].prevMenu=MNU_FILE;
Menu[MNU_EFFECT].Child=FALSE;
Menu[MNU_EFFECT].num_items=5;
for(i=0;i<5;i++)
{
Menu[MNU_EFFECT].Enabled[i]=FALSE;
Menu[MNU_EFFECT].subMenu[i]=NONE;
Menu[MNU_EFFECT].String[i] =
(char*)malloc(15);
Menu[MNU_EFFECT].Tip[i]=(char *)malloc(50);
Menu[MNU_EFFECT].OptionID[i]=11+i;
}
strcpy(&(Menu[MNU_EFFECT].String[0][0]),"Fade
In");
strcpy(&(Menu[MNU_EFFECT].String[1][0]),"Fade
Out");
strcpy(&(Menu[MNU_EFFECT].String[2][0]),"-");
strcpy(&(Menu[MNU_EFFECT].String[3][0]),"Reverse");
strcpy(&(Menu[MNU_EFFECT].String[4][0]),"Playback
Rate");
strcpy(&(Menu[MNU_EFFECT].Tip[0][0]),"Reduce
volume with increasing time");
strcpy(&(Menu[MNU_EFFECT].Tip[1][0]),"Increase
volume with increasing time");
strcpy(&(Menu[MNU_EFFECT].Tip[2][0])," ");
strcpy(&(Menu[MNU_EFFECT].Tip[3][0]),"Reverse
the wave file");
strcpy(&(Menu[MNU_EFFECT].Tip[4][0]),"Vary
the Playnack Rate");
Menu[MNU_EFFECT].subMenu[0]=MNU_FADEIN;
Menu[MNU_EFFECT].subMenu[1]=MNU_FADEOUT;
Menu[MNU_EFFECT].AtX=11;Menu[MNU_EFFECT].
      AtY=2;
// The OPERATION menu option
Menu[MNU_OPERATION].nextMenu=MNU_FILE;
Menu[MNU_OPERATION].prevMenu=MNU_EFFECT;
Menu[MNU_OPERATION].Child=FALSE;
Menu[MNU_OPERATION].num_items=3;
for(i=0;i<3;i++)
{
Menu[MNU_OPERATION].Enabled[i]=FALSE;
Menu[MNU_OPERATION].subMenu[i]=NONE;
Menu[MNU_OPERATION].String[i] =
(char*)malloc(15);
Menu[MNU_OPERATION].Tip[i] =
(char*)malloc(50);
Menu[MNU_OPERATION].OptionID[i]=21+i;
}
strcpy(&(Menu[MNU_OPERATION].String[0][0]),"Play");
strcpy(&(Menu[MNU_OPERATION].String[1]
[0]),"-");
strcpy(&(Menu[MNU_OPERATION].String[2]
[0]),"Record");
strcpy(&(Menu[MNU_OPERATION].Tip[0][0]),"Play
the file that was opened");
strcpy(&(Menu[MNU_OPERATION].Tip[1]
[0]),"-");
strcpy(&(Menu[MNU_OPERATION].Tip[2][0]),
"Record sound through the microphone");
Menu[MNU_OPERATION].AtX=23;Menu
[MNU_OPERATION].AtY=2;
// The FADE-IN menu option
Menu[MNU_FADEIN].nextMenu=Menu
[MNU_FADEIN].prevMenu=NONE;
Menu[MNU_FADEIN].Child=TRUE;
Menu[MNU_FADEIN].num_items=2;
for(i=0;i<2;i++)
{
Menu[MNU_FADEIN].Enabled[i]=FALSE;
Menu[MNU_FADEIN].subMenu[i]=NONE;
Menu[MNU_FADEIN].String[i] =
(char *)malloc(15);
Menu[MNU_FADEIN].Tip[i]=(char *)malloc(50);
Menu[MNU_FADEIN].OptionID[i]=31+i;
}
strcpy(&(Menu[MNU_FADEIN].String[0][0]),"Linear");
strcpy(&(Menu[MNU_FADEIN].String[1][0]),"
      Exponential");
strcpy(&(Menu[MNU_FADEIN].Tip[0][0]),"Apply
Linear attenuation or amplification");
strcpy(&(Menu[MNU_FADEIN].Tip[1][0]),"Apply
Exponential attenuation or amplification");
Menu[MNU_FADEIN].AtX=33;Menu
[MNU_FADEIN].AtY=2;
// The FADE-OUT menu option
Menu[MNU_FADEOUT].nextMenu=Menu
[MNU_FADEOUT].prevMenu=NONE;
Menu[MNU_FADEOUT].Child=TRUE;
Menu[MNU_FADEOUT].num_items=2;
for(i=0;i<2;i++)
{
Menu[MNU_FADEOUT].Enabled[i]=FALSE;
Menu[MNU_FADEOUT].subMenu[i]=NONE;
Menu[MNU_FADEOUT].String[i] =
(char *)malloc(15);
Menu[MNU_FADEOUT].Tip[i] =
(char*)malloc(50);
Menu[MNU_FADEOUT].OptionID[i]=41+i;
}
strcpy(&(Menu[MNU_FADEOUT].String[0][0]),
"Linear");
strcpy(&(Menu[MNU_FADEOUT].String[1][0]),
"Exponential");
strcpy(&(Menu[MNU_FADEOUT].Tip[0][0]),"Apply
Linear attenuation or amplification");
strcpy(&(Menu[MNU_FADEOUT].Tip[1][0]),"Apply
Exponential attenuation or amplification");
Menu[MNU_FADEOUT].AtX=33;Menu
[MNU_FADEOUT].AtY=2;
}
void RemoveMenu(int MenuID)
{
int i,j;
textbackground(BLUE);textcolor(WHITE);
gotoxy(Menu[MenuID].AtX,Menu[MenuID].AtY);
for(i=0;i<30;i++) printf("%c",205);
for(i=1;i<=Menu[MenuID].num_items+2;i++)
{
gotoxy(Menu[MenuID].AtX,Menu[MenuID].AtY+i);
for(j=0;j<30;j++) printf(" ");
}
return;
}
int ShowMenu(int MenuID)
{
MENU *menu;
int *subMenu;
int nextMenu, prevMenu;
char **String, **Tip;
int *OptionID;
BOOL *Enabled;
char IsChild;
int num_items;
int longLength,length;
int StartX,StartY;
int i,j;
int CurSelect=0,ch,RetVal;
menu=&(Menu[MenuID]);
num_items=menu->num_items;
String=menu->String;
nextMenu=menu->nextMenu;
prevMenu=menu->prevMenu;
subMenu=menu->subMenu;
IsChild=menu->Child;
OptionID=menu->OptionID;
Tip=menu->Tip;
Enabled=menu->Enabled;
StartX=menu->AtX;
StartY=menu->AtY;
longLength=strlen(String[0]);
if(subMenu[0]!=NULL) longLength+=3;
for(i=1;i<num_items;i++)
{
length=strlen(String[i]);
if(subMenu[i]!=NULL) length+=3;
if(length>longLength) longLength=length;
}
textbackground(LIGHTGRAY);textcolor(WHITE);
for(i=StartY;i<StartY+num_items+2;i++)
{
gotoxy(StartX,i);printf(" ");
gotoxy(StartX+longLength+5,i);printf(" ");
}
StartX++;
gotoxy(StartX,StartY);printf("%c",218);
for(i=0;i<longLength+2;i++) printf("%c",196);
printf("%c",191);
gotoxy(StartX,num_items+StartY+1);printf("%c",192);
for(i=0;i<longLength+2;i++) printf("%c",196);
printf("%c",217);
for(i=0;i<num_items;i++)
{
if(String[i][0]!=':')
{
textcolor(WHITE);
gotoxy(StartX,StartY+i+1);printf("%c ",179);
if(Enabled[i])
textcolor(BLACK);
else
textcolor(BROWN);
gotoxy(StartX+2,StartY+i+1);
for(j=0;j<longLength+1;j++)
if(j<strlen(String[i]))
printf("%c",String[i][j]);
else
printf(" ");
textcolor(WHITE);
printf("%c",179);
}
else
{
textcolor(WHITE);
gotoxy(StartX,StartY+i+1);printf("%c",195);
for(j=0;j<longLength+2;j++) printf("%c",196);
printf("%c",180);
}
}
for(;;)
{
DisplayTip(Tip[CurSelect]);
textbackground(GREEN);
if(Enabled[CurSelect])
textcolor(BLACK);
else
textcolor(BROWN);
gotoxy(StartX+1,StartY+CurSelect+1);
printf(" ");
for(j=0;j<longLength+1;j++)
if(j<strlen(String[CurSelect]))
printf("%c",String[CurSelect][j]);
else
printf(" ");
ch=getch();
if(ch==0) ch=getch();
ch+=300;
switch(ch)
{
case ESCAPE:
RemoveMenu(MenuID);
return(-1);
case ENTER:
RemoveMenu(MenuID);
if(Enabled[CurSelect]==TRUE)
return(OptionID[CurSelect]);
else
return(-1);
case LEFT_ARROW:
if(IsChild==TRUE)
{

```

```

RemoveMenu(MenuID);
return(0);
}
else
{
if(prevMenu!=NONE)
{
RemoveMenu(MenuID);
return(ShowMenu(prevMenu));
}
}
break;
case RIGHT_ARROW:
if(subMenu[CurSelect]!=NONE)
{
RetVal=ShowMenu(subMenu[CurSelect]);
if(RetVal!=0)
{
RemoveMenu(MenuID);
return(RetVal);
}
}
else
{
if(nextMenu!=NONE)
{
RemoveMenu(MenuID);
return(ShowMenu(nextMenu));
}
}
break;
case DOWN_ARROW:
textbackground(LIGHTGRAY);
if(Enabled[CurSelect])
textcolor(BLACK);
else
textcolor(BROWN);
gotoxy(StartX+1,StartY+CurSelect+1);
cprintf(" ");
for(j=0;j<longLength+1;j++)
if(j<strlen(String[CurSelect]))
cprintf("%c",String[CurSelect][j]);
else
cprintf(" ");
CurSelect++;
if(CurSelect==num_items) CurSelect=0;
while(String[CurSelect][0]!=':')
{
if(CurSelect==num_items)
CurSelect=0;
else
CurSelect++;
}
break;
case UP_ARROW:
textbackground(LIGHTGRAY);
if(Enabled[CurSelect])
textcolor(BLACK);
else
textcolor(BROWN);
gotoxy(StartX+1,StartY+CurSelect+1);
cprintf(" ");
for(j=0;j<longLength+1;j++)
if(j<strlen(String[CurSelect]))
cprintf("%c",String[CurSelect][j]);
else
cprintf(" ");
CurSelect--;
if(CurSelect<0) CurSelect=num_items-1;
while(String[CurSelect][0]!=':')
{
if(CurSelect<0)
CurSelect=num_items-1;
else
CurSelect--;
}
break;
}
}
void ButtonDisplay(int x1,int y1,char state
char *caption)
{
text_info tinfo;
gettextinfo(&tinfo);
int i;
if(state==ENABLE_NOTACTIVE) textcolor
(YELLOW);
if(state==ENABLE_ACTIVE) textcolor(WHITE);
if(state==DISABLE) textcolor(LIGHTGRAY);
textbackground(CYAN);
gotoxy(x1,y1);cprintf(" %s ",caption);
textbackground(LIGHTGRAY);textcolor(YELLOW);
cprintf("%c",220);
gotoxy(x1+1,y1+1);for(i=0;i<8;i++)cprintf("%c",223);
textattr(tinfo.attribute);
}
void ButtonPushed(int x1,int y1,char *caption)
{
text_info tinfo;
gettextinfo(&tinfo);
int i;
textbackground(LIGHTGRAY);textcolor(WHITE);
gotoxy(x1,y1);cprintf(" ");
gotoxy(x1,y1+1);cprintf(" ");
textbackground(CYAN);
gotoxy(x1+1,y1);cprintf(" %s ",caption);
delay(250);
gotoxy(x1,y1);cprintf(" %s ",caption);
textbackground(LIGHTGRAY);textcolor(YELLOW);
cprintf("%c",220);
gotoxy(x1,y1+1);cprintf(" ");for(i=0;i<8;i++)
cprintf("%c",223);
textattr(tinfo.attribute);
}
BOOL DisplayDialog(char mode)
{
int Control=0,ch;
int x=29,y=5,i=0,N=0;
char TempStr[40];TempStr[0]=0;
switch(mode)
{
case FILE_OPEN: Window(10,3,70,9,"Open
File",LIGHTGRAY,YELLOW);break;
case FILE_SAVE: Window(10,3,70,9,"Save
File",LIGHTGRAY,YELLOW);break;
case PLAYBACK_RATE: Window(10,3,70,9,"
Playback Rate",LIGHTGRAY,YELLOW);break;
}
ButtonDisplay(25,7,ENABLE_NOTACTIVE,"
Ok ");
ButtonDisplay(45,7,ENABLE_NOTACTIVE,"Cancel");
textbackground(LIGHTGRAY);textcolor(YELLOW);
gotoxy(13,5);
if(mode==FILE_OPEN || mode==FILE_SAVE)
{
cprintf("Enter Filename: ");
strcpy(TempStr,sFileName);
N=39;
}
else
{
cprintf("Playback Rate: ");
strcpy(TempStr,sPlayBackRate);
N=5;
}
textbackground(BLUE);textcolor(WHITE);
cprintf(" ");
gotoxy(29,5);cprintf("%s",TempStr);
i=strlen(TempStr);
x+=i;
for(;;)
{
switch(Control)
{
case 0:
_setcursortype(_NORMALCURSOR);
textbackground(BLUE);textcolor(WHITE);
ButtonDisplay(45,7,ENABLE_NOTACTIVE,"Cancel");
gotoxy(x,y);
break;
case 1:
_setcursortype(_NOCURSOR);
ButtonDisplay(25,7,ENABLE_ACTIVE," Ok ");
break;
case 2:
ButtonDisplay(45,7,ENABLE_ACTIVE,"Cancel");
ButtonDisplay(25,7,ENABLE_NOTACTIVE,"
Ok ");
break;
}
}
ch=getch();
if(ch==0) ch=getch()+300;
ch+=300;
switch(ch)
{
case TAB:
Control=(++Control)%3;
break;
case ESCAPE:
_setcursortype(_NOCURSOR);
ButtonPushed(45,7,"Cancel");
ch=1; Control=2;
break;
case ENTER:
_setcursortype(_NOCURSOR);
ButtonPushed(25,7," Ok ");
ch=1;Control=1;
break;
case SPACE:
if(Control==2){_setcursortype(_NOCURSOR);
ButtonPushed(45,7,"Cancel");ch=1;}
if(Control==1){_setcursortype(_NOCURSOR);
ButtonPushed(25,7," Ok ");ch=1;}
break;
case BACK_SPACE:
if(Control==0 && i>0)
{
gotoxy(-x,y);
cprintf(" ");
i--;
TempStr[i]=0;
gotoxy(29,5);
cprintf("%s",TempStr);
}
break;
default:
ch=300;
if(ch<300 && i<N)
{
TempStr[i++]=char)ch;
TempStr[i]=0;
gotoxy(29,5);
cprintf("%s",TempStr);
x++;
}
break;
}
if(ch==1) break;
}
textbackground(BLUE);textcolor(WHITE);
for(ch=3;ch<=9;ch++)
}
gotoxy(10,ch);
for(i=10;i<=70;i++)
cprintf(" ");
}
if(Control==1)
{
if(mode==FILE_SAVE || mode==FILE_OPEN)
strcpy(sFileName,TempStr);
if(mode==PLAYBACK_RATE)strcpy(sPlayBackRate,
TempStr);
return(TRUE);
}
return(FALSE);
}

```

```

void SetEnvVariables(){}
void SaveFile(){}
void main()
{
int ch;
textbackground(BLACK);textcolor(LIGHTGRAY);
clrscr();
_setcursortype(_NOCURSOR);
DrawScreen();
MenuInitialise();
sFileName[0]=0;
strcpy(sPlayBackRate,"22400");
for(;;)
{
DisplayTip("Ready");
ch=getch();
if(ch==0) ch=getch();
ch+=300;
switch(ch)
{
case AltF:ch=ShowMenu(MNU_FILE);break;
case AltE:ch=ShowMenu(MNU_EFFECT);break;
case AltO:ch=ShowMenu(MNU_OPERATION);
break;
}
switch(ch)
{
case FILE_EXIT:
ch=AltX;
break;
case FILE_OPEN:
if(DisplayDialog(FILE_OPEN))
if(mOpen())
{
for(int i=0;i<5;i++)
Menu[MNU_EFFECT].Enabled[i]=TRUE;
Menu[MNU_OPERATION].Enabled[0]=TRUE;
for(i=0;i<2;i++)
{
Menu[MNU_FADEIN].Enabled[i]=TRUE;
Menu[MNU_FADEOUT].Enabled[i]=TRUE;
}
}
break;
case FILE_SAVE:
/*if(DisplayDialog(FILE_SAVE))mSave()*/
break;
case FADEIN_LINEAR:
FadeCommon(FADEIN,LINEAR);
break;
case FADEIN_EXP:
FadeCommon(FADEIN,EXPONENTIAL);
break;
case FADEOUT_LINEAR:
FadeCommon(FADEOUT,LINEAR);
break;
case FADEOUT_EXP:
FadeCommon(FADEOUT,EXPONENTIAL);
break;
case REVERSE:
ReverseWave();
break;
case PLAYBACK_RATE:
if(DisplayDialog(PLAYBACK_RATE)==FALSE)
SetPlayBackRate(0);
else
SetPlayBackRate(1);
break;
case PLAY:
mPlay();
break;
}
if(ch==AltX)
{
_setcursortype(_NORMALCURSOR);
textcolor(LIGHTGRAY);
textbackground(BLACK);
clrscr();
printf("MPLAYER Ver.1.0\n");

```

```

printf("-----\n");
printf("\tM.Somasundaram - msoms@vsnl.com\n
\tN.V.Venkatarayalu - v_rayalu@vsnl.com\n\n");
break;
}
}
}

SOUNDS.H
#include "Globals.h"
////////// Playback Sounds ////////////
void mPlay(void)
{
FILE *fp;
unsigned char Sample;
clock_t t1;
long k=0,t=0,i=0;
fp=fopen("test.aud","rb");
t1=clock();
while(clock()-t1<18.2){
if(k<RateOfPlayBack){
fgetc(fp);
outp(0x37a,0);
if(!feof(fp)) break;
t++;
k++;}
i=k/(RateOfPlayBack+2000);
k=0;rewind(fp);
t1=clock();
while(clock()-t1<18.2){
if(k%i==0){
fgetc(fp);
outp(0x37a,0);
if(!feof(fp)) break;
t++;
}
if(k>0) k=k;
k++;}
i=k/(RateOfPlayBack+2000);
k=0;t=0;rewind(fp);
while(!feof(fp)==FALSE)
{
t1=clock();
if(k%i==0){
Sample=(unsigned char)fgetc(fp);
outp(DATA_OUT,Sample);
t++;}
k++;
}
fclose(fp);
outp(DATA_OUT,0);
}
////////// Fade Common Function ////////////
void FadeCommon(char far InOrOut,char far
Type)
{
FILE *fp, *fpt;
long double i;
long double step;
long double attn1;
fp=fopen("test.aud","rb");
fpt=fopen("tmp.aud","wb");
step=1.0/NoSamples;
if(InOrOut==FADEIN)
attn1=0;
else
{
attn1=1;
step=-step;
}
if(Type==LINEAR)
for(i=0.0;i<NoSamples;i++)
{
attn1+=step;
fputc(128+(unsigned char)((long double)(fgetc(fp)-
128)*attn1),fpt);
}
else
for(i=0.0;i<NoSamples;i++)
{

```

```

attn1=exp(i*step);
fputc(128+(unsigned char)((long double)(fgetc(fp)-
128)*attn1),fpt);
}
fclose(fp);
fclose(fp);
unlink("test.aud");
rename("tmp.aud","test.aud");
}
////////// Reverse Wave File ////////////
void ReverseWave(void)
{
FILE *fp, *fpt;
long double i;
fp=fopen("test.aud","rb");
fpt=fopen("tmp.aud","wb");
for(i=0.0;i<NoSamples;i++)
{
fseek(fp,-(long)i,SEEK_END);
fputc(fgetc(fp),fpt);
}
fclose(fpt);
fclose(fp);
unlink("test.aud");
rename("tmp.aud","test.aud");
}
////////// Set Playback rate ////////////
void SetPlayBackRate(long rate)
{
if(rate<65535)
{
if(rate!=0)
{
rate=atol(sPlayBackRate);
RateOfPlayBack=rate;
}
ultoa(RateOfPlayBack,sPlayBackRate,10);
}
return;
}
////////// Open a wav file and set parameters //////////
BOOL mOpen(void)
{
void DisplayTip(char *);
int TYPE_OF_OUTPUT=MONO_OUTPUT;
FILE *fsource, *fdest;
fsource=fopen(sFileName,"rb");
if(fsource!=NULL)
{
fdest=fopen("test.aud","wb");
RIFF riff;
WAVE wave;
DATA data;
fread(&riff,sizeof(riff),1,fsource);
fread(&wave,sizeof(wave),1,fsource);
fseek(fsource,20+wave.fmt.fLen,SEEK_SET);
fread(&data,sizeof(data),1,fsource);
if(strncmpi(data.dID,"FACT",4)==0){
fseek(fsource,data.dLen,SEEK_CUR);
fread(&data,sizeof(data),1,fsource);
}
if(!(strncmpi(riff.rID,"RIFF",4)==0 && strncmpi
(wave.wID,"WAVE",4)==0 && strncmpi(data.dID,
"DATA",4)==0 && strncmpi(wave.fmt.fID,"fmt
",4)==0 && wave.fmt.wFormatTag==PCM &&
wave.fmt.nChannels<=6))
{
printf("\a");
DisplayTip("Unrecognizable Format -Not PCM
8-bit.");
return FALSE;
}
unsigned long dlen=data.dLen;
char array[6];int array[6];
int nChannels=wave.fmt.nChannels;
SamplingFrequency=PBR=RateOfPlayBack=
wave.fmt.nSamplesPerSec;
ultoa(RateOfPlayBack,sPlayBackRate,10);
NoSamples=(dlen/nChannels)*TYPE_OF_

```



```

        OUTPUT;dlen=NoSamples;
    BOOL bits16=FALSE;
    if(wave.fmt.FormatSpecific==BITS16) bits16=
        TRUE;
    if(bits16==FALSE)
    while(dlen>0)
    {
        fread(array,1,nChannels,fsource);
        switch(nChannels)
        {
            case 1: fputc((int)array[0],fdest);
            if(TYPE_OF_OUTPUT==STEREO_OUTPUT)
            fputc((int)array[0],fdest);
            break;
            case 2:  fputc((int)array[0],fdest);
            if(TYPE_OF_OUTPUT==STEREO_OUTPUT)
            fputc((int)array[1],fdest);
            break;
            case 3:  fputc((int)array[0],fdest);
            if(TYPE_OF_OUTPUT==STEREO_OUTPUT)
            fputc((int)array[1],fdest);
            break;
            case 4:  fputc((int)array[0],fdest);
            if(TYPE_OF_OUTPUT==STEREO_OUTPUT)
            fputc((int)array[2],fdest);
            break;
            case 6:  fputc((int)array[1],fdest);
            if(TYPE_OF_OUTPUT==STEREO_OUTPUT)
            fputc((int)array[4],fdest);
            break;
        }
        dlen--;
    }
    else
    {
        NoSamples/=2;
        dlen=NoSamples;
        while(dlen>0)
        {
            fread(arrayi,2,nChannels,fsource);
            switch(nChannels)
            {
                case 1: array[0]=(char)((long)(arrayi[0]+
                    32768)*255/65535);
                    fputc((int)array[0],fdest);
                    if(TYPE_OF_OUTPUT==STEREO_OUTPUT)
                    fputc((int)array[0],fdest);
                    break;
                case 2:  array[0]=(char)((long)(arrayi[0]+
                    32768)*255/65535);
                    fputc((int)array[0],fdest);
                    if(TYPE_OF_OUTPUT==STEREO_OUTPUT)
                    {
                        array[1]=(char)((long)(arrayi[1]+32768)*255/
                            65535);
                        fputc((int)array[1],fdest);
                    }
                    break;
                case 3:  array[0]=(char)((long)(arrayi[0]+
                    32768)*255/65535);
                    fputc((int)array[0],fdest);
                    if(TYPE_OF_OUTPUT==STEREO_OUTPUT)
                    {
                        array[1]=(char)((long)(arrayi[1]+32768)*255/
                            65535);
                        fputc((int)array[1],fdest);
                    }
                    break;
            }
        }
    }
    break;
    case 4:  array[0]=(char)((long)(arrayi[0]+
        32768)*255/65535);
        fputc((int)array[0],fdest);
        if(TYPE_OF_OUTPUT==STEREO_OUTPUT)
        {
            array[2]=(char)((long)(arrayi[2]+32768)*255/
                65535);
            fputc((int)array[2],fdest);
        }
        break;
    case 6:  array[1]=(char)((long)(arrayi[1]+
        32768)*255/65535);
        fputc((int)array[1],fdest);
        if(TYPE_OF_OUTPUT==STEREO_OUTPUT)
        {
            array[4]=(char)((long)(arrayi[4]+32768)*255/
                65535);
            fputc((int)array[4],fdest);
        }
        break;
    }
    dlen--;
}
fclose(fsouce);
fclose(fdest);
return TRUE;
}
else
{
    printf("\a");
    DisplayTip("The file is not available!");
    return FALSE;
}
}

GLOBALS.H
#include <stdio.h>
#include <dos.h>
#include <process.h>
#include <conio.h>
#include <string.h>
#include <math.h>
#include <stdlib.h>
#include <time.h>
#define FALSE 0
#define TRUE 1
#define ENABLE_ACTIVE 1
#define ENABLE_NOTACTIVE 2
#define DISABLE 0
#define NONE -1
#define MNU_FILE 0
#define MNU_EFFECT 1
#define MNU_OPERATION 2
#define MNU_FADEIN 3
#define MNU_FADEOUT 4
#define FILE_OPEN 1
#define FILE_SAVE 2
#define FILE_EXIT 4
#define FADEIN_LINEAR 31
#define FADEIN_EXP 32
#define FADEOUT_LINEAR 41
#define FADEOUT_EXP 42
#define REVERSE 14
#define PLAYBACK_RATE 15
#define PLAY 21
#define RECORD 22

#define AltE 318
#define AltF 333
#define AltO 324
#define AltX 345
#define LEFT_ARROW 375
#define RIGHT_ARROW 377
#define UP_ARROW 372
#define DOWN_ARROW 380
#define ESCAPE 327
#define ENTER 313
#define SPACE 332
#define BACK_SPACE 308
#define TAB 309
#define PCM 1
#define IN 0
#define OUT 1
#define LINEAR 0
#define EXPONENTIAL 1
#define FADEIN 0
#define FADEOUT 1
#define DATA_OUT 0x378
#define BITS16 16
#define BITS8 8
#define STEREO_OUTPUT 2
#define MONO_OUTPUT 1
typedef char BOOL;
typedef struct{
    char rID[4];
    unsigned long rLen;
}RIFF;
typedef struct{
    char fID[4];
    unsigned long fLen;
    unsigned int wFormatTag;
    unsigned int nChannels;
    unsigned long nSamplesPerSec;
    unsigned long nAvgBytesPerSec;
    unsigned int nBlockAlign;
    unsigned int FormatSpecific;
}FORMATCHUNK;
typedef struct{
    char wID[4];
    FORMATCHUNK fmt;
}WAVE;
typedef struct{
    char dID[4];
    unsigned long dLen;
}DATA;
struct MENU
{
    int subMenu[10];
    char *Tip[10];
    char *String[10];
    int OptionID[10];
    BOOL Enabled[10];
    int num_items;
    char Child;
    int AtX,AtY;
    int nextMenu;
    int prevMenu;
} Menu[5];
long RateOfPlayBack=15000.PBR;
long double NoSamples=76455;
double SamplingFrequency=44000;
char sFileName[40];
char sPlayBackRate[6];

```

www.electronicsforu.com

a portal dedicated to electronics enthusiasts

STEPPER MOTOR DRIVER



PIYUSH P. TAILOR

Stepper motors are widely used where precision and accuracy are the primary considerations during rotation or positioning. Microprocessors or microcontrollers are often employed for


controlling their operation. But it may not always be convenient or necessary to use microcontrollers, as it would make the gadget unnecessarily costlier.

Here is a simple and low-cost circuit to drive a stepper motor on full power for any number of whole steps. The present circuit is intended

(IC1) with decoded outputs is used here as a sequence generator (similar to the running-light effect). As we need only four outputs, the fifth output (pin 10) is connected to the RESET pin (pin 15). The

mon terminal to the ground. Now give the lowest possible supply (3V) and check for correct sequence of the remaining three terminals, using trial-and-error method for the maximum six combinations/possibilities. At correct sequence, the motor would rotate in either clockwise or anti-clockwise direction.

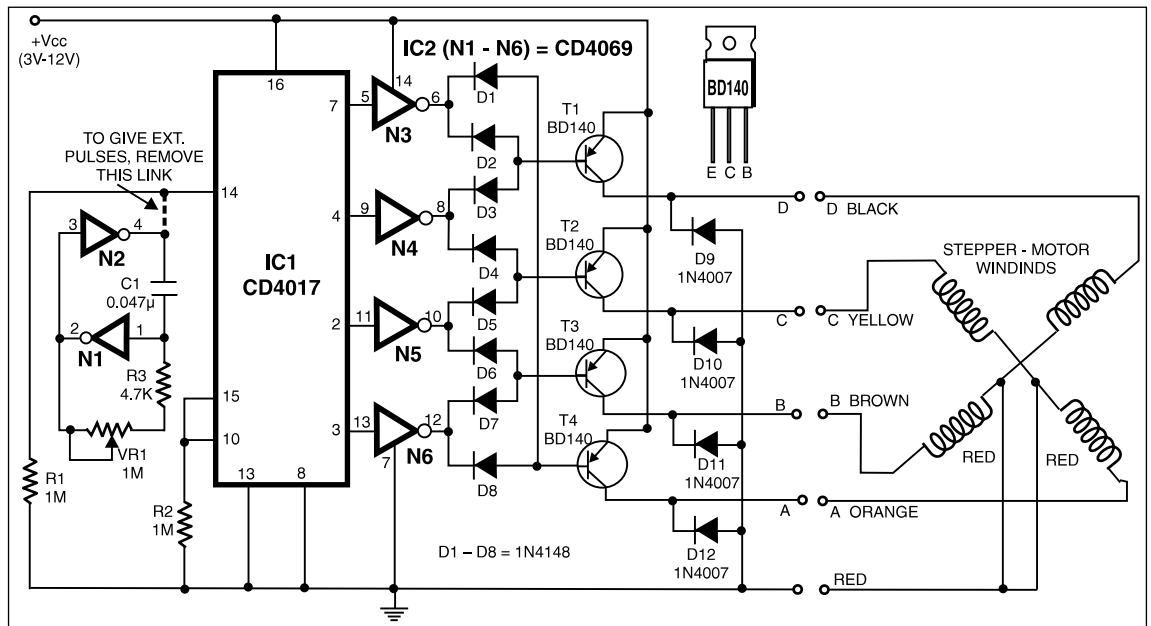To use external clock pulses, simply disconnect pin 14 of CD4017B from pin 8 of CD4069B and then connect external clock pulses to pin 14 of CD4017B. Each



to drive four-winding stepper motors, but one can easily modify it for other types.

The popular decade counter CD4017

four outputs, in conjunction with four npn power transistors, function as half-power full-step drivers. In order to get full power, eight diodes (8 x 1N4148) are used. Truth Table I depicts the half-power operation, while truth Table II depicts the full-power operation.

The use of hex inverter IC2 (CD4069) gives two benefits:

1. The inversion through NOT gates allows the use of npn power transistors (4 x BD140), which make it possible to ground the common terminal of the motor. This is useful in many applications.
2. The two unused inverter gates (N1 and N2) are handy to use as clock generator, in conjunction with preset VR1 and capacitor C1. Varying the preset allows the change in clock frequency and hence the speed of the motor.

If one does not know the sequence of motor terminals to be connected to terminals A through D of the circuit, then first connect any one terminal of motor to terminal A of the circuit and connect com-

pulse drives the motor by one step, which may normally be 1.8° or 3.6°, as shown on the label plate of the motor.

To reverse the direction of rotation, one should interchange terminals A with B and C with D simultaneously.

The colours of motor terminal wires, shown in the diagram, are those of the stepper motor used in head-drive of a 1.2MB floppy disk drive unit, operating on 12V with a 3.6°/step, which the author has used in his prototype.

Notes: 1. Heat-sinks may not be required for the power transistors.

2. Cost of the circuit is less than Rs 100.

3. Supply voltage for the circuit is equal to the operating voltage of the motor (i.e. between 3V and 12V).

4. RPM of motor = $\frac{f \times d}{6}$, where f is the frequency of clock pulses and d the angular displacement in degrees per step.

TABLE I
Half-Power Operation

Step number	Supply to coils			
	A	B	C	D
1	On	Off	Off	Off
2	Off	On	Off	Off
3	Off	Off	On	Off
4	Off	Off	Off	On
5 Repetition	On	Off	Off	Off

TABLE II
Full-Power Operation

Step number	Supply to coils			
	A	B	C	D
1	On	On	Off	Off
2	Off	On	On	Off
3	Off	Off	On	On
4	On	Off	Off	On
5 Repetition	On	On	Off	Off

ELECTRONIC DIGITAL TACHOMETER




ADITYA U. RANE

Tachometer is nothing but a simple electronic digital transducer. It finds many applications in our daily life. Normally, a tachometer is used for measuring the speed of a rotating shaft, gear, or a pulley. A tape or a contrasting stripe is pasted on the rotating part of the machinery. The reflected light from the contrasting stripe falls on the junction

of the sensor module, its output goes low. This output is connected to pin 2 of NE555 (configured as a monostable) to trigger it. The output pulses from pin 3 are connected to clock pin 12 of 74C926. Hence, on receipt of every pulse, the count of IC 74C926 increments by one. For checking the revolutions in a predetermined time period, a stopwatch may be used. Before counting starts, depress reset switch S1

stage consists of a digital counter based on 4-digit counter IC 74C926. When light from any source falls on junction of the infrared module, its output goes low. This output is connected to pin 2 of NE555 (configured as a monostable) to trigger it. The output pulses from pin 3 are connected to clock pin 12 of 74C926. Hence, on receipt of every pulse, the count of IC 74C926 increments by one. For checking the revolutions in a predetermined time period, a stopwatch may be used. Before counting starts, depress reset switch S1

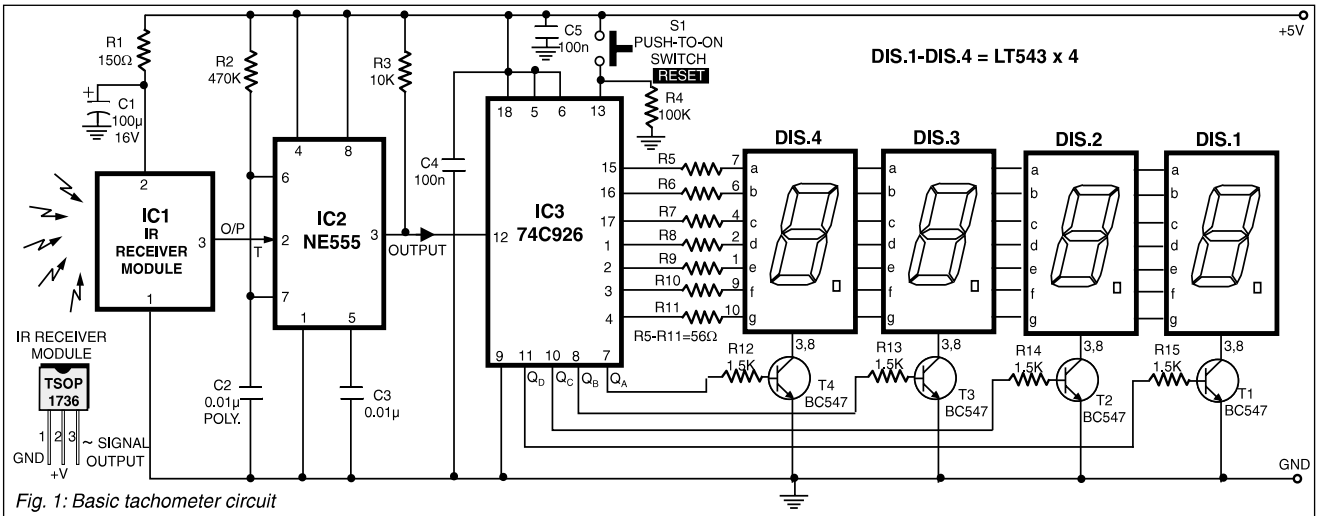



day-to-day life.

Normally, a tachometer is used for measuring the speed of a rotating shaft, gear, or a pulley. A tape or a contrasting stripe is pasted on the rotating part of the machinery. The reflected light from the contrasting stripe falls on the junction

of the sensor module to alternately activate and deactivate it, depending upon the size and width of the tape pasted on the pulley or rotating part of the machine. Hence, one gets the output in the form of sharp pulses for every revolution.

and release it as soon as counting is to start. At the instant when counting is to end, one should immediately withdraw either the sensor module or switch 'off' the light source to see the final reading (revolutions) on the display. Accuracy will be better if the counting period is comparatively larger.

 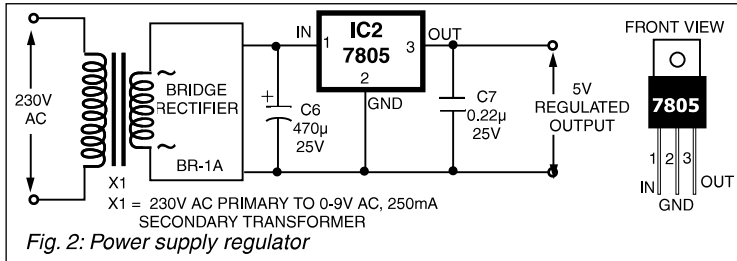
The 74C926 is basically a 4-digit counter module, which can count from 0000 to its maximum possible value of 9999. It can be operated with V_{CC} of 3 to 15 volts. Here, regulated 5-volt supply is



sharp pulses for every revolution.

Apart from counting the revolutions of a moving object, the circuit can also be used for counting the objects on a conveyor belt.

The basic digital tachometer circuit consists of two stages. The first stage is a simple monostable, wired around IC NE555. The second

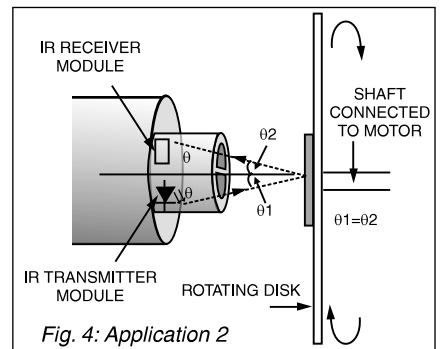

 


Fig. 5: Use of contrasting stripe

used for the entire circuit. The circuit shown in Fig. 2 employs 7805 regulator. This 4-digit counter can be readily interfaced to many circuits such as clock-frequency meter, digital voltmeter, tachom-

 


Fig. 6: Application 3

eter (as explained here), stop watch, etc. A reset switch is connected between pin 13 and V_{CC} .

The chip 74C926 pulls its carry output (pin 4) 'high' when the counter reaches 6,000. This output can be suitably used in clock circuits for resetting; for example, if the clock input is 100 Hz per second, the carry output will be available every minute. However, here we are not using the carry output.

There are different versions of 4-digit counter modules for different applications. For example, in 74C927, the second most significant digit gets divided by 6, rather than 10. Similarly, in 74C928, the most significant digit gets divided by 2, rather than 10, and its carry output goes 'high' at the count of 2000, and 'low' only when the reset switch is pulled 'high'.

Figs 3 and 4 show the applications of the electronic digital tachometer. Basic principle in both these applications is the same. The important factor is that maximum reflected light from the contrasting stripe should fall on the IR detector, i.e. $\theta 1$

 


Fig. 7: IR light source

should be equal to $\theta 2$. The other important thing is that the contrasting stripe may be a mirror with a small piece of tape pasted on it, as

shown in Fig. 5.

Fig. 6 shows another application of the same circuit for counting the objects moving over a conveyer belt. The only difference between applications shown in Figs 3, 4, and 6 is that in the first two applications, one requires a contrasting stripe, whereas in case of Fig. 6, one requires a light source and a sensor module which are kept on the opposite sides of the conveyer belt.

When there is no object between the source (light) and the sensor module, one gets a continuous pulse at the output pin 3 of monostable IC NE555. But as soon as the object on moving conveyer belt obstructs the light path, the output of NE555 goes 'low'. Since output pin 3 of NE555 is connected to the clock input pin 12 of 74C926, the number of objects get counted continuously—up to 9999, using a single 74C926. A simple IR light-source circuit is shown in Fig. 7.

The total cost of fabrication of the complete circuit is approximately Rs 250.

LIGHT-OPERATED LIGHT SWITCH

PRADEEP G.


Here is a light-operated, remote-controlled solidstate switch to operate a lamp. During darkness, the resistance of LDR shoots up to megohm range. Thus, the triac does not get gate drive and hence it does not conduct.

When LDR is illuminated by means of a torch-light beam, the resistance of LDR suddenly decreases (below 10-kilo-ohm). This causes the triac to conduct and switch 'on' the lamp. Light received



from the lamp (not from the torch) keeps LDR's resistance low. So, the lamp remains continuously 'on'. Once the lamp is 'on', it can be switched 'off' again by interrupting the light falling on LDR, by either waving hand in front of it or by interrupting power supply to the circuit for a moment.

 RFC employed here can be made by winding about 15 turns of 18 SWG wire over an insulated ferrite rod.



PRECISION DIGITAL AC POWER CONTROLLER



PRATAP CHANDRA SAHU

SCRs and Triacs are extensively used in modern electronic power controllers—in which power is controlled by means of phase angle variation of the conduction period. Controlling the phase angle can be made simple and easy if we set different firing times corresponding to different firing angles. The design given here is a synchronised program-

one divides the angle described during one complete cycle of the sine wave ($2\pi = 360^\circ$) into equal parts, then time period T of the wave will be divided into identical equal parts. Thus, it becomes fairly easy to set the different programmable timings synchronised with the AC mains sine wave at zero crossing. The main advantage of such an arrangement, as al-

ready mentioned earlier, is that only the firing time has to be programmed to set different firing angles. It is to be noted that the more precise the timer, the more precise will be the power being controlled.

In this circuit, the time period of mains waveform is divided into 20 equal parts. So, there is a time interval of 1 ms between two consecutive steps. The sampling voltage is unfiltered full-wave and is obtained from the diode bridge at the output of the power transformer. The timer is reset at every zero crossing of full wave and set again instantly for the next delay time. This arrangement helps the timer to be set for every half of mains wave—when the positive half of the mains waveform starts building up, the timer is set for that half and as it begins to cross

zero, it gets reset and set again for negative half, when the negative half begins to build up. The process is repeated. Here, instead of using two zero crossing detectors—one for each half of mains wave—a single detector is used to perform both the functions. This is possible because the sampling wave for negative half is inverted by the rectifier diode bridge.

The 18V AC from power transformer is fed to the four diodes in bridge configuration, followed by the filter capacitor which is again followed by a three-terminal voltage regulator IC LM7812. The voltage so obtained drives the circuit. The unfiltered voltage is isolated from the filter capacitor by a diode and is fed to zener diode D8, which acts as a clipper to clip voltage above 6 volts.

This voltage is fed to the base of transistor T1, which is wired as zero crossing detector. When base voltage reaches the threshold, it conducts. It thus supplies a narrow positive pulse which resets the timer at every zero crossing.

A 32.768kHz crystal is used to get stable output of nearly 1 kHz (1,024Hz) frequency after five stages of binary division by an oscillator-cum-divider IC CD4060. The 32.768kHz crystal is used because it can be found in unused

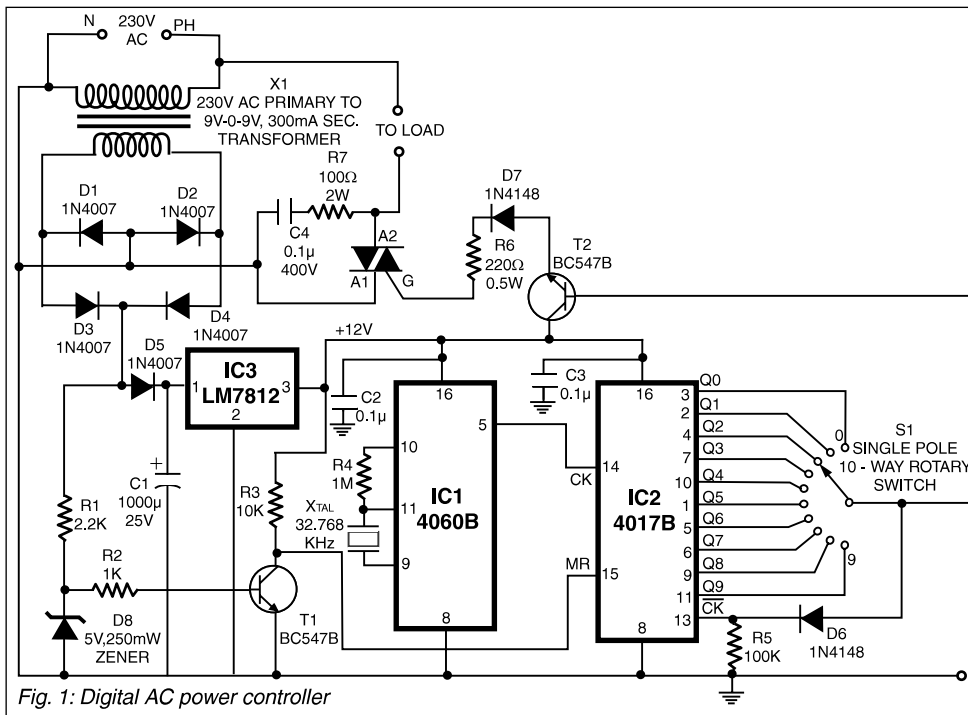


Fig. 1: Digital AC power controller

mable timer which achieves this objective.

The following equation for a sine wave shows how firing time and the phase angle are related to each other:

$$\theta = 2\pi ft \text{ or } \theta \propto t$$

Here, θ is the angle described by a sine wave in time t (seconds), while f is the frequency of sine wave in Hz. Time period T (in seconds) of a sine wave is equal to the reciprocal of its frequency, i.e. $T = 1/f$.

The above equation indicates that if

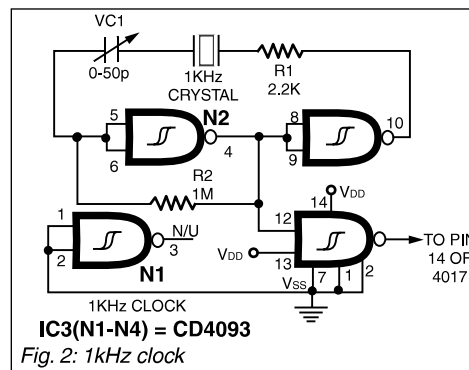


Fig. 2: 1kHz clock

 


Fig. 3: Load current waveforms

quartz clocks and is readily available in the market. But use of a 1kHz crystal using a quad-NAND IC CD4093 as clock generator, as shown in Fig. 2, is better as it provides the exact time interval required. In that case, CD4060 oscillator/divider is not required.

The CD4017B counter-cum-decoder IC then divides this 1kHz signal into ten equal intervals, which are programmed via the single-pole, 10-way rotary switch. Once the delayed output

reaches the desired time interval, the corresponding output of CD4017 inhibits the counter CD4017 (via pole of rotary switch and diode D6) and fires the Triac. Transistor T2 here acts as a driver transistor. The reset pin of 4017 is connected to zero crossing detector output to reset it at every zero crossing. (The load-current waveforms for a few positions of the rotary switch, as observed at EFY Lab, are shown in Fig. 3.)

The circuit can be used as power controller in lighting equipment, hot-air oven, universal single-phase AC motor, heater, etc.

LUGGAGE SECURITY SYSTEM

DHURJATI SINHA



While travelling by a train or bus, we generally lock our luggage using a chain-and-lock arrangement. But, still we are under tension, apprehending that somebody may cut the chain and steal our luggage. Here is a simple circuit to alarm you when somebody tries to cut the chain.

Transistor T1 enables supply to the sound generator chip when the base current starts flowing through it. When the wire (thin enameled copper wire of 30 to 40 SWG, used for winding transformers) loop around the chain is broken by somebody, the base of transistor T1, which was earlier tied to positive rail, gets opened. As a result, tran-


sistor T1 gets forward biased to extend the positive supply to the alarm circuit. In idle mode, the power consumption of the circuit is minimum and thus it can be used for hundreds of travel hours.

To enable generation of different

alarm sounds, connections to pin 1 and 6 may be made as per the table.

Select 1 (Pin6)	Select 2 (Pin1)	Sound effect
X	X	Police siren
V _{DD}	X	Fire-engine siren
V _{SS}	X	Ambulance siren
-	V _{DD}	Machine-gun sound

 Note: X = no connection; "-" = do not care



June

2000

PORTABLE OZONE GENERATOR

K PADMANABHAN, S ANANTHI AND KIRIT PATEL



S.C. DWIVEDI

This article is dedicated to the good health of EFY readers in the year 2000 and beyond. It describes an ozone generator for portable (and portable1) use.

Ozone gas is now-a-days used for treatment of drinking water, disinfection, and air-purification. What one requires is a small and handy unit to be plugged into mains to get ozonated air at suitable pressure flowing out from a tube. It can then be let into environment or bubbled through water or any other polluted liquid. But the gadget must be completely safe to work with.

Ozone generators invariably make

use of a discharge tube to which a high electric field is applied so as to break down the oxygen present in the air. This phenomenon occurs at or near a field strength of 25 kV/cm, and the resulting discharge that takes place is known as corona. The corona has a light bluish glow. It is in this corona field that oxygen becomes ozone (O₃).

Ozone has tendency to revert back to its original form in about 10-20 minutes, in the atmosphere. Therefore, it is necessary in any ozone application to generate ozone as and when required for use since it cannot be kept stored the way chlorine is stored (in cylinders). Chlorine is used in our cities to disinfect drinking water supply. It is highly carcinogenic because when it comes into contact with remnants of pesticides in our foodstuff (vegetables), it generate halomethanes, which

are carcinogenic. That is why, ozone is used today in preference to chlorine.

Complete disinfection of water, in any impure form, is realised with an ozone content of 4 mg/litre. Ozone generator presented here has a capacity of producing 10 mg/minute of ozone combined with atmospheric air. This unit can treat five litres of impure water in just two minutes.

The discharge tube is supplied air from an air-group, which is built into the unit. The unit produces ozonated air at a pressure head of 15-20 cm of water via its outlet. So the exit tube can be let into water containers with water up to a level of 10-15 cm.

Another advantage of this unit is that it is light in weight (less than a kilogram) and carries a very simple control and a microammeter showing the ozone concentration. It employs a high voltage of over 5 kV at a high frequency of 15 kHz to 20 kHz, which would not cause a lethal shock. Shock voltages are not cause a lethal shock. Shock voltages are not dangerous at these high frequencies, while at 50 Hz these high voltages are quite dangerous.

Commercial ozone generators make use of mains 50Hz frequency and are thus very dangerous while assembling. Extreme care is required to be exercised by the user while diagnosing any problem with such apparatus. Ozone generator at the higher frequencies used here

 


Fig. 1: Airflow through cylindrical space of discharge tube

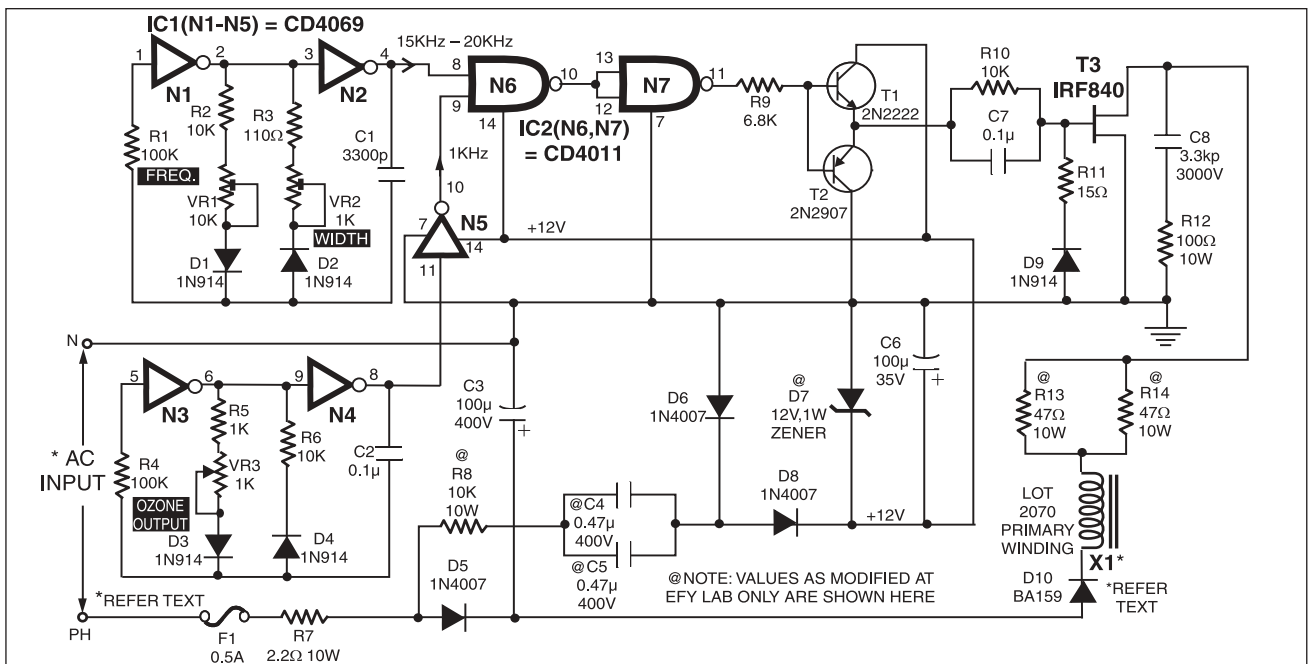


Fig. 2: Schematic Diagram of portable ozone

 


Fig. 3: Actual-size, single-sided PCB layout


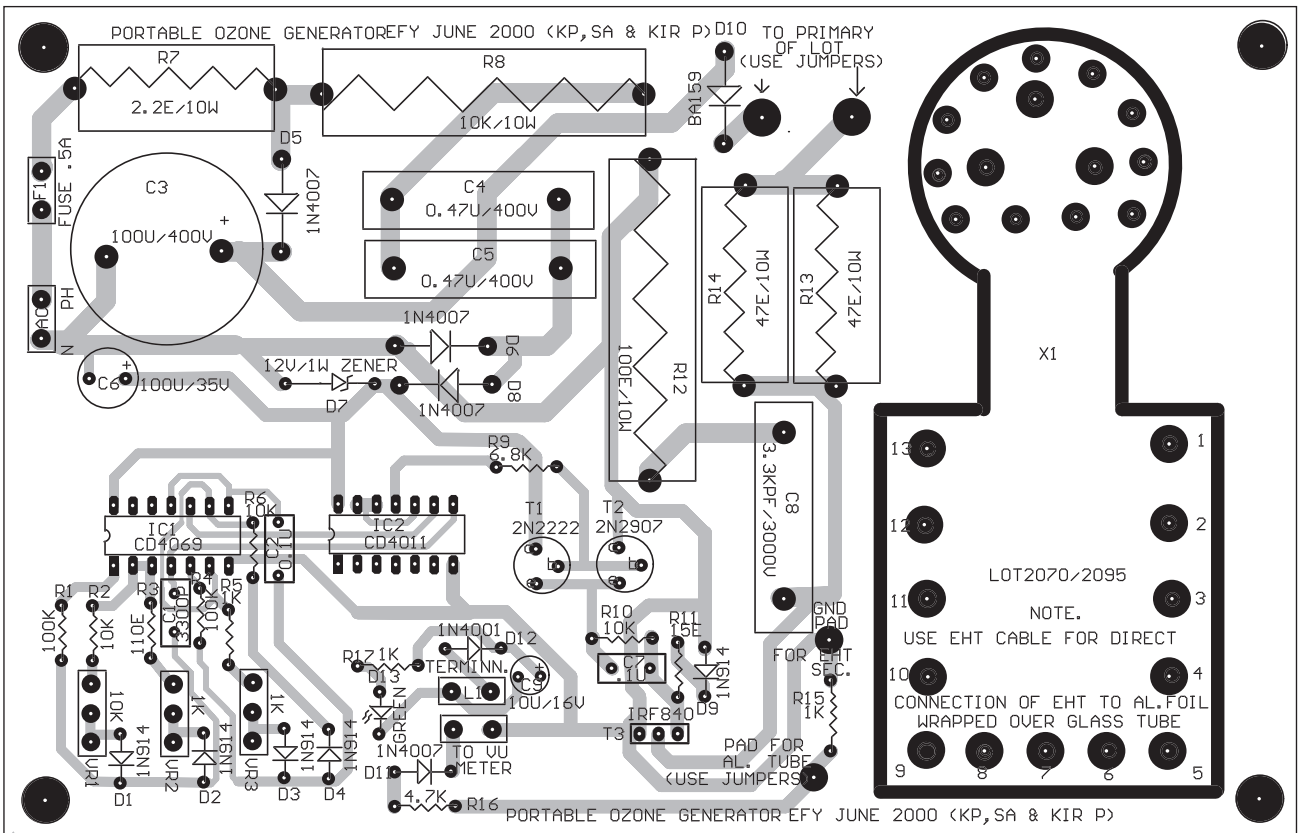


Fig. 4: Component layout for the PCB

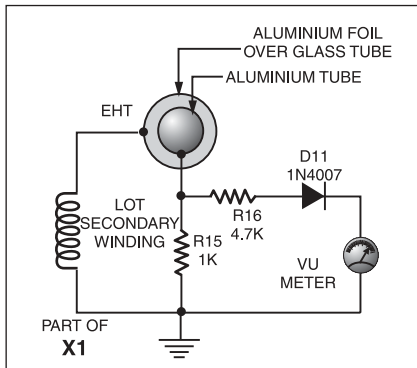

Metering circuit

is more efficient and silent in its discharge. One can easily assemble this portable ozone generator in a plastic breadbox (used for storing one full bread), which is all insulated (with no exposed metal parts). The cost of making a simple unit is much less than Rs 1,000.

The air pump used in this project is an aquarium pump which costs less than Rs 100. This pump works on mains and has a 50Hz vibrator attached to a rubber bellows that provides a pulsating airflow that provides a pulsating airflow. This air flows through the cylindrical space of discharge tube as shown in Fig.1. The discharge tube outlet gives ozonated air.

The circuit as shown in Fig.2 generates a controlled high-frequency AC voltage of above 5 kV. The circuit has been designed such that all components used in the circuit are economical and freely available from TV spares shops.

The single-sided, actual-size PCB layout for the complete circuit and its component layout are shown in Figs 3 and 4 respectively. The entire assembly of the unit—including the air pump, discharge tube, circuit board, and the fuse—can be comfortably fitted within the breadbox, as shown in Fig.8. Because of this compact packaging, no mains transformer (which is generally heavy) is employed. The unit should not be touched after its assembly in the breadbox, nor should its lid be opened after plugging into the mains.

Lab note: During practical testing of the circuit at EFY Lab, an auto-transformer for stepping down the mains voltage to about 120V AC had to be used to avoid build-up of excessively high voltage greater than 30 kV peak. At AC input voltage greater than 160V (RMS), overheating of resistors (parallel combination of resistors R13 and R14) in series with the primary of EHT winding

was also noticed.

The circuit

Pulse generator. A simple pulse generator is realised using two CMOS integrated circuits. The CD4069 is a hex buffer, while CD4011 is a quad NAND gate. Two of the 4069 gates are used to generate 15-20 kHz pulses. The frequency of this oscillator can be varied by 10-Kilo-ohm preset VR1 on the board. The width of the pulse can also be adjusted using preset VR2, but it is left at 33 per cent duty cycle. The circuit uses an RC (resistance-capacitance) feedback for generation of the square-wave oscillations. The 330pF capacitor C1 used here charges during one-half cycle through the 110-ohm resistor R3 and the 1-kilo-ohm width-setting variable resistor VR2. During the other half, capacitor C1 discharges through 10k resistor R2 and the adjustable-frequency preset VR1. Diodes D1 and D2 differentiate between the two half cycles.

Note: In Fig. 2, the line joining resistor R1 to D1, D2, and the 3,300pF capacitor C1 represents a joint only and is not ground.

The second oscillator, shown in Fig. 2, also uses the gates from same IC CD4069. It is, however, wired using 0.1uF capacitor C2, instead of the 330pF used in the former oscillator. The 1k potmeter VR3 in the circuit is for ozone output control. This control is brought out, as shown in Fig. 8, for slightly varying the ozone output. This control is brought out, as shown in Fig. 8, for slightly varying the ozone output. This second oscillator works at around 2 kHz. Therefore when the outputs of the two oscillators are combined using the NAND gate N6 of CD4011 (IC2) and inverted by gate N7, one gets a modulated output of high and low frequencies. Such an excitation of the discharge tube has been found to be very efficient and less heat-producing as compared to a plain high-frequency or a plain low-frequency excitation.

The output pulse train from pin 11 of the CD4011 gate N7, which is of the same polarity after the second inversion (first inversion takes place in gate N6), is sent through the pair of complementary transistors T1 and T2 (2N2222 and 2N2907, respectively). These two buffer the signal for giving adequate charging current to drive the gate capacitance of

MOSFETs during the leading edges of the square wave.

The 15-ohm resistor R11 and switching diode D9 (1N914) are needed to prevent any negative signal input of the power MOSFET IRF840 gate. The power MOSFET is a boon to switch-mode circuit operation. It looks like the 5V regulator 7805 in TO-220 package, with which everyone is familiar. It needs a small aluminium heat-sink

The drain of the MOSFET is connected in series with a 33-ohm, 10-watt wirewound resistor (replaced by EFY Lab with 2 x 47-ohm, 10W resistors R13 and R14, in parallel). It is then connected to EHT primary winding of the ferrite core line output transformer (LOT)-also referred to as EHT transformer. Switching diode BA159 is also placed in series with the primary, as shown in Fig. 2. The supply is the rectified DC voltage, which is derived from the mains voltage directly. (During testing at EFY Lab, the mains voltage was stepped down to 120V AC as mentioned earlier.) An RC series network comprising 33kpF (3000V rating) capacitor C8 and 100-ohm (10W) resistor R12 is placed across drain-source terminal of the MOSFET. The source terminal of the MOSFET is directly grounded.

Low-voltage supply. The ICs 4069 and 4011, and transistors T1 and T2, require a low voltage of around 12V. A separate 12V, 250mA transformer could also be used with a rectifier bridge and filter capacitor to derive the necessary voltage. But, in this compact design, the same is derived from mains using a capacitor and diode pair. The mains supply, through the series limiting resistor of 82-ohm, 1W (replaced at EFY Lab, with a 10-kilo-ohm, 10W resistor R8) sends a current via 0.47uF, 400V polyester capacitor (replaced at EFY Lab with two such capacitors C4 and C5 in parallel) and diode D8 to charge 100uF capacitor C6 during positive half cycle. Zener diode D7, with a breakdown voltage of 12V, limits the voltage across capacitor C6 to 12V. Diode D6 provides an easy path during negative half cycle of the AC input. The stable 12V DC supply developed across capacitor C6 is used for the ICs and transistors 2N2222 and 2N2907.

Ferrite-core transformer. The ferrite core transformer used here is the commonly available B&W television transformer, known as LOT (line output transformer). AT2070 type used in the

circuit has a high-voltage winding for the EHT of the picture tube. This EHT is connected to the electrode (aluminium foil) of the ozone discharge tube.

The LOT used should be two-limb type, i.e, the low-voltage windings should be on the left limb of the ferrite core, and the EHT winding (primary and secondary), which is generally epoxy potted, on the right limb. The LOT should have an external EHT diode and not an internally wired EHT diode, as is common in colour television LOTs. The reason being that only AC voltage is needed here.

Further, it is necessary to remove any coupling between the two limbs, which may be present in the LOT windings. A connection from the left limb to the right limb is used to increase the mutual coupling. In the circuit presented here that coupling leads to over-currents in the event of any discharge tube sparking, thereby damaging the IRF840 instantly. It is therefore necessary to cut off the connection linking the two limb windings before installation. Preferably, a 1,00-ohm, 2#W resistor may be wired in the place of this cut, if an improved performance of ozone generation is desired.

Lab. note. During testing of EFY Lab, transformer stamped as LOT 2070 obtained from the market was found to be single limbed and could generate about 34kV peak voltage at 120V AC input. Therefore a double-limbed Leader brand transformer 2095 was procured and used after removal of the encased TV20 rectifier diode, in a manner exactly as described by the authors. This transformer could produce about 30kV peak with AC input of 120V. The corona discharge across EHT secondary was prominent with an air-gap of up to 125 cm. At only 80V AC input to the circuit, 100pA space current was measured using the metering circuit described below.

The metering circuit (Fig. 5). This employs a simple low-cost 100uA meter used as VU-meter in audio amplifiers and is freely available. Either the edge-mounting type or the plain type may be used. It has a clear front plastic case of 25 sq. cm which is easily mounted on the front side of the plastic box, with a suitable

 


Fig. 6: LED indicator circuit

small cut made in the box with drill and fret saw.

The meter has a top which can be easily removed and replaced, as it is snug fit. Removal of the meter top exposes the meter scale, which can be redrawn in per cent of 0-1 gm/hour O3.

The meter shows the discharge current through the ozone-generating tube. The earth side of the discharge tube (aluminium tube) is connected through a 1-kilo-ohm, 1W resistor to ground. The EHT wire is connected to the electrode (aluminium foil) on top of the glass tube. The 1-kilo-ohm resistor develops a voltage in approximate proportion to the ozone that would have been generated. A series combination of 4.7-kilo-ohm resistor and a diode (1N4001) supply current to the meter coil.

LED indicator (Fig. 6). The indicator LED on panel gets its current through a single turn wound on the top limb of the ferrite transformer. The current is rectified by a 1N4003 diode and filtered by a 10uF, 16V capacitor which supplies the current through 1-kilo-ohm series resistor to the LED. The glowing of the LED indicates that the circuit is working.

Lab. Note: At EFY Lab, about eight turns of insulated wire around top limb of LOT were used.

AC input. The AC mains supply is at 230V AC and has a fuse of 500 mA in series. A switch can be wired in series with the same, though the same is not shown in the circuit here. (Please note that at EFY, 12V AC input was used as mentioned earlier.)

Testing

Prior to operation of the circuit board for ozone generation, it is required to test the circuit properly. This can be done as follows:

1. The low-voltage pulse generation part has to be tested first. For this, in place of the mains-derived 12-volt supply, a separate 12V supply, derived using an external 12-0-12 volts, 1-amp transformer, and a 7812 voltage regulator, can be used. The two oscillators should have frequencies in the specified range and the presets should be able to adjust them over the range mentioned. Otherwise, slight alteration of resistor values may be needed. The 3300pF capacitor used should be of good ceramic or polyester type, with a rating of 100V or more.

PARTS LIST

<i>Semiconductors:</i>	
IC1 (N1-N5)	- CD4069 hex inverter
IC2 (N6-N7)	- CD4011 quad 2-input Nand gate
T1	- 2N2222 np transistor
T2	- 2N2907 pnp transistor
T3	- IRF840 n-channel MOSFET
D1-D4, D9	- 1N914 detector diode
D5-D6, D8, D11	- 1N4007 rectifier diode
D10	- BA159 switching diode
D7	- 12V, 1W zener
D12	- 1N4001 rectifier diode
D13	- Green LED
<i>Resistors (all 1/4-watt, +- 5% carbon, unless stated otherwise):</i>	
R1, R4	- 100-kilo-ohm
R2, R6, R10	- 10-kilo-ohm
R3	- 110-ohm
R5, R15, R17	- 1-kilo-ohm
R7	- 2.2-ohm, 10 watt fusible resistor
R8	- 10-kilo-ohm, 10-watt
R9	- 6.8-kilo-ohm
R11	- 15-ohm
R12	- 100-ohm, 10-watt
R13, R14	- 47-ohm, 10-watt fusible resistor
R16	- 4.7-kilo-ohm
VR1	- 10-kilo-ohm preset
VR2	- 1-kilo-ohm preset
VR3	- 1-kilo-ohm potmeter
<i>Capacitors:</i>	
C1	- 3300pF ceramic disk
C2, C7	- 0.1uF ceramic disk
C3	- 100p, 400V electrolytic
C4, C5	- 0.47uF, 400V polyester
C6	- 100uF, 35V electrolytic
C8	- 3.3 kpF, 300V polyester/mica
C9	- 10u, 16V electrolytic
<i>Miscellaneous:</i>	
X1	- LOT 2070 EHT transformer (without EHT diode) or Leader brand LOT 2095 (diode to be removed)
	- Al tube, length=20cm, diameter=1cm
	- Glass tube, length = 17cm, diameter=1.2cm
	- HT electrode
	- Aluminium full
	- M-seal, small packet
	- Teflon tape, two rolls
	- Cork, two numbers
	- VU meter
	- Short glass tube
	- 1.5cm length, dia=5 mm, 2 numbers
	- Flexible polythene pipe 5mm diameter, one metre length
	- Aquarium pump
F1	- Fuse, 500mA : DC IN socket

2. Then, using a CRO, the pulse train should be observed at the junction of two bipolar transistors. Next, MOSFET IRF 840 is connected in the circuit.

3. Now apply 12V supply to the end

of the LOT winding, in place of the mains rectified 200V DC, as shown in Fig. 2. For testing, one is not required to use 230V directly at all. The same in Fig. 2. For testing, one is not required to use 230V directly at all. The same 12V, or the unregulated 12V prior to the 7812 regulator, can be connected. In Fig. 2, the BA159 anode is shown connected to the mains rectified supply at the positive terminal of the 100uF, 400V electrolytic capacitor. But, for the present, connect the unregulated 12V (may be 16V or slightly more) to the circuit at the anode of BA159.

4. After switching 'on' the supply, observe the voltage on the EHT winding, which comes from the LOT, on a DC multimeter kept at its maximum range (say, 500 or 1,000V DC). The meter should show a deflection of above 500V.

5. The presets in the circuit can be adjusted to tune the ferrite transformer, for this voltage to be a maximum. Then, adjust the 1-kilo-ohm potentiometer VR3 so that it shows the possibility of varying the voltage over a limited range, above a threshold value.

6. Now, the 12V transformer supply can be disconnected. The 12V low-voltage generation part has to be separately tested. For this, remove the connection to the LOT from the MOSFET. Also remove the CMOS ICs from sockets. Then, on the PCB, one can easily check for zener voltage of 12V. If this voltage is less than 12 volts, adjust the value of 82-ohm series resistor to a lesser value, say, 68-ohm.

Lab. note. At EFY, this part of the circuit has been modified, and it is possible to get correct 12V output at AC input voltage of 120 volts. Only the modified circuit is included in Fig. 2.

The circuit will ordinarily work even at 200-volt mains, but not below that. The mains input can go up to 240V, but not more.

Lab note. During testing it was observed that fusible resistors R13 and

R14, rated 10W, got red-hot if voltage was increased beyond 160 V AC.

Construction of the discharge tube (Fig. 7). A simple method for constructing the discharge tube is presented here, which is suitable for any hobbyist. An aluminium tube of 20cm length and about 1cm diameter is taken. Antenna scrap tube can be used, provided the same does not have kinks, bends, or burrs. Fig. 7 shows the construction of the discharge tube. This aluminium tube is blocked on the inside with a small amount of M-seal compound, so that no air can pass directly through its middle hole.

M-seal comes in a pack of two parts. The sealing compound is prepared as and when required, by taking equal quantities of the two and mixing them together thoroughly. One of the compounds is black and the other is of cream colour. The two are taken, each about 1 cc, and then mixed well. This mixture is inserted into the tube with a pencil and spread to attach to the inside wall of the aluminium tube, blocking any air path. Then, two side holes of 2mm diameter are made on the tube at the two ends, about 33 cm from each end. These holes can be on the opposite faces of the aluminium tube.

To provide the discharge gap, a thinwalled glass tube, commonly used as chemistry test tube, is required. It should have an inner diameter about 1.2-1.5 mm greater than that of the aluminium tube, i.e., if a 10mm outer dia aluminium tube is taken, a glass tube of 11.5 mm inner diameter should be used. This will ensure the best performance with an air gap of 0.75 mm all around. If the gap is 0.6 mm, it is still better, but then the metal tube should be extremely perfect.

The glass tube is cut such that it covers the length of the aluminium tube, except for about 1.5 cm at each end. Thus if a 20cm long aluminium tube is taken, the glass tube will be 17 cm long. The metal tube should be able to go freely in it. Now, the glass tube may be

rotated over a gas burner to soften the ends of the tube. It should now be made chamfered on to the metal tube, such that, at the edges, the glass tube fits the metal tube with no gap. Still, the glass tube should be able to slide over the aluminium tube.

After the glass tube is so positioned over the metal tube, the ends of the glass tube are taped using Teflon tape. The tube assembly, with the glass envelope taped, is held at its edge, leaving about 15 cm free at either end, and clamped to the wall of the plastic box, as shown in Fig. 8. Clamps meant for TV antennae, which are made of plastic mouldings, can be used for this purpose.

Preparation of the hot electrode. The hot electrode, to which a voltage greater than 6,000 volts is applied at high frequency, is made by closely wrapping plain aluminium foil around the outer side of the glass tube. The foil is wrapped leaving 1 cm uncovered area on either ends of the tube. The foil is to be taped for tightness on the outer glass, using cellulose tape, and a piece of Teflon-insulated wire connected to the aluminium foil brought out. This wire is connected to the EHT lead from the LOT on the circuit board.

Assembling the unit. The unit is easy to assemble. First, the circuit board is fixed on the bottom of the box with plastic bushes and screws. If screws are not needed externally, the bushes can be pasted on to the box. Then, clamps are fixed for discharge tube. Polythene tubes (transparent plastic) are fitted to the glass tube ends.

At the bottom of box, the air pump, with its outer plastic casing removed, is fixed to the bottom with a screw. The inside of the diaphragm pump is shown in Fig. 8. The casing of the pump is not needed for two reasons: to save space needed for fixing it within the bread box, and the vibrator part is now accessible.

A small plastic sheet is fixed by applying glue (Araldite) to the vibrating armature, so that it serves as a simple fan for the inside. The mains supply is connected to the PCB in parallel with the supply to the air-pump.

 


Fig. 7: Construction details of discharge tube

But now this connection is removed and only the pump is made to work.

The end of the aquarium air-pump, which produces air under pressure, is connected by a s short length of tube to the corked glass tube of the discharge tube assembly. The other end of the tube is fixed to another similar polythene tube of adequate length (say, one metre).

Now, after allowing the air-pump to work, one must check whether there is adequate draft of air through the tube connected to the air-pump, without any leakage. Any air leakage prior to tube entry or through the Teflon tape seals, or through the inner metal tube, can be easily detected with figers or soap bubble test. The leaks have to be plugged and all air that comes out of the pump should go through the annular gap of the discharge path and exit through the out-let tube.

After this check, the meter connection is made from the board's 1-kilo-ohm shunt discharge resistor R15, with series diode D11 and current limiting resistor R16. The meter is fixed, as stated earlier, to the from small edge of the box, which also accommodates the LED and ozone output control potmeter. The LED is wired along with diode D12, resistor R17, and capacitor C9 as shown in Fig. 6.

The lid, on the outside, may be pasted with the warnign label: "DANGER—DO NOT OPEN WHEN IN USE".

After the whole assembly is checked and mains supply is given, one can watch the meter reading and green LED on the panel. The glowing LED indicates that the circuit, along with LOT, is working and the meter shows that the there is a discharge. The sound of the air-pump will be heard of course, but one can also hear the hissing corona sound distinctly. If lights are 'off', a blue glow may also be seen on watching from the end of the glass. A smell like that of rotten fish from the tube indicates presence of ozone. The meter reading needs calibration now.

Calibration

There are two ways ot do the calibration. One is by using an ozone gas analyser, which is an expensive instrument. So, the other method, which is economical, is described here.

Potassium iodide (KI) solution is converted to iodine gas by ozone. Taken a

known quantity of KI solution and bubble the ozonated air from ozone generator through it, for a definite time (one minute). The free liberated iodine can be estimated by titration experiment with thiosulphate. Thus, by knowing how much iodine has been liberated, one can find how much ozone has been absorbed in the solution by quantitative analysis. This gives the gas output form the tube in mg/litre. The gas output can be foud by finding the time taken to replace the 1 litre of water by the bubbling gas. After estimating the output of the unit, marks are made on the meter. This is a prototype marking which can be followed in other units of similar design.

Usage

The unit can be used where a 230V AC mains supply outlet is available. The ozone generated can be let into air or bubbled through the solution or water being treated using ceramic diffusers (available from aquarium equipment shops). The time rating of this unit is very short. Since there is no fan employed for cooling, both the discharge tube and circuit board transistor may quickly heat up The tested rating at ambient temperature of 25o Cis 5 minutes.. This tim is sufficient for all the applications described below.

Lab note: The circuit could be continuously kept 'on' with reduced AC in-

put of 120V AC after changing some of the component values, including LOT, at EFY Lab. The changed components/ values have been incorporated into the final circuit shown in Fig. 2. Since higher AC voltage (greater than 20 kV) was available, we could increase the separation between the aluminium and glass tubes appreciably.

1. Water disinfection. The impure water can be disinfected by bubbling ozone through it for a time so that estimated 4 mg/litre is dissolved.

2. Air purification. You can purify the air of your room by letting out ozonated air upward into it for five minutes, with a fan running.

3. Mosquito repulsion. Same as above, but please shut the windows soon after switching 'off' the ozone generator. This operation is to be done in he morning to drive away the mosquitoes and in the early evening at around 5 pm to prevent them from coming in. The operation may be repeated at midnight when malaria mosquitoes normally attack.

4. Bleaching. The stains of ink on clothes can be bleached by applying ozone gas. On bubbling ozone into the diluted ink contained in a test tube, the water becomes clear within a short time.

5. Pollutant treatment. Ozone in large quantities can be used for treating polluted water in industry, along with bacterial treatment. The BOD (biological oxygen demand) can be brought down to 30 with ozone only.

6. Mouth washing. You may ozonate 200 cc of water and use it for gargling.

7. Vegetable clean. Only ozonated water should be used for cleaning vegetables like cabbage, tomatoes, and carrot. Chlorinated water is harmful.

8. Skin wound healing. An exposure to the ozone gas quickly heals skin wounds and rashes. You may apply ozonated olive oil to speed up healing.

There are may other uses of ozone which one can try. The gas should not, however, be inhaled directly, continuously. □

 


Fig. 8: Photograph of author's prototype

CONFERENCE TIMER

K. UDHAYA KUMARAN VU3GTH

During a conference where speakers are allotted different time slots for completing their speech, it is essential to use a suitable conference timer which could be programmed for the given time slot. It should not only provide indication as to when the allotted time slot. It should not only provide indication as to when the allotted time is over, but also about the leftover time at any given instant. The conference timer presented here is designed to incorporate all such facilities and is expected to prove quite useful.

This conference timer is just a 2-digit (minutes) countdown timer which can be preset from 01 minute to 99 minutes. The time duration is preset using

PARTS LIST

Semiconductors:

IC1, IC2	- CD4511B, BCD-to-7-segment latch/decoder/driver
IC3, IC4	- CD4510 BCD up/down counter
IC5	- 4060B 14-stage counter/divider/oscillator
T1-T4	- BC547 npn transistor
T5	- SL100 npn transistor
D1-D8	- 1N4007 rectifier diode
D9	- 5.1V zener
LED1	- Red LED
DIS1, DIS2	- LTS543 common-cathode display

Resistors (all 1/4-watt, +5% carbon, unless stated otherwise):

R1-R14	- 470-ohm
R16-R18	- 100-kilo-ohm
R24, R28, R31	- 100 ohm
R19	- 100 ohm
R20, R27	- 33-kilo-ohm
R22, R23	- 10-kilo-ohm
R25, R30	- 22-kilo-ohm
R29	- 22-kilo-ohm
R26	- 470-ohm
VR1	- 50-kilo-ohm preset
VR2	- 1-mega-ohm preset

Capacitors:

C1	- 180pF ceramic disk
C2	- 47pF, 25V electrolytic
C3	- 001uF ceramic disk
C4	- 0047uF ceramic disk

Miscellaneous:

RL1	- Relay 6G, 100-ohm
S1	- DPDT slide switch
S2, S3	- Tactile switch
S4	- SPDT slide switch
PB	- Piezo buzzer

tactile switches S2 and S3, with slide switch S1 in 'set' position. Once the time duration is preset, the same is displayed in 7-segment LED displays (DIS.1 and DIS.2).

As soon as the designated speaker starts speaking, switch S1 is flipped from 'set' position to 'start' position. The displayed time will start decrementing once a minute until it becomes 00, i.e

the unit digit (DIS.1) and tens digit (DIS.2) both become zero. At this juncture, the timer stops decrementing further and an interrupted beep sound is heard from the buzzer, indicating that the time allotted to the particular speaker is over.

In this circuit, IC5 (CD4060B, a 14-stage binary counter with internal oscillator) is used for generation of the basic timing pulses. Presets VR1 and VR2 are required to be adjusted for obtaining approximately 1 Hz (1.0666 Hz, to be more precise) pulses from pin 7 (Q4) of IC5, while the pulses from pin 15 (Q10) are available at the rate of one pulse per minute. For countdown timer

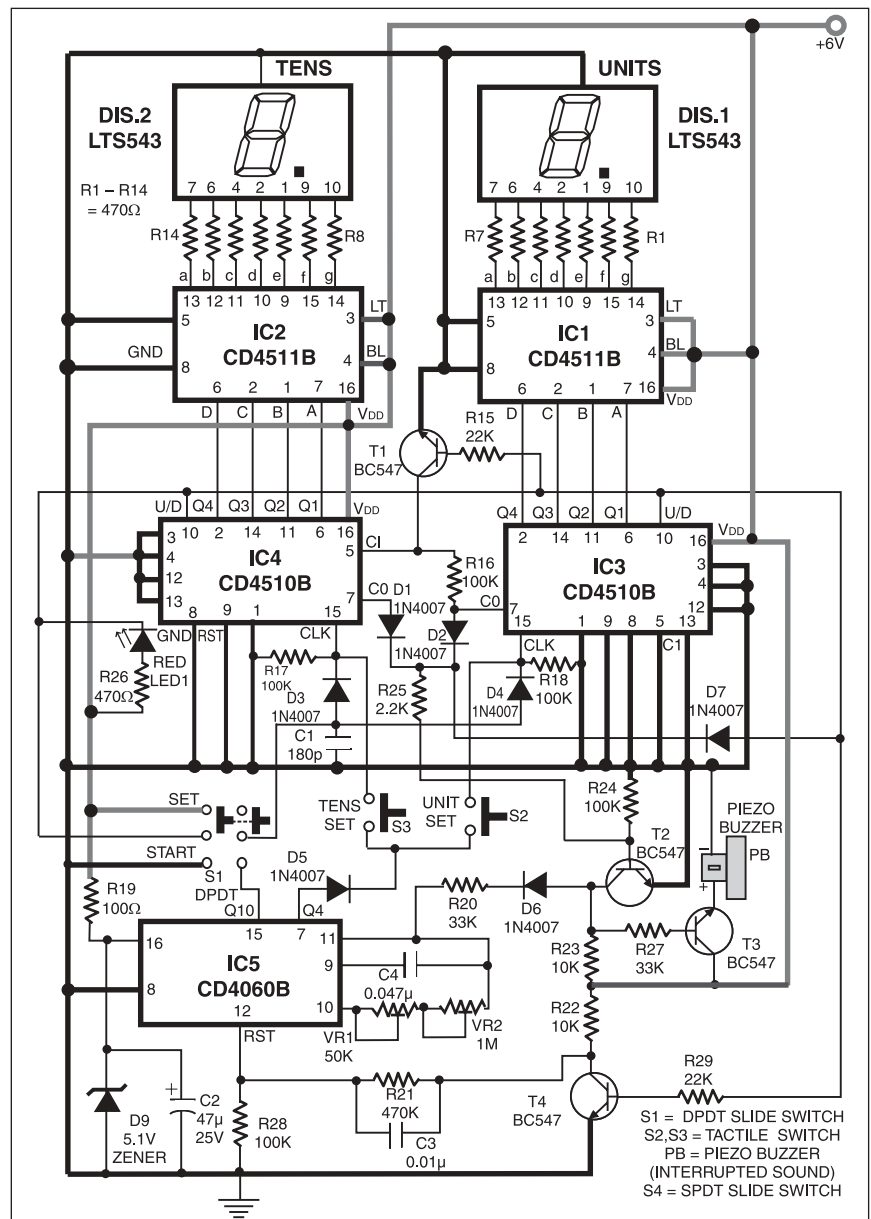


Fig. 1: Circuit diagram of conference timer

 


Fig. 2: Appliance 'on/off' switching application for timer

(CD4510B). They convert the BCD code to 7-segment positive logic output code to display the equivalent decimal digits. While displaying decimal digits 9 and 6, their tails are not displayed. The store function available in these ICs is not used in this circuit and hence the store pin 5 of IC1 and IC2 is made permanently low.

ference timer while its down counting mode is used for normal timer operation.

When presetting, the carry 'pout' pin 7 of IC3 and carry 'in' pin 5 of IC4 are not cascaded, to permit presetting of tens and units digits independently (using push-to-on tactile switches S2 and S3, respectively). In countdown mode carry 'out' pin 7 of IC3 and carry 'in' pin 5 of IC4 are cascaded for 2-digit countdown timer operation. For presetting function, 1Hz (approx.) pulses

are used, while for normal cascaded countdown operation of the timer, pulse rate of one-pulse-per-minute is used. As stated earlier, these two types of pulses are available from pins 7 and 15, respectively, of IC5.

Transistor T2 is used to stop or activate the IC5 binary counter. When transistor T2 is in 'cut-off' state, its collector voltage goes 'high'. As a result, the positive supply rail is extended to pin 11 of IC5 via resistor R23 and diode D6 to stop IC5 from counting further. When transistor T2 conducts, its collector voltage goes low and counter IC5 becomes active. The stop and run functions of IC5 binary counter are used during countdown operation only. While presetting, the IC4 binary counter will be in running condition.

When slide switch S1 is slid to 'set' position, pin 10 of both IC3 and IC4 is taken 'high' to select the countup mode for presetting timer. As the same time, transistor T12 gets forward biased and conducts. As a result, its collector as well as pin 5 of IC4 go 'low'. Pin 5 of IC3 is permanently low and both these ICs are not cascaded. The one-pulse-per-minute

(from pin 15 of IC5) is no longer available to diode D3-D4 junction, while 1Hz pulse (available from pin 7 of IC5) may be applied to the clock input in 15 of IC3 or IC4 by pressing the respective tactile switches S2 and S3. For presetting the timer, depress tactile switch S2 and S3 until desired count is displayed in unit and tens digit (DIS.1 and DIS.2). When desired digit has been displayed in DIS.1 or DIS.2, immediately release switch S2 and S3, as the case

 


Fig. 3: Actual-size, single-sided PCB layout

 


Fig. 4: Component layout for the PCB

operation, this pulse (one-per-minute) is simultaneously applied to pin 15 of IC3 and IC4 through switch S1 (in start position), and diodes D3 and D4. For presetting this timer, bounceless pulses are required at clock pin 15 of both IC3 and IC4. For this reason 1Hz (bounceless) pulses available from pin 7 of IC5 are used to preset the timer.

IC1 and IC2 (CD4511B), 7-segment latch and driver, accept BCD input code from up/down counters IC3 and IC4

CD4510B is a divided-by-10 BCD up/down counter. This counter increments or decrements by one count for every low-to-high transition of the clock pulse applied to its clock pin 15, depending on the logic level at its pin 10. Thus, when pin 10 of IC3 and IC4 are held high, the counters increment by one count for every clock pulse, and when they are held low, the counters decrement by one count for every clock pulse. The up counting mode is used to preset the

may be. Due to conduction of diode D7, transistor T2 will be 'on' state and thus binary counter (IC5) is in running condition. At the same time, 'auto reset' transistor T4 will also be in 'on' state, with its collector pulled low. Thus, IC5 will continue to operate normally.

When slide switch S1 is slid from 'set' position to 'start' position, the red LED1 immediately glows. Transistor T4 goes to 'cut-off' and its collector transits from 'low' to 'high' state. The high-going spike is coupled through capacitor C3 to reset pin 12 of IC5. Thus, IC5 is reset and starts counting from beginning. During this operation, pin 10 of both IC3 and IC4 are held low to select countdown mode of operation. Transistor T1 goes to 'cut-off' state. Thus carry 'out' pin 7 of IC3 and carry 'in' pin 5 of IC4 are cascaded through resistor R16. The one-pulse-per-minute is applied to

pin 15 of both ICs (IC3 and IC4) through diodes D3 and D4. Now the digits displayed in DIS.1-DIS.2 combination start decrementing once every minute. When digits displayed in DIS.1-DIS.2 become '00', carry 'out' pin 7 of both IC3 and IC4 goes 'low' and transistor T2 does not conduct. As a result, collector of transistor T2 goes 'high' and the binary counter stops counting. Simultaneously, transistor T3 conducts and activates the buzzer (functioning in interrupted mode). Thus, interrupted beep sound is heard from the buzzer, indicating that preset time duration has ended. Pin 7 of both IC3 and IC4 goes 'low' during display of digits '00' in DIS.1 and DIS.2. During display of any digits other than '00', the carry 'out' pin 7 of either IC3 or IC4 will be high or both may be 'high'. When the timer is in countdown mode, do not press switch S2 or S3 to avoid

disturbance in timer setting.

This circuit, apart from using as a conference timer, may be converted into programmable 2-digit 'on' or 'off' timer to switch 'on/off' any electrical or electronic appliance after 1 minute to 99 minutes duration by incorporating additional add-on circuit shown in Fig.2. During 'on/off' timer operation, the digits displayed in DIS.1-DIS.2 help one to know the exact leftover time to switch 'on' 'off' the appliance. When using this circuit as 'off' timer, slide switch S4 to 'off' position and, for 'on' timer operation, slide switch S4 to 'on' position. When displayed digits become '00', the relay will be energised to turn 'on/off' the load.

The actual-size, single-sided PCB for the circuit in Fig.1 is shown in Fig. 3, while its component layout is given in Fig. 4. □

ADD-ON STEREO CHANNEL SELECTOR



PRABHASH K.P.

The add-on circuit presented here is useful for stereo systems. This circuit has provision for connecting stereo outputs from four different sources/channels as inputs and only one of them is selected/ connected to the output at any one time.

When power supply is turned 'on', channel A (A2 and A1) is selected. If no audio is present in channel A, the circuit waits for some time and then selects the next channel (channel B). This search operation continues until it detects audio signal in one of the channels. The inter-channel wait or delay time can be adjusted with the help of preset VR1. If still longer time is needed, one may replace capacitor C1 with a capacitor of higher value.

Suppose channel A is connected to a tape recorder and channel B is connected to a radio receiver. If initially


channel A is selected, the audio from the tape recorder will be present at the output. After the tape is played completely, or if there is sufficient pause between consecutive recordings, the circuit automatically switches over to the output from the radio receiver. To manually skip over from one (selected) active channel, simply push the skip switch (S1) momentarily once or more, until the desired channel inputs gets selected. The selected channel (A, B, C, or D) is indicated by the glowing of corresponding LED (LED11, LED12, LED13, or LED14 respectively).

IC CD4066 contains four analogue switches. These switches are connected to four separate channels. For stereo operation, two similar CD4066 ICs are used as shown in the circuit. These analogue switches are controlled by IC CD4017 outputs. CD4017 is a 10-bit ring

counter IC. Since only one of its outputs is high at any instant, only one switch will be closed at a time. IC CD4017 is configured as a 4-bit ring counter by connecting the fifth output Q4 (pin 10) to the reset pin. Capacitor C5 in conjunction with resistor R6 forms a power-on-reset circuit for IC2, so that on initial switching 'on' of the power supply, output Q0 (pin 3) is always 'high'. The clock signal to CD4017 is provided by IC1 (NE555) which acts as an astable multivibrator when transistor T1 is in cut-off state.

IC5 (KA2281) is used here for not only indicating the audio levels of the selected stereo channel, but also for forward biasing transistor T1. As soon as a specific threshold audio level is detected in a selected channel, pin 7 and/or pin 10 of IC5 goes 'low'. This low level is coupled to the base of transistor T1, through diode-resistor combination of D2-R1/D3-R22. As a result, transistor T1 conducts and causes output of IC1 to remain 'low' (disabled) as long as the selected channel output exceeds the preset audio threshold level.

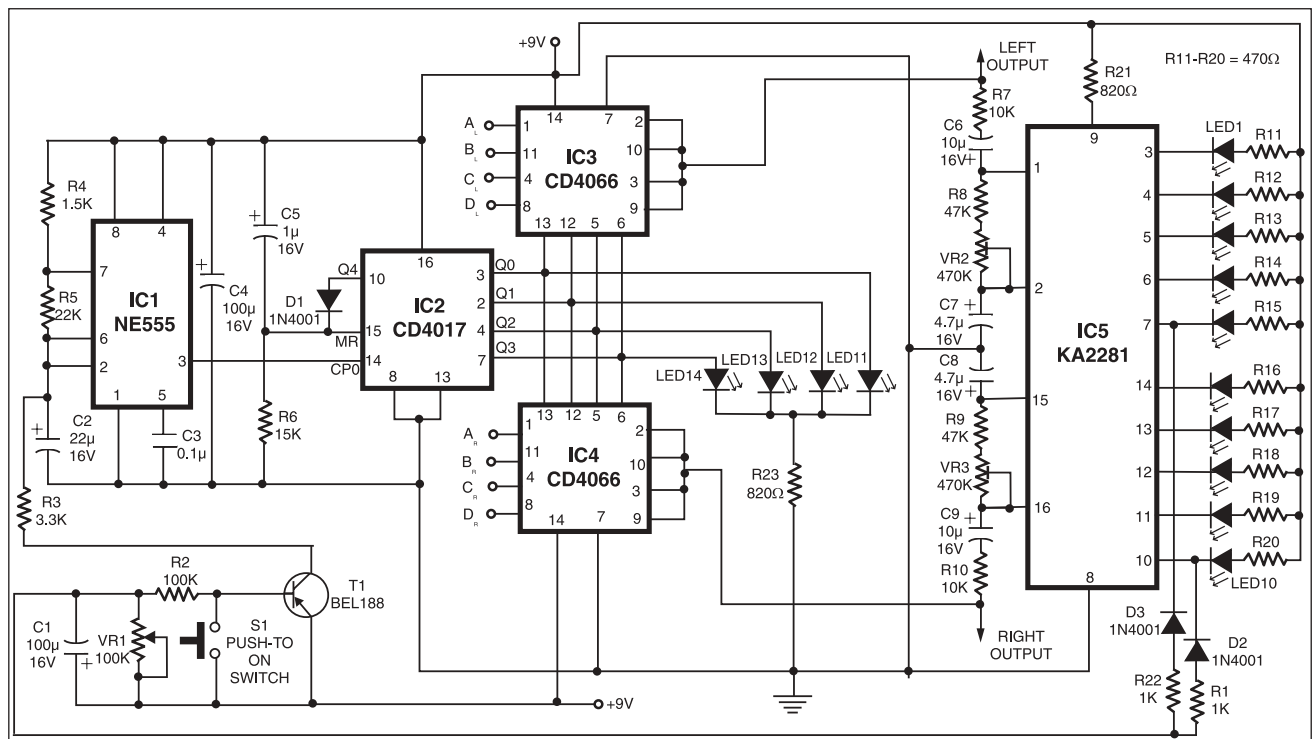Presets VR2 and VR3 have been included for adjustment of individual audio threshold levels of left stereo channels, as desired. Once the multivibrator action of IC1 is disabled, output of IC2 does not change further. Hence, search-



ing through the channels continues until it receives an audio signal exceeding the preset threshold value. The skip

switch S1 is used to skip a channel even if audio is present in the selected channel. The number of channels can be eas-

ily extended up to ten, by using additional 4066 ICs.

WATER TEMPERATURE CONTROLLER




VIJAY D. SATHE

The circuit presented here controls the temperature of water as well as indicates it on an LED

bargraph. When the temperature of water is 0o C, none of the bargraph display LEDs glows. But as the tempera-

ture starts increasing above approximately 30o C, LEDs from LED1 through LED8 of the bargraph start glowing one after the other. When temperature is around 30oC, only LED1 would be 'on'. For temperature greater than 97dig C, all display LEDs will be 'on'.

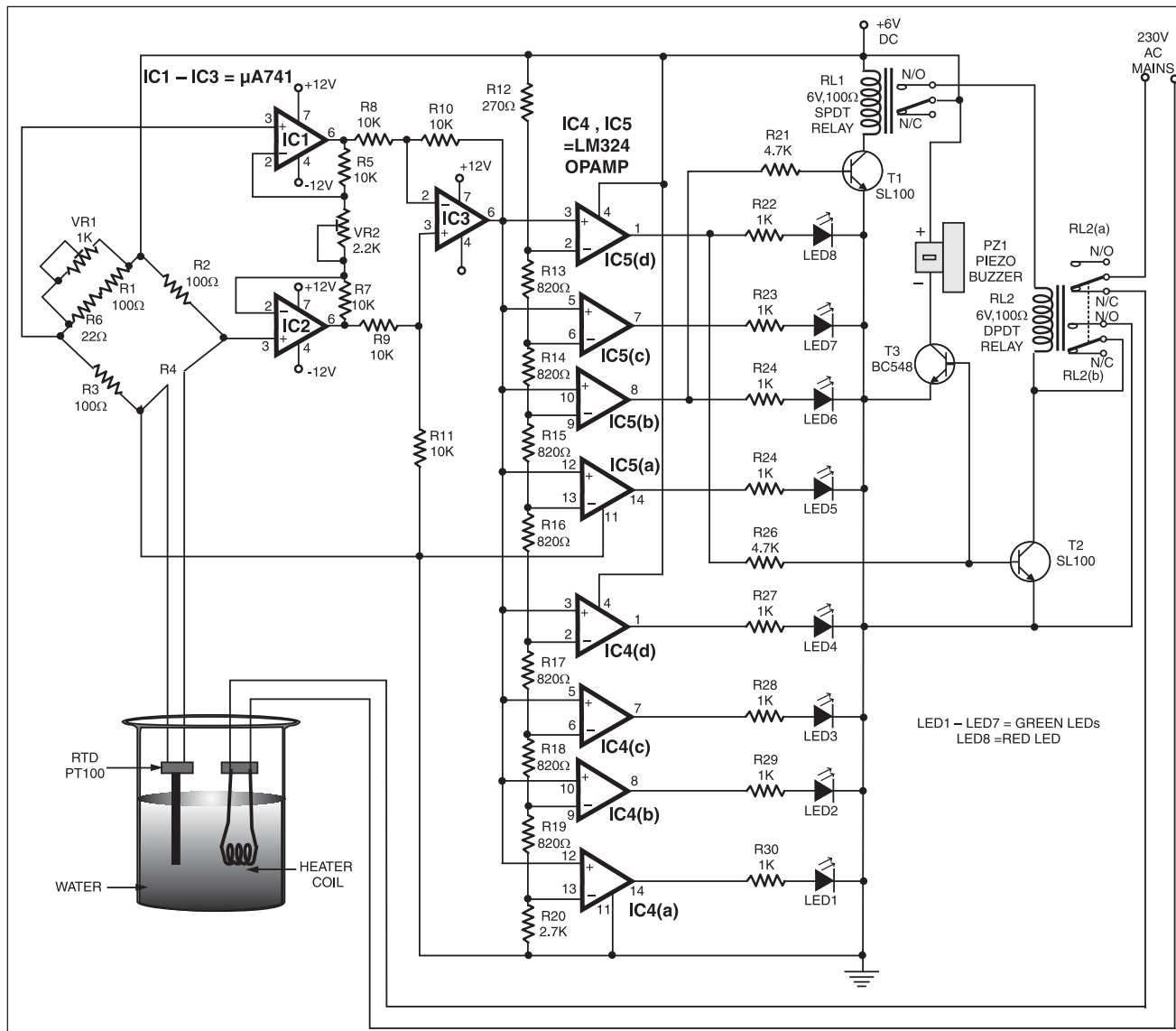To detect the temperature of water, commonly used resistance-temperature detector (RTD) PT100 is used. It is connected to one of the arms of a Wheatstone bridge as shown in the figure RTD PT100 has a resistance of 100 ohms



when surrounding temperature is 0dig C. (To cater to resistance tolerances and calibration, resistor R6 (22-ohm) and 1-kilo-ohm preset VR1 were added at EFY lab. During testing.) Ideally, at 0oC, the bridge has to be in balanced condition and, for other temperatures, the bridge will be unbalanced. The unbalanced voltage of the bridge is converted into suitable value in the range 0V to 5V (corresponding to temperatures 0oC to 100oC, respectively) by the instrumentation amplifier formed by op-amps IC1 through IC3 (uA741). Output of instrumentation amplifier is given to voltage compactors for driving the display LEDs.

Before using this circuit, the following adjustments have to be made. First, immerse the RTD in ice water (0oC) and adjust preset VR1 such that the bridge becomes balanced and the output of IC3 becomes)V. Next, immerse

the RTD in boiling water and slightly adjust preset VR2 such that the output of IC3 becomes 6V. Repeat the above two steps four to five times.

To control the temperature of water, 'on'/'off' type controller is used. Lower threshold point is set at 97oC. An electric heater coil is used for heating the water. When power supply is switched 'on', the heater starts heating the water. When temperature reaches 80oC, output of IC5(b) goes 'high'. This turns 'on' relay driver transistor T1 to energise relay RL1. In this state, relay RL2. Relay RL2 in energised state cuts off power supply to the heater coil. Relay RL2, once energised, remains so due to the latching arrangement provided by its second pair of contacts. Simultaneously, the buzzer also sounds, due to forward biasing of transistor T3.

Since the supply to the heater is cut-off, the temperature of water starts de-

creasing. Gradually, the buzzer goes 'off', as output of IC5(d) goes 'low'. When temperature goes below 80oC, output of IC5(b) goes 'low' to turn 'off' transistor T1 and relay RL1. As a result, the power supply provided to relay RL2 (via RL1 N/O contacts) is cut off and relay RL2 de-energises. This will again turn 'on' the mains electric power supply to the heater coil. Once again, the temperature of water starts increasing and the cycle repeats to maintain water temperature within the limits 80oC to 97oC.

This controller can be used to control the temperature of water in water heaters, boilers, etc. The lower and upper threshold points can be changed by connecting the base terminals of transistors T1 and T2 to different output terminals of voltage comparators (IC4 and IC5). Base terminals of transistors T1 and t2 are meant for lower and upper threshold points, respectively.

EMERGENCY LIGHT



RAJESH KAMBOJ

The circuit of emergency light presented here is unique in the sense that it is automatic, compact, reliable, low-cost, and easy to assemble for anyone. The circuit consists of four sections, namely, battery charging section, inverter section, changeover section, and low battery voltage indication section.

In the battery charging section, 230V AC mains is converted to 9V AC using step-down transformer X1. The diodes

D1 and D2 from a full-wave rectifier, and capacitor C1 filters the rectified voltage. The output of filter is about 12V DC, which is connected to the collector of transistor T1 provides a fixed bias of 8.2V. Thus, transistor T1 works as a regulator and provides a constant voltage for charging the lead-acid battery. LED1 indicates the charging of battery.

The inverter section comprises transformer X2, transistor T2, capaci-

tor C2 and resistor R3. Transformer X2 is ferrite core type. Its winding details are shown in Fig. 2. While core details are shown in Fig. 3. Resistor R3 provides DC bias to the base of transistor T2, while capacitor C2 couples the positive AC feed-back from winding L1 to the base of transistor T2 to sustain the oscillations. The AC power developed across primary winding L2 is transferred to secondary winding L3, which ultimately lights up the fluorescent tubes.

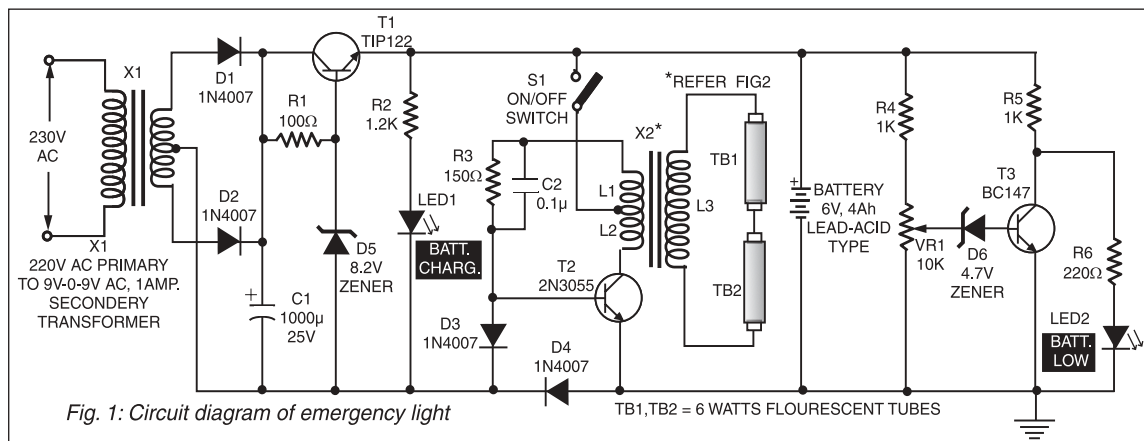


Fig. 1: Circuit diagram of emergency light

The changeover section uses diodes D3 and D4 as an automatic switch. In the presence of AC mains supply, diode D3 keeps transistor T2 in its cut-off state, while diode D4 pro-

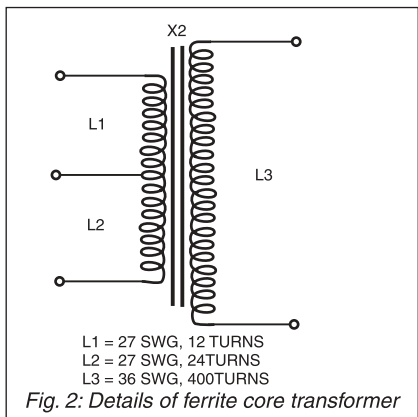


Fig. 2: Details of ferrite core transformer

vides DC path for charging of the battery. But, in the absence of AC mains

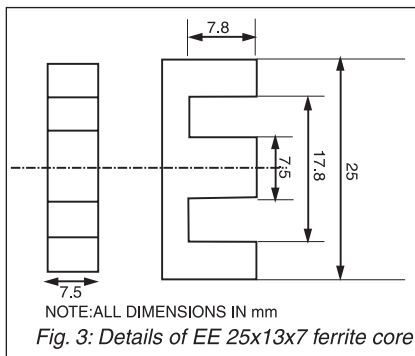


Fig. 3: Details of EE 25x13x7 ferrite core

supply, diode D4 is reverse biased and acts as an 'off' switch, inhibiting the conduction of diode D3, which allows normal functioning of transistor

T2. The inverter can be switched 'off', when not required, by using 'on/off' switch S1.

Low battery voltage indicator circuit comprises transistor T3, sensor diode D6, LED 2, variable resistor VR1, and resistors R4 through R6. The low battery indication can be adjusted from 4.7V to 5V by using variable resistor VR1. When the battery voltage is above 4.7V, zener diode D6 comes out of conduction, keeping transistor T3 at cut-off level. At the same time, LED2 gives the indication of low battery voltage.

The whole circuit can be assembled in a cabinet of emergency light suitably.

PARALLEL TELEPHONES WITH SECRECY



MANUJ PAUL

Often a need arises for connection of two telephone instruments in parallel to one line. But it creates quite a few problems in their proper performance, such as overloading and overhearing of the conversation by an undesired person. In order to eliminate all such problems and get a clear reception, a simple scheme is presented here (Fig. 1).

This system will enable the incoming ring to be heard at both the ends. The DPDT switch, installed with each

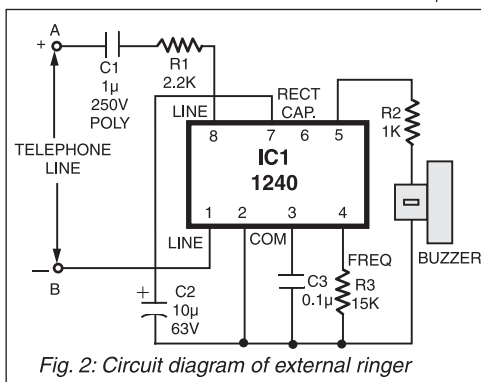


Fig. 2: Circuit diagram of external ringer

to the line.

To receive a call at an end where the instrument is not connected to the line, you just have to flip the toggle switch at your end to receive the call, and act as usual to have a conversation. As soon as the position of the toggle switch is changed, the line gets transferred to the other telephone instrument.

Mount one DPDT toggle switch, one telephone ringer, and one telephone terminal box on two wooden electrical switchboards, as shown in Fig. 3. Interconnect the boards using a 4-pair telephone cable as per

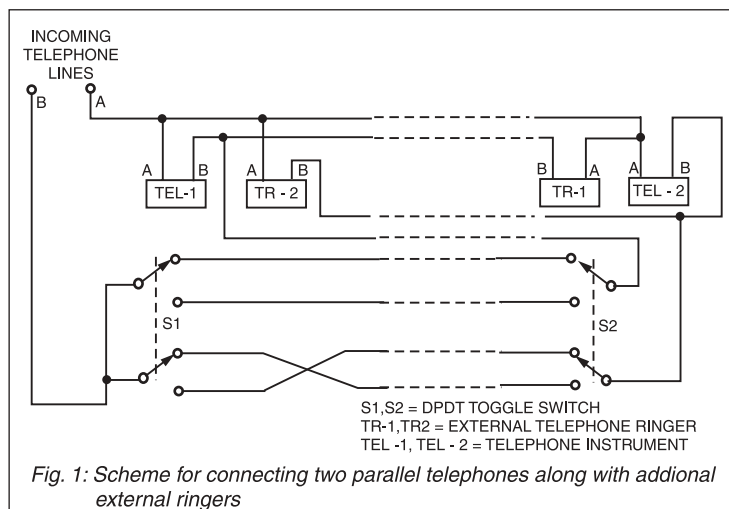


Fig. 1: Scheme for connecting two parallel telephones along with additional external ringers

of the parallel telephones, connects you to the line in one position of the switch and disconnects you in the other position of the switch. At any one time, only one telephone is connected

 


Fig. 3: Mounting details of DPDT switch, RINGER and telephone terminal box

Fig. 1. The system is ready to use. Ensure that the two lower leads of switch S2 are connected to switch S1 after reversal, as shown in the figure.

L a b .

Note: The external ringer for the project as shown in Fig. 2., was designed/fabricated at EFY Lab.

C.K. SUNITH


The circuit described here is different from conventional door bell circuits in the sense that it can produce two different tones—one of a lower frequency and the other of a much higher frequency.

The circuit uses a timer IC 555, which has been wired in free-running mode. When switch S1 is depressed, the circuit oscillates at around 1.5 kHz, resulting in a higher frequency note. When switch S2 is depressed, transistor T1 is turned 'on' and thus it shunts resistor R2 across capacitor C2. As a result, the circuit now oscillates at approximately 150 Hz and a tone of much lower frequency is generated.

The circuit can be conveniently employed as a doorbell for two separate doors at the same floor level. Doorbell switches S1 and S2 can be mounted



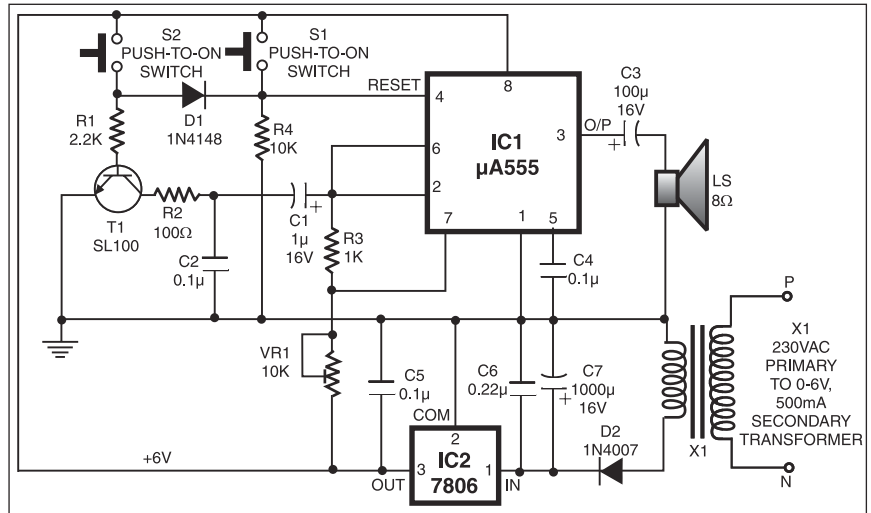a small cabinet. Tone can be adjusted with the help of preset VR1. Before power is switched 'on', it is advisable to adjust VR1 to approximately 5 kilo-ohm, that is, at the centre of the full



near the re-spective doors.

The circuit can be assembled on a general-purpose PCB and housed inside

range of potentiometer VR1. A trimpot can be used as VR1 for convenience of assembly.

PRADEEP G.




A major drawback of some pest repellors is that their power output is low and hence their effectiveness suffers. The pest repeller circuit described here generates powerful ultrasonic signals to repel pests. In addition to the ultrasonic frequency oscillator, separate push-pull power amplifier and transformer are used to boost ultrasonic signals.

Ultrasonic frequency oscillator is built around IC CD4047, which provides complementary outputs. These complementary outputs are amplified by transistors T1 and T2 (BD139) to drive transistorised push-pull power amplifier stage comprising power transistors T3 and T4 (2N3055).

The output of the power amplifier is coupled to a tweeter, through output

transformer X1. Transformer X1 is wound over ferrite core (UU or CC core). Primary winding consists of 150 turns of 28

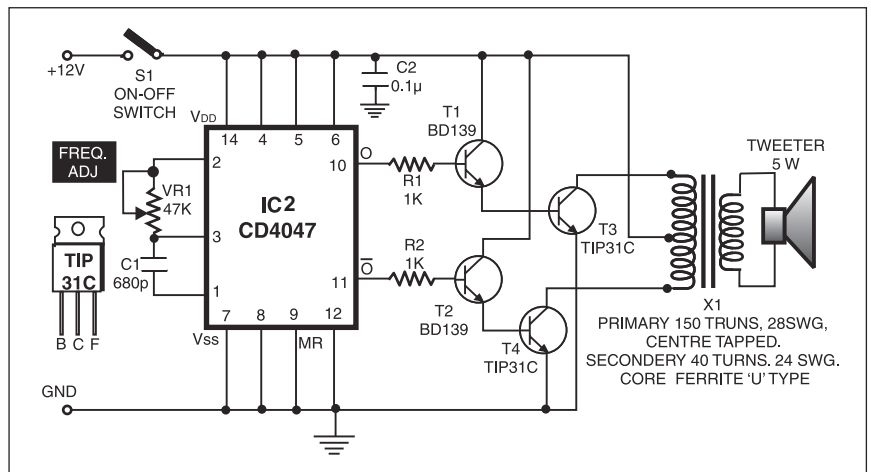SWG while secondary winding comprises 40 turns of 24 SWG wire. Adjust potentiometer VR1 for maximum effectiveness.



July

2000

BUILD YOUR OWN C-BAND SATELLITE TV RECEIVER



S. DAS GUPTA

Satellite TV reception has gained much popularity in India over the last three decades, specially after the live telecasting of the Gulf war by CNN. Both the S-band and C-band satellite signals are available to India. C-band signals are beamed from various satellites like Asiasat, Aralisat, and Insat 2B.

In India, the C-band reception is much more popular compared to the S-band. The popular satellite programmes which can be received on C-band include Star TV, Zee TV, PTV2, CNN, ATN, Sun TV, and Doordarshan. Besides, programmes from Russia, China, France, and Saudi Arabia are also available on C-band channels, although their language is a barrier.

Fundamentals of C-band reception

You are aware that to receive any satellite signals, a dish antenna is required. The mechanical aspects and the dish-orientation principles to receive satellite signals in S-band and C-band remain basically the same. The C-band downlink frequencies range from 3.7 GHz to 4.2 GHz. The direct reception system comprises:

- (i) Dish antenna
- (ii) LNB (low-noise block converter) and feed horn assembly.
- (iii) Satellite receiver.

Dish antenna: There are different types of dish antennae (e.g. fibre and mesh) available in various sizes ranging from 1.8 metres to 4.8 metres. The size of the dish is dependent on the size of the distribution network and the strength of the signal.

The area where the signal is weak requires a large dish, and vice-versa. The strength of the signal can also be recognised from the footprints of different satellites. As an example, the footprint (i.e. the geographic area on ground

covered by a satellite downlink antenna) measured in terms of effective isotropic

which supports the entire dish.

(b) The parabolic reflector.

(c) The electromechanical arrangement to move the dish in the horizontal and vertical planes to track the satellite. (This arrangement is generally used in a dish of 3.7 metre and above sizes.)

(d) LNB mounting arrangement.

Base structure should be strong enough to withstand the entire load of the dish. To withstand the wind load dur-

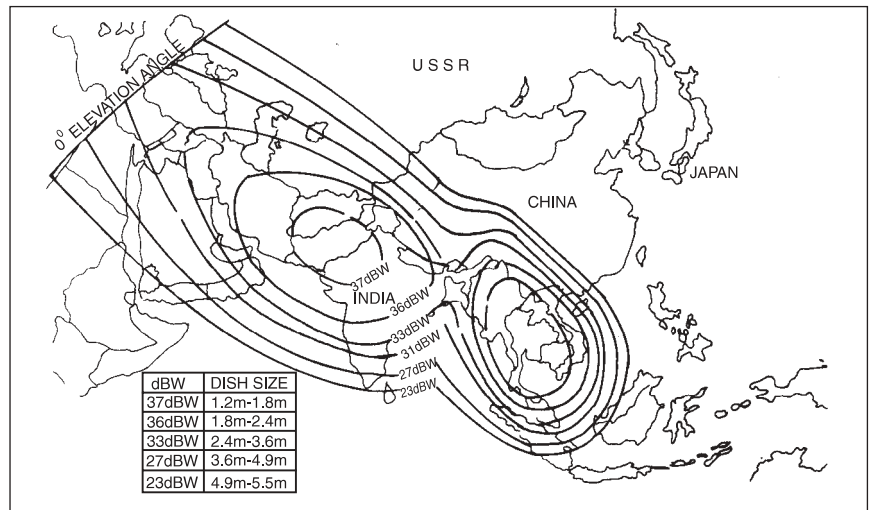


Fig. 1: Footprint of Star TV (Southern)

 


Fig. 2: Feed horn

radiated power (EIRP) in dBW (decibels w.r.t. one watt) of Asiasat satellite (transmitting Star TV programmes) over India is given in Fig.1. Star TV recommends the following sizes of dish antennae for various regions:

	Personal receiving system	Cable distribution system
Delhi	1.8 mtr	3.0 mtr
Mumbai	2.0 mtr	3.0 mtr
Calcutta	3.0 mtr	4.8 mtr
Chennai	3.7 mtr	6.0 mtr

In order to maintain optimum carrier-to-noise ratio (C/N ratio), a larger size of dish is required for the larger cable distribution network. A dish consists of the following parts:

- (a) The stand or the base structure

ing heavy wind or storms, the base structure should be firmly grounded in concrete.

The parabolic reflector. It is the most important part of the dish. The reflector

TABLE I Relationship between F/d and X	
F/d	X (mm)
0.42	0
0.40	5
0.38	10
0.36	15
0.34	20

TABLE II Specification of the DBS tuner with FM demodulator	
Receiving frequency	950 MHz to 1750 MHz
Input impedance	75-ohm
IF	479.5 MHz
Channel select (SY)	By electronic tuning
ODU supply in-and-out	18-25V DC
Tuning voltage	0.6V to 20V DC
IF bandwidth	27 MHz (3 dB down)
Output impedance	75-ohm
Demodulation (SY)	PLL

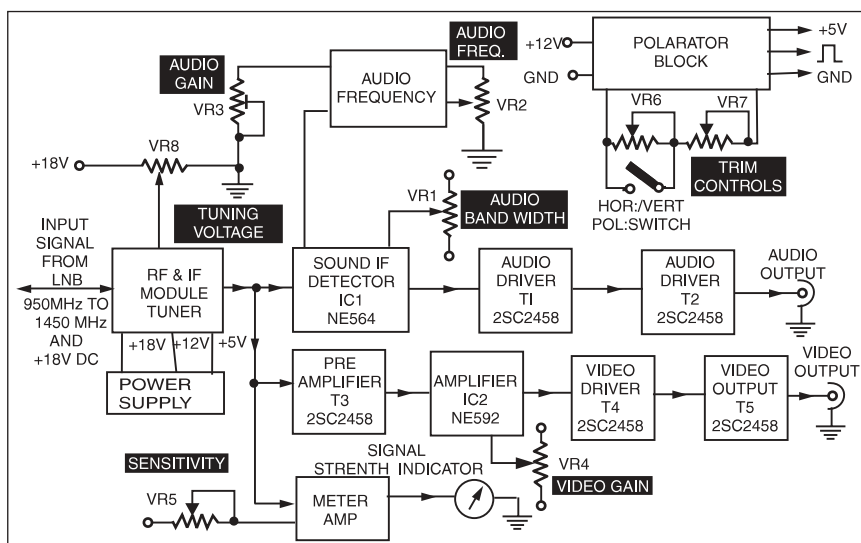


Fig. 3(a): Block diagram of C-band satellite receiver

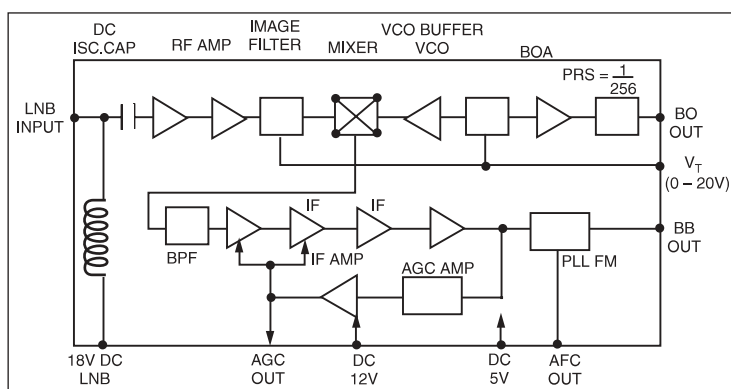


Fig. 3(b): Pin out of DBS timer with FM demodulator

receives the signals from the satellite and focuses them to the focal point where the feed horn is positioned. The focused signal picked up by the feed horn is fed into the LNB, which is mounted on feed horn itself. The dish antenna kits are now-a-days readily available and can be easily assembled.

LNB assembly. The LNB assembly consists of the following three parts: the scalar ring, polarator, and LNB.

(a) *The scalar ring:* There are two types of scalar rings, namely, adjustable and fixed.

(i) *Adjustable scalar ring:* In this, the scalar ring slides on the feed horn and can be positioned to suit the focal distance to diameter ratio (F/d) of the dish (refer Fig. 2). The focal distance 'X' is related to the F/d ratio, as shown in Table I.

ii) *Fixed scalar ring:* Here, the scalar ring is an integral part of the feed horn and the distance 'X' is fixed. It may not always suit the F/d ratio of the dish being used. Hence it is not preferred.

large dish assemblies, a motorised polarator is preferred. The motor used in a polarator has three terminals: +5V, ground, and pulse.

The motor responds to the width of the pulse supplied by the receiver. The pulsewidth can be varied from 0.8 to 2.8 ms with the help of the 'trim' controls in the receiver and the position of the V/H (vertical/horizontal polarisation) switch. In 'H' position, the probe can rotate by almost 140°. For a stream of pulses with fixed width, the probe position will be fixed. The probe will move only when the pulsewidth is changed. Keeping the 'trim' control in mean position and changing the V/H switch from V to H or H to V results in pulsewidth changes in one step, enabling the probe to rotate through 90°. To know as to why the probe movement is required, we have to know about the 'polarisation'.

There are three types of polarisations: (a) vertical, (b) horizontal, and (c) circular. Electromagnetic waves have two

fields—electric field and magnetic field—which are mutually at right angle to each other and also at right angle to the direction of motion.

In vertical polarisation, the electric field is along the North-South axis of the satellite.

In horizontal polarisation, the electric field is at 90° to the North-South axis of the satellite.

In circular polarisation the electric field advances like a cork screw. It can be either left-hand circular (LHC) or right-hand circular (RHC).

To convert this circularly polarised waves into linearly polarised waves (vertical or horizontal), a 6.4mm thick fibre glass piece is fixed in the feed horn along its diameter. For example, CNN transmission has circular polarisation, and therefore the fibre glass piece is essential to get maximum signal pick-up. On the other hand, Star TV signal is vertically polarised, and hence the fibre glass piece is not required. It should in fact be removed to avoid 3dB loss.

For maximum signal pick-up, the probe should be in line with the polarisation of the signal it is receiving. Probe movement is therefore required for alignment purpose. If the probe is aligned to receive a horizontally polarised signal and the signal being received is vertically polarised, the probe has to be moved through 90° for maximum signal pick-up. This will give a crystal-clear picture. This can be done either by trim control or with the help of V/H switch, with the trim control in its centre position.

(c) *LNB.* The LNB stands for low-noise block converter. LNB comprises an amplifier and a frequency converter. The signals in C-band (3.7 GHz to 4.7 GHz), which are received and reflected by the dish, are fed to the amplifier inside LNB via the feed horn probe, as mentioned earlier. The signal-to-noise ratio of the amplifier has to be rather good because the received signals are very weak. The lower the noise, the better will be picture quality.

The converter inside the LNB comprises a fixed frequency oscillator running at 5150 MHz, which beats with the incoming signal frequency. The difference frequencies obtained range from 5150 - 4200 = 950 MHz, to 5150 - 3700 = 1450 MHz, i.e. the input frequency range of 4.2 GHz to 3.7 GHz is converted to 950 to 1450 MHz range. The gain of LNB is typically around 50 dB.

(b) *Polarator:* Inside the feed horn, there is a probe, which is required to move according to the polarisation of the satellite signals.

For

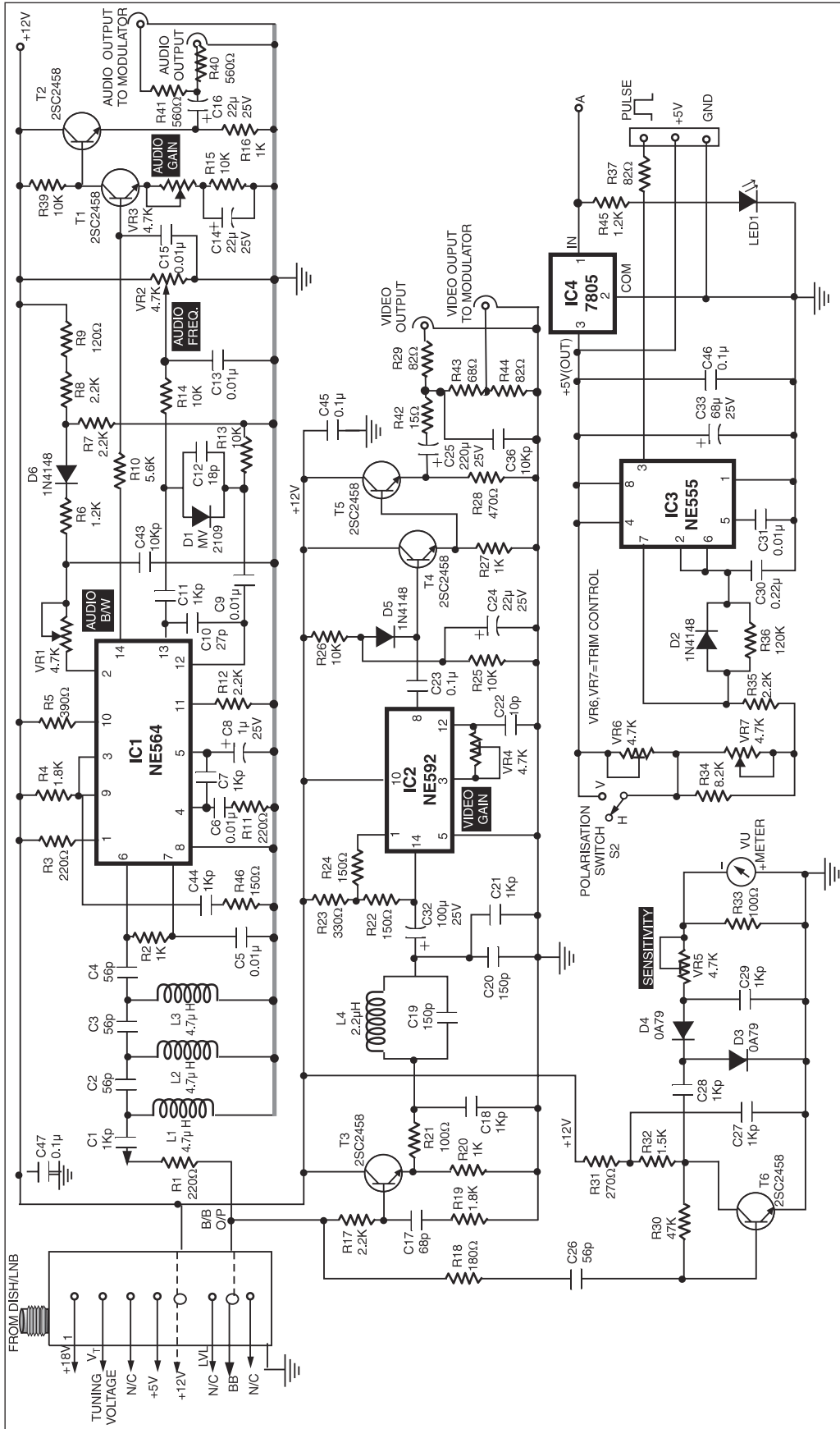


Fig. 4: Circuit diagram of C-band satellite receiver

Another important parameter of the LNB is its noise temperature. The noise equivalent temperature of most of the good-quality LNBs ranges from 26°K to 40°K (K stands for kelvin). The picture on a 26°K LNB will show less noise compared to that of a 40°K LNB, especially when the received signal is weak. Theoretically, the noise power is related to the temperature as follows:

Noise power = KTB watts

where K is the Boltzman's constant = 1.381×10^{-23} T is temperature in °K; and B is the system bandwidth in Hz.

A coaxial cable connected between the LNB and receiver serves two purposes: (i) it feeds +18V DC to the LNB, to power the amplifier and converter circuits inside LNB, and (ii) the converted frequency (950 MHz to 1,450 MHz) is fed from LNB to 'C-band' receiver.

C-band receiver.

The main function of the receiver is to select a particular channel from the converted block of frequencies (between 950 and 1450 MHz) and retrieve the audio and video signal information. The audio and video output signals are finally fed to the TV monitor's audio and video-input terminals, respectively. If the TV does not have separate audio and video input points, then feed the audio and video output signals from receiver to an RF modulator which modulates the RF and provides a modulated VHF RF output (corresponding to anyone of the channels in the VHF

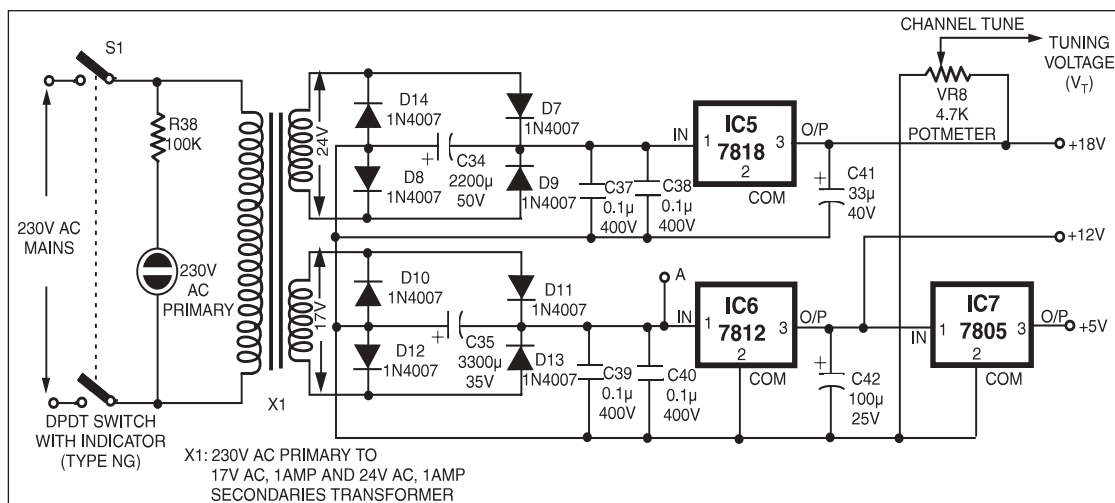


Fig. 5: Power supply unit

band from channel 2 to channel 12) to operate the domestic receiver directly.

The block diagram of a satellite receiver is shown in Fig. 3(a).

The coaxial cable from LNB is connected to the tuner (which contains RF and IF modules) through 'F' socket. To simplify the design for an average constructor, the Mitsumi TSU2-EOIP tuner is used in the circuit. Pinout of the tuner are shown in Fig. 3(b) while its specifications are given in Table II. It is a readymade tuner with tunable range from 950 MHz to 1450 MHz, giving baseband output directly with audio sub-carrier.

The tuner module is tuned with a voltage (V_T) between 0 and 20V and requires no high/low band switch. It has a terminal for applying the supply voltage for LNB, which is carried to the LNB via the down lead, coaxial cable type RG-8 or RG-11. The module itself is fed +12V and +5V DC for its operation. The complete circuit diagram of the receiver is shown in Fig. 4.

The baseband output from the tuner module is fed to the audio stage, video stage, and signal-strength indication circuit.

Audio section. It consists of three stages: sound intermediate frequency (SIF) stage, sound driver stage, and sound output stage.

The audio signal from the baseband output of tuner module is separated with the help of an LC (inductance-capacitance) tuned wave-trap circuit comprising capacitors C1 through C4 and inductors L1 through L3. SIF signal is fed to pin 6 (limiter section) of IC1 (NE564). The positive DC voltage is fed to pins 1, 3, 9, and

10 of IC1.

Audio IF frequency can be varied by varying the voltage of VCO (voltage-controlled oscillator) of the IC. The VCO voltage is controlled with the help of potentiometer VR2, which is connected to pin 13 of IC1 and acts as an audio IF frequency-controller. Varactor diode D1 (MV2109) is connected across pins 12 and 13 through capacitors C9 and C11.

Audio bandwidth can also be adjusted

PARTS LIST

Semiconductors:	
IC1	- NE564 phase locked loop
IC2	- NE592 video amplifier
IC3	- NE555 timer
IC4, IC7	- 7805, 5V regulator
IC5	- 7818, 18V regulator
IC6	- 7812, 12V regulator
T1 - T6	- 2SC2458 npn transistor
D1	- MV2109 varicap diode
D2, D5, D6	- 1N4148 switching diode
D3, D4	- OA79 detector diode
D7 - D14	- 1N4007, 1-amp silicon diode
LED	- Red LED
Resistors (all 1/4W, ± 5% carbon, unless stated otherwise)	
R1, R3, R11	- 220 ohm
R2, R16, R20	- 1 kilo-ohm
R4, R19	- 1.8 kilo-ohm
R5	- 390 ohm
R6	- 1.2 kilo-ohm
R7, R8, R12	- 2.2 kilo-ohm
R17, R35	- 120 ohm
R9	- 120 ohm
R10	- 5.6 kilo-ohm
R13, R14, R15	- 10 kilo-ohm
R18	- 180 ohm
R21, R33	- 100 ohm
R22, R24	- 150 ohm
R23	- 330 ohm
R28	- 470 ohm
R29	- 82 ohm
R30	- 47 kilo-ohm
R31	- 270 ohm
R32	- 1.5 kilo-ohm
R34	- 8.2 kilo-ohm
R36	- 120 kilo-ohm
R37, R44	- 82 ohm
R38	- 100 kilo-ohm
R40, R41	- 560 ohm
R42	- 15 ohm
R43	- 68 ohm
VR1, VR2,	- 4.7 kilo-ohm linear potentiometer
VR3, VR4,	- 4.7 kilo-ohm presets
VR5, VR6	- 4.7 kilo-ohm presets

Capacitors:	
C1, C7, C11, C18	- 1kpF ceramic disc
C21, C27	- 1kpF ceramic disc
C28, C29, C44	- 56pF ceramic disc
C2, C3, C4, C26	- 56pF ceramic disc
C5, C6, C9, C13	- 0.01µF ceramic
C15, C31	- 1µF, 25V electrolytic
C8	- 27pF ceramic disk
C10	- 18pF ceramic disk
C12	- 68pF ceramic disk
C14, C16, C24	- 22µF, 25V electrolytic
C17	- 150pF ceramic disk
C19, C20	- 10pF ceramic disk
C22	- 0.1µF ceramic disk
C23	- 220µF/25V electrolytic
C25	- 0.22µF ceramic disk
C30	- 100µF, 25V electrolytic
C32	- 68µF, 25V electrolytic
C33	- 2200µF, 50V electrolytic
C34	- 3300µF, 50V electrolytic
C35	- 10 kpF ceramic disk
C43	- 0.1µF, 400V, ceramic disk
C46, C36	- 33 µF, 40V electrolytic
C41	- 100 µF, 25V electrolytic
C42	- 100 µF, 25V electrolytic
Miscellaneous:	
	- VU meter (250µA)
	- Mitsumi tuner (TSU2-EOIP)
	- PCB
	- Chassis, knobs, on/off switch
	- Heat-sink for regulators
L1, L2, L3	- 4.7µH inductor (fixed)
L4	- 2.2µH inductor (fixed)
	- 3-pin screw type connector for motorised feed horn pulse
X1	- 230V AC primary to 17V AC, 1-amp and 24V AC, 1-amp secondary transformer
S1	- DPDT rocker switch
S2	- On/off switch

 


Fig. 6: PCB layout for the circuits in Figs 4 and 5 (track-side)

with the help of potmeter VR1 (audio B/W control) by changing the voltage at pin 2 (phase comparator section) of IC. Potmeter VR1 generally changes the phase of the audio signal.

After processing of the audio IF signal, including its amplification and rectification, an AF output is available at pin 14. The audio output is further amplified by transistor amplifiers built around tran-

sistors T1 and T2 (2SC2458), which develop 1-volt peak-to-peak audio output across resistor R16.

Potmeter VR3 acts as an audio gain control.

Video section: This is divided into four stages, namely, video amplifier, video detector, video driver, and video-output stage.

Signal from baseband output of tuner

module is fed via resistor R17 (2.2 kilo-ohm) to the base of video amplifier comprising transistor T3 (2SC2458). Capacitor C17 and resistor R19 are used to suppress the interference. R20 (1k) is used for emitter bias.

Video signal is taken from the emitter of transistor T3 and fed to video detector IC2 (NE592) through an LC network comprising capacitors C18 through C20 and inductor L4 (a video take-off coil). Pin 1 of IC is taken as reference input and pin 14 is taken as signal input. A suitable positive bias is given to pin 1 and pin 14 through resistors R22 to R24.

The output is taken from pin 8 of IC (positive video) and fed to the video driver as well as the output stage comprising transistors T4 and T5. After amplification of video signal, 1V peak-to-peak video output is taken from the emitter of transistor T5 through capacitor C25 and resistor R29. Potmeter VR4 (4.7k) is a video gain control, which is used to adjust the contrast of picture.

Signal-strength indicator. To indicate the signal strength of the incoming signal, a 250 μ A ammeter (or VU meter used in stereo decks) is employed. To drive the meter, an amplifier comprising transistor T6 (2SC2458) is used. The signal from baseband output of tuner module is fed to the base of transistor T6 through resistor R18 and capacitor C26. Positive bias is

given to the base of transistor through resistor R30 (47k). The high-frequency AC output is taken from the collector of transistor T6 through capacitor C28 and fed to the voltage doubler circuit comprising diodes D3 and D4 and capacitors C28 and C29. The output is fed to microammeter via potmeter VR5, which can be adjusted for convenient deflection.

A double-sided PCB has been used,

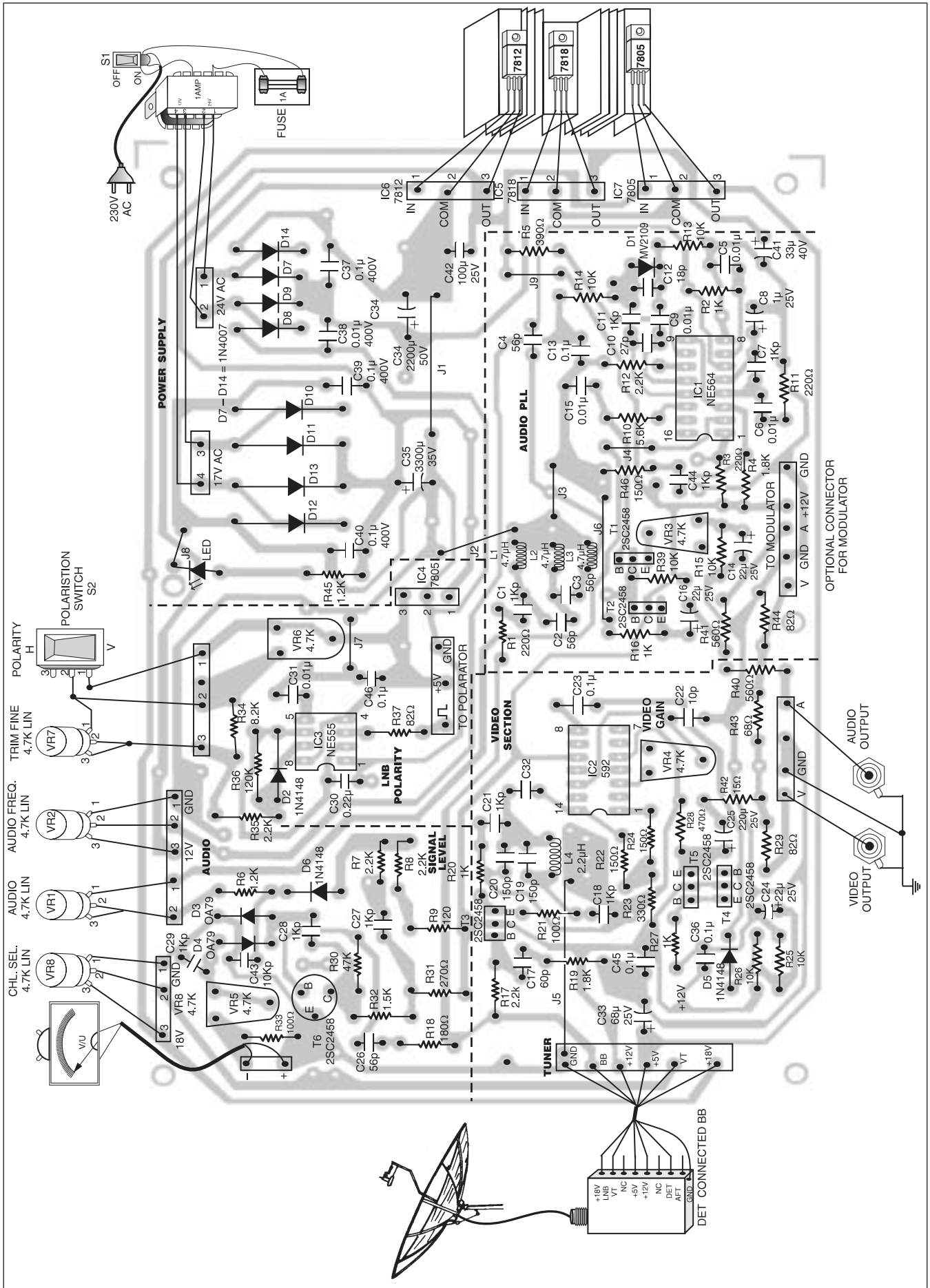


Fig. 7: Component layout for the PCB of Fig. 6

TABLE III

IC1 (NE 564)										
Pin no:	1	2	3	4	5	6	7	8		
Voltage (V):	7.5	1.5	1	6.5	6.5	3	1	0		
Pin no:	9	10	11	12	13	14	15	16		
Voltage (V):	1	4.5	1	2	2	4	1.5	0.5		
IC2 (NE592)										
Pin	1	2	3	4	5	6	7	8	8	10
Volt	9V	0V	9V	8.5V	0V	0V	9V	9V	0V	12V
Pin	11	12	13	14						
Volt	8.5V	8.5V	0V	9V						
Transistors										
	Base	Emitter	Collector							
T1	3.2V	3.2V	7V							
T2	7V	7V	12V							
T3	8.2V	8.2V	12V							
T4	7V	7V	12V							
T5	7V	7V	12V							
T6	2V	0V	2V							

 


Fig. 8

with component side serving as a ground plane. From component side, copper foil has been etched from around all holes except those connected to ground. Actual-size solder-side track layout is shown in Fig. 6. Component layout for the PCB is shown in Fig. 7. The author's prototype is shown in Fig. 8.

Testing

After completion of assembly and construction, check the +12V and +18V DC from power-supply regulator, before connecting it to the PCB. Now connect both the supplies to PCB and check that +18V is available at the input 'F' socket of tuner module. Then connect the dish/LNB lead to the tuner and connect the audio and video output from receiver either to the modulator or to the audio- and video-input terminals of the TV set.

Switch 'on' the receiver and adjust channel-selection potentiometer VR1 to select the desired channel. Audio can be fine tuned using potmeters VR1 and VR2. Audio amplitude can be adjusted with the help of potmeter VR3. Picture contrast is to be adjusted using potmeter VR4.

In case the receiver does not work properly, refer to the circuit diagram and check its connections. Check thoroughly all the connections and resolder if you find any dry joints. Finally, check the voltages at the pins of IC5 and transistors, as given in Table III, for any major discrepancies. □

EPROM-BASED PROGRAMMABLE NUMBER LOCK



JUNOMON ABRAHAM

Most of the code lock/number lock circuits presented in EFY so far have been based on discrete

Please note that its reset pin 4 is connected to output A = B (O_{A=B}) pin 3 of comparator IC4 (CD4585). Thus, as long

pin 3 is at logic 1 and thus monostable IC1 is enabled. When magnitude of input A is not equal to B, the output pin 3 of IC4 is at logic 0 and as a result IC1 is disabled.

In enabled state, the monostable IC1 generates an output pulse when switch S1 (marked zero) is momentarily pressed. This output pulse from IC1 is used as a clock pulse for counter IC2 and shift register IC5. While IC2 counts on high-to-low transition of the clock, IC5 shifts on low-to-high going transition of the clock.

TTL and/or CMOS ICs. This circuit is based on a familiar EPROM 27C32, wherein the required code is stored. It is a number lock, which can be programmed to any coded number. The length of the number can also vary.

To make a code-lock for a particular number (octal, decimal, or hexadecimal), that number is first converted to its binary equivalent. It is then entered bit-by-bit into consecutive memory locations of EPROM 2732 (IC3), starting with the MSB and ending with the LSB (D0). Assume that the required number is 12 (hex). Its equivalent binary number is 00010010. This binary number is entered into the EPROM at memory locations starting with 001(hex),

as shown in Table I. The first memory location is always loaded with binary byte XXXXXXX0 (here, X means "do not care"). The data is stored in consecutive locations, starting with location 001H, as stated earlier.

Description

The circuit comprises six ICs, including the EPROM and the voltage regulator. IC1 is a timer NE555, which is configured as a monostable flip-flop.

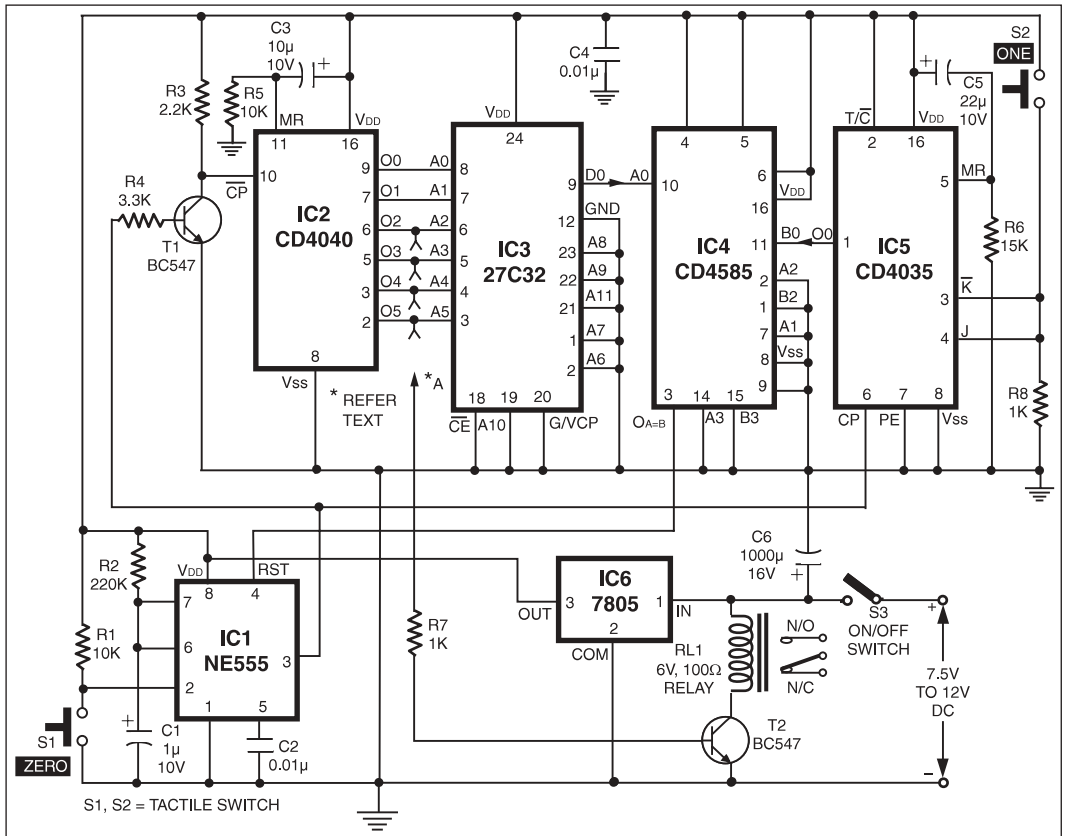


Fig. 1: Complete circuit diagram of number lock

TABLE I		
Memory address (Hex)	Data	
	Hex	Binary Equivalent
000	X0	XXXXXXXX0
001	X0	XXXXXXXX0
002	X0	XXXXXXXX0
003	X0	XXXXXXXX0
004	X1	XXXXXXXX1
005	X0	XXXXXXXX0
006	X0	XXXXXXXX0
007	X1	XXXXXXXX1
008	X0	XXXXXXXX0

Note: X means do not care

as 4-bit magnitude of input A to IC4 is equal to magnitude of the other input B (to IC4), its output

Hence, to synchronise the operation of IC2 and IC5, the clock pulse to IC2 is inverted by the transistorised inverter stage around transistor T1.

At power on, IC2 is reset due to power-on-reset circuit built using capacitor C3 and resistor R5. Hence, all its outputs (including O0 through O5 connected to addresses A0 through A5 of EPROM IC3) are initially at logic 0. In other words, initial address selection for EPROM is 000H, since address lines A6 through A11 of EPROM are permanently

 


Fig. 2: Actual-size, single-sided PCB layout

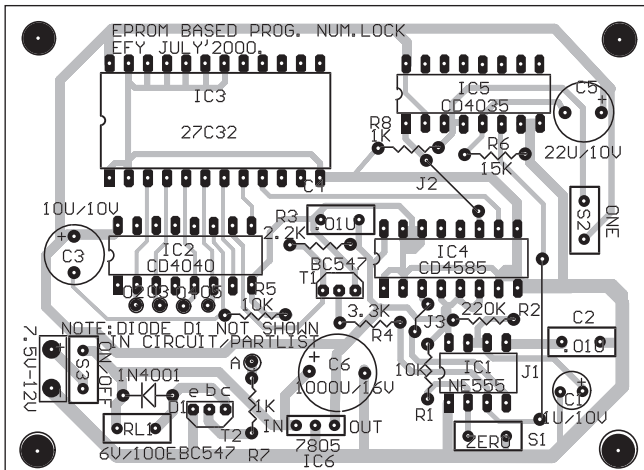


Fig. 3: Component layout for the PCB

grounded in this circuit. With each clock pulse from IC1, the counter IC2 output increments by one and so also the address of EPROM. Since the clock pulses from IC1 are also being applied to clock pin 6 of 4-bit shift register IC5 (CD4035), let us examine how the data at its input pins 3, 4 (\bar{K} , J) and output pin 1 (O0) changes. Please note that O1 through O3 (at pins 15, 14 and 13 respectively) of the shift register are not used in this circuit.

On initial switching 'on' of power supply to the circuit, IC5 is reset due to the

power-on reset circuit comprising capacitor C5 and resistor R6, connected to its master reset pin 5. Thus, initially its output O0 at pin 1 is at logic 0. On receipt of first clock pulse from IC1, the data pin states of J and \bar{K} pins (4 and 3) get shifted to output pin 1. The logic level at these two pins (3 and 4) is normally zero as they are pulled to ground via resistor R3, when push to 'on' switch is in its normal (off) position. However, if switch S2 is kept pressed when clock pulse is generated by IC1 (by pressing switch S1 momentarily), logic 1 is output to pin 1 of shift register IC5.

In this circuit, the final opening or closing of lock is achieved through energisation of relay RL1 via relay-driver transistor T1, whose base is connected to either O2, O3, O4, or O5 outputs of IC2 via resistor R7. The selection of the position where point A is to be connected would depend on the binary digits in the code. If binary code is of 4-bit length (equivalent to one hex digit), then four clock pulses are needed for advancing the EPROM address by four locations. On fourth pulse, O2 will be at logic 1 (unless IC1 gets disabled due to non-matching of the code in comparator CD4585, earlier) to energise relay RL1. For 8-bit long code (equivalent to two hex

digits), the tap A needs to be connected to O3. Similarly, for 16-bit code, point A is to be connected to O4, and so on.

PARTS LIST

Semiconductors:

IC1	- NE 555 timer
IC2	- CD 4040 12-bit binary counter
IC3	- 27C32 EPROM
IC4	- CD 4585 4-bit magnitude comparator
IC5	- CD 4035 4-bit shift register
IC6	- 7805 regulator
T1, T2	- BC 547 npn transistor

Resistors (all 1/4-watt, ±5% carbon, unless stated otherwise):

R1, R5	- 10-kilo-ohm
R2	- 220-kilo-ohm
R3	- 2.2-kilo-ohm
R4	- 3.3-kilo-ohm
R6	- 15-kilo-ohm
R7, R8	- 1-kilo-ohm

Capacitors:

C1	- 1µ/10V electrolytic
C2, C4	- 0.01µ ceramic disk
C3	- 10µ/10V electrolytic
C5	- 22µ/10V electrolytic
C6	- 1000µ/16V electrolytic

Miscellaneous:

RL1	- 6V/100-ohm relay
S1, S2	- tactile switch
S3	- On/off switch
	- DC power supply (7.5V to 12V)

Operation

When the power supply to the circuit is initially switched 'on', IC2 and IC5 are reset, as explained earlier. Both A0 and B0 inputs to IC4 are zero and thus its output at pin 3 is 'high' and hence IC1 is enabled. But, since pin 2 of IC1 is pulled 'high' via resistor R1, output of IC1 is initially 'low'. Initially, all ICs are in their reset positions because of the capacitors connected to their reset pins.

Assume that the required code number is lodged in the EPROM and point A is joined to appropriate output of IC2 depending on the length of lodged code, as discussed in the description of relay operation. Then, lock relay can be energised by inputting the correct binary code seri-

ally via IC5 with the help of switches S1 (marked zero) and S2 (marked one). A 'zero' is entered by momentarily depressing switch S1 alone, and a 'one' is entered by depressing switch S1 momentarily, after holding switch S2 in the pressed condition.

The 'D0' bit of EPROM and 'O0' bit of shift register (CD4035) are compared by magnitude comparator (CD4585). If the two data bits are equal, the output of comparator remains 'high' and it does not interrupt/inhibit the operation of monostable IC1 (NE555). However, if there is a mismatch, the output of com-

parator goes 'low' and it inhibits IC1. Thus, further data would not get entered in the absence of clock pulse from IC1. If data at each location of EPROM keeps matching with the data input via switches S1 and S2, the output of comparator (at pin 3) will continue to stay 'high' to keep IC1 enabled until all the bits of the code have thus been compared. At the end of the code, the tap A will be at logic 1, to energise relay RL1. If you have by mistake entered wrong code via switches S1 and S2, you can try again by switching 'off' and then switching 'on' the circuit once again, using 'on'/'off'

switch S3.

Please note that for locking, the circuit need not play any role. The locking operation could be performed manually. Only for opening of the lock, this code lock may be used. However, you are at liberty to use the lock the other way around.

An actual-size, single-sided PCB for the circuit of Fig. 1 is shown in Fig. 2, while Fig. 3 shows its component layout. One may extend/modify the circuit by utilising other seven unused data bits of EPROM as well (presently only bit D0 has been used in this circuit). □

POWER-SUPPLY FAILURE ALARM

M.K. CHANDRA MOULEESWARAN



Most of the power-supply failure indicator circuits need a separate power-supply for themselves. But the alarm circuit presented here needs no additional supply source. It employs an electrolytic capacitor to store adequate charge, to feed power to the alarm circuit which sounds an alarm for a reasonable duration when the mains supply fails.


During the presence of mains power supply, the rectified mains voltage is stepped down to a required low level. A zener is used to limit the filtered voltage to 15-volt

level. Mains presence is indicated by an LED. The low-level DC is used for charging capacitor C3 and reverse biasing switching transistor T1. Thus, transistor T1 remains cut-off as long as the mains supply is present. As soon as the mains power fails, the charge stored in the capacitor acts as a power-supply source for

transistor T1. Since, in the absence of mains supply, the base of transistor is pulled 'low' via resistor R8, it conducts

the components are not critical. If the alarm circuit is powered from any external DC power-supply source, the mains-supply section up to points 'P' and 'M' can be omitted from the circuit. Following points may be noted:

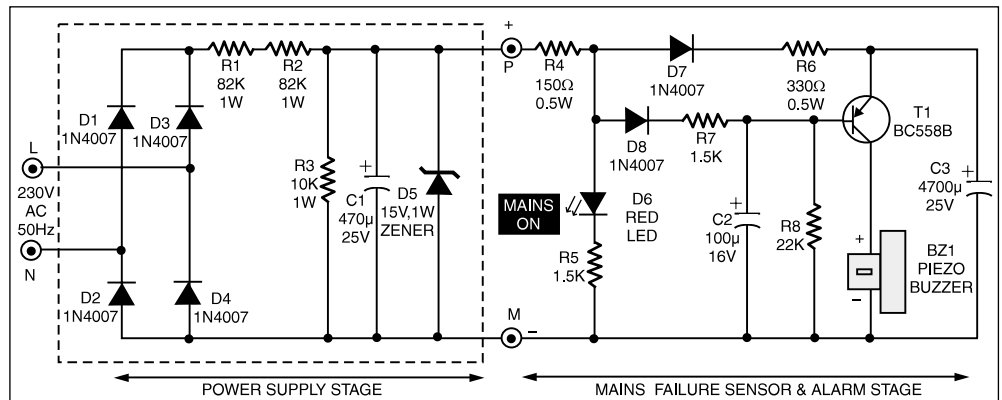1. At a higher DC voltage level, transistor T1 (BC558) may pass some collector-to-emitter leakage current, causing a continuous murmuring sound from the



and sounds the buzzer (alarm) to give a warning of the power-failure.

With the value of C3 as shown, a good-quality buzzer would sound for about a minute. By increasing or decreasing the value of capacitor C3, this time can be altered to serve one's need.

Assembly is quite easy. The values of

buzzer. In that case, replace it with some low-gain transistor.

2. Piezo buzzer must be a continuous tone version, with built-in oscillator.

To save space, one may use five small-sized 1000µF capacitors (in parallel) in place of bulky high-value capacitor C3.

STOPWATCH USING COB AND CALCULATOR

ANANDAN M.A.



The heart of this circuit is a COB which is used in quartz clocks. SCR1 is used for 'start' and 'stop' operations. LED1 used in the circuit serves two purposes. It provides the path to satisfy the minimum holding current

requirement (about 6 mA for a low-power SCR) for the SCR, to maintain it in 'on' state. By placing the LED in the vicinity of LCD, one can read the display even during darkness. The positive going output pulses from the two points of the COB

(from Ajanta timepiece used by EFY) are combined to obtain one pulse per second output across resistor R4.

(EFY Lab note: Please note that COBs used in different clocks may give different outputs—frequency as well as polarity—which may necessitate reversal of diodes, use of additional transistor inverter stage, and modification of key operation sequence of calculator.)

The voltage developed across resistor R4 provides forward bias for transistor T1. Transistor T1 conducts and switches 'on' the optocoupler, whose output (across col-

www.electronicsforu.com

a portal dedicated to electronics enthusiasts


lector and emitter of the in-built transistor) is connected to the two terminals of the '=' (of Casio FX-82LB used during actual testing at EFY) button's keypad tracks, with collector connected to the more positive terminal than the emitter. Thus, once every second the '=' button is activated.

To operate the calculator in stopwatch mode, switch on the calculator and press the keys in the following sequences:

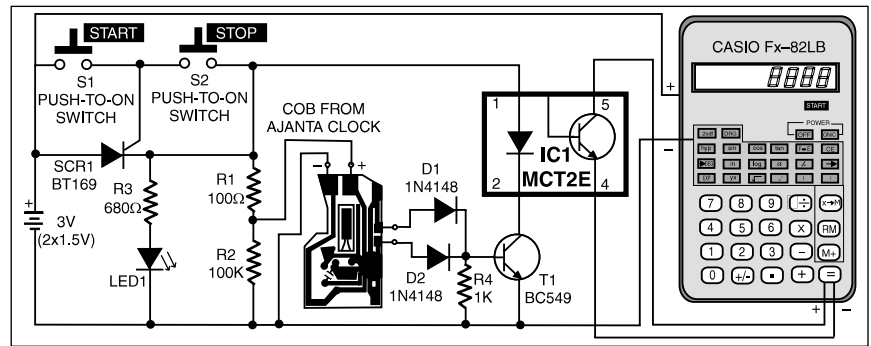- (a) For seconds mode: [1][+][+]
- (b) For minutes mode: [6][0][1/x][+][+]
- (c) For hours mode: [3][6][0][0][1/x][+][+]

Note: The invoking of function (1/x) in different calculators may require pressing of a function key marked 'INV' or 'SHIFT' or '2ndF', etc. Hence, use the appropriate key in your calculator for 1/x operation.

For accurate starting, press the '0' key to reset the count immediately after pressing the start switch. (However, if you desire upcounting from a number other than '0' second/minute/hour in respective modes, you may do so by keying that number immediately after pressing start switch.) The final reading can be taken by pressing the stop switch. The fractional portion of the results obtained during minutes mode and hours mode can be converted to sexagesimal



notation (i.e. degree, minute, second) by invoking '° ' ' ' key. For example, a display of 5.87 in hour mode will get converted to 5, 52, 12 (5 hrs, 52 min., and 12 sec.) when one invokes '° ' ' ' function key.

For downcounting in seconds, minutes, or hours mode, the procedure as outlined in the preceding paragraphs is to be followed except that keys [-][-] should be depressed in place of [+][+].

Pause/hold can be achieved by pressing the '=' key continuously, or pressing switch S2. Intermediate time can be stored by pressing the 'Min' key. This reading can be retrieved by pressing the 'MR' key, after the stop switch has been pressed.

This circuit can easily be installed inside the calculator. There is a vacant space

of 60x22x6 mm inside the Casio FX-82B calculator. By using a chip LED, the size restriction for installing the LED can be overcome. It can be placed near the LCD display to provide indication of the functioning of the stopwatch. The whole circuit can be assembled on a 55x20 mm PCB. The start/stop tactile switches can also be installed inside, with their operating lever popping out through a cutout above the keypad.

You may find certain keypad buttons such as 'hyp' which you may never require to use. Two such buttons can be removed to create place for 'start' and 'stop' switches, if required. By this arrangement, you can start or stop the clock, without affecting its working.

DIAL A VOLTAGE

RATHINDRA NATH BISWAS



In a conventional voltage-divider setup, the fixed voltage is applied across the entire network and the output is taken from across a selectable tap. Although this approach provides precision voltage output, it involves complex switching and usually large number of resistors. Thus, it is not economical, as precision resistors are quite expensive.

A bridge that pro-

vides precision DC voltages from 0 to 10 volts, in steps of 0.01V, can be easily and economically built using a circular voltage divider. In this simple divider arrangement, the points across which the output

is taken remain fixed, while the voltage source is moved from one pair of points to another.

As shown in the diagram, a total of 31 resistors are required to provide settability to within 0.01V. There are a total of three such dials. Each dial has ten resistors, except the last one (dial III), which contains eleven resistors. Dial 1 has ten resistors, having a value of 1 kilo-ohm each. It is marked from 0 to 9 volts


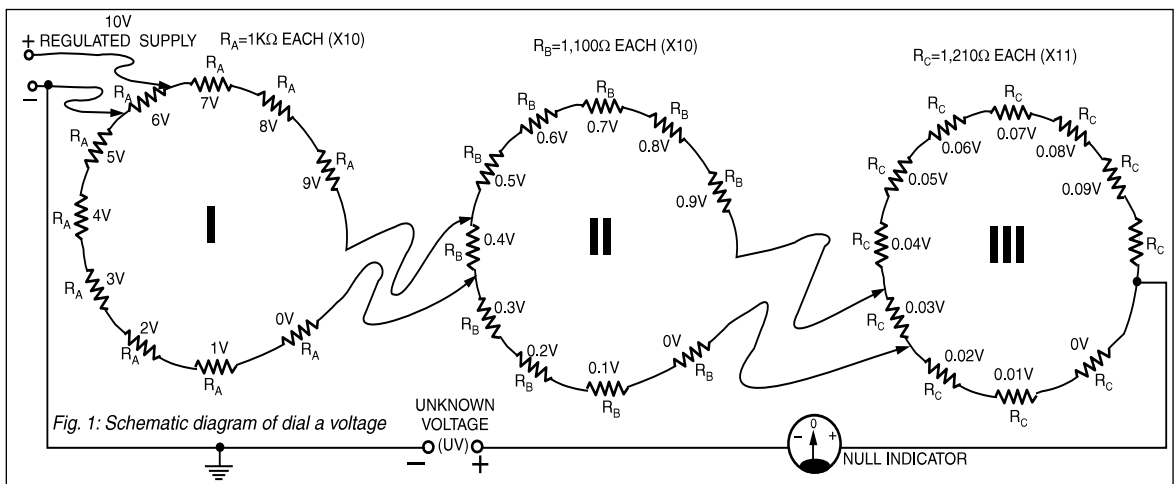


Fig. 1: Schematic diagram of dial a voltage

in 1-volt steps. Dial II has ten resistors of 1,100-ohm value each. This dial is marked from 0 to 0.9 volt in 0.1 volt steps. Dial III has eleven resistors, having a value of 1,210-ohm each, with dial marking from 0 to 0.09 volt in 0.01 volt steps. The values of the resistors in a given ring are 1.1 times the values of the resistors in the preceding ring. The bridge shown in the illustration would read the value of unknown voltage as 6.43 volt (when the null detector reads '0') as detailed below:

- Dial I - 6 volts
- Dial II - 0.4 volt
- Dial III - 0.03 volt
- Total : 6.43 volt

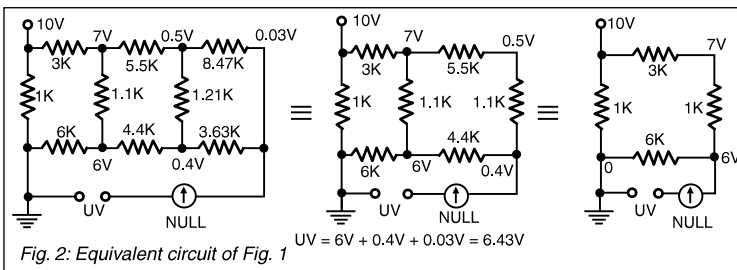Note: 1. For the above example, the equivalent circuit has been reduced to a simpler form by EFY- in three stages, as shown in Fig. 2, for the benefit of the readers.



2. Please do not confuse the dial voltages mentioned inside each of the three dials with the actual voltages across the associated resistors, which would be different.

The tighter the tolerance of the resistors, the more accurate will be the measurement of the unknown voltage. For null detection, any micro-ammeter or galvanometer can be used. However, the more sensitive the null detector is, the

output impedance becomes lower. However, this would increase the power dissipation in the bridge.

The principal limitation of this arrangement is the allowable power dissipation of the resistor in the first ring, across which the full supply voltage is applied. Resistors in dial I must be able to withstand the full supply voltage of 10 volts. Regulated power supply (10-volt) only should be used in this circuit.

more closely the bridge output can be read. If lower value resistors are used, the

ELECTRONIC DANCING PEACOCK

C.K. SUNITH




All of you must have observed a dancing peacock, spreading out its beautiful feathers, turning

around, closing them, and then doing it all over again. The author has attempted to reproduce a similar effect using a set

of LEDs arranged according to a predetermined pattern.

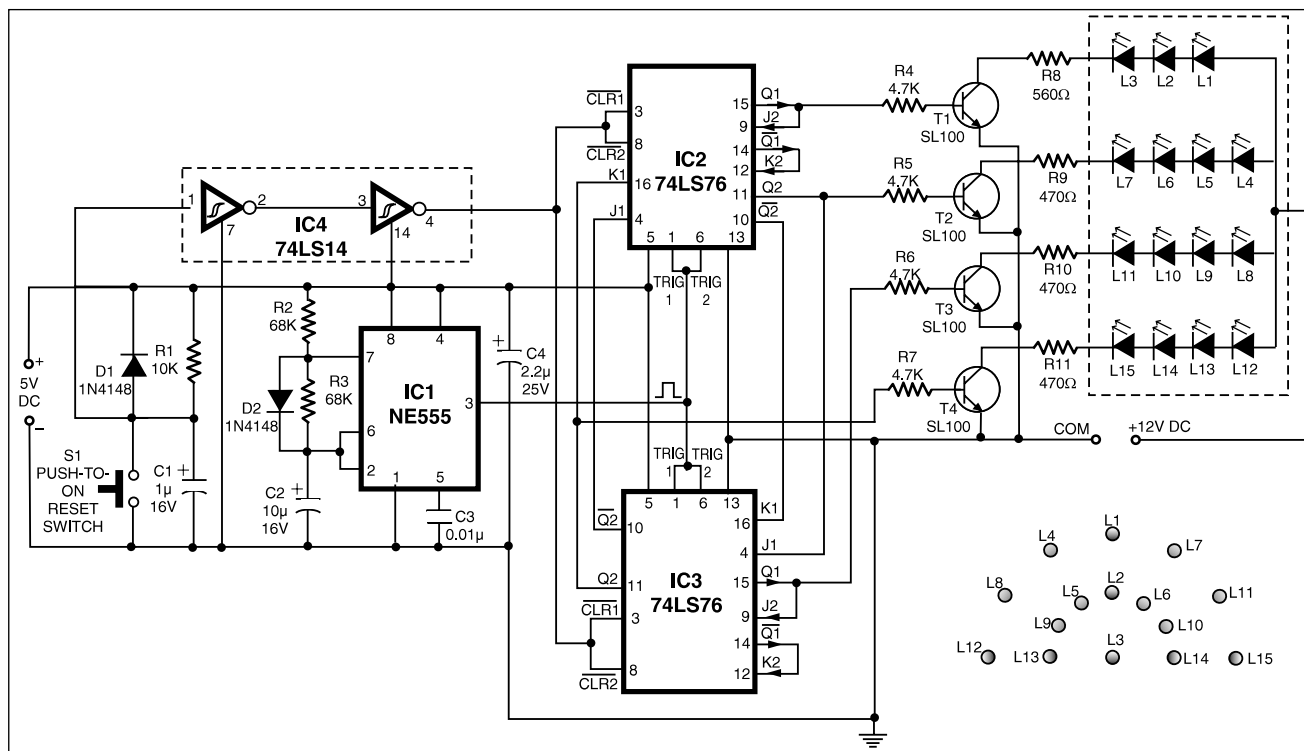The circuit is built around two dual JK flip-flop ICs 7476, which have been wired as a Johnson counter. The count sequence of this counter is shown in Table I. The free running oscillator built around IC1, a popular timer NE555, gen-



D MSB	C	B	A LSB	Decimal Count	LED's LIT Upon Count
0	0	0	0	0	Nil
0	0	0	1	1	L1 to L3
0	0	1	1	3	L1 to L7
0	1	1	1	7	L1 to L11
1	1	1	1	15	L1 to L15
1	1	1	0	14	L4 to L15
1	1	0	0	12	L8 to L15
1	0	0	0	8	L12 to L15
0	0	0	0	0	Nil

erates approximately 1Hz waveform. The output of IC1 serves as the clock input for the counter built around IC2 and IC3.

The circuit can be reset by momentarily depressing switch S1. When the circuit is powered on, capacitor C1 will be initially uncharged, with the result that all the flip-flops are cleared. Now, as the capacitor starts charging toward the positive rail, the clear inputs of all the flip-flops go to logic 1 (and stay there) and the flip-flops are enabled. The counter be-

gins to count in a particular sequence, as shown in Table I. Whenever the output of a flip-flop goes high, the associated transistor connected at its output saturates. It drives current through the array of LEDs connected as collector load, thereby causing them to turn 'on'.

Upon arrival of first clock pulse, the LSB will be set. The counter will now count 0001. This means that the array of LEDs at the centre of the display panel will be lit. When the next clock pulse arrives, logic 1 will also be copied to its preceding flip-flop and the counter will read 0011. As a result, the array of LEDs adjacent to the centre array (on both sides) will be lit. In this fashion, the count progresses upwards till it reaches 1111, when all the arrays of LEDs will be lit. Now the wings of the peacock are fully spread. At this stage, you may manually swing the display board both ways, holding it at its centre bottom by

your thumb and forefinger to resemble a dancing peacock.

The countdown sequence of the counter will be initiated upon the arrival of the next clock pulse, which causes the count to read 1110. At this stage, the array of LEDs at the centre of the display panel will be turned 'off'. The counter then counts down to 1100 upon the arrival of the next clock when the array of LEDs adjacent to the centre array (on both sides) will also be turned 'off'. In this manner, the counter continues to count down till the contents read 0000, when the whole array of LEDs are turned 'off' and one full cycle is completed. The counter then starts the counting sequence all over again.

The circuit can be assembled on a general-purpose PCB. The LEDs can be stacked into an array as per the pattern shown in the figure. The circuit requires both +5V and +12V DC supplies. The circuit can be used as a festival display.

INVERTER OVERLOAD PROTECTOR WITH DELAYED AUTO RESET



SIDDHARTH SINGH

An overload condition in an inverter may permanently damage the power transistor array or burn off the transformer. Some of the domestic inverters sold in the market do not feature

an overload shutdown facility, while those incorporating this feature come with a price tag.

The circuit presented here is an overload detector which shuts down the in-

verter in an overload condition. It has the following desirable features:

- It shuts down the inverter and also provides audio-visual indication of the overload condition.
- After shutdown, it automatically restarts the inverter with a delay of 6 seconds. Thus, it saves the user from the inconvenience caused due to manually resetting the system or running around in darkness to reset the system at night.
- It permanently shuts down the inverter and continues to give audio warning, in case there are more than three

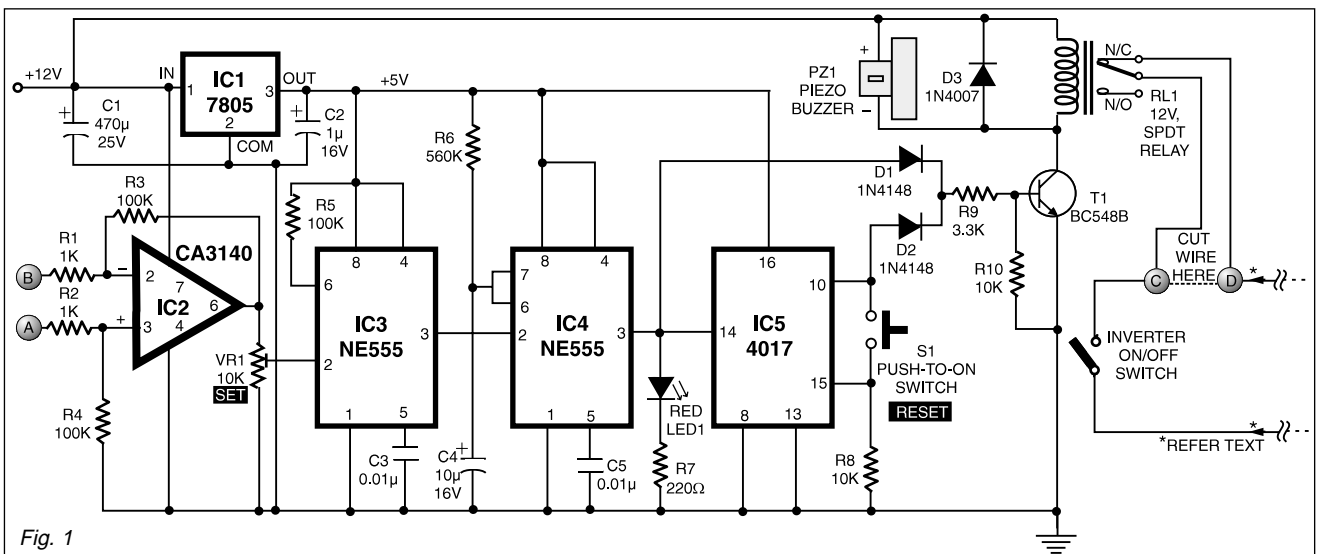


Fig. 1

 


Fig. 2

successive overloads. Under this condition, the system has to be manually reset. (Successive overload condition indicates that the inverter output is short-circuited or a heavy current is being drawn by the connected load.)

The circuit uses an ammeter (0-30A) as a transducer to detect overload condition. Such an ammeter is generally present in almost all inverters. This ammeter is connected between the negative supply of the battery and the inverter, as shown in Fig. 2. The voltage developed across this ammeter, due to the flow of current, is very small. It is amplified by IC2, which is wired as a differential amplifier having a gain of 100. IC3 (NE555)

counter which counts the three overload conditions, after which the system has to be reset manually, by pressing push-to-on switch S1.

The circuit can be powered from the inverter battery. In standby condition, it consumes 8-10 mA of current and around 70 mA with relay (RL1), buzzer (PZ1), and LED1 energised. Please note the following points carefully:

- Points A and B at the input of IC2 should be connected to the corresponding points (A and B respectively) across the ammeter.
- Points C and D on the relay terminals have to be connected in series with the already existing 'on'/off switch leads

of inverter as shown in Fig. 1. This means that one of the two leads terminated on the existing switch has to be cut and the cut ends have to be connected to the pole and N/O contacts respectively of relay RL1.

• The ammeter should be connected in series with the negative terminal of the battery and inverter, as shown in Fig. 2.

Move the wiper of preset VR1 to the extreme position which is grounded. Switch 'on' the inverter. For a 300W inverter, connect about 250-260W of load. Now adjust VR1 slowly, until the inverter just trips or shuts down. Repeat the step if necessary. Use good-quality preset with dust cover (e.g. multi-turn trimpot) for reliable operation.

The circuit can be easily and successfully installed with minimum modifications to the existing inverter. All the components used are cheap and readily available. The whole circuit can be assembled on a general-purpose PCB. The cost of the whole circuit including relay, buzzer, and PCB does not exceed Rs 100.

TELEPHONE LINE BASED AUDIO MUTING AND LIGHT-ON CIRCUIT

DHURJATI SINHA




Very often when enjoying music or watching TV at high audio level, we may not be able to hear a telephone ring and thus miss an important incoming phone call. To overcome this situation, the circuit presented here can be used. The circuit would automatically light a bulb on arrival of a telephone ring and simultaneously mute the music system/TV audio for the duration the telephone handset is off-hook. Lighting of the bulb would not only indicate an incoming call but also help in locating the telephone during darkness.

On arrival of a ring, or when the handset is off-hook, the inbuilt transistor of IC1

(opto-coupler) conducts and capacitor C1 gets charged and, in turn, transistor T1 gets forward biased. As a result, transis-

tor T1 conducts, causing energisation of relays RL1, RL2, and RL3. Diode D1 connected in anti-parallel to inbuilt diode of IC1, in shunt with resistor R1, provides an easy path for AC current and helps in limiting the voltage across inbuilt diode to a safe value during the ringing. (The RMS value of ring voltage lies between 70 and 90 volts RMS.) Capacitor C1 maintains necessary voltage for continuously forward biasing transistor T1 so that the relays are not energised during the nega-

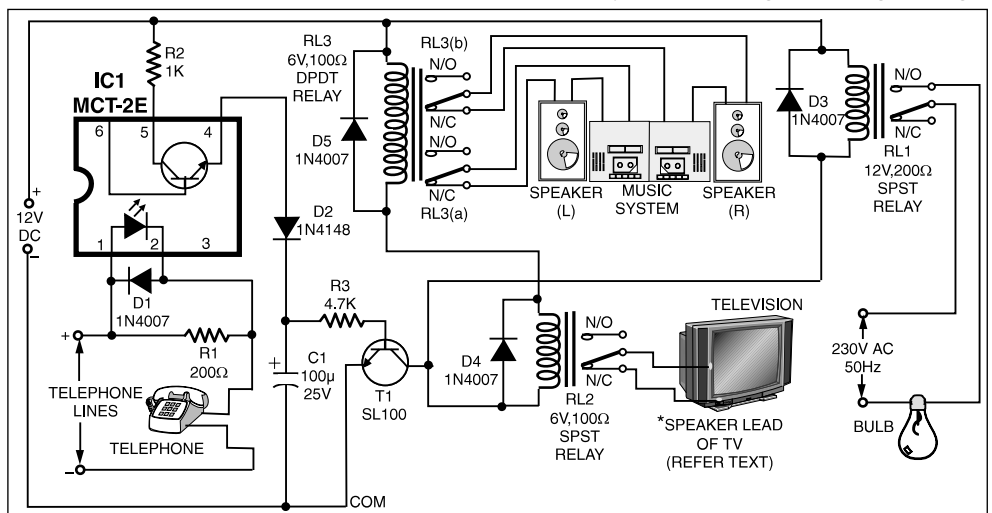

tive half cycles and off-period of ring signal. Once the handset is picked up, the relays will still remain energised because of low-impedance DC path available (via cradle switch and handset) for the in-built diode of IC1. After completion of call when handset is placed back on its cradle, the low-impedance path through handset is

no more available and thus relays RL1 through RL3 are deactivated.

As shown in the figure, the energised relay RL1 switches on the light, while energisation of relay RL2 causes the path of TV speaker lead to be opened. (For dual-speaker TV, replace relay RL2 with a DPDT relay of 6V, 200 ohm.) Similarly,

energisation of DPDT relay RL3 opens the leads going to the speakers and thus mutes both audio speakers. Use 'NC' contacts of relay RL3 in series with speakers of music system and 'NC' contacts of RL2 in series with TV speaker. Use 'NO' contact of relay RL1 in series with a bulb to get the visual indication.

August

2000

DISPLAY SCHEMES FOR INDIAN LANGUAGES—PART I

(HARDWARE AND SOFTWARE)

K. PADMANABHAN, S. ANANTHI, K. CHANDRASEKHARAN,
AND P. SWAMINATHAN

For displaying text of Hindi, English, or any other Indian language on a TV-like screen, as may be required for public announcements or for educational programs etc, presently there are two possible ways:

1. Use a personal computer (PC), with all its hardware, such as the hard disk, monitor etc, and develop or buy a suitable software to display such text on its screen using its keyboard.

2. Develop a dedicated low-cost microprocessor based system employing a CRT controller circuit, with suitable firmware for each of the languages.

This article provides the software for use with a PC based system as well as use of a dedicated microprocessor based system, complete with circuitry and firmware programs. Incidentally, it introduces an important aspect concerning coding of text characters for Indian languages and provides an efficient solution. The software developed for both the above schemes of display is based on the proposed simplified coding solution.

ASCII codes and Indian languages

The typewriter for the English language, along with its mechanism, has been already adopted for almost all of our Indian languages with practically no change in its layout. The positions of keys and their operation remain unchanged. It has the same four rows of keys, including shift and space keys, with top row for numerals, and so on.

The combination vowels in Indian languages such as 'oo' are made as separate 'hook' characters, which upon stroke are non-space-moving. Persons involved in development and adoption of the English keyboard have cleverly tackled the problem of typing the large number of charac-

ters involved in most of the Indian languages, in contrast to a mere 52 (2 x 26) characters in English language. In spite of the fact that Hindi, or for that matter Tamil or Telugu etc, have to deal with a large number of basic consonants, which combine, singly or doubly, with a similarly large set of vowels, the four-row keyboard deals with all of them adequately to ensure fast typing. Our trained typists are able to make up to 40 strokes per minute (approximately 15 words per minute) in the most intricate of Indian languages.

Today, there is both a concern and talk in several circles, e.g. computer, telecommunications, and other hi-tech industries, to develop a new type of keyboard layout for Indian languages, with the aim of making the software development task easy enough. In this context, phonetic keyboards have been proposed and are also in vogue already, with a great deal of software available commercially. These keyboards do not make use of hook characters, but then such a keyboard is not well suited for training.

Generally, typewriting is a process based on direct eye-to-limb reflex signal generation, with little thinking going on deep down in the brain. If the typist looks at a letter 'hu', he presses the 'ha' key first, and as he sees a hook 'oo' below it, he strikes the corresponding hook key, and so on. Thus the process can be speeded up with practice and is not easily forgotten. We know of language typists, who even after 30 years of work, continue to type as fast as they did when they were young. Some of them can even talk while typing without missing anything.

Now, consider the phonetic keyboard typist. He has to split each letter mentally into its vowel and consonant parts; find out the consonant key and the hook key, and then press them in proper se-

quence. Here, the direct eye-to-finger reflex does not take place, because there is a thinking process involved. For example, for typing 'hoom', he has to know the grammar to split that into a 'ha', a 'oo', and an 'mm'. Thus the typist does not pick up speed even after considerable practice, and as a result fatigue sets in quickly for him.

As mentioned earlier, the Indian languages have more characters than those in the English language. The well-known ASCII codes for English are just 128 in number, including several control characters and punctuation marks. Each code occupies one byte and hence the total code space is 7FH for the complete English set. With our Indian languages, we have varied sets of characters. Consonants are quite many, and therefore it is not easy to accommodate all characters within the same set space of 128. For this purpose, the author proposed a scheme of forming such ASCII-like codes for Hindi as well as other Indian languages, which occupy a space of 128 bytes only for each. Based on the standard typewriter format for English, Hindi, Tamil etc, a method for typing text of these and other languages, all simultaneously, is described in this article.


This proposed scheme of coding would not cause any disturbance to the present typists of these languages. They do not have to undergo fresh training for using the proposed keyboard.

The method of making the ASCII code set for any Indian language is based on the typist's existing keyboard. For example, in English, the letter 'd' has its code as 64H. So, the code for the Hindi letter 'ka' (क) is also 64 hex. For Tamil ASCII code 64 hex is used for 'na', and so on...for the other languages. A table of such codes for the three languages Hindi, English, and Tamil is shown in Table I.

Character generator for Indian languages. While characters of any language need a character generator, which puts dots in a rectangular matrix to depict the shape of the character on the screen, the English language, in its simplest form of display, manages to write all its characters within a 5 x 7 matrix. Therefore, within an 8 x 8 matrix, there is enough gap to allow for inter-character and inter-row space. But, in Hindi and

for all the text characters in a manner as shown in Table I, it is now required to put the dots for each code into the character generator. Thus, we specify text only by its codes. For example, for English letter ADD, the code is 41, 44, 44. The actual dots are available within the character generator, and hence the space needed for storing text is just limited to the characters or strokes. But, in other schemes generally employed in other software, the text is stored as graphic patterns and hence quite a large

Fig. 1(a): Schematic diagram of 8085 microprocessor based multilingual display system (memories and decoder portion)

 

our other Indian languages, we cannot manage to use even a simple font within this 8 x 8 matrix (which needs one byte per line or 8 bytes per character). The smallest size in Indian language requires a 12 x 12 matrix, and hence we need 1.5-byte space horizontally and a total of 12 x 1.5 = 18 bytes space for each letter. Further, if one wants better looking fonts,

for instance like the standard Time Roman of English, more dots need to be shown, and hence the character slot size will be even greater than 12 x 12 dots.

In the proposed scheme a 12 x 12 dot font size is used, both for the dedicated microprocessor based display scheme as well as for the PC based scheme.

Since we have already specified codes

amount of memory is needed.

Now take a look at the keyboard—row by row. The top row contains numerals. Next row starts with 'Q' and 'q' (in English) and is used for 'PHA' and 'u' hook in Hindi with and without shift key pressing, respectively. So, these have the same ASCII equivalent codes, i.e., 51 hex and 71 hex, respectively.

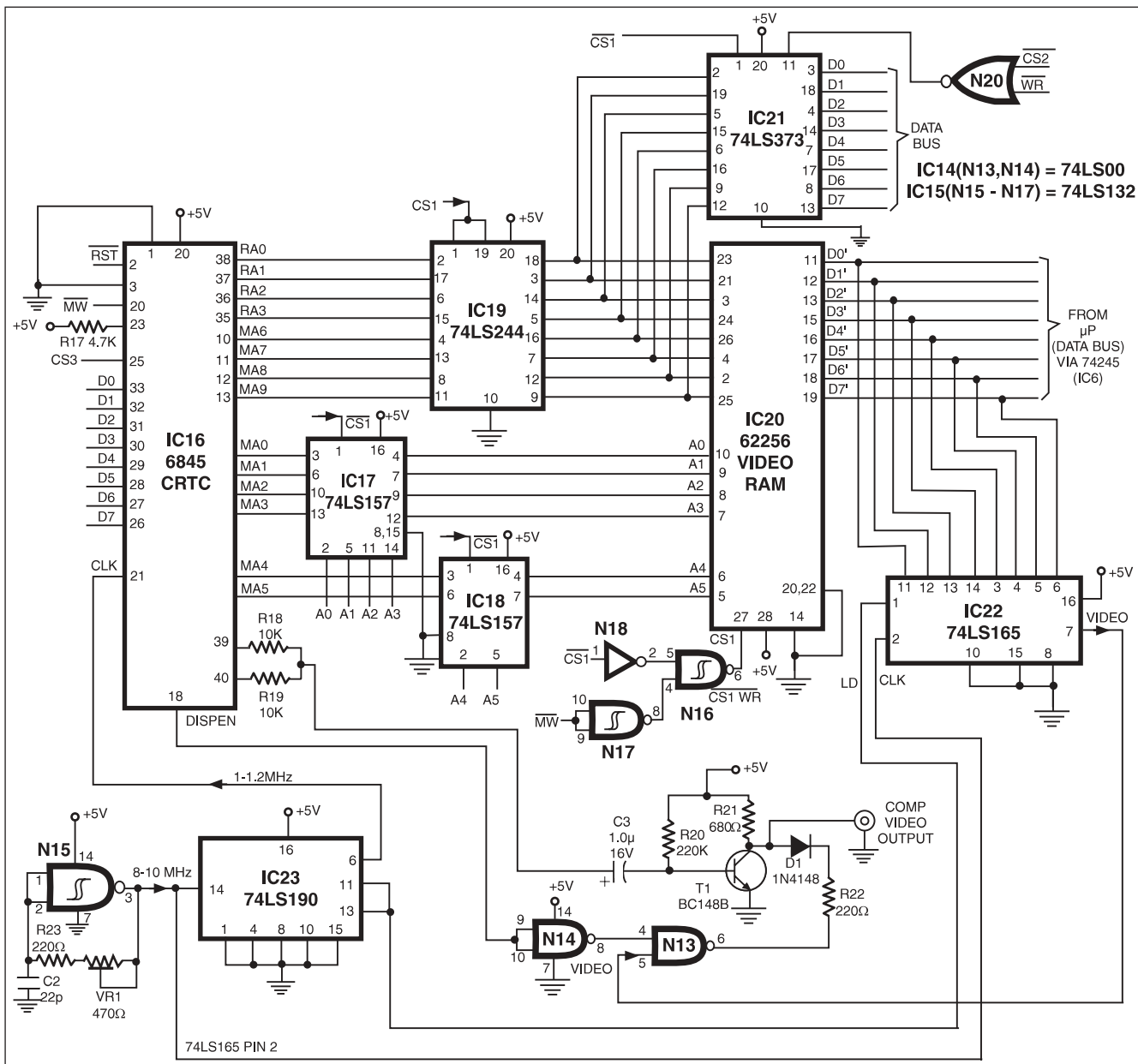


Fig. 1(b): 6845 character and video generator portion of multilingual display system

The character generator is just a list of dots for the characters in an order. It does not necessarily require any hardware. Though such a list of dots, if stored in this order in an EPROM, can be a hardware component. In the PC based design, this is just a file containing the dot patterns, while in the design using a dedicated CRT controller with a microprocessor, this is actually a hardware component, i.e. an EPROM.

Addressing mode for character generator file scheme. Let us take letter 'd' in Hindi, which has the ASCII-equivalent code of 64 hex. We need a high address and a low address as usual. Supposing

the high address for Hindi starts at page 10 and it goes up to page 17 (with each page comprising 256 bytes). In page 10, locations 00 through 7F are used for storing the low addresses while 80 through FF are used for storing high addresses for each character. Accordingly for 'd', the low address is stored at 10 64 and the high address at 10 E4 (1064 + 80 = 10E4). If we have a look at the hex contents of these two locations, we shall find:

Address	Data	Comments
10 64	B4	LS Byte of Address
10 E4	04	MS Byte of Address

Note: The page/location-wise hex contents of file containing these indi-

rect addresses and dot codes are proposed to be issued in EFY-CD during Sept. 2000.

It means that the actual code is starting from the address 14 B4 (1000 + 04B4). So, this is indirect addressing mode. The actual hex values of the dots for each of the twelve lines (in 18 bytes) for 'd' are stored at consecutive locations, starting with address 14B4, as stated earlier.

This indirect addressing scheme is used because it enables us to use different types of fonts later, by just pointing to a different address table. Also, the address table corresponds to the ASCII code,

 


Fig. 2: Keyboard for English, Hindi, and Tamil languages

 


Fig. 3: Character code generation in 12x12 format

just as in 'd', with 64 being the code. The table low-address is also 10 64 and the high address equals 10 64 + 80, and so on. Further,

we need not even write these codes in any order, because we are at liberty to write any address in the look-up table! (That works really when we ask several persons to prepare the font codes and mix them together!)

How exactly does one prepare the table of dots? Take a graph sheet and make 12 x 12 rectangles. Paint the character in this slot, as it would appear when printed. The dots must be darkened to show up the character. Positioning is important; one has to make sure that hooks, if appended to this character, will fall within the space of 12 x 12 without cutting or merging. For example, 'kra' and 'ku' and 'koo' writing must be possible by adding these respective hooks to the character, if required. Then, looking at Fig. 3, for 'ka' (क), we read the dots (in nibbles) in complimentary form and write them down as under:

Line 1 ...000 Line 5 ...010 Line 9 ...1D6
 Line 2 ...000 Line 6 ...1D6 Line 10 ...010
 Line 3 ...000 Line 7 ...139 Line 11 ...000
 Line 4 ...FFF Line 8 ...139 Line 12 ...000

The values are complemented and written as two nibbles at a location. Complementing is necessary to make FF appear as blank on the screen. The table thus obtained for 'ka' (क), occupying 18 bytes (36 nibbles), is shown below:

Address	Code
14 B4	FF FF FF FF F0 00 FE FE
14 BC	29 EC 6E EE F0 1E FE FF

14 C5 FF FF

The table for each language will not need more than 8 pages in an EPROM or 2k bytes in a file. Thus in one 2764, it is possible to house the character generator codes for four languages, say English and three other Indian languages.

PC based design

In the PC based design, the software written in BASIC loads a table of codes from a file. This file is having the same data as the EPROM in the dedicated micro-processor based design.

The software for the computer based display is made simple enough to be used with any PC, without the need for large memory or disk space. It could work even with one floppy system, with just a 386 based PC even. The C++ or other languages are more library oriented and require a hard disk to work with. The C++ library already has different fonts and sizes for English and we use this library to write varied size of text on screen in English. But, until the library for Indian languages becomes similarly available, the C++ is of no use here. Software makers would have made fonts for several Indian languages, but they have not put them in a library form as the promoters of the 'C' language did it for English language. No libraries for video display for Indian languages are currently available exploiting the compactness of the C++. Until then, we need to write code as and when we want, and hence BASIC is better suited.

Hence this program has been developed in BASIC rather than C++ or other Windows based software, for the simple reason that it could be used for education by institutes possessing even simple PC-AT computers.

The program for a computer based

Hindi, English, and Tamil display is given in BASIC language on page 49. This works on an IBM PC with no restrictions of memory, and can work directly from a single floppy. This minimises the cost of the computer system for the display. The program given is based on Turbo BASIC version 1.0, but the same is compatible with Quick BASIC or other similar BASIC interpreter-compilers working on the PC.

The program first loads the file for characters for four languages. Then the user is asked to enter F1 to F4 keys to select the language and S or L (capital) for selecting small or large-size font. Any time during typing text on screen, the function keys may be pressed to change the language, if desired.

- F1 ...Tamil
- F2 ...English
- F3 ...Tamil
- F4 ...Fourth language

The character generator here is a file. It contains the same set of codes that are used for the hardware based design that follows. This is stored as file 'chtamil2', which is read and saved in the array 'ad (lan%,I%)' that stores the dots. This array is used in the program throughout.

That makes it convenient to type several sentences, up to 30 in a VGA monitor screen on the computer, and then on the next screen. For example, on one screen, a Hindi poem could be typed together with its English and Tamil translations.

Printing a page is simply done using the 'Graphics.com' program, which comes with DOS. This must be run prior to running BASIC as:

- A> Graphics
- Then
- A> BASIC

After entering text on one page, it can be printed using shift + print screen keys.

This program is a simple version, and other versions with file storage and printing facility can be prepared with extra statements.

For the use of the typist, it is necessary to write the character strokes of the respective language(s) on key tops of the IBM PC keyboard, at least during the initial typing stage.

Note: The program in BASIC, together with its compiled .EXE file, will be presented in Sept. 2000 EFY-CD. The 8 kilo-byte 'chtamil2' file containing the

TABLE I: ASCII Key Codes for English, Hindi, and Tamil languages

ASCII CODE	ENGLISH	HINDI	TAMIL	ASCII CODE	ENGLISH	HINDI	TAMIL
20	SPACE	SPACE	SPACE-	41	A	᳚(h)	அ
21	!	X	ஸ	42	B	᳛	ஆ
22	"	/	“	43	C	᳜	இ
23	£	::	%	44	D	᳝	ஊ
24	\$	=	ஐ	45	E	᳞	஋
25	%	-	ஐ	46	F	᳟	஌
26	&	"	ஓ	47	G	᳠	஍
27	'	?	ஔ	48	H	᳡	ஞ
28	(ஆ	ஔ	49	I	᳢	ஐ
29)	ஔ	(4A	J	ஔ	ஊ
2A	*	ஔ	ஔ ^(h)	4B	K	க	஋
2B	+	ஔ	ஔ ^(h)	4C	L	஖	஌
2C	,	᳚	ஔ	4D	M	஗	஍
2D	-	᳚(ஔ)	/	4E	N	஘	ஞ
2E	.	᳚	,	4F	O	ங(ஔ)	ஔ
2F	/	᳚	::	50	P	ஐ(ஔ)	ஔ ^(h)
30	0	0	0	51	Q	஑(ஔ)	ஔ
31	1	1	1	52	R	ஒ(ஔ)	ஔ
32	2	2	2	53	S	ஓ(ஔ)	ஔ
33	3	3	3	54	T	ஔ(ஔ)	ஔ
34	4	4	4	55	U	க(ஔ)	ஔ
35	5	5	5	56	V	஖(ஔ)	ஔ
3A	:	ஔ	ஔ	57	W	஗(ஔ)	ஔ
3B	;	ஔ	ஔ	58	X	஘(ஔ)	ஔ
3C	<	ஔ	ஔ	59	Y	ங(ஔ)	ஔ
3D	=	ஔ(ஔ)	ஔ	5A	Z	ஐ(ஔ)	ஔ
3E	>	ஔ	?	5B	[ஔ	ஔ
3F	? :	ஔ	-	5C	\	ஔ	ஔ
40	@	ஔ	T	5D]	ஔ	ஔ
				5E	^	ஔ	ஔ
				5F	_	ஔ	ஔ
60	`	ஔ	ஔ (ஔ)	6E	n	ஔ	ஔ
61	a	ஔ ^(h)	ஔ	6F	o	ஔ	ஔ
62	b	ஔ	ஔ	70	p	ஔ	ஔ(h)
63	c	ஔ	ஔ	71	q	ஔ	ஔ
64	d	ஔ	ஔ	72	r	ஔ	ஔ
65	e	ஔ	ஔ	73	s	ஔ	ஔ
66	f	ஔ	ஔ	74	t	ஔ	ஔ
67	g	ஔ	ஔ	75	u	ஔ	ஔ
68	h	ஔ	ஔ	76	v	ஔ	ஔ
69	i	ஔ	ஔ	77	w	ஔ	ஔ
6A	j	ஔ	ஔ	78	x	ஔ	ஔ
6B	k	᳚(ஔ)	ஔ	79	y	ஔ	ஔ
6C	l	ஔ	ஔ	7A	z	ஔ	ஔ
6D	m	ஔ	ஔ	7B	{	ஔ	ஔ
				7C		ஔ	ஔ
				7D	}	ஔ	ஔ

(h) denotes hook character.

Program in BASIC for Computer Based Display for English, Hindi, Tamil, etc Languages

```

dim C(3,2048),ad(3,257),d(12),q(8)
open "chtamil2" for random as #1 len=1
field #1, 1 as AS
cls
total%= LOF(1)
for lan%=1 to 3
for i%= 0 to 255 'total%
get #1 'get one byte
rem pick and store the address for all 256
                                codes

a= asc(a$)
' print a;
ad(lan%,i%) = a
rem low address in 00-7F and high add. in 80
                                -FF

n=n+1
next
for i%= 3 to 1024*2 -254'total% -256
get #1
? i%-3,asc(a$)
c(lan%,i%-3)= asc(a$)
next
next lan%
CLOSE #1
lang%=2
on key(1) gosub 500:key(1) on
on key(2) gosub 510:key(2) on
on key(3) gosub 520:key(3) on
ON KEY(11) GOSUB 540: KEY(11) ON
ON KEY(12) GOSUB 550: KEY(12) ON
ON KEY(13) GOSUB 560: KEY(13) ON
ON KEY(14) GOSUB 570: KEY(14) ON
690 CLS: locate 10,15: ?"Type  F1 key for
                                Tamil, F2 for English and F3 Hindi"
? "Want small or large size font ? Press S or
                                L"

ad$= input$(1)
if ad$="S" then screen 12 : goto 700
if ad$="L" then screen 2: goto 700
goto 690
700 cls:  s=0:row=0
i=0
s=1:R=1:L=0
hook=0
2 if lang%=2 then hook=0
if hook=1 then s=s-1
if s<0 then row=row-1: s=40
21 AS=inPUT$(1): 'got a key
N= ASC(AS)
'locate 20,51 :print n
'goto 2
REM remove old cursor
x=s*12:y=row*16+11
for jj%=1 to 10
pset(x+jj%,y),0 :next
if S>40 then s=0 :Row=Row+1
if n=8 then s=s-1:gosub 300 'backspace
if N=32 then s=s+1:gosub cur: goto 2 'space
if N=10 then row = row + 1 :goto 2 'return
if N=13 then row=row +1:s=0: goto 2 'line feed
if lang%=1 then
REM This is for TAMIL HOOK characters
if N=80 then hook=1 :goto 23
if N=112 then hook=1 :goto 23
if N=91 then hook=1 :goto 23

```

```

if N= 123 then hook=1 :goto 23
if N=43 then hook =1:goto 23
if N= 59 then hook=1:goto 23
hook=0
end if
if lang%=3 then gosub 400
' if N= 8 then s=s-1 : goto 300: 'hook=1:
                                goto 23

'if n=28 then s=s+1:goto 300
'if n=30 then row=row+1:goto 2
hook =0
23 n1= ad(lang%,n) :n5=n1
n2=ad(lang%,n+128)
n3=(n2-1)*256 +n1
N1=(n3):
j=0: for i= 0 to 17 step 3
i=i1
d(j) = 16*c(lang%,n1+i) + C(lang%,n1+i+1)\ 16
d(j+1) =256*(c(lang%,n1+i+1) mod 16) +
                                c(lang%,n1+i+2)

j=j+2
next i1 :j=0
for i = 0 to 11
?i; hex$(d(i))
next : ?n,n5,n2
for l =0 to 11
n= d(l):i=0 :k%=15
gosub 10 'put pixels
next l
s=s+1
gosub cur
goto 2
'put cursor
cur:
x=s*12:y=row*16+11
for jj%=1 to 10
pset(x+jj%,y),15 :next
return
end
rem given a number <256*8 put pixels
10 r = n mod 2
? r ;
q(i)=r
x=S*12: y=Row*16+1
100 i=i+1
if i >= 12 then 200
n=n\2
goto 10
200 for j%=0 to 11
if q(11-j%)=0 then pset(x,y),15
x=x+1
next
return
300 for l =0 to 12
x=s*12: y =row *16+l
for j% = 1 to 12
' n= 4096 : i=0
pset (x+j%,y),0
'gosub 40 'put pixels
next j%
next l
goto 2
40 r = n mod 2
? r ;
q(i)=r

```

```

x=S*12: y=Row*16+1
101 i=i+1
if i >= 12 then 201
n=n\2
goto 10
201 s=s-1
for j%=0 to 11
'pset(x,y),0
if q(11-j%)=1 then pset(x,y),0
x=x+1
next
't$=input$(1)
return
500 rem language selection
lang%=1
return
510 lang%=2:return
520 lang%=3:return
REM HINDI HOOKs
400 if n=45 then hook=1:goto 630
if n=61 then hook=1:goto 23 ; The sanskrit
                                hook for word ends
if n=81 then hook=1: goto 23 ; The adjunct to
                                "Pa" to make "PPa"
if n=113 then hook=1 :goto 610 ; The u hook
                                as in Pushpa
if n=65 then hook=1 :goto 23 ; the "n" part of
                                "Gend"
if n=83 then hook=1 : goto 23 ; the Ttha part
                                of kuttha
if n=87 then hook=1: goto 23 ; The OOm
                                symbol as in hoom
if n=90 then hook=1: goto 23 ;as in "rka",
                                the top "rr"
if n=119 then hook=1:goto 620 ; oo as in Koo
if n=97 then hook=1: goto 23 ;dot top as in
                                "mm"
if n=115 then hook=1:goto 23 ; The "Ey"
                                hook as in "Gend"
if n=122 then hook=1: goto 23 ; "Pna" as in
                                APna

return
540 gosub remcur:ROW=ROW-1 :RETURN
550 GOSUB REMCUR :S=S+1: RETURN
560 GOSUB REMCUR: S=S-1:RETURN
570 GOSUB REMCUR: ROW=ROW+1:
                                RETURN

600 rem hindi 13th line hook points
610 x= s*12: y= row*16+12
i =3
pset(x+i,y),15: i=8:pset(x+i,y),15:goto 23
620 x=s*12: y=row*16+12
i =12
pset(x+i,y),15
goto 23
630 x=s*12: y=row*16+12
i=12:
pset(x+i,y),15:goto 23
REMCUR:
x=s*12:y=row*16+11
for jj%=1 to 10
pset(x+jj%,y),0 :next
RETURN

```

dot patterns for the four languages is required to be present in the working directory for the PC based program to work. This file is also proposed to be issued with Sept. 2000 EFY-CD.

Dedicated display unit design

A unit of this type is a low-cost solution for a public display. The circuits described in this section can be assembled on an

integrated single board within a cost of Rs 2,000. The TV display of a 36cm (14-inch) monitor costs less than Rs 1,000 today, and the same video signal can be used for multiple positions.

This involves a simple 8085 microprocessor and an additional CRT controller. The dedicated CRT controller chip 6845 has been popular ever since it was first used by the IBM in its display controller cards. The circuit of this board is shown in Figs 1(a) and 1(b). It comprises:

1. Video generation circuitry including dot and character clocks.
2. Pixel or video RAM.
3. Character dot pattern EPROM for four languages
4. 8085 firmware on EPROM for four languages
5. 6845 CRT controller IC.

Fig. 1(a) shows the 8085 microprocessor and its signals. Crystal of 4 MHz between its pins 1 and 2 provides the clock for the processor to tick and work. Reset pin 36 is connected to get itself reset upon power on. Manual resetting is also possible using reset switch S1. The address-cum-data signal lines AD0-AD7 are connected to a 74LS373 latch to separate the address signals A0-A7, using the ALE pulse from pin 30 of 8085. The data-bus connects to all devices such as EPROMs, RAM, and the 74245 bidirectional transceiver. Some of the data lines are also connected to output port (at I/O address 80) using a 7475 IC for providing four bits of outputs (D0' to D3'). The input port (also at I/O address 80) employing a 74365 caters to six bits of input. The PC keyboard data and clock signals are connected to data bus via two of its input lines.

The Address decoder is a 74156, which has open collector outputs. It enables one or two of the chip select decoded signals to be combined by just joining them (in wired-OR fashion). Using the address lines A12, A11, and A10, the decoder provides eight chip select signals for the address ranges as shown in the figure. Each output covers a 1k memory range. Thus pins 9 and 10 (shorted) serve as the chip select signal for EPROM1 covering a 2k memory address space. (Although we use 2764, an 8k EPROM actually since now-a-days only 8k EPROM ICs are easily available and easily programmable while 2k capacity EPROMs are almost obsolete and difficult to program—we need 25V programming pulse etc.) The address range for EPROM-1 is 0000-07FF. Similarly, pins 11 and 12 are joined together to provide address range from 0800-0FFF. This is the chip select signal for the second EPROM, which stores the character dot patterns for the

PARTS LIST

PARTS LIST	
<i>Semiconductors:</i>	
IC1	- 8085 8-bit microprocessor
IC2, IC21	- 74LS373 octal transparent latch
IC3, IC4	- 2764 8k byte EPROM
IC5	- 6264 8k byte RAM
IC6	- 74LS245 octal transceiver
IC7	- 74LS156 dual 2-line to 4-line decoder
IC8	- 74LS365 8-line to 1-line multiplexer
IC9	- 74LS75 4-bit latch
IC10, IC13	- 74LS02 quad NOR gate
IC11	- 74LS04 hex inverter
IC12, IC14	- 74LS00 quad NAND gate
IC15	- 74LS132 quad NAND Schmitt trigger
IC16	- 6845 CRT controller
IC17, IC18	- 74LS157 quad 2-line to 1-line data selector
IC19	- 74LS244 octal bus buffer/driver
IC20	- 62256, 32k byte static RAM
IC22	- 74LS165 parallel-in shift register
IC23	- 74LS190 synchronous decade counter
T1	- BC148B npn transistor
D1	- 1N4148 switching diode
LED1-LED4	- Red LEDs
<i>Resistors (all 1/4-watt, ±5% carbon, unless stated otherwise):</i>	
R1-R5	- 1-kilo-ohm
R11-R16, R6, R17	- 4.7-kilo-ohm
R7-R10, R22-R23	- 220-ohm
R18, R19	- 10-kilo-ohm
R20	- 220-kilo-ohm
R21	- 680-ohm
VR1	- 470-ohm preset
<i>Capacitors:</i>	
C1, C3	- 1 µF, 16V electrolytic
C2	- 22 pF ceramic disk
<i>Miscellaneous:</i>	
XTAL1	- 4 MHz crystal
PCKBD	- Keyboard interface connector

four languages. This too is a 2764, and the chip select signal ranges only 2k, but the total 8k range is for storing four language dot patterns, each in one 2k range. Thus the selection of the range/language is done by signals from the 7475-output port bits D0' and D1', which are wired to A11 and A12 address lines of the 2764 character generator EPROM, which can be selected using the function keys as explained below.

The input port 80H, using 74365, is for reading the language selection made. The language is selected by pressing keys F1 through F4 on the PC's keyboard. This causes bits D0 and D1 to be output on the 7475 output ports to indicate the selection by two of the LEDs wired at its output. Two other bits, D4 and D5 of this input port, are connected to the data and clock pins of the IBM PC keyboard connector.

The RAM chip 6264 (8k memory) is used in the circuit. However, only 1k (1000-13FF) of its address space is utilised. So, its 'high' address pins A11 and A12 are permanently made 'high'.

A chip-select 1 (CS1) is obtained from pin 6 of the 74156 IC, which covers 1400-17FF address range. This goes to select the video RAM 62256. Though a 62256 of 32k memory is used, only 16k is actually utilised. Its pin 1 is made permanent 'high'. This chip select uses the address lines A0 to A5 having an address range of just 64 bytes, just the low order memory of the video RAM.

A chip-select 2 (CS2) signal is used to select a 74LS373 latch used with the video RAM circuit. This is used to supply the high order addresses (A6 through A13) to the video memory.

An additional chip-select 3 (CS3) signal is used for accessing the 6845 CRT controller to program its mode of operation, so as to get a raster of 312 lines and 50 Hz frame frequency.

In the earlier design by the authors, an ASCII keyboard had been used. This ASCII keyboard used a dedicated keyboard controller IC, and the keys were wired in the fashion of the typewriter keys, making use of switches fixed on to a plain PCB and wiring the contacts to the IC as per its data sheet. There are ICs for making such an ASCII keyboard. The AY3-5376 is one such IC. The ASCII code for the key pressed is output as a 7-bit code by this IC.

In this new design, the authors have used an IBM PC (AT) keyboard. The authors have given such a PC keyboard for their Home Computer Project (Refer EFY Electronics Projects, Vol. 11). This was a keyboard of the older type, the XT keyboard, but now the freely available (for Rs 300) AT keyboard has been employed for the current design.

The keyboard is labeled with English, Hindi, and Tamil characters, as per the standard typewriter format. The format for Hindi and Tamil characters are shown in Fig. 3.

The 8085 generates the control signals $\overline{IO/M}$, \overline{WR} , \overline{RD} (active low signals). These are used in conjunction with 74LS02 and 74LS00 gates shown in Fig. 2(a) to obtain separate read and write control signals for memory or input-output, i.e. \overline{MR} , \overline{MW} , \overline{IOR} , \overline{IOW} for use in the circuit.

To be continued next month

8085 μ P-KIT BASED SIMPLE IC TESTER

S. RAJKUMAR



All electronic laboratories in engineering colleges and other institutions need a digital IC tester to verify the serviceability of frequently used digital ICs, e.g., ICs 7400 (NAND), 7408 (AND), 7432 (OR), 7486 (EXOR), 7404 (Hex Inverter), 7407 (Buffer) etc. The truth tables of all such ICs are available in digital IC data books. Based on their truth tables one can write suitable sub-routines to test them using an 8085 microprocessor kit and a minimal of interface circuitry. An 8085 microprocessor kit, having requisite peripheral devices, is normally available in most electronic labs, and as such one does not have to buy costly IC testers for testing simple type of ICs, as mentioned above.

It is assumed that the kit has at least two 8255 PPI (programmable peripheral interface) ICs whose input/output ports have been extended via suitable connectors, for external usage. The configura-

TABLE I
Control Words

S.No.	Port A	Port C (Upper)	Port B (Lower)	Port C (Lower)	Control Word (Hex)
1	O	O	O	O	80
2	O	O	O	I	81
3	O	O	I	O	82
4	O	O	I	I	83
5	O	I	O	O	88
6	O	I	O	I	89
7	O	I	I	O	8A
8	O	I	I	I	8B
9	I	O	O	O	90
10	I	O	O	I	91
11	I	O	I	O	92
12	I	O	I	I	93
13	I	I	O	O	98
14	I	I	O	I	99
15	I	I	I	O	9A
16	I	I	I	I	9B

Note: O = Output; I = Input

tion of the interface circuit required for testing of the digital 14-pin ICs using 8085 microprocessor kit is shown in Fig. 1. The interface circuit comprises simply a 14-

pin ZIF socket and two hex buffer 7407 ICs. The +5V supply needed for the interface circuit (and ground) is obtained from the kit's power supply itself. The total cost of the interface circuit would be less than Rs 300.

Both the 8255s have been configured for mode '0' operation (which is a basic input/output mode) with registers A and B as output and register C (both upper and lower half) as input. The required control word for the mentioned configuration is 89 hex. The characteristics of mode '0' operation of 8255 are:

1. Two 8-bit ports referred to as registers A and B respectively.
2. Two 4-bit ports referred to as C register (lower-comprising bits C0 through C3) and C register (upper-comprising bits C4 through C7).
3. Ports configured as output have latched outputs while input ports are not latched.

4. Any port can be made input or output. There are 16 possible input/output configurations. (Please refer Table I for a summary of the configurations and the control word required to be used during initialisation of an 8255 for each configuration.) Control word can also be formed with the help of Fig. 2.

The hex buffer/driver IC 7407 has open collector outputs. The outputs of 'IC under test,' which is placed in the ZIF socket, are combined with those of 7407 in a wired-OR (actually wired-AND) fashion. To realise this function, a logic 1 is always output on the 7407 gates connected to output pins of 'IC under test.' All possible logic input combinations are given to input pins of 'IC under test,' while logic 1 is placed at all its output pins via 8255's registers A and B, through IC 7407 buffers. For each input combination, the logic state of the ZIF socket pins (as modified by the 'IC under test') is read (after a short delay) via 'C' registers of the two 8255s. The expected results for each combination of inputs, for above-mentioned ICs, are shown in Table II in hex digits. These are stored in memory, in consecu-

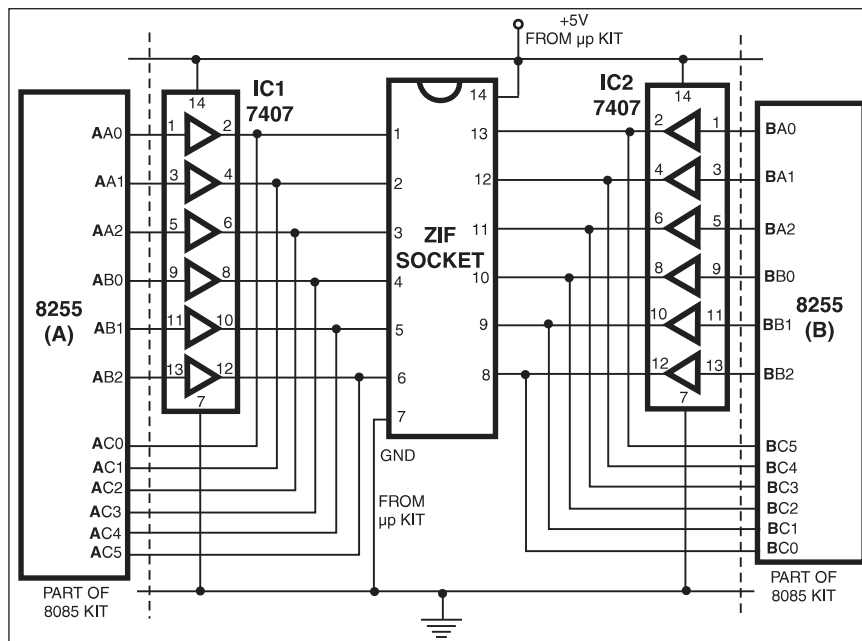


Fig. 1: Circuit for interfacing IC under test to 8255 PPIs on 8085 microprocessor kit

IC Tester Program Environment

MEMORY MAP (MAY VARY FROM KIT TO KIT):
 RAM LOCATIONS USED FOR PROGRAM : 9200H - 9450H
 STACK POINTER INITIALISED : 9FFFH
 PORTA (OUTPUT) OF A8255/B8255 : 08/10
 PORTB (OUTPUT) OF A8255/B8255 : 09/11
 PORTC (INPUT) OF A8255/B8255 : 0A/12
 CONTROL WORD REGISTER OF A8255/B8255 : 0B/13

PROGRAM LISTING

Add.	Opcode	Label	Mnemonics	Comments
9200	31FF9F		LXI SP,9FFFH	
9203	21A093		LXI H,93A0H	
9206	3E00		MVI A,00H	
9208	0600		MVI B,00H	
920A	CD160B*		CALL OUTPT	; (UTILITY SUBROUTINE IN THE KIT ; TO DISPLAY ACC CONTENT)
920D	CD640A*		CALL RDKBD	; (UTILITY SUBROUTINE IN THE KIT ; TO ACCEPT ONE HEX DIGIT FROM THE ; KEYBOARD AND STORE IN THE ACC)
9210	0E04		MVI C,04H	
9212	07	A:	RLC	; SHIFTED TO SECOND(TENS) PLACE
9213	0D		DCR C	
9214	C21292		JNZ A	
9217	325094		STA 9450H	
921A	CD640A		CALL RDKBD	; (UTILITY SUBROUTINE IN THE KIT ; TO ACCEPT ONE HEX DIGIT FROM ; THE KEYBOARD AND STORE IN ; THE ACC)
921D	215094		LXI H,9450H	; COMBINE TWO KEYBOARD ENTRIES
9220	86		ADD M	
9221	47		MOV B,A	
9222	210093		LXI H,9300H	
9225	FE00		CPI 00H	; (NAND IC)
9227	CA5E92		JZ TYPE1	
922A	211093		LXI H,9310H	
922D	FE08		CPI 08H	; (AND IC)
922F	CA5E92		JZ TYPE1	
9232	212093		LXI H,9320H	
9235	FE32		CPI 32H	; (OR IC)
9237	CA5E92		JZ TYPE1	
923A	213093		LXI H,9330H	
923D	FE86		CPI 86H	; (EXOR IC)
923F	CA5E92		JZ TYPE1	
9242	214093		LXI H,9340H	
9245	FE04		CPI 04H	; (NOT IC)
9247	CA7592		JZ TYPE2	
924A	215093		LXI H,9350H	
924D	FE07		CPI 07H	; (BUFFER IC)
924F	CA7592		JZ TYPE2	
9252	216093		LXI H,9360H	
9255	FE02		CPI 02H	; (NOR IC)
9257	CA9092		JZ TYPE3	
925A	76		HLT	; IN SOME 8085 KITS SUCH AS THAT FROM DYNALOG ; PROGRAM IS TERMINATED WITH 'RST1' IN PLACE OF 'HLT'
; NAND, AND, OR, EXOR GATE CHECK				
925E	0E00	TYPE1:	MVI C,00H	; SET GATE INPUTS
9260	79	LP1:	MOV A,C	
9261	F604		ORI 04H	; SET GATE OUTPUT 1
9263	47		MOV B,A	; STORE GATE INPUTS FOR I/P & O/P PINS IN REG B
9264	CDB192		CALL PROCESS	
9267	0C		INR C	; NEXT INPUT COMBINATION
9268	79		MOV A,C	
9269	FE04		CPI 04H	; CHECK IF ALL INPUT COMBINATIONS ARE OVER
926B	C26092		JNZ LP1	
926E	C3EB92		JMP GOOD	; OR JMP GOOD1
; BUFFER, INVERTER CHECK				
9275	0E00	TYPE2:	MVI C,00H	; SET GATE INPUT
9277	79	LP2:	MOV A,C	
9278	F602		ORI 02H	; SET GATE OUTPUT 1
927A	47		MOV B,A	; STORE GATE INPUT FOR I/P & O/P PINS IN B
927B	CDB192		CALL PROCESS	

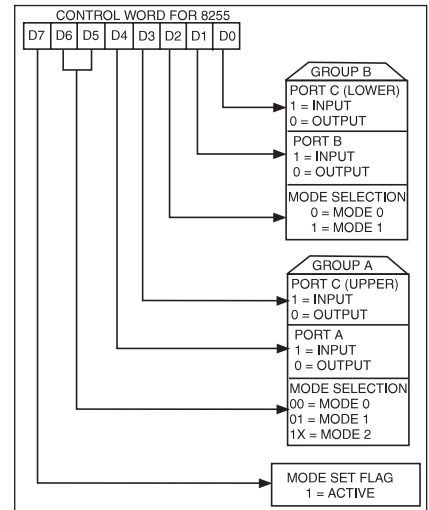


Fig. 2: Control word logic diagram for mode

tive locations for each IC, for every combination of inputs. If actual data read tallies with the stored data for all combinations of inputs, message 'GOOD' is displayed on the kit's display. If any of the result fails, i.e. if any of the gates is not working properly, message 'BAD' is displayed on the 8085 kit.

For convenience, the ICs having identical input/output pins and requiring identical input combinations, have been grouped under one type. (7400, 7408, 7432, and 7486 have been grouped as 'Type 1', while 7404 and 7407 have been grouped as 'Type 2', and 7402 as 'Type 3'.)

When the software program (modified at EFY for working on Dynalog's Micro Friend-ILC-V2 kit) is executed on the 8085 kit, the display shows 'ICIC'. Now enter the last two digits of the IC number to be tested (the last but one followed by the last one, for instance, for IC 7404 enter 0 followed by 4). Please take care to place the IC in the ZIF socket with proper orientation and press 'Next'. Depending on performance of all the gates of 'IC under test', the message 'GOOD' or 'BAD' will appear on its display.

For addressing peripheral devices (8255, 8279), I/O mapped address scheme has been employed. At EFY, the addresses have been modified in accordance with the Dynalog kit used for the purpose. Other users would need to modify the program address space as well as input-output addresses for the peripherals suitably, in accordance with the specific kit used by them. Such opcodes which are input-output address dependent have been annotated with an asterisk mark. The al-


```

927E 0C          INR C          ; NEXT INPUT COMBINATION
927F 79          MOV A,C
9280 FE02        CPI 02H ; CHECK IF ALL INPUT COMBINATIONS ARE OVER
9282 C27792      JNZ LP2
9285 C3EB92      JMP GOOD          ; OR JMP GOOD1
;NOR GATE CHECK
9290 0E00        TYPE3: MVI C,00H ; SET GATE INPUTS
9292 79          LP3:  MOV A,C
9293 07          RLC
9294 F601        ORI 01H          ; SET GATE OUTPUT 1
9296 47          MOV B,A
9297 CDB192      CALL PROCESS
929A 0C          INR C          ; NEXT INPUT COMBINATION
929B 79          MOV A,C
929C FE04        CPI 04H ; CHECK IF ALL INPUT COMBINATION ARE OVER
929E C29292      JNZ LP3
92A1 C3EB92      JMP GOOD          ; OR JMP GOOD1
92B1 3E89        PROCESS: MVI A,89H ; (8255 CONTROL WORD FOR CONFIGURING REG.
; A & B AS O/P AND REG. C (LOWER 4 BITS &
92B3 D30B*       OUT 0BH          ; UPPER 4 BITS) AS I/P)
92B5 D313*       OUT 13H
92B7 78          MOV A,B
92B8 D308*       OUT 08H ;OUTPUT THE COMBINATION FROM PORT A(A8255)
92BA D309*       OUT 09H ;OUTPUT THE COMBINATION FROM PORT B(A8255)
92BC D310*       OUT 10H ;OUTPUT THE COMBINATION FROM PORT A(B8255)
92BE D311*       OUT 11H ;OUTPUT THE COMBINATION FROM PORT B(B8255)
92C0 16FF        MVI D,FFH          ; DELAY
92C2 15          LP4:  DCR D
92C3 C2C292      JNZ LP4
92C6 DB0A*       IN 0AH          ; READ DATA INTO PORT C OF A8255
92C8 E63F        ANI 3FH          ; DON'T CARE FOR BIT 7 & 8
92CA BE          CMP M          ; COMPARE RESULT WITH DATA IN MEMORY
92CB C2DA92      JNZ BAD          ; OR JMP BAD1
92CE 23          INX H
92CF DB12*       IN 12H          ; READ DATA INTO PORT C OF B8255
92D1 E63F        ANI 3FH          ; DON'T CARE FOR BIT 7 & 8
92D3 BE          CMP M          ; COMPARE RESULT WITH DATA IN MEMORY
92D4 C2DA92      JNZ BAD          ; OR JMP BAD1
92D7 23          INX H
92D8 C9          RET
;RESULT DISPLAY USING 8279(BAD)
92DA 3E04*       BAD:  MVI A,04H
92DC D301*       OUT 01H
92DE 3E7F*       MVI A,7FH          ; 7 SEG CODE-B
92E0 D300*       OUT 00H
92E2 3E77*       MVI A,77H          ; 7 SEG CODE-A
92E4 D300*       OUT 00H
92E6 3E3F*       MVI A,3FH          ; 7 SEG CODE-D
92E8 D300*       OUT 00H
92EA 76          HLT
;RESULT DISPLAY USING 8279(GOOD)
92EB 3E04*       GOOD: MVI A,04H
92ED D301*       OUT 01H
92EF 3E3D*       MVI A,3DH          ; 7 SEG CODE-G
92F1 D300*       OUT 00H
92F3 3E5C*       MVI A,5CH          ; 7 SEG CODE-O
92F5 D300*       OUT 00H
92F7 3E5C*       MVI A,5CH          ; 7 SEG CODE-O
92F9 D300*       OUT 00H
92FB 3E3F*       MVI A,3FH          ; 7 SEG CODE-D
92FD D300*       OUT 00H
92FE 76          HLT
@ ;RESULT DISPLAY USING UTILITY SUBROUTINE OF KIT AT EFY(BAD)
9370 31FF9F      BAD1: LXI SP,9FFFH
9373 210094      LXI H,9400H
9376 3E00        MVI A,00H
9378 0600        MVI B,00H
937A CD160B      CALL OUTPT          ; (UTILITY SUBROUTINE IN THE KIT TO
; DISPLAY ACC CONTENT)
937D 76          HLT
@ ;RESULT DISPLAY USING UTILITY SUBROUTINE OF KIT AT EFY(GOOD)

```

www.electronicsforu.com

a portal dedicated to electronics enthusiasts

```

9380 31FF9F      GOOD1:LXI SP,9FFFH
9383 211094      LXI H,9410H
9386 3E00        MVI A,00H
9388 0600        MVI B,00H
938A CD160B      CALL OUTPT      ; (UTILITY SUBROUTINE IN THE KIT TO
; DISPLAY ACC CONTENT)

938D 76          HLT

;DATA TABLE
;NAND      ;AND      ;OR      ;EXOR      ;NOT      ;NOR
9300 24      9310 00      9320 00      9330 00      9340 2A      9360 09
9301 09      9311 00      9321 00      9331 00      9341 15      9361 26
9302 2D      9312 09      9322 2D      9332 2D      9342 15      9362 12
9303 2D      9313 24      9323 2D      9333 2D      9343 2A      9363 12
9304 36      9314 12      9324 36      9334 36      9344 2A      9364 24
9305 1B      9315 12      9325 1B      9335 1B      ;BUFFER      9365 09
9306 1B      9316 3F      9326 3F      9336 1B      9350 00      9366 36
9307 36      9317 3F      9327 3F      9337 36      9351 00      9367 1B
;          ;          ;          ;          ;          ;
;          ;          ;          ;          ;          ;
;ICIC      ;BADD      ;GOOD
93A0 0C      ;          9400 0D      9410 0D
93A1 01      9401 0D      9411 00
93A2 0C      9402 0A      9412 00
93A3 01      9403 0B      9413 0C

SYMBOL TABLE :
A          9212          TYPE1 925E LP1 9260          TYPE2 9275
LP2        9277          TYPE3 9290 LP3 9292          PROCESS 92B1
LP4        92C2          BAD 92E0          GOOD 92F5          BAD1 9370
GOOD1      9370
    
```

NOTE: 1. * INDICATES THAT OPCODE IS DEPENDENT ON I/O ADDRESS USED IN THE SPECIFIC KIT
2. @ INDICATES THE ROUTINE MODIFIED BY EFY FOR DYNALOG KIT

 


Fig. 3: PCB layout for interface

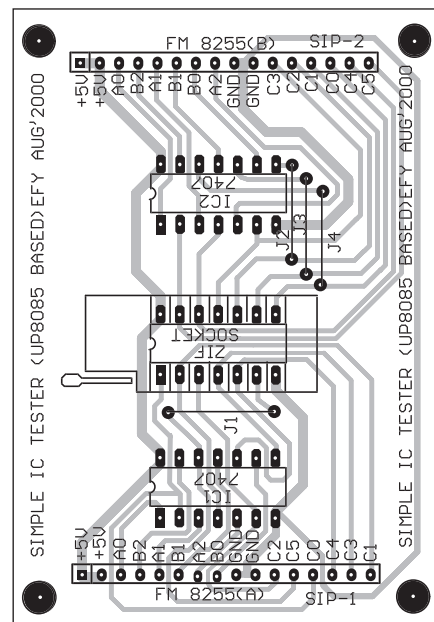


Fig. 4: Component layout for PCB

TABLE II: LOGIC STATES OF 8255 PORTS														
ZIF Socket Pin No.	8255 (A)						HEX	8255 (B)						HEX
	6	5	4	3	2	1		C5	C4	C3	C2	C1	C0	
Reg. C Ports	C5	C4	C3	C2	C1	C0	Eq.	A0	A1	A2	B0	B1	B2	Eq.
Reg. A/B Ports	B2	B1	B0	A2	A1	A0	Eq.	A0	A1	A2	B0	B1	B2	Eq.
IC Description	O	I ₂	I ₁	O	I ₂	I ₁		I ₁	I ₂	O	I ₁	I ₂	O	
NAND (7400) (Type 1)	1	0	0	1	0	0	24	0	0	1	0	0	1	09
	1	0	1	1	0	1	2D	1	0	1	1	0	1	2D
	1	1	0	1	1	0	36	0	1	1	0	1	1	1B
	0	1	1	0	1	1	1B	1	1	0	1	1	0	36
AND (7408) (Type 1)	0	0	0	0	0	0	00	0	0	0	0	0	0	00
	0	0	1	0	0	1	09	1	0	0	1	0	0	24
	0	1	0	0	1	0	12	0	1	0	0	1	0	12
	1	1	1	1	1	1	3F	1	1	1	1	1	1	3F
OR (7432) (Type 1)	0	0	0	0	0	0	00	0	0	0	0	0	0	00
	1	0	1	1	0	1	2D	1	0	1	1	0	1	2D
	1	1	0	1	1	0	36	0	1	1	0	1	1	1B
	1	1	1	1	1	1	3F	1	1	1	1	1	1	3F
Ex-OR (7486) (Type 1)	0	0	0	0	0	0	00	0	0	0	0	0	0	00
	1	0	1	1	0	1	2D	1	0	1	1	0	1	2D
	1	1	0	1	1	0	36	0	1	1	0	1	1	1B
	0	1	1	0	1	1	1B	1	1	0	1	1	0	36
Invertor (7404) (Type 2)	O	I	O	I	O	I		I	O	I	O	I	O	
	1	0	1	0	1	0	2A	0	1	0	1	0	1	15
	0	1	0	1	0	1	15	1	0	1	0	1	0	2A
Buffer (7407) (Type 2)	0	0	0	0	0	0	00	0	0	0	0	0	0	00
	1	1	1	1	1	1	3F	1	1	1	1	1	1	3F
NOR (7402) (Type 3)	I ₂	I ₁	O	I ₂	I ₁	O		O	I ₂	I ₁	O	I ₂	I ₁	
	0	0	1	0	0	1	09	1	0	0	1	0	0	26
	0	1	0	0	1	0	12	0	1	0	0	1	0	12
	1	0	0	1	0	0	24	0	0	1	0	0	1	09
	1	1	0	1	1	0	36	0	1	1	0	1	1	1B

I = INPUT; O = OUTPUT; Hex Eq = Hex digits read via Reg. C
Note:- Pin 7 of ZIF socket is connected to ground and pin 14 is connected to +5V.

ternate result-indicating subroutines specifically used at EFY lab during testing are also included for benefit of the readers. The complete details of address space used for the program and peripheral devices are given before the actual program. The program is self-explanatory, with suitable comments added wherever required.

Although hardware interface circuit can be assembled easily on a general-purpose PCB, nevertheless an actual-size single-sided PCB pattern for the same is shown in Fig. 3 and its component layout is given in Fig. 4. □

LOW-COST PCO BILLING METER

DHURJATI SINHA



The circuit presented here can be used in PCOs for displaying the actual bill. The overall cost of this circuit is less than Rs 200 while a commercial equipment serving similar pur-

pose may cost more than Rs 10,000 in the market. The comparative disadvantages of the presented circuit are as follows:

1. The calculator used along with this circuit is required to be switched 'on' manually before making a call.

2. Certain manual entries have to be made in the calculator; for example, for a pulse rate of Rs 1.26, number 1.26 is to be entered after switching 'on' the calculator followed by pressing of '+' button twice. However, possibility exists for automating these two functions by using additional circuitry.

In telephony, on-hook condition is represented by existence of 48V to 52V across the line. Similarly, the off-hook condition is represented by the line voltage dropping to a level of 8V to 10V (depending upon the length of the local lead line from telephone exchange to the subscriber's premises as well as upon the impedance of telephone instrument). Handset is normally lifted either for dialing or in response to a ring.

In the circuit shown in Fig. 1, when the handset is off-hook, the optocoupler MCT2E (IC1) conducts and forward biases transistor T1, which, in turn, forward biases transistor T2 and energises relay RL1. In energised condition of relay, the upper set of relay contacts connects the positive supply rail to PLL (phase-locked loop) IC2 (LM567) pin 4, while the lower set of relay contacts couples the positive telephone lead to input pin 3 of LM567 via capacitor C1 and resistor R3.

The negative telephone lead is permanently capacitively coupled via capacitor C2. As soon as call matures, 16kHz tone pulses would be pumped into the telephone line by



the telephone exchange at suitable intervals. This interval depends on the pulse rate of the place called and also the time of the day and whether it's a working-day or holiday. On receipt of 16kHz pulse, output pin 8 of IC LM567 (which is tuned for centre frequency of 16 kHz) goes 'low' for the duration of the pulse. The output of IC2 is coupled via transistor T3 to optocoupler IC3. The output of this optocoupler is used to bridge the '=' button on a calculator (such as Taksun make), which has the effect of pressing the '=' button of the calculator.

Considering that pulse rate for a specific town/time/day happens to be Rs 1.26 per pulse, then before maturity of the call one enters 1.26 followed by pressing of '+' key twice. Now, if a total of ten billing pulses have been received from exchange for the duration of the call, then on completion of the call, the calculator display would show 12.60. The telephone operator has to bill the customer Rs 14.60 (Rs 12.60 towards call charges plus Rs 2.00 towards service charges).

For tuning of the PLL circuit around IC2, lift the handset and inject 16kHz tone across the line input points. Tune IC2 to centre frequency of 16 kHz with the help of preset VR1. Proper tuning of the PLL will cause LED1 to glow even with a very low-amplitude 16kHz tone.

EFY Lab note. Arrangement used for simulating a 16kHz pulsed tone is shown in Fig. 2. Push-to-on switch is used for generation of fixed-duration pulse for modulating and switching on a 16kHz oscillator.

 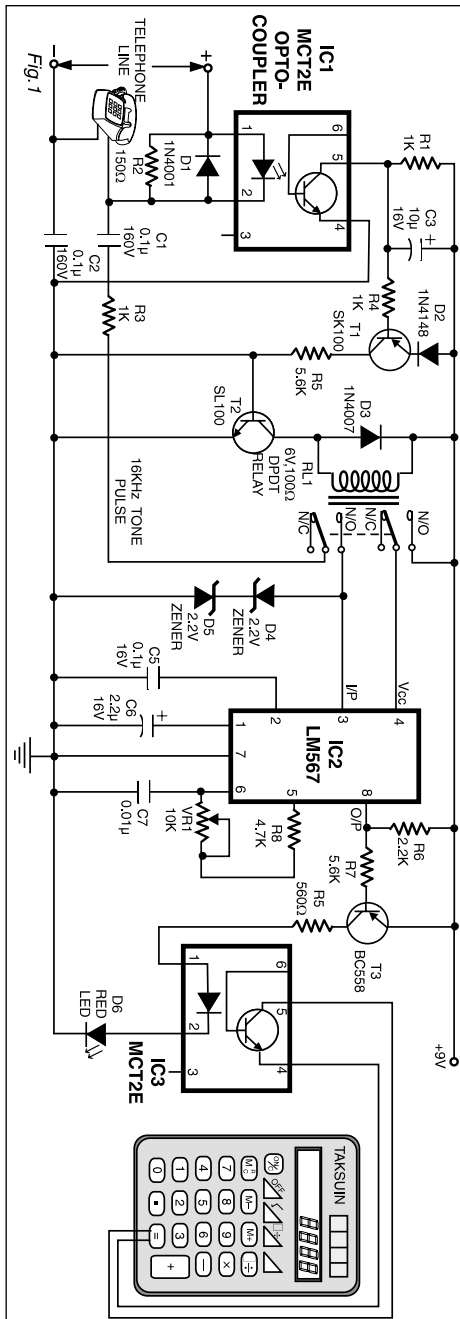For more details regarding pulse rates, pulse codes, etc, readers are advised to go through the tariff rates and pulse code information given in the beginning pages of telephone directories, such as MTNL, Delhi directory, Vol. I. One may also dial 183 for getting more details.



AUTOMATIC MUTING CIRCUIT FOR AUDIO SYSTEMS




SUNISH P.

Fig. 1 shows a muting circuit, which makes use of IC LB1403. Signal from any pre-amplifier, such as HA1032, LA3161, or LA3160, is connected to the base of amplifier transistor T1. Variable resistor VR1 is used to control the gain of input signal.

Comparator 2 output at pin 2 of LB1403 is used for generation of muting signal at the emitter (point A) of transistor T2, which can be directly connected to muting pin 4 of amplifier employing IC LA4440. As long as the audio input to the circuit of Fig. 1 is below a certain level (say,

150 mV peak to peak), the output at point A will be high (the value measured at EFY Lab was around 4.5V). Once the input crosses this threshold level, the output will be around 0V. Capacitor C4 de-

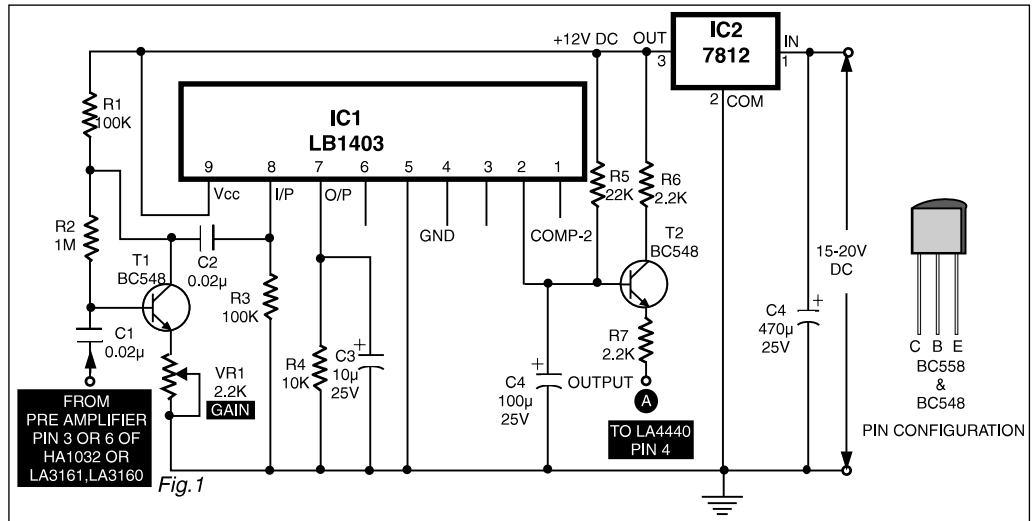termines the 'on'/'off' muting delay. Higher the value of this capacitor,



greater will be the muting delay period.

Slight circuit modification will be needed if this circuit is used with STK series amplifiers, such as STK 4141, 4142, 4152, and 4191, because they need nega-

 


Fig. 2

tive polarity voltage for muting. The additional circuit to be connected at point A in that case is shown in Fig. 2.

2-LINE INTERCOM-CUM-TELEPHONE LINE CHANGEOVER CIRCUIT



J. SRINIVASAN

The circuit presented here can be used for connecting two telephones in parallel and also as a 2-line intercom.

Usually a single telephone is connected to a telephone line. If another telephone is required at some distance, a parallel line is taken for connecting the other telephone. In this simple parallel line operation, the main problem is loss of privacy besides interference from the other

phone. This problem is obviated in the circuit presented here.

Under normal condition, two telephones (telephone 1 and 2) can be used as intercom while telephone 3 is connected to the lines from exchange. In changeover mode, exchange line is disconnected from telephone 3 and gets connected to telephone 2.


For operation in intercom mode, one has to just lift the handset of phone 1

and then press switch S1. As a result, buzzer PZ2 sounds. Simultaneously, the side tone is heard in the speaker of handset of phone 1. The person at phone 2 could then lift the handset and start conversation. Similar procedure is to be followed for initiation of the conversation from phone 2 using switch S2. In this mode of operation, a 3-pole, 2-way slide-switch S3 is to be used as shown in the figure.

In the changeover mode of operation, switch S3 is used to changeover the telephone line for use by telephone 2. The switch is normally in the intercom mode and telephone 3 is connected to the exchange line. Before changing over the

change line to telephone 2, the person at telephone 1 may inform the person at telephone 2 (in the intercom mode) that he is going to changeover the line for use by him (the person at telephone 2). As soon as changeover switch S3 is flipped to the other position, 12V supply is cut off and telephones 1 and 3 do not get any voltage or ring via the ring-tone-sensing unit.

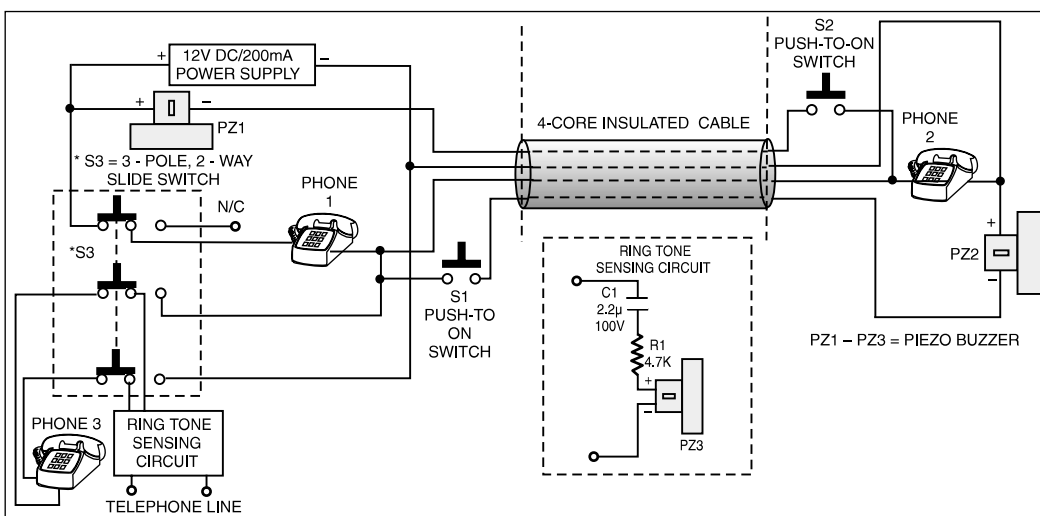Once switch S3 is flipped over for use of exchange line by the person at telephone 2, and the same (switch S3) is not flipped back to normal position after a telephone call is over, the next telephone call via



exchange lines will go to telephone 2 only and the ring-tone-sensing circuit will still work. This enables the person at phone 3 to know that a call has gone through. If

the handset of telephone 3 is lifted, it is found to be dead. To make telephone 3 again active, switch S3 should be changed over to its normal position.

GUARD FOR REFRIGERATORS AND AIR-CONDITIONERS

THOMAS SEBASTIAN




A myriad of circuits have appeared in EFY for protection of refrigerators and air-conditioners against voltage fluctuations and brown-outs. Here is a useful and economic cir-

cuit blending three features, namely, under-/over-voltage protection, switch 'on' delay, and regulation.

The circuit with commonly available components is a combination of familiar

building blocks. The ladder resistance-trimpot configuration in conjunction with modified bridge comparator ensures reliable sequential operations of boosting, low-voltage cut-in, bucking, and high-voltage cut-off.

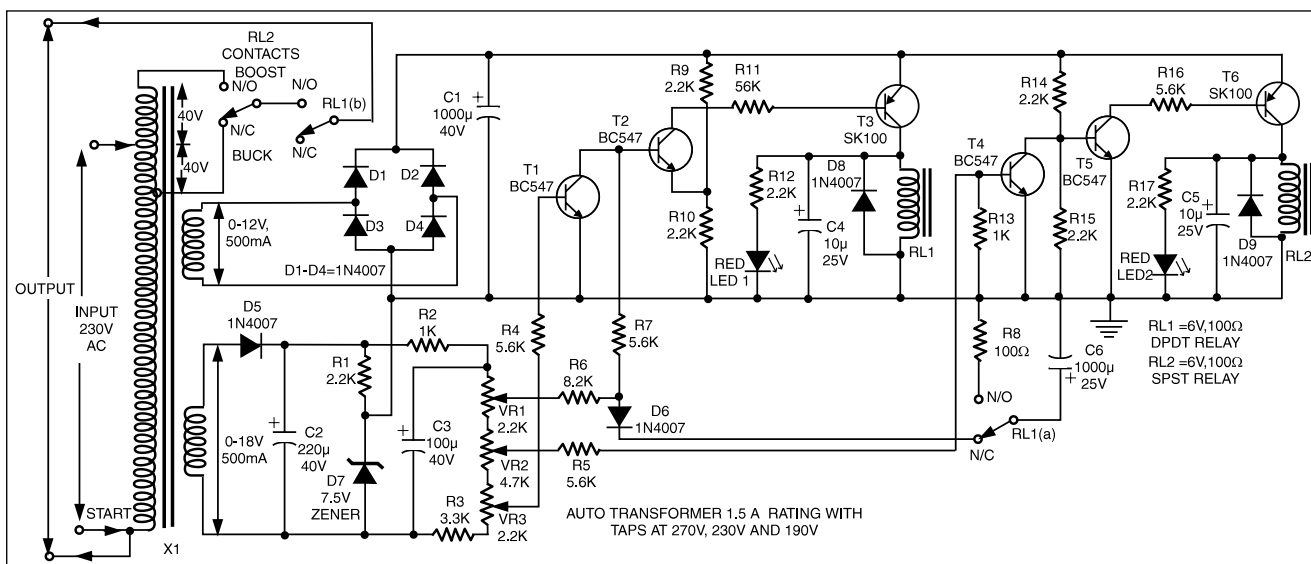When the input line voltage is above 140V, relay RL2 energises and the boosted voltage appears at the N/O contact RL1(b) of relay RL1. However, relay RL1 remains de-energised under two conditions: first, if the input is below 170V threshold voltage (being controlled by trimpot VR1), and second, due to the initial shunting effect of capacitor C6 at the base junction of



transistor T2. The transistor T2 will be enabled only when the charging capacitor raises its base potential to overcome the reverse bias voltage at its emitter. Thus, capacitor C6 and resistor R6 determine the duration of the on-delay, which is approximately three minutes for the given values.

As soon as relay RL1 energises due to the switching action of transistor T2, the boosted voltage appears at the output. The adjustment of trimpot VR2 controls the

bucking point. The output is isolated when the input reaches prohibitive voltage (say 270V), over-voltage sensing being controlled by trimpot VR3 to saturate transistor T4, which, in turn, cuts off relay RL1 via transistors T5 and T6. As a consequence, no output is available from the auto-transformer.

The resistor R8 discharges the timing capacitor C6 when RL1 energises. This is done to ensure that when capacitor C6 is connected back to the base junction

of transistor T2, on resumption after a power failure or an over-voltage condition, repeatability of on-delay is taken care of.

By selecting the current rating of relay contacts (5A or 30A) and auto-transformer (500VA or 4000VA), the circuit can be adapted suitably for a refrigerator or air-conditioner to obtain a regulation of 200V to 240V for an input variation of 170V to 270V.

RADIO-BAND-POSITION DISPLAY

M.K. CHANDRA MOULEESWARAN




This circuit is an add-on unit for radio receivers that lack band-position display. The circuit presented here can show up to nine bands.

It also incorporates a novel feature to make the display dance (blink) with the audio level from the receiver. The power-supply for the circuit can also be derived from the radio-set.

The conversion of selected channel to BCD format is achieved using diodes D1 through D15 in conjunction with resistors R4 to R7. The voltages developed across these resistors (R4 through R7) serve as logic inputs to BCD inputs of BCD to 7-segment decoder IC1 (CD4511). When all switches are in 'off' state, the voltage across resistors R4 through R7 is logic zero, but when any of the switches S1 through S9 is slid to 'on' position, the output across these resistors changes to output proper BCD code to represent the selected channel. This BCD code is converted to 7-segment display by IC1. By

this arrangement of diodes, the need for another decimal-to-BCD converter IC and associated parts is obviated. Switches S1 through S9 are actually parts of existing

wired around transistors T1 and T2. A small part of the audio signal from the speaker terminals is applied to rectifier diode D16 and filter capacitor C1 to produce a pulsating DC across preset VR1. The sliding contact of preset VR1 is connected to the base of emitter-follower stage comprising transistor T2. The output of transistor T2, as amplified by transistor T1, is connected to pin 4 of IC1. Thus turning 'on/off' of display is con-

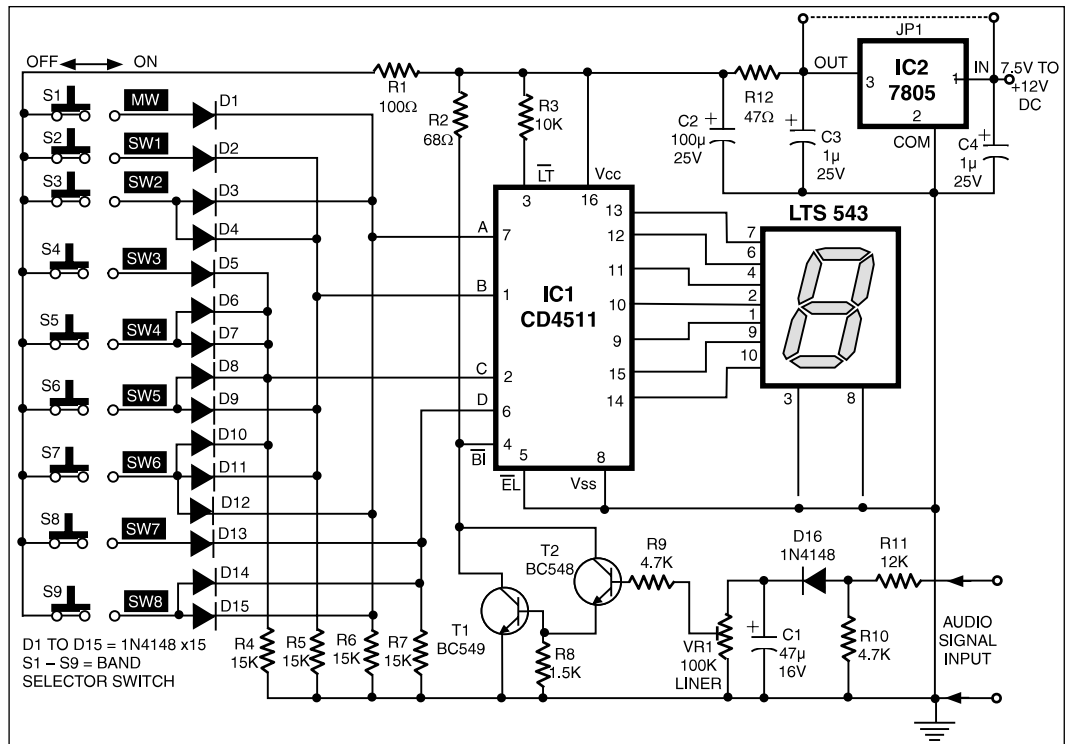

band-switch of the radio. Usually, one or two changeover contacts would be found extra in the modular pushbutton-type band-switches of the radios.

IC1's display blanking pin 4 is connected to a display-blinker-control circuit

trolled by the pulsating voltage developed from audio output of radio.

The power-supply regulator stage is needed only when radio power-supply is greater than 6V DC.

September

2000

DISPLAY SCHEMES FOR INDIAN LANGUAGES—PART II

(HARDWARE AND SOFTWARE)

K. PADMANABHAN, S. ANANTHI, K. CHANDRASEKHARAN,
AND P. SWAMINATHAN

The 6845 is a programmable CRT controller, which can be programmed so as to generate a raster with the desired number of horizontal and vertical raster lines [refer Fig. 1(b)]. For detailed explanation of its programming method for an application using 6845 CRT, you can refer chapter 16 of the book 'Learn to Use Microprocessors' published by EFY.

There are two registers in the 6845, which are selected with the help of ad-

dress line A0. When A0 and CS3 are low (selected), the program code accesses the first register. If A0 is high and CS3 is low, the second of the two registers is accessed. In addition, the 6845 has 16 internal registers. The selection of the internal registers for writing is done via the first register while the second register is written with the data to be transferred into the selected register.

Here, we need 16 lines for a character slot. The width of each character slot is

only 8, because that is what the shift register can handle. But our multilingual characters themselves are written in a font of size 12 x 16. Therefore the characters classification for the 6845 does not really mean the actual characters shown, because we have to use one-and-a-half character slots for each of the multilingual character.

This was the problem faced earlier while attempting use

of CRT controller chip (6845). Therefore the authors went in to design a separate CRT controller circuit using discrete CMOS ICs, which was successfully tested. Later, at the behest of EFY (proposing use of dedicated chips to make it a standalone compact project), the authors developed the present modified circuit using the 6845 CRT controller itself.

Once programmed, the 6845 CRT generates the vertical and horizontal sync signals for the raster at pins 39 and 40, respectively. The 6845 also provides MA0-MA13 signals for addressing the video memory. The video memory is used here to store the dot patterns for the data displayed on the TV screen. The video memory address lines and raster address lines have been used as under:

MA0-MA5 (6 lines) .. To choose one of 64 character slots in every character row.

RA0-RA3 (4 lines) .. To select one among the 16 lines on each such row.

MA6-MA9 (4 lines) .. To select one of the 16 character rows on screen.

During each character row, the 16 row lines are selected using RA0-RA3 signals, which are sequentially incremented from 0 to 15. This mode of wiring the CRT controller to the video memory is not the usual one. It is unlike the one referred to in chapter 16 of 'Learn to Use Microprocessors' book mentioned earlier. There, the MA0, MA1, ...lines address the video RAM, but the video RAM data goes to the character generator. The character generator gets the RA0-RA3, to let it know which line of the character the data is to be output at any instant—because there are many lines of dots for each character. Here the character generator is not used, but the video RAM directly stores the dot points of the display text. They are written by the program into the video RAM. Here RA0-RA3 are the four line-count signals L1 to L4 for the 16 lines, which are the heights of each Indian language character (here it includes English as well).

The four row-count signals MA6-MA9 are used here for generating 16 rows of text per screen. At the end of the 64th character byte (representing 43rd character) display, the display enable signal is blanked. This is to cater to the horizontal flyback period. The sync signal for the video output is obtained by combining the H-sync and V-sync outputs from pins 39 and 40 of CRT via two resistors (of 10k

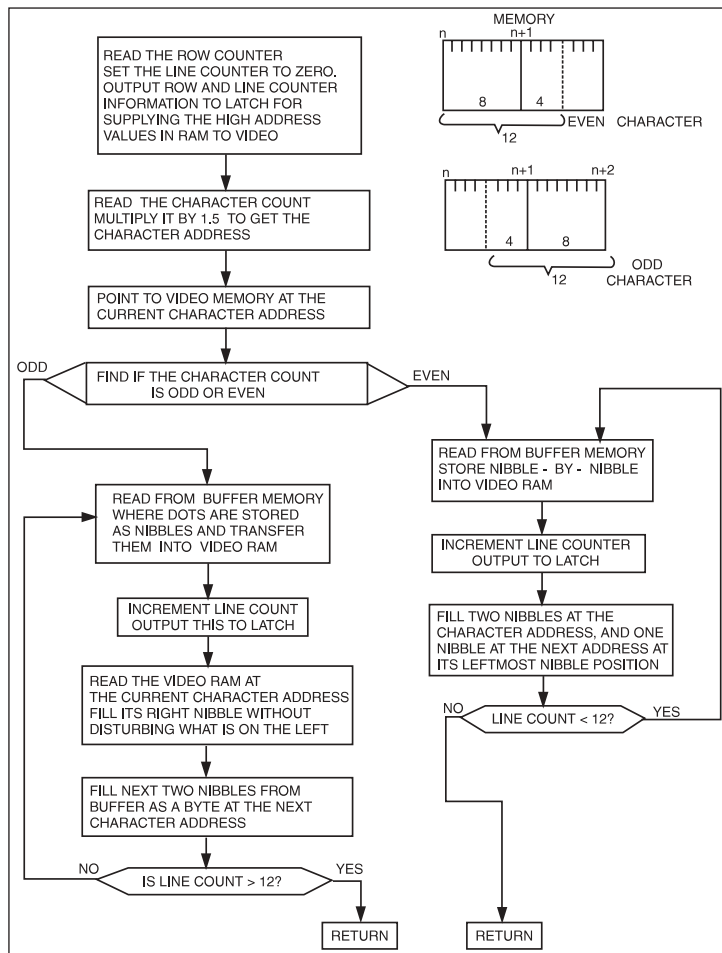


Fig. 4: Video RAM storage flowchart

 


Fig. 5: Actual-size, component-side track layout for the schematic diagram of Fig. 1

each) and then coupling it to the base of transistor BC148B to invert the sync signals at its collector.

The video signal is the dot pattern

obtained from the shift register IC 74LS165. This register is loaded at each character-clock beginning. The shifting is accomplished by the dot clock. Pin 7 of IC

74LS165 outputs the dot pattern. This is combined with the sync signal at the collector of transistor BC148B using a diode and a series resistor. Composite video output is available for connection to the TV monitor from the collector of transistor BC148B.

Video RAM. The 62256 is a 32k x 8-bit static RAM; but only 16k address space has been used here, which makes for a raster of 512 x 256 pixels, or 128k pixels, or 128/8=16kB. The RAM 62256 has A0-A13 address lines for its 16k capacity. The MA0-MA5, the character-count outputs, are given to its first six address pins A0-A5. Either the 8085 or these character-count signals can select these low-order video memory addresses. A set of quad 2-line to 1-line data selector ICs 7 and 8 (74157) is used under control of CS1 (not $\overline{CS1}$) to switch between them. Normally, the MA0-MA5 lines have access so as to continuously display the video memory contents, but when the 8085 writes fresh data, it switches to A0-A5.

Memory access of the video RAM is done on the basis of a high-order address and a low-order address. The eight high-order address values are written into 74LS373 latch (IC21) by the 8085 using CS2. The output enable of this latch is under control of $\overline{CS1}$, so that the data previously written into this latch can be accessed when $\overline{CS1}$ is enabled (active low). The latched outputs of IC21 are for selecting the A6 to A13 pins of the video memory.

By this scheme of low-order and high-order addressing, the memory group of 16k of video RAM is conveniently accessed by just 2k space of the 8085's memory area. Further, it also facilitates software writing. The high address data is that of the row and line-select information. These are decided by the software based on what row of character and which line of that row is to be filled from the character code EPROM, as a specific key is depressed. The character slot information in any row is then written by a memory write into the low-order address of the RAM.

By using 74LS373, the data into the latch is written with its output in tri-state condition (pin 1 high). When pin 1 of 74LS373 is enabled (low), the RAM chip is written with the character slot data by the 8085 into its low-order address. Normally, the lines RA0-RA3 and MA6-MA9

 


Fig. 6: Actual-size, solder-side track layout

are extended by buffer IC 74LS244 to the RAM high address lines if CS1 is low. If CS1 goes high, the buffer is tri-stated at its output, allowing the latch (74LS373)

data to reach the address lines A6-A13 of the video RAM chip. In this way, the video RAM is addressable by both the CRTC 6845 circuitry as well as the 8085, when

a new key is typed.

The data bus lines are likewise connected by a 74LS245 bidirectional buffer. The pixel data for the typed-in character must be written into the video RAM, after reading the table of dots stored in the character code EPROM and writing the same into the video RAM. The table of data (dots) for each language occupies a 2k memory area, and hence four languages can be selected by address lines A11 and A12 of the character generator EPROM. For each character currently being entered, the set of pixels are read byte-by-byte, stored as nibbles temporarily in buffer memory by the program, and then output into the video RAM nibble-by-nibble.

If desired, four languages may be typed on the same row using function keys F1-F4 under software control. The selected language is indicated by two of the LEDs (LED1 and LED2) at the output of 7475. The same outputs are also wired to the A11 and A12 address lines of the character EPROM. You may press F1 and start typing in English, then press F2 and start typing in Hindi, and so on.

The 74165 video shift register (commonly used with all CRT display-based circuits) is used to shift the dot signals loaded in parallel (8 bits) from the memory into a serial form to get the actual video line signal.

In Fig. 1(b), the dot clock is generated using a 74132 gate (N15) in conjunction with a capacitor-resistor combination of R23 (and preset VR1) and C2 to function as an oscillator. The frequency is about 10 MHz, which is divided by 8 in 74190 divider/counter. This gives the character-slot clock. The load command to the shift register is obtained from pin 11/13 (shorted) of the 74190 IC which goes to pin 2 of IC 74LS165. The 2764 EPROM is filled with control program at its highest address range of 2k (i.e. 1800-1FFF), because its pins A11 and A12 are pulled high.

Basic principles

The basic principles of Indian language display software are summarised below while a flowchart for storage of pixel data in the video RAM is given in Fig. 4.

1. Multiple language fonts are stored in an 8k or bigger memory space, if necessary. EPROM occupies 2k locations for each font of a language. Thus, four language fonts can be stored using 8k

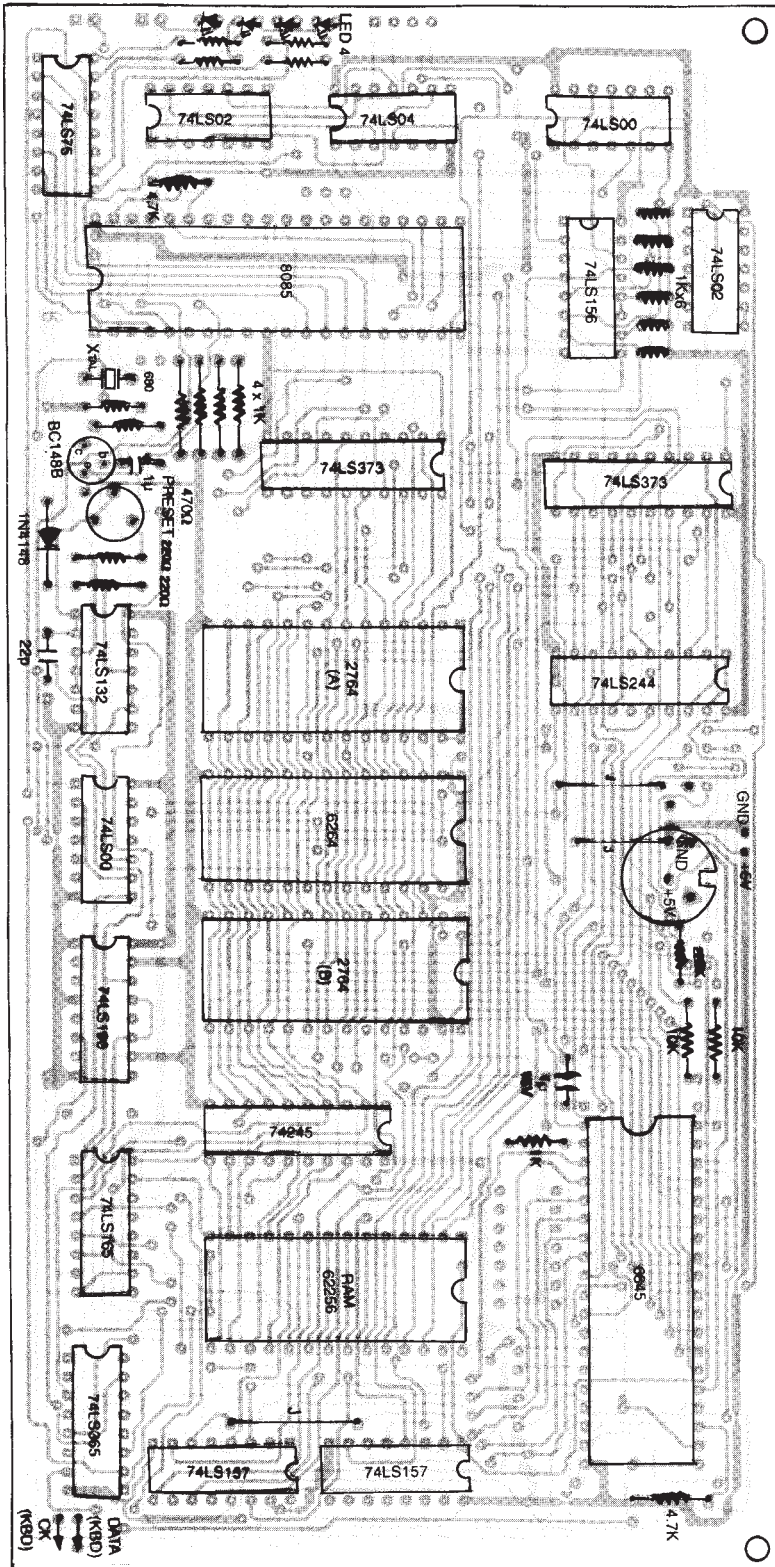


Fig. 7: Component layout for PCB

EPROM.

2. Since 12 horizontal dots per character are insufficient for an Indian language, a 12 x 12 matrix is chosen, though

English appears as an expanded font. The hook characters in Hindi like 'Hu' and 'hoo' need one more dot—the 13th dot—vertically. The hook characters are non-

www.electronicsforu.com

a portal dedicated to electronics enthusiasts

space-moving characters in the standard typewriters of the Indian languages. Particularly in Hindi, there are multiple hooks, such as in 'hoom'. In the typewriter, the hook characters do not advance (move space) after they are typed. The program checks the code, and if it is a hook code, it does not write immediately the dots corresponding to that hook into the video memory, but waits for the succeeding keyboard stroke(s) for a non-hook character to follow before shifting the cursor. Thereupon, the program combines the dot pattern of the hook characters with that of the following main character, and then places the net dot pattern into the video memory.

3. Since memory contains only 8 bits per location, one-and-a-half memory locations are assigned for each character shown on screen, thus providing 12 dots per horizontal row in TV format. (This is more like the computer format.) In this way, even characters start at a memory byte and extend up to the next byte (its higher order nibble). Odd numbered characters start at the right nibble (lower order nibble) of a byte and extend to the next complete byte (refer Fig. 4). With 64 bytes on each horizontal row, up to 43 characters can be shown per row. The hardware caters to a 64 x 16 character display comprising 512 x 256 pixels.

The control software in the 8085 board for the entire unit does the job of reading the keyboard, selecting the language, writing the key code into video RAM, and doing minor editing as well.

A double-sided PTH PCB is required for assembling the circuit. The actual-size component-side and solder-side track layouts for the PCB are shown in Figs 5 and 6, respectively. Fig. 7 shows the component layout.

Testing the board

The board may be tested by a sequence of small programs written into the control EEROM. Verifications are done as per the guidelines given below:

1. The first thing to test is whether the data bus and address lines are functional and the output port 80H is also functional. Here is a simple program for the same:

```
MVI A,55H
OUT 80H
HLT
```

This can be written into an EEROM (using any 8085 kit or the one published in Nov. '99 issue of EFY) and is fixed into the board, and then the LEDs on the left bottom of the board wired at the 7475 (IC9) outputs would indicate the No. 5 as they glow.

If this is not observed, one has to check for proper connections from the data lines to the 7475, connections to the 74156 address decoder, and the gate signals to pins 4.13 of the 7475 as per Fig. 1.

Further, the connections to the video RAM 62256 through the buffer IC 74244 and 74157 (pair of ICs 17 and 18) should be checked for their correctness. When the CPU 8085 is writing to the video RAM, the 74157 (pair) connects A0-A5 address lines of the 8085 to those of the video RAM. Then, pin 1 of the 74157 ICs should be pulsing low.

Thus, the following program to write to 1800H in a loop would check for pulse at pin 1 of 74157 and a high pulse at pins 1 and 19 of 74244. When the IC 74244 is passing the 6845 signals, the IC 74373 is in tri-state condition because its pin 1 is then high.

```
P: MVI A,55
STA 1800H
LDA 1800H
OUT 80H
HLT
```

Or, in place of HLT, a loop may be executed as under:

```
JMP P
```

The above short programs will enable the checks to be made.

2. Another program to initialise the 6845 as per the routine given in the listing is to be entered in the EEROM and then tested for proper H sync and V sync signals from pins 39 and 40 of 6845.

3. The video clock signals and the video output should be checked for proper random display raster.

4. Another program for checking ERASE memory should be entered into the EEROM and then tested for the erasure of clear screen of the raster.

5. The keyboard program should be tested as per the KBD routine.

Only after successful testing of the board as per above-mentioned guidelines, the full program as per the listing given in Appendix 1 should be programmed into control EPROM at its highest 2k address range (1800-1FFF) and

fixed on the board.

Conclusion

The two designs, the first one based on a simple PC and the second one based on dedicated hardware/software using computer keyboard, for display of Indian language text on a monitor and TV screen respectively are illustrative of the techniques of video display and software programming for Indian languages. The former is useful in an industrial or office environment, while the latter can be used in public display systems.

The main intention of this article is not merely to show the design of either the dedicated display unit or the program on PC for typing multilingual text, but to demonstrate the coding scheme for Indian languages with just 128 8-bit codes instead of the currently talked about 16-bit codes. Further, the coding scheme suggested here does not disturb existing typists of the 11 Indian languages, for which typewriters already exist.

The memory saving is a vital factor when one uses such codes for the Indian languages like English. Presently, all such Indian text is treated on a computer or on the Internet as graphic patterns only and consumes large memory space. If 1k of memory is taken for one page of screen with coding like this, it would take 8k in an ordinary graphics mode. When archives of text are to be kept in databases, the ASCII-like coding is the best.

With program PIXEL.bas or with the dedicated display unit using IBM PC-compatible keyboard, one can type in three languages using the ASCII-like codes.

Note: The following softwares pertaining to this project, which could not be issued with September EFY-CD due to unavoidable circumstances, will now be included in October EFY-CD:

1. Pixel6.BAS
2. Pixel6.EXE
3. Chtamil2

(The above files pertain to computer based display scheme).

4. Tam.LST
5. Tam.EPR
6. Chtamil3

(The files at sl. no. 4 and 5 pertain to control program and its hex dump for control EPROM while file at sl. no. 6 contains hex code for character generator EPROM.

Errata for Part I of the article

1. **Refer Fig. 1(a).** Please renumber data pins 9 through 11 and 13 through 17 of

both 2764 ICs (IC3 and IC4) as 11 through 13 and 15 through 19.

2. **Refer Fig. 1(b).** Interchange connections between pin numbers 1 and 2 of

74LS165 (IC22) (i.e. pin 11/13 of IC23 to go to pin 2 while pin 14 of IC23 to go to pin 1 of IC22).

(Appendix I)

CONTROL PROGRAM LISTING

Addr.	Code	Label	Mneumonics	Remarks			
0000			.ORG 0000H				of "S"
	26 11		LINE_NUMB: EQU 1126H		00F6	16 00	MVI D,00
	28 11		ROW_NUMB: EQU 1128H		00F8	21 00 11	LXI H,NIBL_BUF ;BUFFER MEMORY STORING
	29 11		CHAR_NUMB: EQU 1129H				NIBBLE BY NIBBLE
	25 11		NIB_FL: EQU 1125H		00FB	0A B2:	LDAX B
	00 11		BUFFER_MEM: EQU 1100H		00FC	5F	MOV E,A
	00 11		NIBL_BUF: EQU 1100H		00FD	1F	RAR
	29 11		CHAR_NO: EQU 1129H		00FE	1F	RAR
	50 11		AUX_STORE: EQU 1150H		00FF	1F	RAR
	27 11		CHAR_POS: EQU 1127H		0100	1F	RAR
	05 00		F1KEY: EQU 05H		0101	E6 0F	ANI 0FH
	D6 00		F2KEY: EQU D6H		0103	77	MOV M,A
	04 00		F3KEY: EQU 04H		0104	23	INX H
	DC 00		F4KEY: EQU DCH		0105	14	INR D
0000	31 FF 13		LXI SP,13FFH		0106	7B	MOV A,E
0003	F3		DI		0107	E6 0F	ANI 0FH
0004	C3 80 00		JMP 0080H		0109	77	MOV M,A
0080			.ORG 80H		010A	23	INX H
0080	CD E6 04		CALL CRTCON_INIT ;initialise c.r.t.c.		010B	14	INR D
0083	CD 0B 05		CALL CLEAR ;clear video memory		010C	7A	MOV A,D
0086	3E 00		MVI A,00		010D	FE 24	CPI 24H
0088	D3 80		OUT 80H		010F	CA 16 01	JZ EN
008A	CD 12 04		CALL KBD ;CALL KEYBOARD		0112	03	INX B
008D	4F	BEG:	MOV C,A		0113	C3 FB 00	JMP B2
008E	DB 80		IN 80H		0116	E1	POP H
0090	E6 03		ANI 03H		0117	D1	POP D
0092	FE 01		CPI 01		0118	C1	POP B
0094	CA CA 00		JZ HINDI		0119	C9	RET
0097	FE 00		CPI 0				;Data storage in 100-1123 buffer memory over
0099	CA A9 00		JZ ENGLISH				;VIDEO RAM STORE ROUTINE
009C	FE 02		CPI 02H				;ROW NO.AND CHARACTER NUMBER AT ENTRY, STORED IN 1128 AND 1127
009E	CA BE 00		JZ TAMIL		011A	3A 27 11	VDUST: LDA CHAR_POS ;CHARACTER POSITION ON
00A1	FE 03	FL:	CPI 03H				SCREEN
00A3	CA A6 00		JZ LANG3		011D	CD 8A 01	CALL CH_NUMB ;CALCULATES CHAR. SLOT FROM
00A6	C3 8D 00	LANG3:	JMP BEG ;YET UNDEFINED.				CHAR.NO.
00A9	79	ENGLISH:	MOV A,C		0120	5F	MOV E,A
00AA	CD 98 01	E:	CALL CL_CH_CHK ;CONTROL CHARACTER CHECK		0121	16 14	MVI D,14H
00AD	D2 B6 00		JNC CURSORA		0123	3E FF	MVI A,FFH
00B0	CD E5 00		CALL NIBST ;NIBBLE STORE		0125	32 26 11	STA LINE_NUMB ;LINE NO. STORED IN 1126
00B3	CD 1A 01		CALL VDUST ;VdU STORE MEANS WRITE VdRAM		0128	21 00 11	LXI H,BUFFER_MEM ;POINT TO BUFFER MEMORY
00B6	CD 22 02	CURSORA:	CALL INC_SP ;CURSOR NEXT		012B	3A 26 11	NXTLIN: LDA LINE_NUMB
00B9	C3 8D 00		JMP BEG		012E	3C	INR A
00BC	00		NOP		012F	32 26 11	STA LINE_NUMB ;lines 0 -11 decimal
00BD	00		NOP		0132	3A 28 11	LDA ROW_NUMB ;rows 0 -15 decimal
00BE	79	TAMIL:	MOV A,C		0135	17	RAL
00BF	CD B4 02		CALL CHOOKT ;COMPARE HOOK CHARACTERS IN TAMIL		0136	17	RAL
					0137	17	RAL
00C2	DA D4 00		JC TAMHKFIL ;TAMIL HOOK FILLING		0138	17	RAL
00C5	C3 AA 00		JMP E		0139	E6 F0	ANI F0H
00C8	00		NOP		013B	47	MOV B,A
00C9	00		NOP		013C	3A 26 11	LDA LINE_NUMB
00CA	79	HINDI:	MOV A,C		013F	B0	ORA B
00CB	CD D2 02		CALL HIHOOK ;COMPARE HOOK CHARACTER HINDI		0140	32 00 18	STA 1800H ;STORE IN VIDEO LATCH 74374
00CE	DA DA 00		JC HINHK ;HINDI HOOK FILLING ROUTINE		0143	3A 26 11	LDA LINE_NUMB
00D1	C3 AA 00		JMP E		0146	FE 0C	CPI 0CH ;CHECK FOR > 12 LINES
00D4	CD 13 03	TAMHKFIL:	CALL HIHKFIL ;CALL HOOK CHARACTER FILL		0148	C2 4C 01	JNZ STORE
00D7	C3 B6 00		JMP CURSORA		014B	C9	RET
00DA	F5	HINHK:	PUSH PSW		014C	3A 25 11	STORE: LDA NIB_FL ;1125 H IS USED FOR STORING
00DB	CD 8A 03		CALL ROW13FIL ;CALL 13TH ROW FILL				ODD/EVEN CHAR. IN D0 BIT
00DE	F1		POP PSW		014F	1F	RAR
00DF	CD 48 03		CALL HI_HO_CHFIL ;CALL HINDI HOOK FILL		0150	DA 73 01	JC LOAD_RT ;RIGHT HALF IS TO BE LOADED
00E2	C3 B6 00		JMP CURSORA		0153	7E	LEFT: MOV A,M
					0154	17	RAL
					0155	17	RAL
					0156	17	RAL
					0157	17	RAL
00E5	C5	NIBST:	PUSH B		0158	E6 F0	ANI F0H ;move nibble left
00E6	D5		PUSH D		015A	47	MOV B,A ;save in B
00E7	E5		PUSH H		015B	23	INX H ;point to next nibble buffer
00E8	5F		MOV E,A		015C	7E	MOV A,M
00E9	16 08		MVI D,8 ;Start address of char.gen ROM		015D	B0	ORA B ;join with left nibble
00EB	1A		LDAX D ;GET LOW ADDRESS OF CHARACTER TABLE		015E	12	STAX D ;store in video ram
					015F	13	INX D
00EC	4F		MOV C,A		0160	23	INX H ;get address of next char.slot
00ED	3E 80		MVI A,80H ;ADD 80H TO A		0161	7E	MOV A,M ;Read from buffer
00EF	83		ADD E		0162	07	RLC ;Move left
00F0	5F		MOV E,A		0163	07	RLC
00F1	1A		LDAX D ;Get high address of cha. table		0164	07	RLC
00F2	C6 08		ADI 8		0165	07	RLC
00F4	47		MOV B,A		0166	E6 F0	ANI F0H
00F5	0A		LDAX B ;b-c contain start address of char.table				

C O N S T R U C T I O N

0168	47	MOV B,A		:Save in B	01F2	37	P9:	STC	
0169	1A	LDAX D		:Read video RAM	01F3	3F		CMC	
016A	E6 0F	ANI 0FH			01F4	C9		RET	
016C	B0	ORA B			01F5	37	P10:	STC	:Not any control code!
016D	12	STAX D		:store in video RAM (only alter left nibble)	01F6	C9		RET	
016E	23	INX H			:CURSOR ROUTINE				
016F	1B	DCX D			01F7	0E 00	CUR_ROUT:	MVI C,00	
0170	C3 2B 01	JMP NXTLIN		:JUMP TO NEXT LINE	01F9	CD 07 02		CALL CUR_FILL	
0173	46	MOV B,M	LOAD_RT:	:NIBBLE IN B	01FC	CD 12 04		CALL KBD	
0174	1A	LDAX D		:Get from video ram	01FF	F5		PUSH PSW	
0175	E6 F0	ANI F0H		:save left nibble	0200	0E FF		MVI C,FFH	
0177	B0	ORA B			0202	CD 07 02		CALL CUR_FILL	:Erases cursor after key-entry
0178	12	STAX D			0205	F1		POP PSW	
0179	23	INX H			0206	C9		RET	
017A	7E	MOV A,M		:get next nibble	:CURSOR FILL ROUTINE:				
017B	17	RAL			0207	3A 28 11	CUR_FILL:	LDA ROW_NUMB	
017C	17	RAL			020A	17		RAL	
017D	17	RAL			020B	17		RAL	
017E	17	RAL			020C	17		RAL	
017F	47	MOV B,A		:save in B, left part	020D	E6 F0		ANI F0H	
0180	23	INX H			020F	47		MOV B,A	
0181	7E	MOV A,M			0210	3E 0C		MVI A,0CH	:UNDERLINE,13TH LINE
0182	B0	ORA B		:now a fullbyte	0212	B0		ORA B	
0183	13	INX D			0213	32 00 18		STA 1800H	:SAVE IN VIDEO LATCH
0184	12	STAX D			0216	16 14		MVI D,14H	
0185	1B	DCX D			0218	3A 27 11		LDA CHAR_POS ;	
0186	23	INX H			021B	CD 29 11		CALL CHAR_NO	
0187	C3 2B 01	JMP NXTLIN		:NEXT LINE	021E	5F		MOV E,A	:SAVE CHAR. NO. IN e
:CHARACTER NO. SUBROUTINE					021F	79		MOV A,C	
:A CONTAINS CHARACTER NUMBER IN THE ROW					0220	12		STAX D	:STORE UNDERLINE PIXELS
:a RETURNS SLOT NUMBER. 1125H STORES 0 OR 1 FLAG					0221	C9		RET	
:ACCORDING AS CHARACTER NUMBER GIVES EVEN OR ODD.					:INCREMENT SPACE ROUTINE				
018A	C5	CH_NUMB:PUSH B			0222	3A 27 11	INC_SP:	LDA 1127H	:Character no.
018B	47	MOV B,A			0225	FE 2A		CPI 2AH	:(42 characters/row)
018C	1F	RAR		:to divide by 2	0227	D2 34 02		JNC Q1	
018D	4F	MOV C,A		:store in C	022A	3C		INR A	:Increment char.no.
018E	3E 00	MVI A,0			022B	32 27 11		STA 1127H	:store it
0190	17	RAL			022E	CD F7 01	S1:	CALL CUR_ROUT	
0191	32 25 11	STA NIB_FL		:Store in nibble flag	0231	37		STC	:carry flag to indicate main program
0194	79	MOV A,C			0232	3F		CMC	:cleared and return
0195	80	ADD B			0233	C9		RET	
0196	C1	POP B			0234	3A 28 11	Q1:	LDA 1128H	:to increment row number
0197	C9	RET			0237	FE 0F		CPI 0FH	
:CONTROL CHARACTERS CHECKING ROUTINE					0239	D2 40 02		JNC Q2	
0198	FE 20	CL_CH_CHK: CPI 20H		:space code?	023C	3C		INR A	
019A	C2 A3 01	JNZ P1			023D	32 28 11		STA ROW_NUMB	
019D	CD 22 02	CALL INC_SP ;			0240	3E 00	Q2:	MVI A,00H	
01A0	37	STC		:carry flag cleared to	0242	32 27 11		STA 1127H	:clear character number -
01A1	3F	CMC		:indicate main program that it was control code	:first character, next row				
01A2	C9	RET		:ret	0245	C3 2E 02		JMP S1	
01A3	FE 08	CPI 08H	P1:	:BACKSPACE CODE	:DECREMENT BACKSPACE				
01A5	C2 AE 01	JNZ P2			0248	3A 27 11	DECR_SP:	LDA 1127H	:load char.no.
01A8	CD 48 02	CALL DECR_SP ;			024B	3D		DCR A	:decrement
01AB	37	STC			024C	DA 5E 02		JC Q4	:check not first character
01AC	3F	CMC			024F	32 27 11		STA 1127H	:store one less
01AD	C9	RET			0252	CD 61 02		CALL ERASE	:erase all 13 rows
01AE	FE 0A	CPI 0AH	P2:		0255	3A 27 11		LDA 1127H	
01B0	C2 C2 01	JNZ P3			0258	3D		DCR A	
01B3	3A 28 11	LDA 1128H			0259	32 27 11		STA 1127H	
01B6	3C	INR A			025C	37		STC	
01B7	FE 10	CPI 10H			025D	C9		RET	
01B9	D2 BF 01	JNC P4			025E	3F	Q4:	STC	
01BC	32 28 11	STA 1128H			025F	3F		CMC	
01BF	C3 C9 01	JMP P5	P4:		0260	C9		RET	
01C2	FE 0C	CPI 0CH	P3:	: (CTRL-L =CURSOR LINE LEFT)	:ERASE CHARACTER:				
01C4	C2 CF 01	JNZ P6			0261	3A 29 11	ERASE:	LDA CHAR_NUMB ;	:find char.slot No.
01C7	3E 00	MVI A,0			0264	CD 29 11		CALL CHAR_NO	
01C9	32 27 11	STA 1127H	P5:		0267	5F		MOV E,A	
01CC	37	STC			0268	16 14		MVI D,14H	:video RAM high addr.
01CD	3F	CMC			026A	3E FF		MVI A,FFH	:ONE LESS THAN ZERO
01CE	C9	RET			026C	32 26 11		STA LINE_NUMB	
01CF	FE 0B	CPI 0BH	P6:	(CURSOR UP control-K)	026F	3A 26 11	NXTL:	LDA LINE_NUMB	
01D1	C2 E1 01	JNZ P7			0272	3C		INR A	:line no. increases from 0
01D4	3A 28 11	LDA 1128H			0273	32 26 11		STA LINE_NUMB	
01D7	3D	DCR A			0276	3A 28 11		LDA ROW_NUMB	:row no. is output on left nibble
01D8	DA DE 01	JC P8			0279	17		RAL	
01DB	32 28 11	STA 1128H			027A	17		RAL	
01DE	37	STC	P8:		027B	17		RAL	
01DF	3F	CMC			027C	17		RAL	
01E0	C9	RET			027D	E6 F0		ANI F0H	
01E1	FE 09	CPI 09H	P7:	:Ctrl-I cursor goes down	027F	47		MOV B,A	
01E3	C2 F5 01	JNZ P10			0280	3A 26 11		LDA LINE_NUMB	
01E6	3A 28 11	LDA 1128H			0283	B0		ORA B	:line no. is output on right nibble
01E9	3C	INR A			0284	32 00 18		STA 1800H	:IN VIDEO LATCH
01EA	FE 10	CPI 10H		:not greater than 16 rows	0287	3A 26 11		LDA LINE_NUMB	
01EC	D2 F2 01	JNC P9			028A	FE 0D		CPI 0DH	:is it the 14th line?
01EF	32 28 11	STA 1128H		:Stores 11, but the left L is not useful, so becomes 01	028C	C2 90 02		JNZ STORE1	:if between 0 and 13, save
					028F	C9		RET	
					0290	3A 25 11	STORE1:	LDA NIB_FL	:check for odd or even slot position
					0293	1F		RAR	

CONSTRUCTION

03CA	3A 29 11	THIRL:	LDA CHAR_NUMB		0456	C9	RET		
03CD	CD 29 11		CALL CHAR_NUMB		0457	16 01	SH_PRES:	MVI D,01H	
03D0	5F		MOV E,A		0459	C3 28 04		JMP PK	
03D1	16 14		MVI D,14H		045C	16 02	CONTROL:	MVI D,02H	
03D3	3A 28 11		LDA ROW_NUMB		045E	C3 28 04		JMP PK	
03D6	17		RAL		0461	79	LANGCH:	MOV A,C	
03D7	17		RAL		0462	FE 05		CPI FIKEY	
03D8	17		RAL		0464	CA 77 04		JZ L1	
03D9	17		RAL		0467	FE D6		CPI F2KEY	
03DA	E6 F0		ANI FOH		0469	CA 7C 04		JZ L2	
03DC	47		MOV B,A		046C	FE 04		CPI F3KEY	
03DD	3E 0C		MVI A,0CH		046E	CA 81 04		JZ L3	
03DF	B0		ORA B		0471	FE DC		CPI F4KEY	
03E0	32 00 18		STA 1800H	;STORE IN VIDEO LATCH	0473	CA 86 04		JZ L4	
03E3	3A 25 11		LDA NIB_FL		0476	C9		RET	
03E6	1F		RAR		0477	3E 00	L1:	MVI A,0	;OUTPUT 0 ON leds
03E7	DA F1 03		JC R		0479	D3 80		OUT 80H	
03EA	7E		MOV A,M	;LOAD FIRST ONE BYTE	047B	C9		RET	
03EB	12		STAX D		047C	3E 01	L2:	MVI A,1	1
03EC	23		INX H		047E	D3 80		OUT 80H	
03ED	7E		MOV A,M		0480	C9		RET	
03EE	13		INX D		0481	3E 02	L3:	MVI A,2	2
03EF	12		STAX D	;THEN NEXT BYTE	0483	D3 80		OUT 80H	
03F0	C9		RET		0485	C9		RET	
03F1	7E	R:	MOV A,M	;fills as for right nibble store	0486	3E 03	L4:	MVI A,3	3
03F2	0F		RRC		0488	D3 80		OUT 80H	
03F3	0F		RRC		048A	C9		RET	
03F4	0F		RRC		048B	7A	ASCII_C		
03F5	0F		RRC				ONV:	MOV A,D	
03F6	E6 0F		ANI 0FH		048C	E6 01		ANI 01H	
03F8	47		MOV B,A		048E	CA 9E 04		JZ SHIFT_CODE	
03F9	1A		LDAX D	;read video ram	0491	E6 02		ANI 02H	
03FA	E6 F0		ANI FOH	;DO NOT DISTURB LEFT NIBBLE	0493	CA A4 04		JZ CONT_CODE	
03FC	B0		ORA B		0496	21 00 07		LXI H,TABLE1	;TABLE1 FOR LOWER CASE
03FD	12		STAX D	;COMBINE AND STORE					NORMAL
03FE	13		INX D		0499	79	SA1:	MOV A,C	
03FF	7E		MOV A,M	;NEXT BYTE NIBBLE BY NIBBLE	049A	85		ADD L	
0400	07		RLC		049B	6F		MOV L,A	
0401	07		RLC		049C	7E		MOV A,M	
0402	07		RLC		049D	C9		RET	
0403	07		RLC		049E	21 80 07	SHIFT_		
0404	E6 F0		ANI FOH				CODE:	LXI H,TABLE2	;TABLE2 FOR SHIFT CODE
0406	47		MOV B,A		04A1	C3 99 04		JMP SA1	
0407	23		INX H		04A4	21 00 07	CONT_		
0408	7E		MOV A,M				CODE:	LXI H,TABLE1	;TABLE3 FOR CONTROL CODE
0409	0F		RRC		04A7	79		MOV A,C	
040A	0F		RRC		04A8	85		ADD L	
040B	0F		RRC		04A9	6F		MOV L,A	
040C	0F		RRC		04AA	7E		MOV A,M	
040D	E6 0F		ANI 0FH		04AB	E6 3F		ANI 3FH	
040F	B0		ORA B		04AD	C9		RET	
0410	12		STAX D	;STORE IN VIDEO RAM	04AE	06 08	PULSE_		
0411	C9		RET				READ:	MVI B,08H	
;KEYBOARD ROUTINE					04B0	0E 00		MVI C,00	
0412	E5	KBD:	PUSH H		04B2	DB 80	PP:	IN 80H	
0413	D5		PUSH D		04B4	E6 20		ANI 20H	
0414	C5		PUSH B		04B6	C2 B2 04		JNZ PP	
0415	CD AE 04		CALL PULSE_READ		04B9	DB 80	QQ:	IN 80H	
0418	79		MOV A,C		04BB	E6 20		ANI 20H	
0419	FE 12		CPI 12H		04BD	CA B9 04		JZ QQ	
041B	CA 57 04		JZ SH_PRES		04C0	DB 80	PK1:	IN 80H	
041E	FE 59		CPI 59H	;IS IT SHIFTT RIGHT KEY?	04C2	E6 20		ANI 20H	
0420	CA 57 04		JZ SH_PRES		04C4	C2 C0 04		JNZ PK1	
0423	FE 2D		CPI 2DH	;IS IT CONTROL KEY ?	04C7	DB 80		IN 80H	
0425	CA 5C 04		JZ CONTROL		04C9	17		RAL	
0428	CD AE 04	PK:	CALL PULSE_READ		04CA	17		RAL	
042B	79		MOV A,C		04CB	17		RAL	
042C	FE F0		CPI FOH		04CC	17		RAL	
042E	C2 28 04		JNZ PK		04CD	79		MOV A,C	
0431	CD AE 04		CALL PULSE_READ		04CE	1F		RAR	
0434	FE 12		CPI 12H		04CF	4F		MOV C,A	
0436	CC 4D 04		CZ SH_REL		04D0	DB 80	QQ1:	IN 80H	
0439	FE 59		CPI 59H		04D2	E6 20		ANI 20H	
043B	CC 4D 04		CZ SH_REL		04D4	CA D0 04		JZ QQ1	
043E	FE 2D		CPI 2DH		04D7	05		DCR B	
0440	CC 52 04		CZ CONT_REL		04D8	C2 C0 04		JNZ PK1	
0443	CD 61 04		CALL LANGCH	;CHECK IF LANGUAGE CHANGING	04DB	CD DF 04		CALL DELAY	
				F1.. KEYS PRESS'D	04DE	C9		RET	
0446	CD 8B 04		CALL ASCII_CONV		04DF	1E 20	DELAY:	MVI E,20H	
0449	C1		POP B		04E1	1D	D1:	DCR E	
044A	D1		POP D		04E2	C2 E1 04		JNZ D1	
044B	E1		POP H		04E5	C9		RET	
044C	C9		RET		;845 INITIALISE ROUTINE				
044D	7A	SH_REL:	MOV A,D		04E6	11 FB 04	CRTCON_		
044E	E6 FE		ANI FEH				INIT:	LXI D,TABLEINIT	
0450	57		MOV D,A		04E9	06 00		MVI B,0	
0451	C9		RET		04EB	21 00 1C	IP:	LXI H,1C00H	
0452	7A	CONT_REL:	MOV A,D		04EE	70		MOV M,B	
0453	E6 FD		ANI FDH		04EF	23		INX H	
0455	57		MOV D,A		04F0	1A		LDAX D	

C O N S T R U C T I O N

```

04F1 77          MOV M,A
04F2 04          INR B
04F3 13          INX D
04F4 78          MOV A,B
04F5 FE 10       CPI 10H
04F7 C2 EB 04    JNZ IP
04FA C9          RET
04FB 55 40 46 09 TABL .DB 55H,40H,46H,09,12H,08H,10H,11H,0,10H,0,0BH,
      EINT:       0,0,0,0

04FF 12 08 10 11
0503 00 10 00 0B
0507 00 00 00 00
;CLEAR SCREEN ROUTINE
050B C5          CLEAR: PUSH B
050C E5          PUSH H
050D 0E 00       MVI C,00
050F 0D          A1:   DCR C
0510 CA 28 05    JZ A2
0513 26 14       MVI H,14H
0515 2E 00       MVI L,00
0517 79          MOV A,C
0518 32 00 18    STA 1800H
051B 3E FF       A3:   MVI A,FFH
051D 77          MOV M,A
051E 2C          INR L
051F 7D          MOV A,L
0520 FE 80       CPI 80H
0522 C2 1B 05    JNZ A3
0525 C3 0F 05    JMP A1
0528 E1          A2:   POP H
0529 C1          POP B
052A C9          RET
0700             .ORG 700H

0700 TABLE1:
0700 FF FF FF FF   .DB FFH,FFH,FFH,FFH,FFH,FFH,FFH,FFH
0704 FF FF FF FF
0708 FF FF FF FF   .DB FFH,FFH,FFH,FFH,FFH,FFH,FFH,FFH
070C FF FF FF FF
0710 FF FF FF FF   .DB FFH,FFH,FFH,FFH, FFH,71H,31H,FFH,FFH,FFH,
      7AH,73H,61H,77H,32H,FFH

0714 FF 71 31 FF
0718 FF FF 7A 73
071C 61 77 32 FF
0720 FF 63 78 64   .DB FFH, 63H, 78H, 64H, 65H, 34H, 33H, FFH, FFH,
      20H, 76H, 66H,7AH,72H,35H,FFH

0724 65 34 33 FF
0728 FF 20 76 66
072C 7A 72 35 FF
764 0730 FF 6E 62 68 .DB FFH, 6EH, 62H, 68H, FFH, 79H, 36H, FFH, FFH,
      FFH, 6DH, 6AH, 75H, 37H, 38H,FFH

0734 FF 79 36 FF
0738 FF FF 6D 6A
073C 75 37 38 FF
0740 FF 3C 6B 69   .DB FFH, 3CH, 6BH, 69H, 6FH,30H,39H,FFH, FFH,3EH,
      3FH,FFH, 3BH,70H,2DH,FFH

0744 6F 30 39 FF
0748 FF 3E 3F FF
074C 3B 70 2D FF

0750 FF FF 2C FF   .DB FFH, FFH, 2CH, FFH, 5BH,2BH,FFH,FFH, FFH,
      FFH,0DH,5DH, FFH,21H,FFH,FFH

0754 5B 2B FF FF
0758 FF FF 0D 5D
075C FF 21 FF FF
0760 FF FF FF FF   .DB FFH, FFH, FFH, FFH, FFH,FFH,08H,FFH, FFH,
      31H,FFH,34H, 37H,09H,FFH,FFH

0764 FF FF 08 FF
0768 FF 31 FF 34
076C 37 09 FF FF
0770 30 FF 32 35   .DB 30H, FFH, 32H, 35H, 36H,38H,FFH,FFH, FFH,
      FFH,33H,2DH, 2BH,39H,FFH,FFH

0774 36 38 FF FF
0778 FF FF 33 2D
077C 2B 39 FF FF
0780 TABLE2:
0780 FF FF FF FF   .DB FFH,FFH,FFH,FFH,FFH,FFH,FFH,FFH
0784 FF FF FF FF
0788 FF FF FF FF   .DB FFH,FFH,FFH,FFH,FFH,FFH,FFH,FFH
078C FF FF FF FF
0790 FF FF FF FF   .DB FFH, FFH, FFH, FFH, FFH, 51H, 21H, FFH,FFH,
      FFH,5AH,53H,41H,57H,40H,FFH

0794 FF 51 21 FF
0798 FF FF 5A 53
079C 41 57 40 FF
07A0 FF 43 58 44   .DB FFH, 43H, 58H, 44H, 45H, 24H, 33H, FFH, FFH,
      20H, 56H, 46H, 5AH, 52H, 25H, FFH

07A4 45 24 33 FF
07A8 FF 20 56 46
07AC 5A 52 25 FF
07B0 FF 4E 42 48   .DB FFH, 4EH, 42H, 48H, FFH, 59H, 36H, FFH, FFH,
      FFH, 4DH, 4AH, 55H, 26H, 2AH,FFH

07B4 FF 59 36 FF
07B8 FF FF 4D 4A
07BC 55 26 2A FF
07C0 FF 2C 2B 49   .DB FFH, 2CH, 2BH, 49H, 4FH,29H,28H,FFH, FFH,2EH,
      2FH,FFH, 2BH,50H,5FH,FFH

07C4 4F 29 28 FF
07C8 FF 2E 2F FF
07CC 2B 50 25 FF
07D0 FF FF 22 FF   .DB FFH, FFH, 22H, FFH, 7BH,2BH,FFH,FFH, FFH,
      FFH,0D,5DH, FFH,21H,FFH,FFH

07D4 7B 2B FF FF
07D8 FF FF 00 5D
07DC FF 21 FF FF
07E0 FF FF FF FF   .DB FFH, FFH, FFH, FFH, FFH,FFH,08H,FFH, FFH,
      31H,FFH,34H, 37H,09H,FFH,FFH

07E4 FF FF 08 FF
07E8 FF 31 FF 34
07EC 37 09 FF FF
07F0 30 FF 32 35   .DB 30H, FFH, 32H, 35H, 36H,38H,FFH,FFH, FFH,FFH,
      33H,2DH, 2BH,39H,FFH,FFH

07F4 36 38 FF FF
07F8 FF FF 33 2D
07FC 2B 39 FF FF
0800
END

```

www.electronicsforu.com

A PORTAL DEDICATED TO ELECTRONICS ENTHUSIASTS

DIGITAL CODE LOCK

BISWAJIT GUPTA



A versatile digital code lock circuit is presented here, which can have up to 32-digit long secret code. The length of the secret code can be easily varied by changing the position of jumpers. The available options are to make the code 2-, 4-, 8-, 16-, or 32-digit long. When the keyed-in code matches with the stored secret code, a relay gets energised. The contacts of the relay may be used appropriately to operate, lock, or unlock any device or appliance, as desired by the user.

The circuit makes use of a RAM to store and output the stored code to enable in-situ coding and changing of the code easily. To retain the contents of RAM in case of power failure and to save power, a 4.5V battery backup arrangement is provided, so that the system may operate in power-down mode with the battery catering to the retention of only the RAM's contents. Thus, the power supply to the circuit can be switched off to minimise the power consumption to about 0.6 mA.

The Circuit

Memory organisation. A 6116 static RAM (2048 x 8-bit) IC5 is used in the circuit with A9 and A10 address pins connected to the ground. Thus, here we are effectively using an address space of 512 locations only. This address space of 512 locations is further divided into 16 pages of 32 locations each. Page selection is done using 4-way DIP switch S2 in the circuit. Thus, in each page, an address space of 32 is available for storing the secret code.

Each digit of the code comprises a hex digit, which can be stored as a nibble, requiring only 4-bit data space. It is stored as data bits D4 through D7 in each location. Data bits D0 through D3 are not used and the corresponding pins are therefore pulled to ground via 10-kilo-ohm resistor R3. Thus, maximum length of a code can be up to 32 hex digits. One can, however, keep one's secret code spread over all the 16 pages randomly. For ex-

ample, one can arrange to store an eight hex-digit secret code as first two digits in 1st page, next three digits in 8th page, next one digit in 3rd page, and the last two digits in 14th page.

PARTS LIST

Semiconductors:

IC1	- 74C922 hexadecimal keyboard encoder
IC2	- 74HC244 octal tri-state buffer
IC3	- 74HC688 8-bit comparator
IC4, IC7	- 74HC132 quad 2-input NAND gate with Schmitt trigger input
IC5	- 6116 2k x 8-bit SRAM
IC6, IC8	- 74HC4040 12-stage binary counter
IC9	- 74LS32 quad 2-input OR gate
IC10	- 74LS74 dual J-K Flip-Flop
IC11	- 7805 regulator 5V
T1	- BS170 n-channel MOSFET
T2	- BC548B npn transistor
D1, D2, D5	- 1N4148 switching diode
D3, D4	- 5.1V, 0.25W zener diode
D6	- 1N4001 rectifier diode
D7, D8	- 1N4007 rectifier diode
LED1	- Red LED
LED2	- Yellow LED
LED3	- Green LED

Capacitors:

C1, C3	- 1 μ F, 10V tantalum
C2	- 100nF ceramic disk
C4	- 470nF ceramic disk
C5	- 10 μ F, 10V electrolytic
C6	- 2200 μ F, 25V electrolytic
C7	- 100nF, ceramic disk

Resistors (all 1/4-watt, $\pm 5\%$ carbon, unless stated otherwise):

R1	- 100-kilo-ohm
R2, R3, R5,	
R7, R10, R11-	10-kilo-ohm
R4	- 1.5-kilo-ohm
R6, R8, R9	- 470-ohm
R12	- 27-ohm
R13	- 2.7-kilo-ohm
RN1	- 4x10-kilo-ohm resistor network (5-pin SIP)

Miscellaneous:

RL1	- 12V, 500-ohm relay, PCB mountable
S1	- SPDT switch
S2	- 4-way DIP switch
S3	- Push-to-on switch
BZ1	- 12V DC buzzer with inbuilt oscillator
X1	- 230V AC primary to 12V-0-12V, 500 mA secondary transformer

SRAM 6116 is a volatile type memory. Therefore battery backup is required to retain data during power failures. The circuit around transistor T1, comprising diodes D1 through D4, resistors R4 and R5, capacitor C4, and a 4.5V battery pack connected to pins 24 and 18 of IC5 (SRAM 6116), allows the changeover of the circuit to operate in power-down mode during power failures. In this mode, the static RAM chip retains data, while consuming very little power with as low a current as 0.03 mA to 0.6 mA—depending upon the chip used. For example, HM611L-5 will draw 0.03 mA at 2V V_{dd} (in power-down mode), as per databook. This gives a long life to the battery.

Address counter. IC8 (74HC4040) is a 12-stage binary counter, in which the five least significant address lines A0 through A4 (for addressing 32 locations) are sequentially selected on receipt of clock pulses. Selection for the required number of hex digits to be used as secret code can be made by jumpering one of the output pins (7, 6, 5, 3, or 2) of IC8 to pin 2 of IC9 (74LS32), using jumper JPN1 for obtaining 2-, 4-, 8-, 16-, or 32-digit long secret code, respectively.

Keyboard encoding. 16-key keyboard encoder IC1 74C922 from National Semiconductor is used in conjunction with a 16-digit keypad for encoding the pressed key data. It comprises an internal oscillator for clock generation for its own use and an inbuilt key debounce circuitry. Capacitors C2 and C3 connected to its pins 6 and 5 determine the key scanning frequency and debounce period, respectively.

This chip gives a 4-bit data output from pin 14 through 17, corresponding to a pressed key. Whenever a key is pressed, DA (data available) output pin 12 goes to logic 1, to indicate availability of fresh data at its output pins (14 through 17). This pin 12 reverts to its logic low state when the pressed key is released. The data outputs of IC1 are tri-state. Its output enable (OE) pin 13 is grounded through resistor R2 to keep this chip in enabled state. The DA output signal at its pin 12 is used for the following functions via the gates of quad NAND Schmitt IC4 and IC7:

(a) As a clock for 12-stage binary counter IC8 (74HC4040) via Schmitt NAND gates N1 and N8, which advances the counter by one count for every clock.

(b) For sounding of buzzer BZ1 and

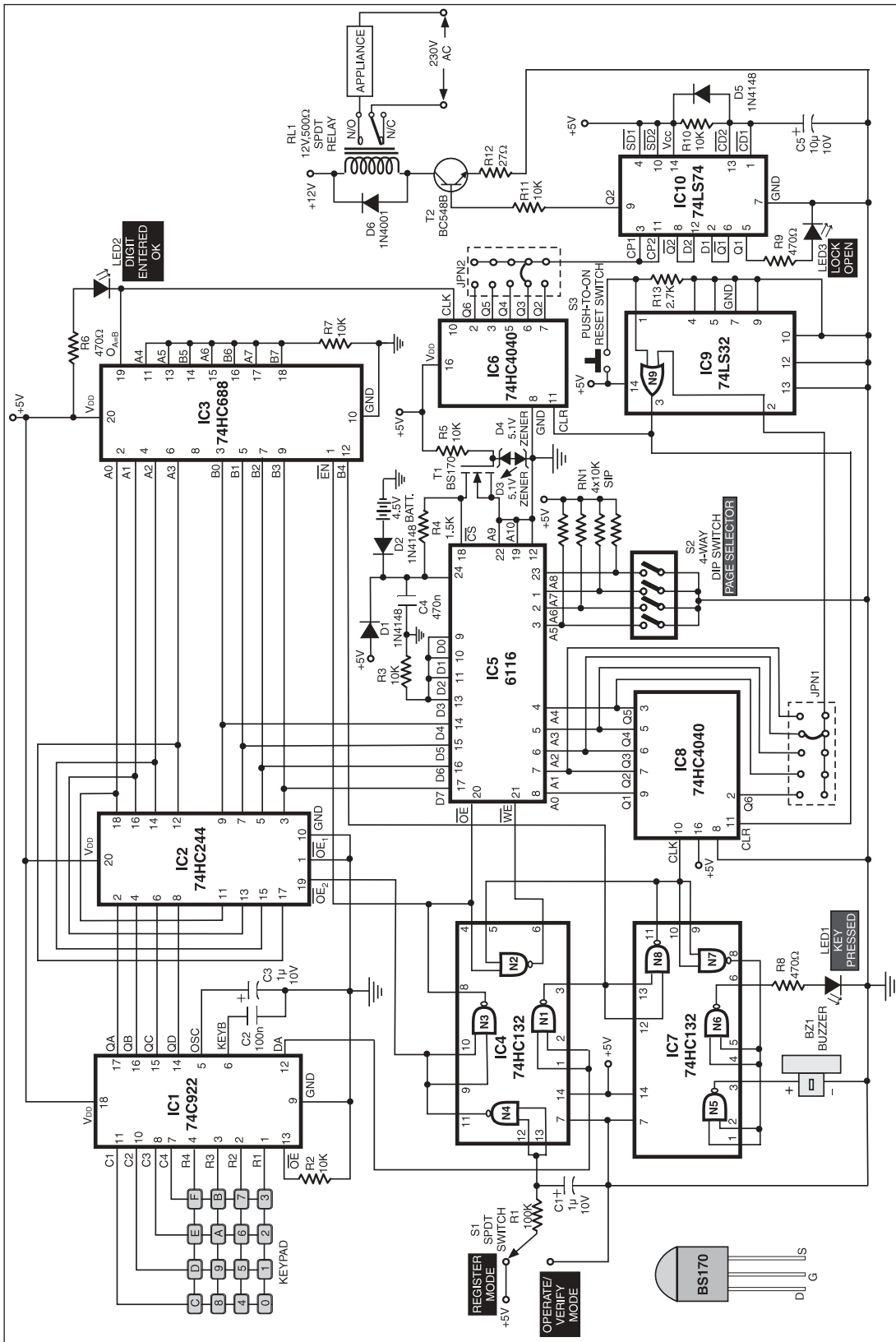


Fig. 1: Schematic diagram of versatile digital code lock

lighting of LED1 via Schmitt NAND gates N7, N5, and N6 to provide audio-visual indication to the effect that the data cor-

responding to the pressed key has been generated for further processing.

Auto-reset circuit. IC9 (74LS32) is a

quad 2-input OR-gate chip, of which only one gate is used here. This gate is wired as a reset circuit (both for auto and manual reset operation) for IC8 and IC6. One can reset both the counters (IC6 and IC8) manually, by pressing reset switch S3.

Auto-reset function will take place whenever preset number of digits of secret code has been entered, either for verification/operation or for registration. In verification mode, the secret code would either be right or wrong. Basically, the auto-reset function keeps the secret code really secret, and is smart enough to confuse an intruder.

Operational mode control circuitry

The R1-C1 combination around mode switch S1 functions as a bounce eliminator. Switch S1 is a secret code verification and registration mode selector switch.

Register mode.

When switch S1 is kept in register mode, logic '0' output of gate N4 enables second section of octal 3-state buffer IC2 (74HC244) via pin 19 (OE2). At the same time, OE and WE pins of RAM are taken to logic 1 and logic 0 states, respectively, to enable writing

 


Fig. 2: Power supply for the code lock

of data into the RAM, while 8-bit comparator IC3 is disabled. Thus, the keyboard data (corresponding to a pressed key) at the output of IC1, buffered by IC2, is present at D4 through D7 pins of RAM (IC5). This data gets stored at an address corresponding to the selected page, via 4-way DIP switch S2, and its location is determined by outputs Q1 through Q5 of 12-bit counter IC8.

If the first key-press operation occurs soon after pressing reset switch S3, the first data gets entered at address '0' of the selected page. On release of the key, the counter (IC8) increments by one (address also increments by one), as a result of clock pulse applied to its pin 10. Hence, the next key-pressed data will get written at the incremented address. Thus,

verify mode position of switch S1, the state of $\overline{OE2}$ (pin 19) of IC2, and OE^* and \overline{WE} signals (at pin 20 and 21 of RAM 6116) is reverse of that at register mode. Thus, RAM is selected for reading the data corresponding to the address selected via counter IC8. At the same time, IC3 (74HC688), an 8-bit comparator (configured here as a 5-bit comparator), is enabled. It will compare the entered digit of secret code with the SRAM contents at the location selected by counter IC8, assuming that before the start of verification operation, counter IC8 is reset with the help of reset switch S3 so that first address selected is '0'.

When data is entered via keypad for verification, i.e. to open or close the lock, address of SRAM (IC5) will be

data corresponding to each depression of key is written into sequential locations of the selected page/pages

Operate/verify mode.

In operate/

 


Fig. 3: Actual-size, single-sided PCB for circuits shown in Figs 1 and 2

www.electronicsforu.com

a portal dedicated to electronics enthusiasts

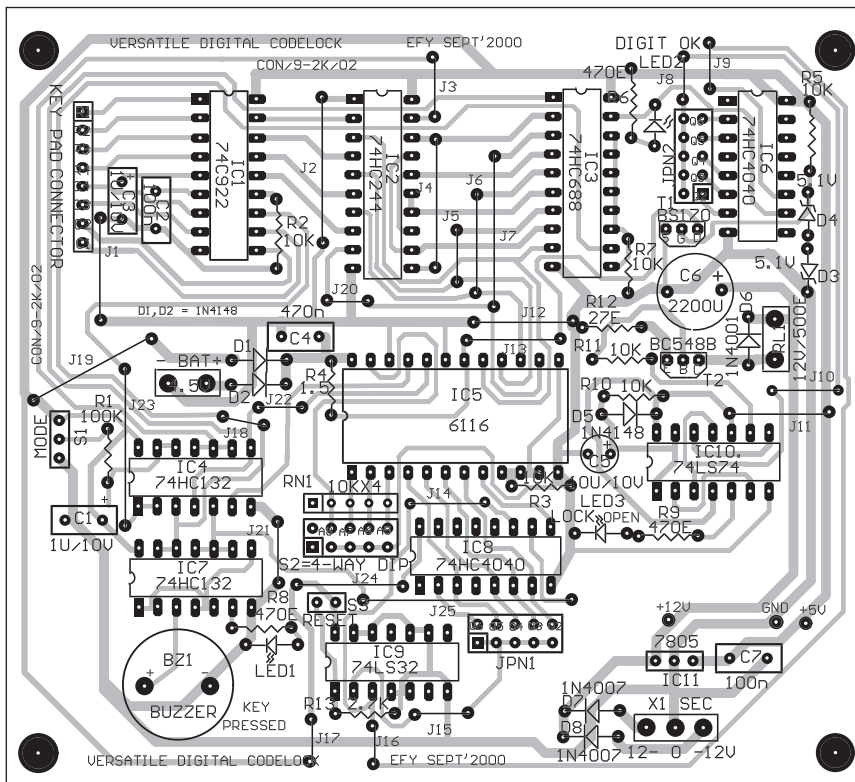


Fig. 4: Component layout for the PCB

incremented automatically whenever a pressed key is released (as during register operation). If the data entered via keyboard is found equal on comparison with stored data, the output (O_{A-B}) pin 19 of magnitude comparator IC3 will go to logic low for the period the keypad key is kept pressed. On release of the key, pin 19 will come back to its previous state (logic 1), thus creating a pulse.

During logic 0 state at pin 19 of IC3, LED2 will glow to indicate correctness of the code entered. When this LED goes 'off', you may enter the next digit of the secret code. If LED2 does not flash, it means that the digit you entered was not the right one. Now press reset switch S3, and start entering the secret code from the first digit onward again. This kind of error and reset operation will, however, not effect the lock status.

Pin 19 of IC3 is connected to clock input pin 10 of IC6 (74HC4040). In verification mode, whenever a correct digit of secret code is entered, LED2 will flash and IC3 will generate a pulse at its pin 19. This pulse will advance the counter IC6, until the auto-reset function (dependent on position of jumper JPN1) is invoked by current count value of IC8. If all the digits of secret code match the

entered digits correctly, IC6 will provide a pulse at one of its output pins (i.e. 7, 6, 5, 3, or 2), depending upon the selected secret code length. Pin 7 will give this pulse for 2-digit length, pin 6 for 4-digit length, pin 5 for 8-digit length, pin 3 for 16-digit length, and pin 2 for 32-digit length of secret code. One of these outputs has to be jumpered to pins 3 and 11 of IC10 using jumper JPN2. In fact, the identical output pins of IC6 and IC8 have to be connected to pins 3/11 (shorted) of IC10 and pin 2 of IC9, respectively, through jumpers JPN2 and JPN1.

IC10 (74LS74) is a dual J-K flip-flop chip, in which both the flip-flops are configured to work in toggle mode. Both the flip-flops get same trigger input through pins 3 and 11 respectively. One of the flip-flops drives LED3 connected to Q1 (pin 5), while output Q2 at pin 9 connected to the base of transistor T2, through resistor R11, drives relay RL1, whose contacts may be used for switching 'on/off' supply to a lock or appliance. One could even use it for locking/unlocking of mains supply to any appliance. When the lock is in 'open' state (i.e. RL1 energised), LED3 will be 'on'. LED3 when 'off', will mean 'closed' state of the lock.

The whole circuit (excluding keypad)

can be assembled on a 12x10 cm single-sided, general-purpose PCB, using a few wire jumpers. However, an actual-size, single-sided PCB for the complete circuit shown in Fig. 1, and that of power supply in Fig. 2, is shown in Fig. 3. The component layout for the PCB is shown in Fig. 4.

The total cost of construction of this circuit will not exceed Rs 800. The use of IC bases for ICs will be a good practice. MOSFET BS170 used in the circuit is very sensitive to static electricity, so it needs to be handled with care. A 100nF bypass capacitor should be used with each chip.

Operation

1. After assembling the circuit, recheck all the connections and apply power without putting the ICs into their bases. Verify the supply and ground pin voltages at all the IC bases. Then plug-in all the chips into their bases, after turning off the power.

2. Put switch S1 in 'register mode' position. Decide a secret code. Suppose it is a 4-digit long code; select a page using 4-way DIP switch S2.

3. Use jumper JPN1 to extend pin 6 of IC8 to pin 2 of IC9 and jumper JPN2 to extend pin 6 of IC6 to pins 3/pin 11 of IC10.

4. Turn 'on' power and press reset switch S3 momentarily. Now press the keypad key corresponding to the first digit of your secret code. LED1 will light up and buzzer will sound briefly. Then enter the rest of the three digits of your secret code one-by-one in a similar way.

5. Flip switch S1 to 'operate/verify' position, since secret code registration is over. You have to remember the switch S2 combination (i.e. page number) and the secret code. To open or close the lock, make sure that switch S2 is in the same position as used during secret code registration. Now press reset switch S3 momentarily and enter secret code digits one-by-one. On entry of each secret code digit correctly, you will get a confirmation signal through flashing of LED2. After entering all digits, the lock will respond (relay will energise). If the code entered was correct, then LED3 will light up. If secret code has not been entered correctly, re-enter the same after pressing reset switch S3. Switch S1, along with the whole circuit, must be kept hidden while in use, except for the keyboard and switches S2 and S3. □

BINARY TO DOTMATRIX DISPLAY DECODER/DRIVER



JUNOMON ABRAHAM

Dotmatrix display is suitable for displaying alphanumeric characters and symbols. Dedicated dotmatrix display driver ICs are available, but these are costly and not easily available commercially. It would therefore be wise to make your own dotmatrix display, using easily available common ICs. One speciality of the circuit design presented here is that you can yourself decide the size and shape of the characters. Further, you can design it for any language.

The principle of displaying a charac-

ter is that, for each character, a corresponding bit pattern is stored in an EPROM. When we supply a particular binary number, corresponding to the input hex digits shown in Table I, bitmap of the character shown against that number gets transferred to the dotmatrix display. For example, for letter 'Z', you are required to enter hex 23 (referred as page address), i.e. 010 on address lines A9 through A7, and 0011 on address lines A6 through A3. Addresses A2 through A0 (location addresses) are supplied by oscillator-cum-

Displayed character	Hex input	Displayed character	Hex input
0	00	L	15
1	01	M	16
2	02	N	17
3	03	O	18
4	04	P	19
5	05	Q	1A
6	06	R	1B
7	07	S	1C
8	08	T	1D
9	09	U	1E
A	0A	V	1F
B	0B	W	20
C	0C	X	21
D	0D	Y	22
E	0E	Z	23
F	0F	+	24
G	10	-	25
H	11	÷	26
I	12	x	27
J	13	=	28
K	14		


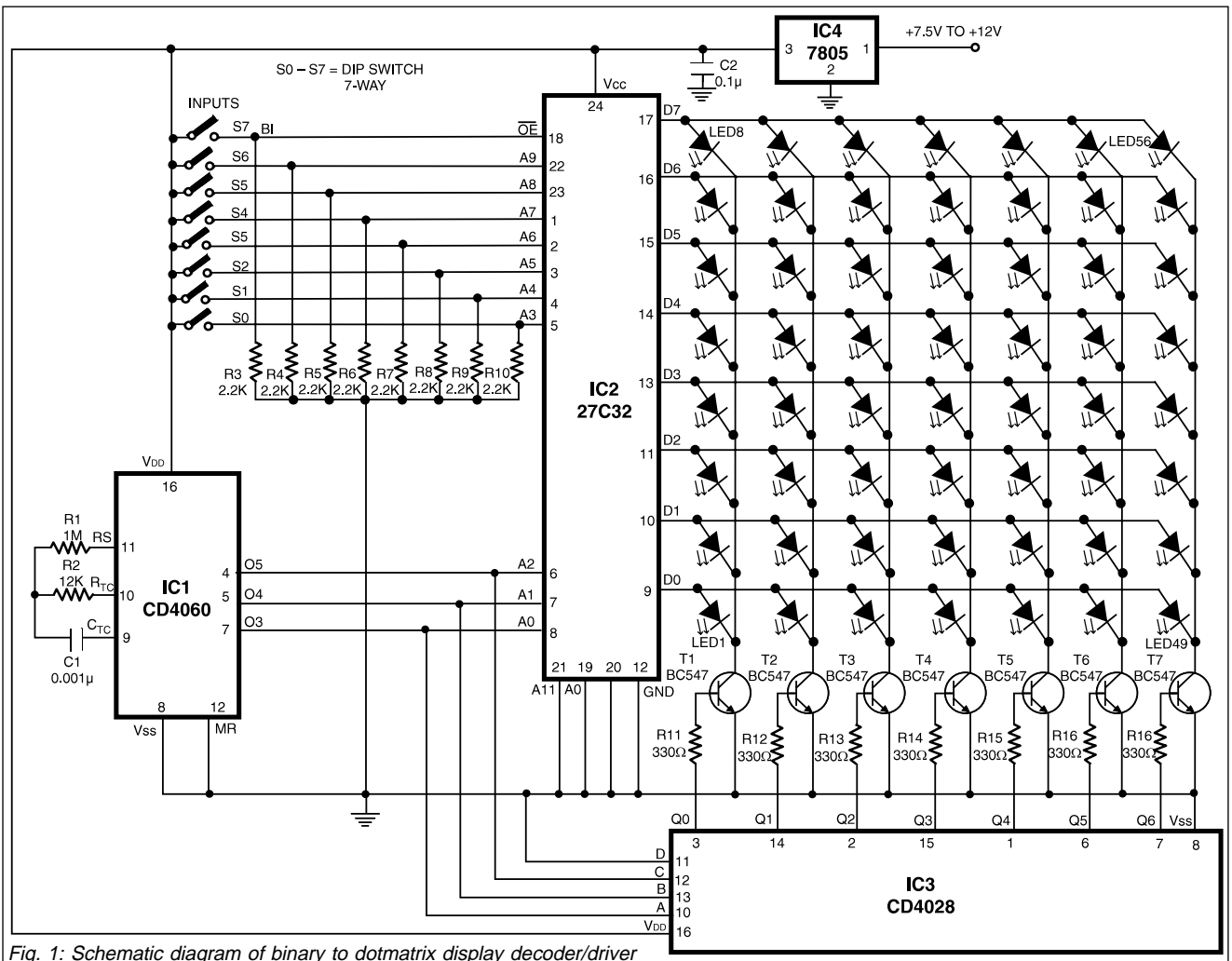


Fig. 1: Schematic diagram of binary to dotmatrix display decoder/driver

 

counter IC CD4060, repetitively outputting the required bit pattern, corresponding to bit pattern for 'Z' in this case.

Let us

Address		050	051	052	053	054	055	056	057
Binary Data	D7	0	0	0	1	0	0	0	X
	D6	0	0	1	1	1	1	0	X
	D5	0	1	0	0	0	0	0	X
	D4	1	0	0	0	0	0	1	X
	D3	1	1	1	1	1	1	1	X
	D2	1	1	0	0	0	0	1	X
	D1	1	0	0	0	0	0	1	X
	D0	1	0	0	0	0	0	1	X
Hexdata		1F	28	48	88	48	28	1F	XX

see how the bitmap of a character is formed to display any specific character. Here we have used an 8 (rows) x 7 (columns) LED display. We can use either a readymade LED matrix display or assemble one ourselves. Fig. 2 shows the LED pattern for letter 'A' whose corresponding bitmap in memory is shown in Table II. Each memory location represents one column of the display. Since seven columns are used, we need seven locations (though counter supplies eight locations/addresses) for each character. The bitmap of each character is stored in one memory page (segment) of eight locations (8th location is not used). The data from the corresponding pages/locations are transferred to the display by scanning the memory locations and columns of the display simultaneously.

The EPROM used for the purpose is 27C32, with a memory capacity of 4 kB. If you want to utilise its full capacity, you can store codes for up to 512 characters. The circuit shown here uses 1 kB of memory space and can show up to 128 characters.

Each character bitmap is stored in a memory page, and a particular memory page (character) is selected by giving its address. This page address is selected via DIP switches S0 through S7. Each page is scanned with the help of counter CD4060, which has an inbuilt oscillator, whose outputs are connected to A0, A1, and A2 lines. The same lines are con-

nected to a decoder (4028) to drive the columns of the display. The rows are connected to the data outputs D0 through D7 of the EPROM. Thus, when a memory location is addressed, its data is output on the corresponding column. The eight memory locations corresponding to the se-

lected letter are consecutively scanned. This process repeats itself at a fast rate. Due to persistence of vision, one sees a steady display of the corresponding memory map.

Table III shows the data needed to be stored in specific EPROM locations. It ca-

Address	Data	Address	Data	Address	Data	Address	Data	Address	Data	Address	Data
000	3C	038	C1	070	FF	0A8	FF	0E0	62	118	81
001	42	039	82	071	91	0A9	01	0E1	91	119	83
002	81	03A	84	072	91	0AA	01	0E2	91	11A	85
003	81	03B	98	073	91	0AB	01	0E3	91	11B	99
004	82	03C	90	074	91	0AC	01	0E4	91	11C	A1
005	42	03D	B0	075	81	0AD	01	0E5	91	11D	C1
006	3C	03E	C0	076	81	0AE	01	0E6	4E	11E	81
007	xx	03F	xx	077	xx	0AF	xx	0E7	xx	11F	xx
008	00	040	6E	078	FF	0B0	FF	0E8	80	120	10
009	00	041	91	079	90	0B1	40	0E9	80	121	10
00A	41	042	91	07A	90	0B2	20	0EA	80	122	10
00B	FF	043	91	07B	90	0B3	10	0EB	FF	123	
00C	01	044	91	07C	90	0B4	20	0EC	80	FE	
00D	00	045	91	07D	80	0B5	40	0ED	80	124	10
00E	00	046	6E	07E	80	0B6	FF	0EE	80	125	10
00F	xx	047	xx	07F	xx	0B7	xx	0EF	xx	126	10
010	61	048	64	080	3C	0B8	FF	0F0	FE	127	xx
011	83	049	92	081	42	0B9	40	0F1	01	128	10
012	85	04A	91	082	81	0BA	20	0F2	01	129	10
013	89	04B	91	083	8D	0BB	18	0F3	01	12A	10
014	91	04C	91	084	89	0BC	04	0F4	01	12B	10
015	61	04D	92	085	4A	0BD	02	0F5	01	12C	10
016	00	04E	7C	086	2C	0BE	FF	0F6	FE	12D	10
017	xx	04F	xx	087	xx	0BF	xx	0F7	xx	12E	10
018	82	050	1F	088	FF	0C0	3C	0F8	F8	12F	xx
019	81	051	28	089	10	0C1	42	0F9	04	130	10
01A	81	052	48	08A	10	0C2	81	0FA	02	131	10
01B	91	053	88	08B	10	0C3	81	0FB	01	132	10
01C	B1	054	48	08C	10	0C4	81	0FC	02	133	54
01D	D1	055	28	08D	10	0C5	42	0FD	04	134	10
01E	8E	056	1F	08E	FF	0C6	3C	0FE	F8	135	10
01F	xx	057	xx	08F	xx	0C7	xx	0FF	xx	136	10
020	08	058	FF	090	00	0C8	FF	100	FF	137	xx
021	18	059	91	091	00	0C9	90	101	02	138	00
022	28	05A	91	092	81	0CA	90	102	04	139	44
023	48	05B	91	093	FF	0CB	90	103	08	13A	28
024	BF	05C	91	094	81	0CC	90	104	04	13B	10
025	08	05D	91	095	00	0CD	90	105	02	13C	28
026	08	05E	6E	096	00	0CE	60	106	FF	13D	44
027	xx	05F	xx	097	xx	0CF	xx	107	xx	13E	00
028	E1	060	3C	098	86	0D0	3C	108	83	13F	xx
029	A1	061	42	099	81	0D1	42	109	44	140	28
02A	A1	062	81	09A	81	0D2	81	10A	28	141	28
02B	A1	063	81	09B	81	0D3	81	10B	10	142	28
02C	A1	064	81	09C	FE	0D4	85	10C	28	143	28
02D	92	065	42	09D	80	0D5	42	10D	44	144	28
02E	8C	066	24	09E	80	0D6	3D	10E	83	145	28
02F	xx	067	xx	09F	xx	0D7	xx	10F	xx	146	28
030	3C	068	FF	0A0	FF	0D8	FF	110	80	147	xx
031	4A	069	81	0A1	10	0D9	90	111	40	Note: xx =	
032	91	06A	81	0A2	10	0DA	90	112	20	Don't care	
033	91	06B	81	0A3	28	0DB	98	113	1F		
034	91	06C	81	0A4	44	0DC	94	114	20		
035	4A	06D	42	0A5	82	0DD	92	115	40		
036	24	06E	3C	0A6	81	0DE	61	116	80		
037	xx	06F	xx	0A7	xx	0DF	xx	117	xx		

ters only to numerics, capital English letters, and some symbols. You are at liberty to store bit patterns for any other data, in any other style, in the EPROM.

The input 'BI' indicating blanking input (actually this is the OE signal of EPROM) can be used for blanking the

display. You can also use this line for converting it into a blinking display by connecting it to a suitable output pin of counter CD4060.

You can also adapt the circuit for responding to ASCII input values by storing the character bit pattern in memory

pages, their address being equal to the ASCII value of that character. Moreover, it is possible to display characters of any language and, if needed, the size of the display can also be modified by using some additional hardware.

AUTOMATIC SPEED-CONTROLLER FOR FANS AND COOLERS



PRADEEP VASUDEVA

During summer nights, the temperature is initially quite high. As time passes, the temperature starts dropping. Also, after a person falls asleep, the metabolic rate of one's body decreases. Thus, initially the fan/cooler needs to be run at full speed. As time passes, one has to get up again and again

after some time, and to slow later on. After a period of about eight hours, the fan/cooler is switched off.

Fig. 1 shows the circuit diagram of the system. IC1 (555) is used as an astable multivibrator to generate clock pulses. The pulses are fed to decade dividers/counters formed by IC2 and IC3. These

The first two outputs of IC3 (Q0 and Q1) are connected (ORed) via diodes D1 and D2 to the base of transistor T1. Initially output Q0 is high and therefore relay RL1 is energised. It remains energised when Q1 becomes high. The method of connecting the gadget to the fan/cooler is given in Figs 3 and 4.

It can be seen that initially the fan shall get AC supply directly, and so it shall run at top speed. When output Q2 becomes high and Q1 becomes low, relay RL1 is turned 'off' and relay RL2 is switched 'on'. The fan gets AC through a resistance and its speed drops to medium. This continues until output Q4 is high.

When Q4 goes low and Q5 goes high, relay RL2 is switched 'off' and relay RL3 is activated. The fan now runs at low speed.

Throughout the process, pin 11 of the IC is low, so T4 is cut off, thus keeping T5 in saturation and RL4 'on'. At the end of the cycle, when pin 11 (Q9) becomes high, T4 gets saturated and T5

is cut off. RL4 is switched 'off', thus switching 'off' the fan/cooler.

Using the circuit described above, the fan shall run at high speed for a comparatively lesser time when either of Q0 or Q1 output is high. At medium speed, it will run for a moderate time period when any of three outputs Q2 through Q4 is high, while at low speed, it will run for a much longer time period when any of the four outputs Q5 through Q8 is high.

If one wishes, one can make the

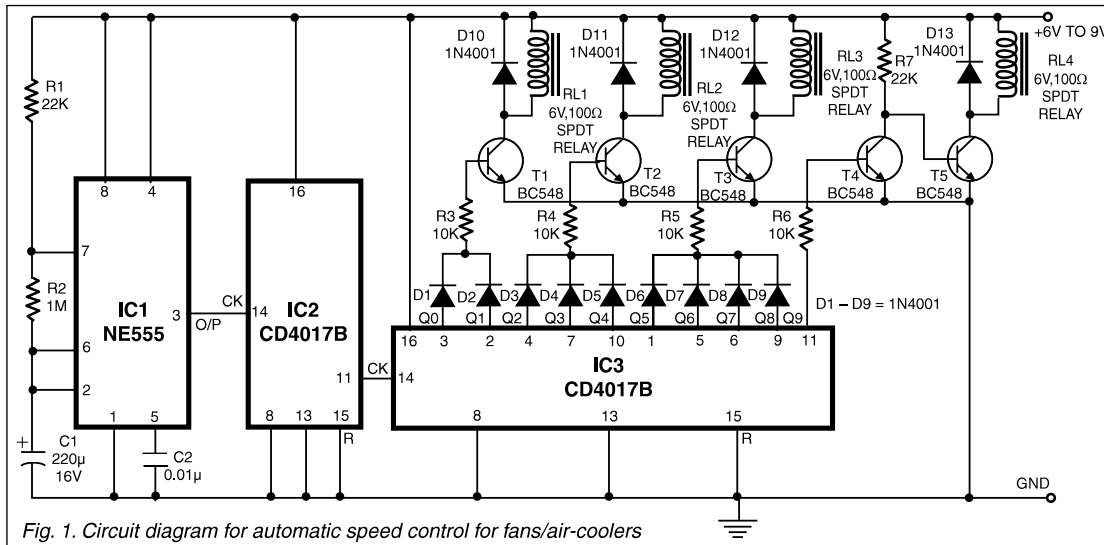


Fig. 1. Circuit diagram for automatic speed control for fans/air-coolers

to adjust the speed of the fan or the cooler.

The device presented here makes the fan run at full speed for a predetermined time. The speed is decreased to medium

ICs act as divide-by-10 and divide-by-9 counters, respectively. The values of capacitor C1 and resistors R1 and R2 are so adjusted that the final output of IC3 goes high after about eight hours.

 


Fig. 2. Existing arrangement for fan speed control

 


Fig. 3. Modified arrangement for speed control

 


Fig. 4. Speed-control arrangement for cooler with different windings for various speeds

fan run at the three speeds for an equal amount of time by connecting three decimal decoded outputs of IC3 to each of the transistors T1 to T3. One can also get more than three speeds by using an additional relay, transistor, and associated components, and connecting one or more outputs of IC3 to it.

In the motors used in certain coolers

there are separate windings for separate speeds. Such coolers do not use a rheostat type speed regulator. The method of connection of this device to such coolers is given in Fig. 4.

The resistors in Figs 2 and 3 are the tapped resistors, similar to those used in manually controlled fan-speed regulators. Alternatively, wire-wound resistors of suitable wattage and resistance can be used.

BLOWN FUSE INDICATOR

ASHUTOSH KUMAR SINHA

Generally, when an equipment indicates no power, the cause may be just a blown fuse. Here is a circuit that shows the condition of fuse through LEDs. This compact circuit is very useful and reliable. It uses very few components, which makes it inexpensive too.

Under normal conditions (when fuse is alright), voltage drop in first arm is $2V + (2 \times 0.7V) = 3.4V$, whereas in second

arm it is only 2V. So current flows through the second arm, i.e. through the green LED, causing it to glow; whereas the red LED remains off.

When the fuse blows off, the supply to green LED gets blocked, and because only one LED is in the circuit, the red LED glows. In case of power failure, both LEDs remain 'off'.

This circuit can be easily modified to produce a siren in fuse-blown condition (see Fig. 2). An optocoupler is



used to trigger the siren. When the fuse blows, red LED glows. Simultaneously it switches 'on' the siren.

In place of a bicolour LED, two LEDs

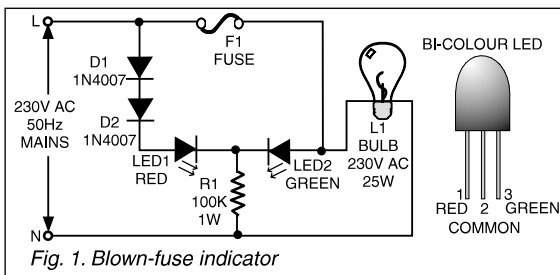


Fig. 1. Blown-fuse indicator

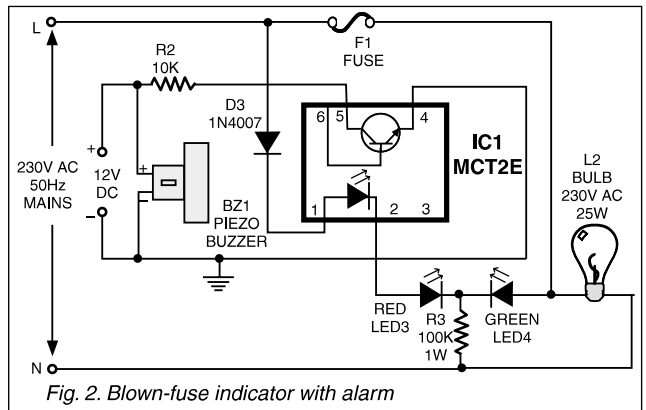


Fig. 2. Blown-fuse indicator with alarm

of red and green colour can be used. Similarly, only one diode in place of D1 and D2 may be used. Two diodes are used to increase the voltage drop, since the two LEDs may produce different voltage drops.

OVER-/UNDER-VOLTAGE CUT-OFF WITH ON-TIME DELAY

K. UDHAYA KUMARAN, VU3GTH

Here is an inexpensive auto cut-off circuit, which is fabricated using transistors and other discrete components. It can be used to protect loads such as refrigerator, TV, and VCR from undesirable over and under line voltages, as well as surges caused due to sudden failure/resumption of mains power supply. This circuit can be used directly

as a standalone circuit between the mains supply and the load, or it may be inserted between an existing automatic/manual stabiliser and the load.

The on-time delay circuit not only protects the load from switching surges but also from quick changeover (off and on) effect of



over-/under-voltage relay, in case the mains voltage starts fluctuating in the vicinity of under- or over-voltage preset points. When the mains supply goes out of preset (over- or under-voltage) limits, the relay/load is turned 'off' immediately, and it is turned 'on' only when AC mains voltage

settles within the preset limits for a period equal to the 'on' time delay period. The on-time delay period is presettable for 5 seconds to 2 minutes dura-

 


Fig. 1: Power supply

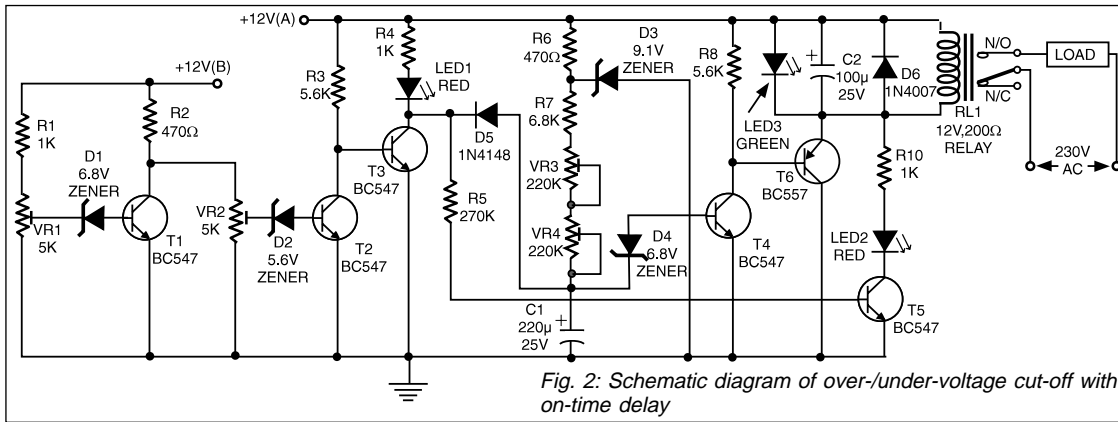


Fig. 2: Schematic diagram of over-/under-voltage cut-off with on-time delay

base of T4 via zener D4 is connected to capacitor C1, which was in discharged condition. Thus, LED3 and relay RL1 or load remain 'off'.

Capacitor C1 starts charging slowly towards +12V(A) rail via resistors R6 and R7, and presets

tion, using presets VR3 and VR4. For electronic loads such as TV and VCR, the on-time delay may be set for 10 seconds to 20 seconds. For refrigerators, the delay should be preset for about 2 minutes duration, to protect the compressor motor from frequently turning 'on' and 'off'.

In this circuit, the on-time and off-time delays depend on charging and discharging time of capacitor C1. Here the discharge time of capacitor C1 is quite less to suit our requirement. We want that on switching 'off' of the supply to the load, the circuit should immediately be ready to provide the required on-time delay when AC mains resumes after a brief interruption, or when mains AC voltage is interrupted for a short period due to over-/under-voltage cut-off operation. This circuit is also useful against frequent power supply interruptions resulting from loose electrical connections; be it at the pole or switch or relay contacts, or due to any other reason.

Here supply for the over- and under-voltage sampling part of the circuit [marked +12V(B)] and that required for the rest of the circuit [marked +12V(A)] are derived separately from lower half and upper half respectively of centre-tapped secondary of step-down transformer X1, as shown in Fig. 1. If we use common 12V DC supply for both parts of the circuit, then during relay 'on' operation, 12V DC to this circuit would fall below preset low cut-off voltage and thus affect the proper operation of the sampling circuit. The

value of filtering capacitor C4 is so chosen that a fall in mains voltage may quickly activate under-voltage sensing circuit, should the mains voltage reach the low cut-off limit.

In the sampling part of the circuit, wired around transistor T1, presets VR1 and VR2 are used for presetting over- or under-voltage cut-off limits, respectively. The limits are set according to load voltage requirement, as per manufacturer's specifications.

Once the limits have been set, zener D1 will conduct if upper limit has been exceeded, resulting in cut-off of transistor T2. The same condition can also result when mains voltage falls below the under-voltage setting, as zener D2 stops conducting. Thus, in either case, transistor T2 is cut-off and transistor T3 is forward biased via resistor R3. This causes LED1 to be 'on'. Simultaneously, capacitor C2 quickly discharges via diode D5 and transistor T3. As collector of transistor T3 is pulled low, transistors T4 and T5 are both cut-off, as also transistor T5. Thus, LED2 and LED3 are 'off' and the relay is de-energised.

Now, when the mains voltage comes within the acceptable range, transistor T2 conducts to cut-off transistor T3. LED1 goes 'off'. Transistor T5 gets forward biased and LED2 becomes 'on'. However, transistors T4 and T5 are still 'off', since

VR3 and VR4. When the potential across capacitor C1 reaches 6.8V (after a delay

Circuit condition	LED1	LED2	LED3	Relay/Load
Over or under voltage cut-off in operation	ON	OFF	OFF	OFF
On-time delay in operation	OFF	ON	OFF	OFF
AC voltage normal after on-time delay	OFF	OFF	ON	ON

termed as on-time delay) to breakdown zener D4, transistor T4, as also transistor T5, gets forward biased, to switch 'on' LED3 and relay RL1 or load, while LED2 goes 'off'. Should the mains supply go out of preset limits before completion of the on-time delay, capacitor C1 will immediately discharge because of conduction of transistor T3, and the cycle will repeat until mains supply stabilises within preset limits for the on-time delay period.

The on-time delay is selected by adjusting presets VR3 and VR4, and resistor R6. Zener diode D3 is used to obtain regulated 9.1 volts for timing capacitor C1, so that preset on-time delay is more or less independent of variation in input DC voltage to this circuit (which would vary according to the mains AC voltage). To switch 'off' the relay/load rapidly during undesired mains condition, the timing capacitor C1 is discharged rapidly to provide complete control over turning 'on' or 'off' of relay RL1 (or the load). The functioning of the LEDs and relay, depending on the circuit condition, is summarised in Table I.

ONE BUTTON FOR STEP, RUN, AND HALT COMMANDS



(BASED ON MOTOROLA APPLICATION NOTE)

The logic signals to step, run, and halt a computer or other appropriate digital devices or system may be generated by this circuit, which is operated by just a single pushbutton. The only active devices used are a dual

monostable and a dual flip-flop ICs. The run command occurs if the button is held down for a time exceeding about 300 ms.

This time (300 ms) represents an excellent compromise between circuit speed and accuracy. If this duration is made

be halted if the pushbutton is depressed momentarily when the circuit is in the run mode.

As shown in the figure, module A1 acts as an effective switch debouncer for the pushbutton. For a step command, poking the button quickly will cause 'Q' output of A1 to go high and trigger module A2 (the monostable for run-and-step operations). The Q output of A1 is also fed to 'D' input of module A3 (the run-and idle latch). At the same time, the active low \bar{Q} output of A1 triggers the step one-shot A4, yielding the step function.

The sequence of events discussed above

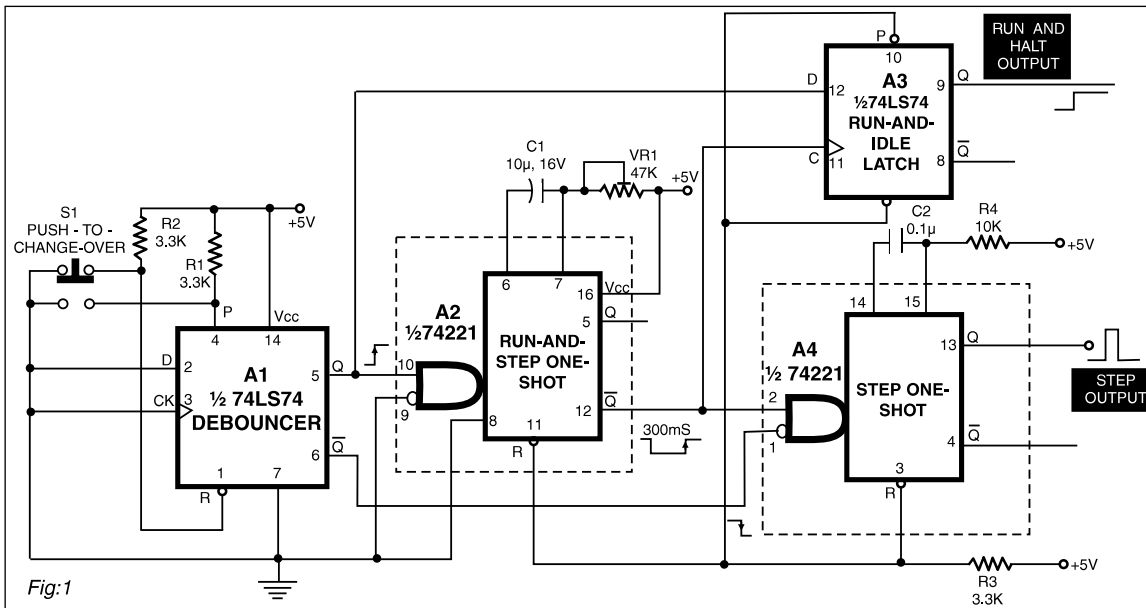


Fig:1

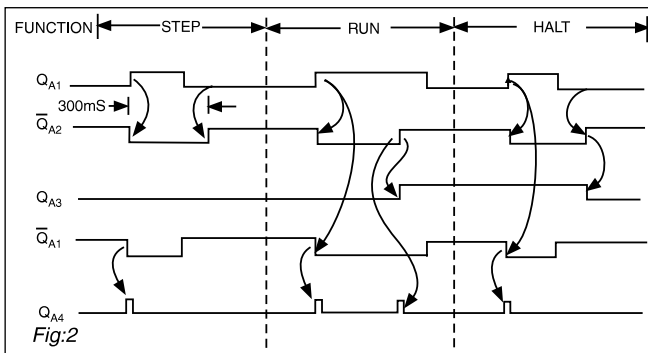


Fig:2

one-shot and a dual flip-flop ICs.

The step command is generated each time the pushbutton is depressed momen-

tarily. The run command occurs if the button is held down for a time exceeding about 300 ms. Finally, the device will

much shorter, the circuit may fail to differentiate between the step and run commands, and may generate the run command when the step command is desired, or vice versa. Also, repeatedly pressing the button rapidly to initiate step functions will generate the run

command if the duration is set for much more than 300 ms. Finally, the device will

300 ms after the pushbutton is depressed. The positive going (trailing) edge of this pulse then clocks the state of the pushbutton (as detected by A1) into A3. If the circuit/computer is in run mode, then pressing of the button will cause the circuit to halt the computer by clocking in a logic '0' (synchronously available at data input pin) to the run-and-idle latch A3. Note that the step pulse generated at the start of the halt sequence, as shown in the timing diagram, is of no consequence, since when the step is received, the machine is already in the run mode and will override that command.

October

2000

MOSFET-BASED 50Hz SINEWAVE UPS-CUM-EPS



R.V. DHEKALE AND S.D. PHADKE

Most of the UPS (uninterrupted power supplies) available in the market internally use a frequency ranging from 100 Hz to 50 kHz. The regulation of output voltage is done using the pulse width modulation technique, which produces a quasi-square waveform output from the inverter transformer. Such an output waveform produces lots of noise, which is not desirable for a computer and other sensitive equipment. This voltage waveform can drive a computer, but not the tubelight, fan, EPBAX, TV, VCR, etc properly. The advantage offered by a UPS is that its changeover period is quite low, so that the computer or any other sensitive load is not interrupted during the mains failure.

EPS (emergency power supply) of various brands, providing 50Hz squarewave output, can drive the computer, tubelight, TV, VCR, fan, etc, but considerable noise is produced from the EPS or the load. Another drawback of an EPS is that its changeover period is relatively high, so the computer may get reset or continuity of the play mode of the VCR may get interrupted on mains failure.

The circuit

A 50Hz sinewave offline UPS-cum-EPS circuit is presented here which produces a sinewave output with very low noise level. It drives the equipment/load (< 250 watts), which normally operates on 230V, 50Hz AC. Changeover period of this system is less than 1 millisecond so that no

interruption in operation of a computer or continuity of the play mode of a VCR and TV is caused. The complete schematic diagram of the circuit is shown in Fig. 2.

When mains is present and is within the specified limits, the same is fed to the load. At the same time, battery is charged. If mains voltage goes below 170 volts (or mains power fails) or above 270 volts, system changes over from mains to back-up mode. In the back-up mode, battery voltage of 12V DC is converted into 230V AC and applied to the load within 1 millisecond.

However, if battery voltage drops below 10V DC, or output voltage goes below 225V AC, there will be a visual and audible indication of low-battery state. During this warning period, one can save the data and switch off the computer safely. But during the low-battery indication, if the computer or load is not switched off, it remains on back-up mode. After the end of back-up time, system switches off automatically, due to activation of battery's deep discharge cut-out circuit, which reduces the power consumption from the battery to a negligible value (only 90 mA).

Inverter control circuit. It uses the basic squarewave (astable multivibrator) oscillator employing IC 555, with 5.1V supply voltage derived from 12V battery by using 5.1V zener ZD3 in series with a resistance. Astable multivibrator is designed for a frequency of 100 Hz, which can be varied above or below 100 Hz using preset PR1. The frequency 'f' of astable multivibrator is given by the relationship:

$$f = \frac{1.44}{(R_A + 2R_B)C} \text{ Hz}$$

where R_B = In-circuit resistance of preset PR1.

If R_A = 220 ohms and R_B = 15 kilo-ohms, then f = 100 Hz. Due to the tolerance of the component values, observed frequency may not be exactly

equal to 100 Hz, and therefore preset PR1 may need to be suitably adjusted.

The output of the astable multivibrator is given to pin 5 of the bistable multivibrator wired around IC

PARTS LIST

Semiconductors:

IC1	- NE555 timer
IC2	- 7473 dual JK-flip-flop
IC3	- 7812 regulator, 12V
IC4	- DB107 bridge rectifier, 1A
IC5	- TL062 dual op-amp
IC6, IC7	- μ A741 op-amp
D1, D2, D5,	
D6, D7	- 1N4148 switching diode
D3, D3',	
D4, D4'	- 1N5408 rectifier diode, 3A
D8	- Rectifier diode, 16A-(TO3)
ZD1-ZD7	- 5.1V, 1W zener diode
T1-T3	- BEL187 npn transistor
TR	- BT136 triac
SCR1	- BT169 SCR
M1-M6	- IRF250 MOSFET
LED1-LED6	- 3mm LED

Resistors (all $\frac{1}{4}$ -watt, $\pm 5\%$ carbon, unless stated otherwise):

R_A	- 220-ohm
R_C	- 4.7-ohm, W/W 20W
R1, R3-R6, R8	
R12-R15, R18	
R20, R21	- 1-kilo-ohm
R2	- 100-ohm, 1W
	- 4.7-kilo-ohm
R7	- 4.7-ohm
R9	- 220-ohm
R10, R11	- 68-kilo-ohm
R16	- 100-ohm
R17	- 470-ohm
R19, R23	- 1.2-kilo-ohm
R22	- 39-kilo-ohm
PR1 (R_B)	
PR2, PR3,	- 22-kilo-ohm preset
PR6	- 10-kilo-ohm preset
PR4, PR5	- 1-Meg-ohm preset

Capacitors:

C1	- 0.01 μ F ceramic disk
C2	- 3 x 0.47 μ F, 600V polyester
C3, C13	- 0.1 μ F ceramic disk
C4-C7	- 1000 μ F, 16V electrolytic
C8	- 100 μ F, 25V electrolytic
C9	- 2200 μ F, 40V electrolytic
C10	- 0.47 μ F, 25V electrolytic
C11, C12	- 0.22 μ F polyester

Miscellaneous:

F1	- 5A cartridge fuse
F2	- 16A cartridge (slow-blow) fuse
X1	- Primary 9-0-9V/20A Sec. 230V section (1A), Sec. 600V section (300mA used as L1) transformer
X2	- 230V AC primary to 16V-0-16V, 3A secondary transformer.
X3	- 230V AC primary to 0-12V, 500mA secondary transformer
SW1	- DPDT switch, 5A
SW2	- SPDT slide switch
CB	- MCCB 4A
BZ1	- Piezo buzzer
L1	- 1 Henry (part of X1, 600V tapping)
L2, L3	- 100 μ H (20T, 22SWG, air-core, 8mm dia.)
RLY	- 57DP-12-2C2 O/E/N 12V, 150-ohm (2-changeover) relay

 


Fig. 1: Proposed front and rear panel layouts

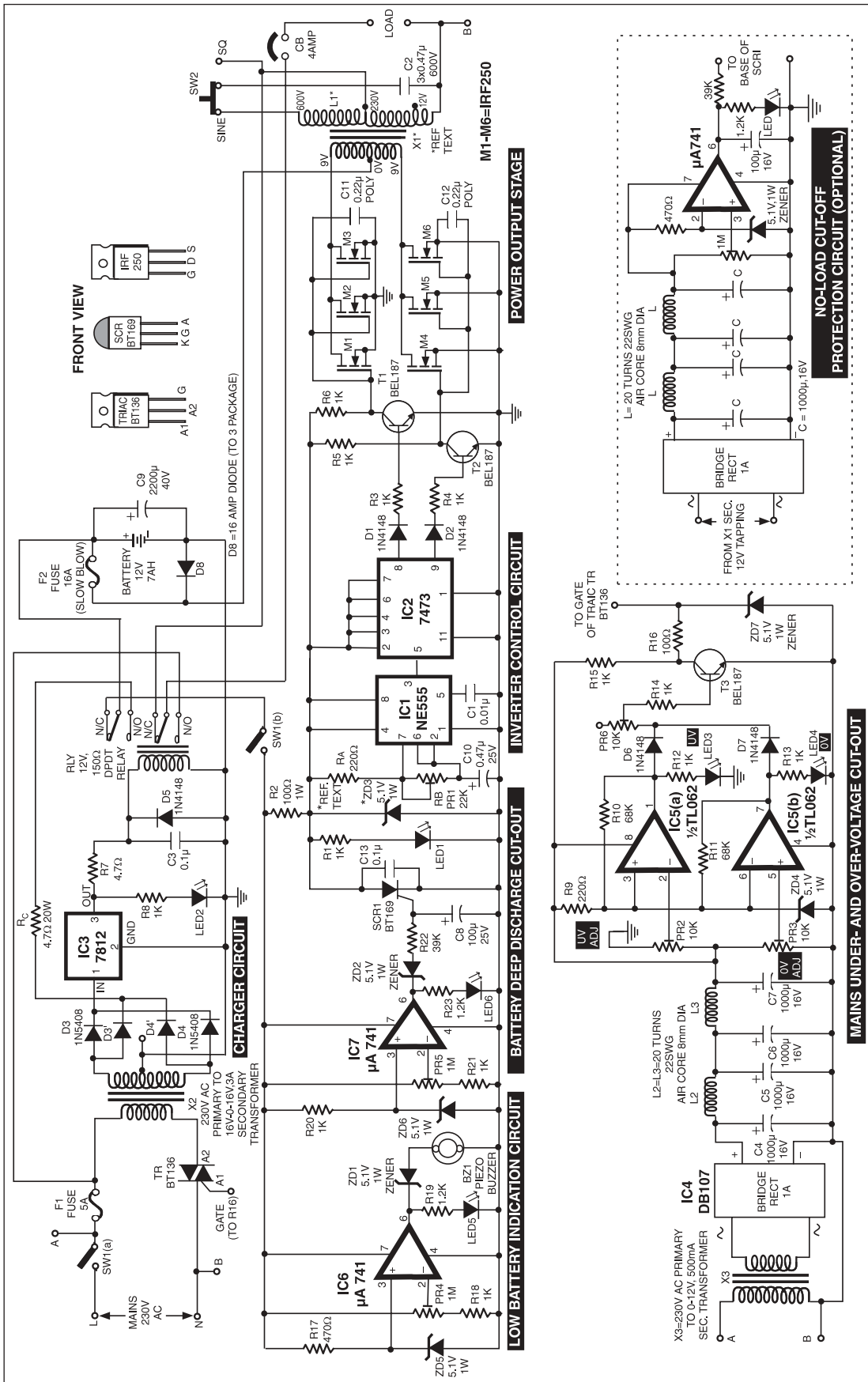


Fig. 2: Schematic diagram of MOSFET-based sine wave inverter optional circuit of no-load/over-load protector (within dotted lines)

7473, which produces the two 50Hz square-wave outputs at its pins 8 and 9 with a phase difference of 180 degrees between the two. One of the outputs is coupled to the base of transistor T1 through diode D1 and series current-limiting resistor R3, while the second output is given to the base of transistor T2 through diode D2 and series resistor R4. Transistors T1 and T2 act as MOSFET drivers.

Power output stage. The collector of transistor T1 is connected to the gates of MOSFETs M1 through M3 (referred to as bank 1), while that of transistor T2 is connected to the gates of MOSFETs M4 through M6 (referred to as bank 2). MOSFETs M1 through M3 are connected in parallel—gates of MOSFETs M1 through M3 and those of MOSFETs M4 through M6 are made common. Similarly, drains and sources of MOSFETs in each bank are paralleled as

 


Fig. 3: Battery current vs load (squarewave O/P)

 


Fig. 4: Battery current vs load (sinewave O/P)

the collector of transistor T2 is 0.7V. Hence, MOSFETs of bank 2 are cut-off while those of bank 1 conduct. This results in a large DC current swing through the other half of the inverter transformer X1 primary. In this way, two banks of the MOSFETs conduct alternately to produce 230V AC, 50 Hz across the secondary of the inverter transformer X1. Inductance L1

shown in the circuit. Drains of MOSEFTs of one bank are connected to one extreme taping of 9-volt primary of the inverter transformer X1, and that of the MOSEFTs of the second bank are connected to the other extreme 9-volt taping of the same transformer. Centre tap of the primary is directly connected to the positive terminal of 12V, 7Ah battery. Capacitor C2 is connected across the secondary of the inverter transformer, either directly or via inductor L1 (wound on the same core as extension of secondary winding), using sine/square slide switch SW2.

When mains power fails, relay gets de-energised and 12V battery supply is fed to the control circuit through top contacts of the relay to produce squarewave outputs at pin Nos. 8 and 9 of IC 7473 with a frequency of 50 Hz. At any instant, if voltage at pin 8 of IC2 is +5V, the voltage at pin 9 of IC2 is 0V, and vice versa. Therefore, when transistor T1 conducts, transistor T2 is cut off, and vice versa. When transistor T1 conducts, the voltage at collector of transistor T1 drops to 0.7 V, and therefore MOSFETs of bank 1 remain cut off while collector of transistor T2 is at 5V. Thus, MOSFETs of bank 2 conduct and the current flows through one-half of inverter transformer X1 primary. During the next half cycle, the voltage at pin 8 of IC2 is 0V and that at pin 9 is +5V. As a result, the voltage at the collector of transistor T1 is +5V and that at

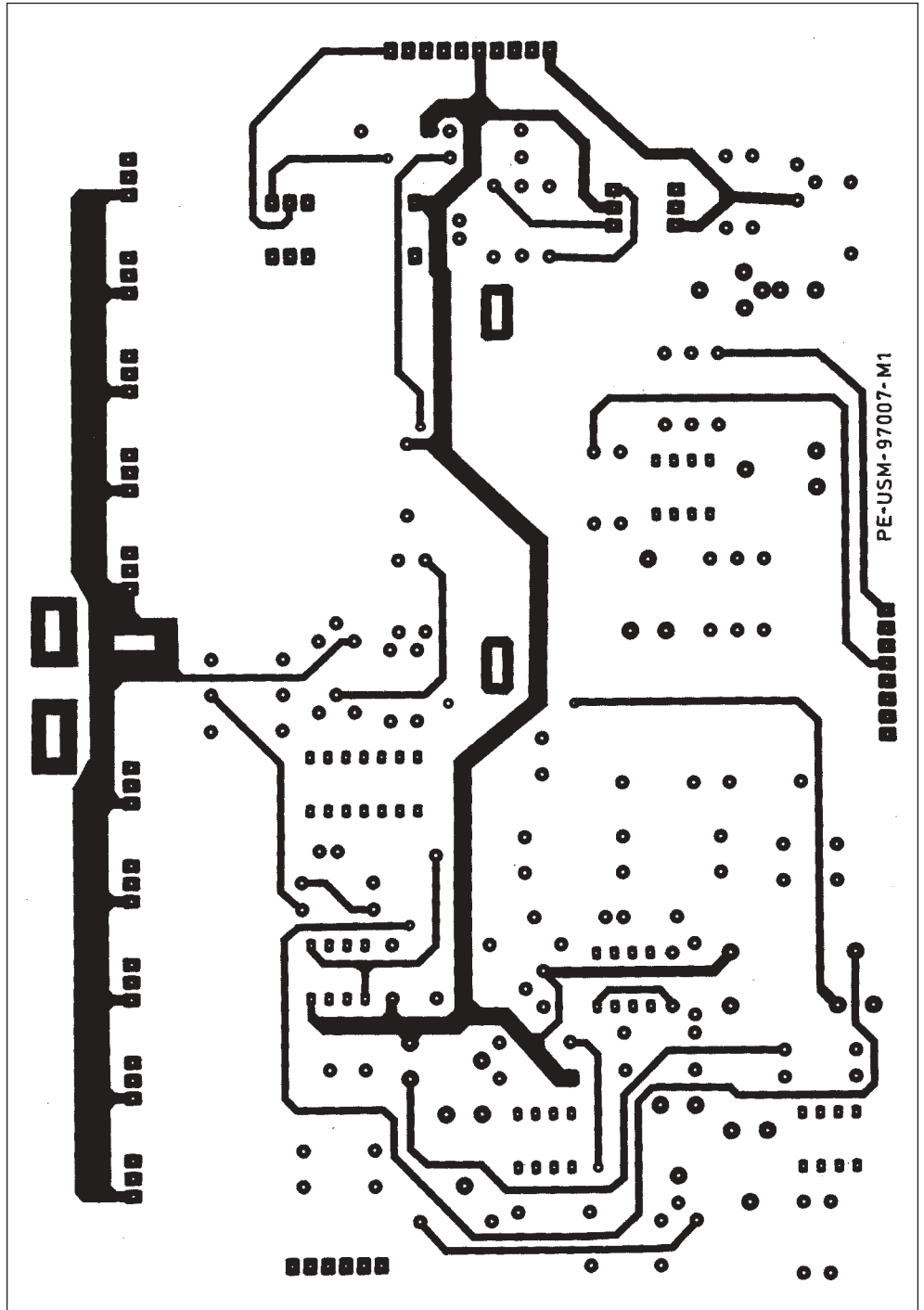


Fig. 5: Actual-size component-side track layout for the PCB

 


Fig. 6: Actual-size solder-side track layout for the PCB.

and capacitor C2 on the secondary side act as filter/resonant circuit (at 50 Hz) to produce a waveform approaching a sine wave. LED1, when 'on', indicates that the system is on back up.

Charger circuit. This circuit comprises step-down transformer X2, followed by rectifier, regulator, and double-changeover 12V relay RLY. Mains supply of 230V AC is applied across the primary

of the transformer through triac BT136. The gate of the triac is connected to the output of over-/under-voltage cut-off circuit. As long as the mains voltage is between 170 and 270 volts, +5V is provided to the gate of the triac and hence it conducts. If AC mains voltage goes out of the above-mentioned limits, the gate voltage falls to 0.7 volt and the triac does not

conduct. When triac conducts, 16-0-16V AC voltage is developed across the secondary of X2. It is converted into DC voltage by the diodes D3 and D4, and the rectified output is given to the input of the 12V regulator 7812 (IC3). The output of the regulator is connected across the relay coil through series resistor R7, which ensures that the relay just operates when AC mains is at 170 volts (or more).

When mains voltage is within the range of 170-270 volts, relay activates. In this mode, mains voltage is directly routed to the load through N/O contacts (lower) of relay RLY and 4-amp rated contact breaker (CB). LED2 indicates that the system is on mains. At the same time, the rectified voltage from diodes D3' and D4' is made available through N/O contacts (upper) of relay RLY for charging the battery via charging resistance R_c. If the mains supply fails or goes out of the range of 170-270 volts, relay de-energises and the battery supply of 12V is connected to the inverter circuit through N/C contacts (upper). The voltage developed by the inverter goes to the output socket of UPS through the N/C contacts (lower) via 4-amp CB.

Under-/over-voltage cut-out. The 230V AC mains is stepped down to 12V AC, using transformer X3. It is rectified by the bridge rectifier and filtered by two Pi (π) section filters to reduce the level of ripple voltage. The filtered DC voltage is applied to dual op-amp IC5 (used as dual comparator). The reference voltage for the comparators is devel-

oped across zener diode ZD4, which is connected to the filtered DC positive rail via resistor R9. Even if the AC mains voltage varies between 170V and 270V, the voltage across zener ZD4 remains constant at 5.1 volts. The cathode of zener diode ZD4 is connected to the inverting input of the comparator IC5(b) and non-inverting input of the comparator IC5(a).

Preset PR2 can be used to vary the

inverting terminal voltage of the comparator IC5(a) above and below the reference voltage of 5.1V. Similarly, non-inverting input of the comparator IC5(b) can also be varied above and below the 5.1V reference voltage applied to the inverting input of IC5(b), using preset PR3.

Preset PR2 is adjusted such that when AC mains voltage goes below 170 volts, the voltage at inverting input of comparator IC5(a) goes below 5.1 volts, so that its output goes high. As a result, transistor T3 conducts and its collector voltage (connected to the gate of triac TR) drops to 0.7 volt, and hence the triac cuts off. This causes relay RLY to de-energise and the system changes over to back-up mode of operation. Glowing of LED3 indicates the under-voltage condition.

Similarly, preset PR3 is adjusted such that when mains voltage goes above 270V AC, the voltage at non-inverting input of the comparator IC5(b) goes above 5.1 volts, so that its output goes high to eventually cut-off the triac, and the system again operates in the backup mode. The over-voltage indication is shown by glowing of LED4.

This means that as long as the mains voltage is within the range of 170V AC to 270 V AC, the voltage at the collector of transistor T3 is 12 volts, and hence triac TR conducts fully and relay RLY activates. As a result, the system remains on mains mode. Diodes D6 and D7 act as 2-input wired-OR gate for combining the outputs from the two comparators and prevent the output of one comparator going into the output terminal of other comparator. Zener diode ZD6 is used to limit the gate voltage of the triac to 5.1 volts.

Low-battery indicator. This circuit is wired around op-amp μ A741 (IC6), which functions as a comparator here. Battery voltage is applied across pins 7 and 4. Voltage at non-inverting input of IC6 is maintained constant at 5.1 volts by zener diode ZD5 and series resistor R17. Voltage at the inverting input of IC6 can be varied above and below 5.1 volts using preset PR4. Preset PR4 is adjusted in such a way that if battery voltage goes below 10V, the voltage at inverting input goes below 5.1 volts, so that output voltage at pin 6 of IC6 goes high (about 10 V). Hence, LED5 glows and produces intermittent sound from the buzzer, indicating low-battery status.

At the beginning of the indication, the output voltage of inverter would be around

225V AC. This enables the user to take timely action such as saving data (in case load comprises a computer).

Battery deep-discharge cut-out. If the UPS system keeps operating in the inverter mode, the battery voltage will drop eventually to prohibitively low level (say, 5 volts). If such condition occurs frequently, the life of the battery will be considerably reduced. To remove this drawback, it is necessary to use battery deep-discharge cut-out circuit. If battery voltage goes below 9.5 volts, this circuit will cause the UPS to shut down, which prevents the battery from further discharge.

This circuit is also built around op-amp μ A741 (IC7) working as a comparator. Voltage at non-inverting input of IC7 is 5.1 volts, which is kept constant by zener diode ZD6 and resistor R20. Preset PR5 is adjusted in such a way that if battery voltage goes below 9.5 volts, IC7 output would go high to turn on SCR. Once SCR conducts, the supply voltage for control circuit drops to near 0V. As a result, the control circuit is unable to produce gate drive pulses for the two MOSFET banks and the inverter stops producing AC output.

Suppose the mains supply is not available and you want to switch on the UPS on load (say, computer). If battery deep-discharge cut-out is set for a battery voltage of 9.5 volts, this means that you want to 'cold' start the UPS. On initial switching 'on' of the UPS, the starting current requirement from the battery is quite high to cause a drop in battery voltage, due to which battery deep-discharge cut-out circuit would be activated and inverter is not switched 'on'. To overcome this problem, 100 μ F capacitor C8 is connected across gate-source terminals of SCR. It provides necessary delay for the battery current/voltage to settle down to its stable value after switching on.

Reverse battery protection. A 16A to 20A diode (D8) in conjunction with fuse F2 provides reverse battery protection, in case battery is connected with reverse polarity. In case of reverse polarity, fuse F2 will blow and battery supply to the circuit will be immediately switched off.

Protection against no-load. An optional circuit for 'no load' condition, during which the output voltage may shoot up to 290V AC or more, is shown in Fig. 2 (within dotted lines). The rectifier and filter used are identical to that of under-voltage or over-voltage protection circuit,

www.electronicshobby.com

a portal dedicated to electronics enthusiasts

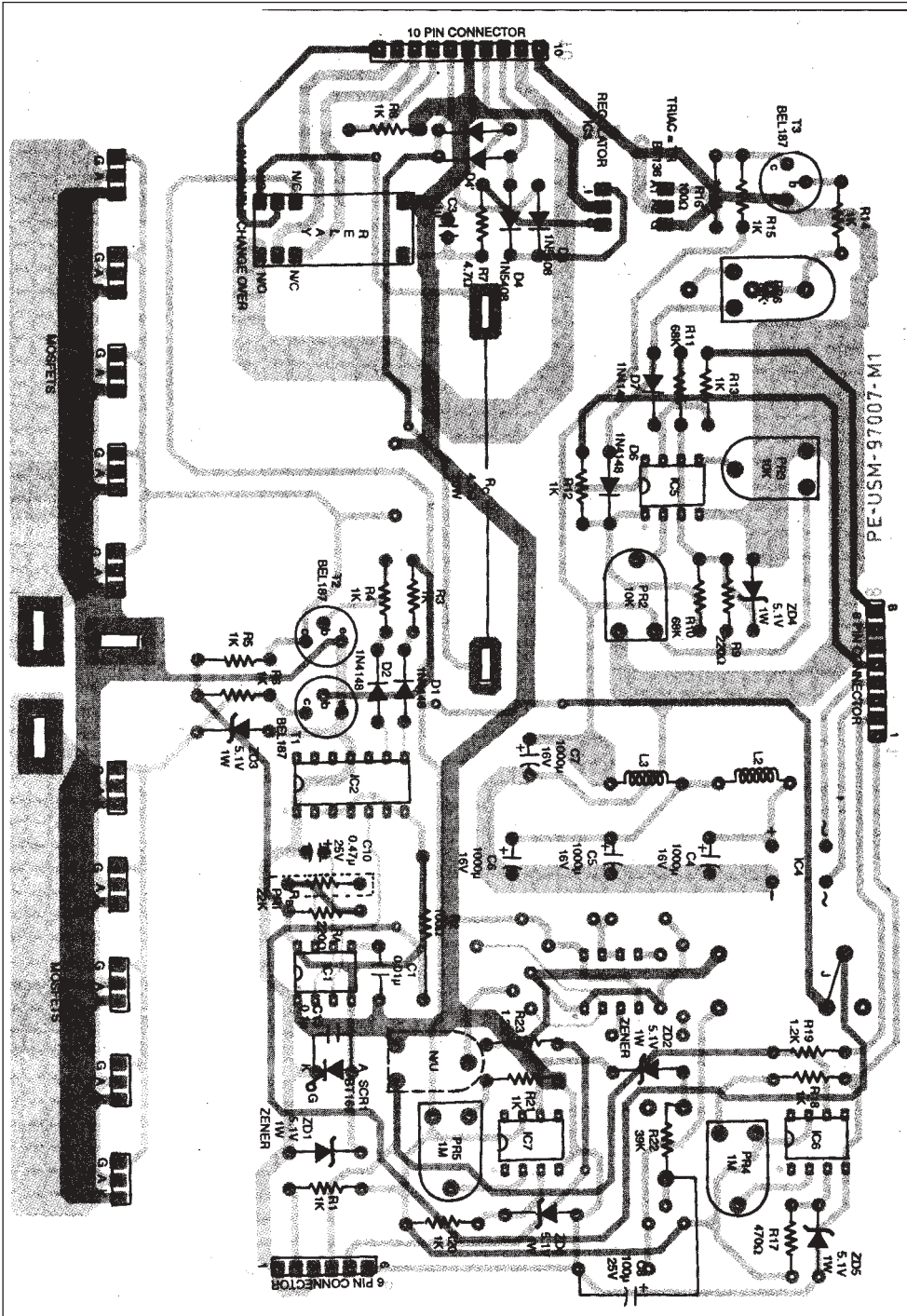


Fig. 7: Component layout for the PCB

while the comparator circuit is identical to over-voltage comparator. And hence, no separate explanation is required to be included. The output of the circuit is connected to the gate of SCR1 in Fig 2.

Spike suppression. Since triac TR is connected in series with the primary of charging transformer X2 and gate voltage is obtained from the under-/over-voltage cut-out, a spike is treated on par with

the over-voltage (>270V) condition. If mains voltage spike goes above 270V AC, gate voltage of triac TR becomes 0.7 volt, and hence triac does not conduct. As voltage across the coil of relay RLY is zero, the relay is de-energised and system changes over to back-up mode during voltage spike period. Thus the load is protected from the voltage spikes in the mains.

Back-up time. Using a single battery of 12V, 7Ah with a load (100 to 120W) comprising computer along with colour monitor, the back-up time is 10 to 15 minutes with squarewave output (half with sinewave output). With a battery of 12V, 180Ah, the back-up time is 4 to 5 hours with squarewave output (2 to 2.5 hours with sinewave output).

Charging resistance. For 12V/7Ah battery, charging resistance R_c should be 10 ohms/20 watts so that the battery will not be heated during charging. Similarly, for 12V/90Ah battery, charging resistance R_c should be 4.7 ohms/25 watts, and for 12V/180Ah battery, 3.3 ohms/30 watts.

Square/sinewave output selection. The selection of sinewave or squarewave output is done using slide switch SW2. In squarewave position, capacitor C2 is directly shunted across 230V terminal of the secondary of transformer X1, while in sinewave position, coil L1 (extension of 230V secondary, marked 600V) is added in series with capacitor C2 to resonate at 50 Hz. The power consumption from the battery increases in sinewave output position of switch SW2. The graphs of supply (battery) current versus the load for each position of switch SW2, indicating the comparative values, are shown in Figs 3 and 4. (**Note.** The secondary winding current rating for 230V section for 200W output may be chosen as 1 amp, and that for 600V extension forming inductor L1, the current rating of the winding may be chosen as 300 mA.)

Output power. Using six MOSFETs (three per bank) with proper heat sinks with inverter transformer of 16-ampere primary rating, the UPS-cum-EPS provides power up to 250 watts. With this power, two computers with B&W monitors, or one computer with colour monitor and a small printer can be driven. Using the same circuit, if you use ten MOSFETs (five per bank) and inverter

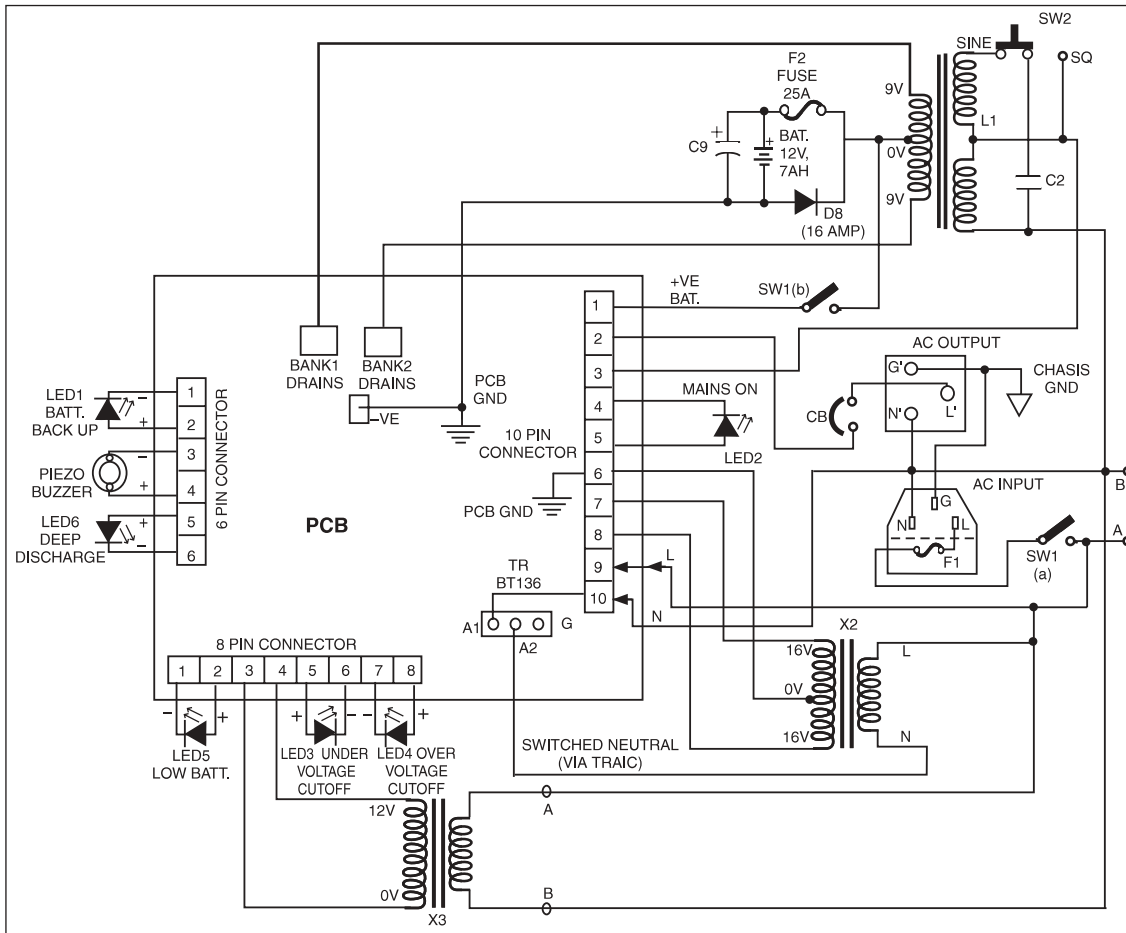


Fig. 8: Wiring diagram of chassis/panel mounted components to the PCB

nent-side and solder-side track layouts for the PCB are shown in Figs 5 and 6, respectively. Fig. 7 shows the component layout scheme. The wiring diagram for the chassis and panel-mounted components connected to the PCB via connectors (and few directly to pads) is shown in Fig. 8.

The pads for a few components are not existing in the PCB using existing pads/tracks. The same may have to be mounted externally using the available pads in accordance with the

transformer of 32-amp primary rating, the power of the UPS-cum-EPs can be increased to 500 watts or 625 VA.

The transformer ratings as mentioned above are applicable for squarewave output. The transformer primary rating will be 25 per cent higher in case of sinewave output. Also the number of MOSFETs per bank should also be correspondingly higher. Provision is made for mounting 5


MOSFETs in each bank.

PCB and component layout. A double-sided PCB is proposed for the circuit of Fig. 2. Except the optional circuit of 'no load protection', all switches, fuse, CB, LEDs, and transformers are required to be mounted inside the cabinet

and front-/back-panels of the cabinet suitably (refer Fig. 1


for the proposed front- and back-panel layouts). Large battery terminals may be used for terminating the battery leads. The tracks connecting drains and sources of MOSFETs may be suitably strengthened by depositing solder over the same.

The actual-size compo-

 

Sinewave output waveform as seen on the oscilloscope

 circuit diagram of Fig. 2. The affected components are: (a) C9—across battery terminals, (b) D8—reverse polarity battery protection diode, (c) C11 and C12—capacitors across source and gates of bank 1 and bank 2, (d) C2—across pole of SW2 and neutral of transformer X1 secondary, (e) C8—positive end to junction of R22 and gate of SCR1 and negative end to ground.



Photograph of author's prototype

R-2R D/A CONVERTER-BASED FUNCTION GENERATOR USING PIC16C84 MICROCONTROLLER

PRASANNA WAICHAL



Digital to analogue conversion is a process wherein the analogue output voltage or current is a function of the digital input word (binary

code). D to A converters (DACs) find extensive application in analogue input-output (I/O) systems, waveform generators, signal processors, motor speed-controllers, voice synthesisers, attenuators, etc.

DACs are characterised by the following two main performance criteria:

1. Resolution. It is defined as the smallest incremental change in the

required for the output to stabilise, or change from its previous value to the new value corresponding to fresh digital input word. For a given converter, the output does not change instantaneously when a change in the input occurs.

For an ideal linear DAC, the transfer curve is a linear function of input code which produces a single analogue discrete value and has a zero settling time

Basic classifications

A DAC can be classified into one of the following three types:

1. Current output. Here the output is a current proportional to the input digital word.

2. Voltage output. Here the output is a voltage proportional to the input digital word.

3. Multiplying output. In this type of DAC the output voltage or current is a function of input digital word multiplied by the reference input (i.e. the voltage applied or current fed into its reference terminal).

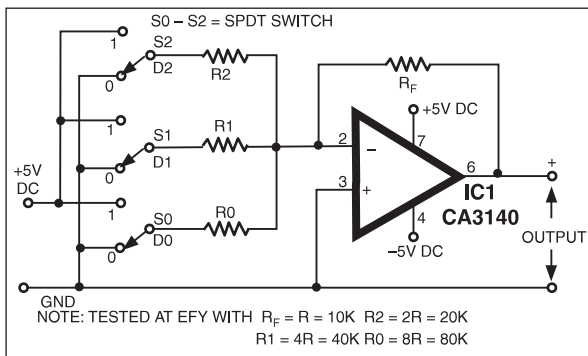


Fig. 1: Binary weighted resistance DAC

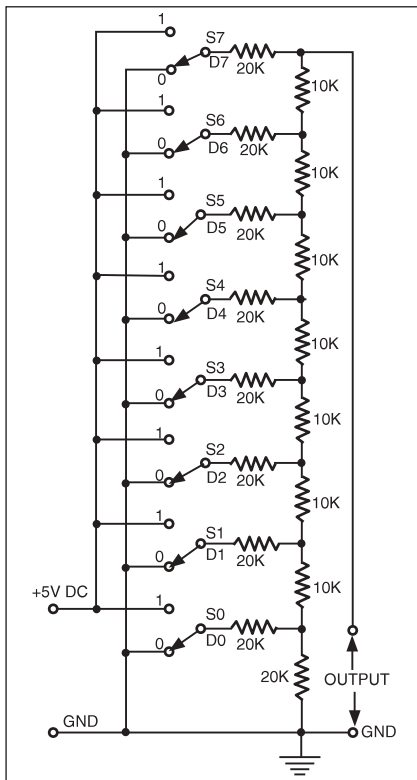


Fig. 2: 8-bit R-2R DAC

output voltage that can be resolved by a linear DAC and is equal to $1/2^n$ (or 2^{-n}) of the full-scale span of the DAC. Here, 'n' represents the number of bits the DAC can process. Resolution can also be expressed in percentage of full-scale or in bits. Higher the number of bits that a DAC can process, the better will be its resolution.

2. Settling time. It is the time re-

 


Fig. 3: Input code versus output voltage transfer function of R-2R DAC

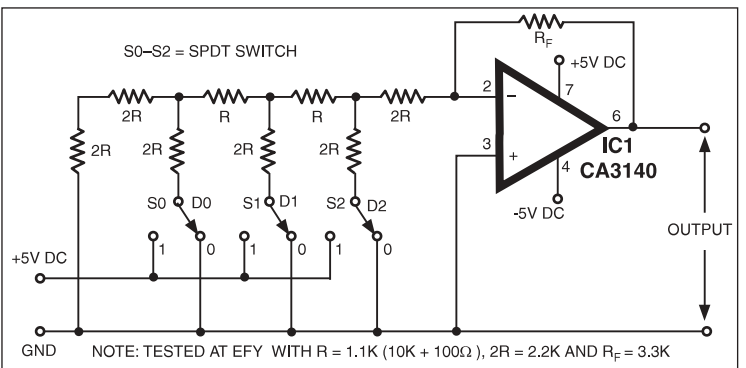


Fig. 4: R-2R network used in conjunction with an op-amp for 3-bit application

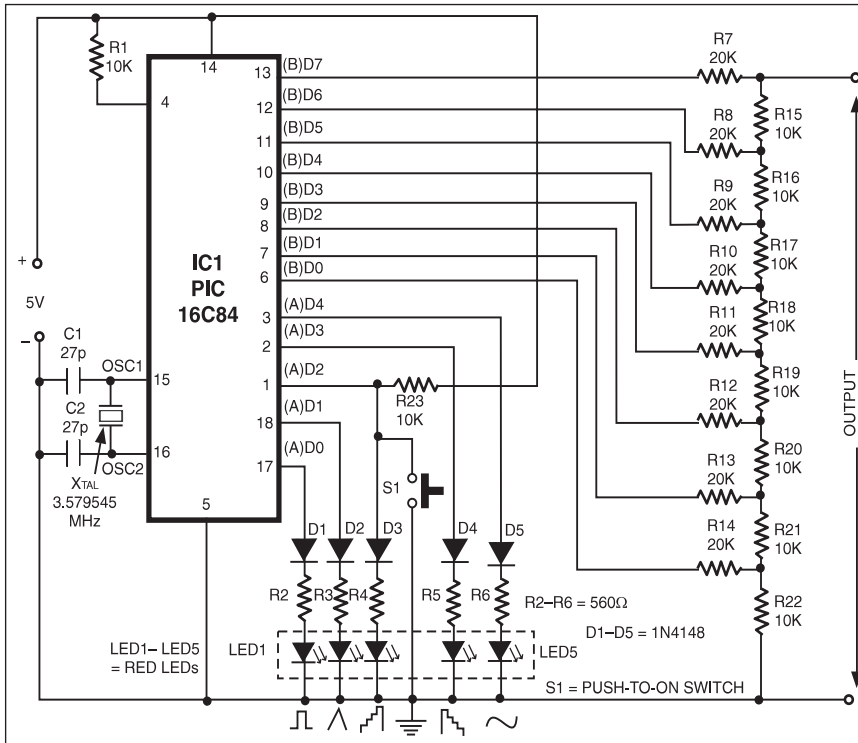


Fig. 5: PIC16C84-based R-2R DAC

One of the basic DAC circuits, which uses precision binary weighted resistors

and an op-amp for the conversion process, is shown in Fig. 1. The requirement of precision resistors (from R through

$2^{n-1} \times R$ values) is the main drawback of this design. It is overcome in the R-2R ladder network type DAC. Such a DAC, as shown in Fig. 2, uses only two values of resistors for any combination of bits.

In either of the above two cases, the maximum output voltage V_{out} , with all input bits at logic 1,

is given by the expression: $V_{out} = [(2^n - 1)/2^n] \times V_{in}$, and the output voltage with only the LSB at logic 1 will be: $V_{out} = 1/2^n \times V_{in}$. Here, V_{out} is the output voltage, n are the number of bits, and V_{in} is the reference input voltage (usually, +5 volt in a logic system). For example, an 8-bit DAC, with a reference voltage level of 5V, will have a range from 19.53 mV (with only the LSB at logic 1) to 4.98V (with all eight bits at logic 1). Because of its simplicity, the R-2R ladder network or

 


Fig. 6: Actual-size single-sided PCB layout for the schematic diagram of Fig. 5

PARTS LIST

Semiconductor:	
IC1	- PIC16C84, microcontroller
D1-D5	- 1N4148 switching diode
LED1-LED5	- 0.3-inch dia red LED
Resistors (all 1/4-watt, ±5% carbon, unless stated otherwise):	
R1, R15-R23	- 10-kilo-ohm
R2-R6	- 560-ohm
R7-R14	- 20-kilo-ohm
Capacitors:	
C1, C2	- 27pF ceramic disk
Miscellaneous:	
X _{TAL}	- 3.575545MHz crystal
S1	- Push-to-on switch

its variants are used in most of the integrating type DACs. While using integrated-type DACs, the following knowledge will come handy:

- (a) Power supply. Single +5V to +15V or double ±5V to ±15V
- (b) Reference input. Varies from chip to chip.
- (c) An operational amplifier is needed at the output to convert current into voltage.
- (d) The cost increases drastically as the number of bits (resolution) and/or the speed increases.
- (e) Sometimes it is not feasible to use a dual-supply converter for a single-polarity (usually positive) signal or in battery-powered systems.

TABLE II

Important features of PIC16C84

Architecture:	RISC CPU
Clock:	10MHz, 400ns instruction cycle
Instructions:	14-bit wide
Program memory:	1k x 14-bit (EEPROM).
RAM:	36 x 8-bit (SRAM)
Data memory:	64 x 8-bit for user data
Supply voltages:	2.7V to 5.5V with very low current consumption
I/O ports:	13 I/O lines with individual control having 25mA current sinking and 20mA current-sourcing capability
Timer:	8-bit timer/counter with 8-bit pre-scaler
Watchdog timer with on-chip RC oscillator, and 8-level deep hardware lock.	

 


Fig. 7: Component layout for PCB of Fig. 6

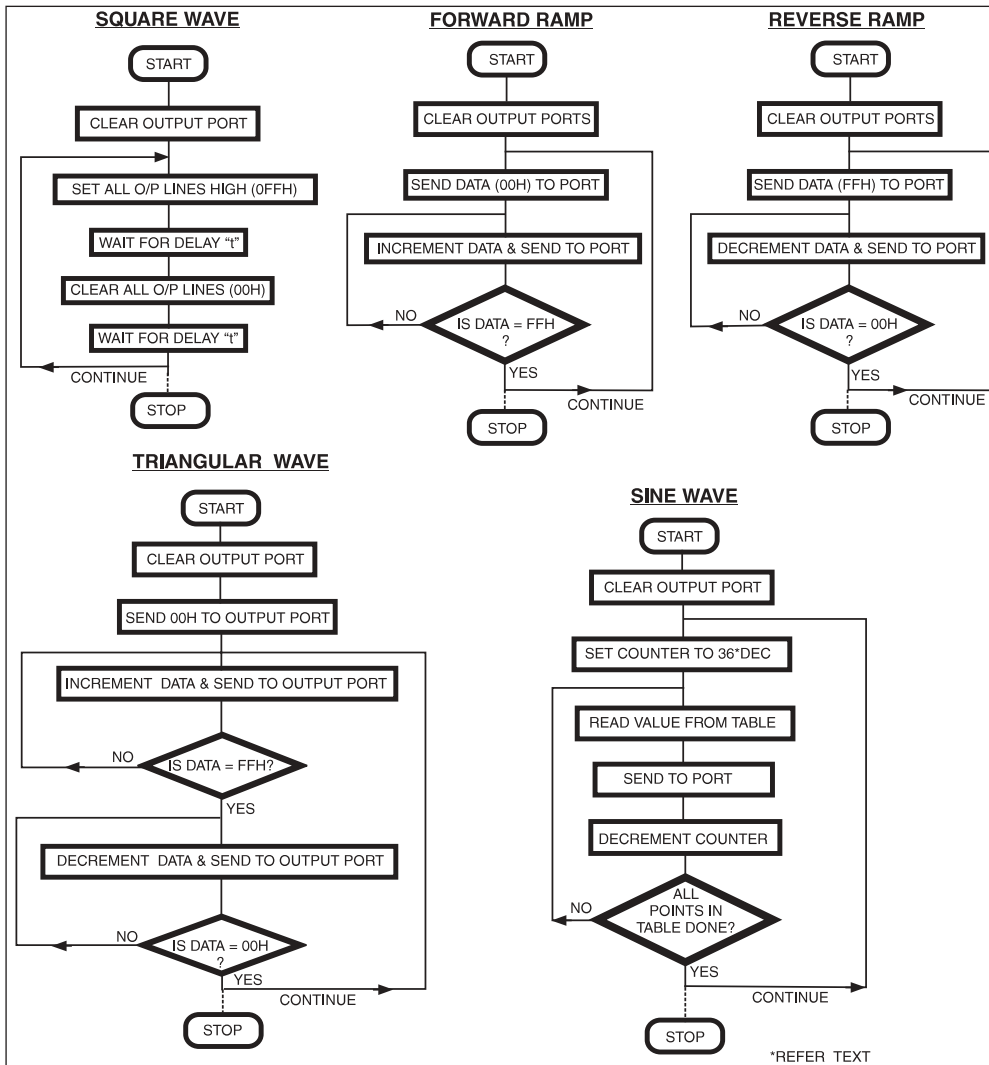


Fig. 8: Software flowcharts for generation of various waveforms

The low-cost R-2R ladder-type DAC (Fig. 2) requires no power supply at all, nor any active components such as buffers, op-amps, and storage registers. Its linearity is very good. Just give the digital input and take the analogue output. It is incredible! At a cost of Rs 5 only for 8-bit resolution or Re 1 only per bit above 8 bits, you can practically implement any application, which may otherwise require an integrated circuit. You do not have to bother about control signals, memory, or I/O mapping of your micro-system. Just

hook it up to your parallel port and start working.

Fig. 3 shows the transfer function or the linearity behaviour of the DAC of Fig. 2, while Table I compares the cost of a typical low-cost, 8-bit integrated chip (along with power supply and other parts) with that of R-2R, 8-bit DAC of Fig. 2. The R-2R DAC can be used for most of the applications. An R-2R network can also be used in conjunction with an op-amp. A 3-bit application circuit of the same is shown in Fig. 4.

Application

A waveform generator using R-2R and a low-power CMOS microcontroller PIC16C84 (by Microchip Technology Inc., USA) is presented here. All standard waveforms such as sine, square, tri-wave, forward and reverse ramp are successfully generated using the R-2R DAC, in conjunction with the above-mentioned microcontroller. Waveforms other than sine are generated quite easily. The sine wave, however, needs a different approach, which makes use of lookup-table technique.

The circuit of the function generator is shown in Fig. 5. The 8-bit data is sent to the DAC by the microcontroller, through one of its ports. The desired function/waveform is selected with the help of a push-to-on switch. The selection is also indicated by a corresponding LED. To keep the application as simple as possible, only fixed-frequency waveform generation is described in this article.

PIC16C84 microcontroller is a CMOS device from Microchip, which is used here in conjunction with an R-2R DAC to realise a function generator, as stated earlier. The important features of this device are reproduced in Table II.

Besides this, the device has some code protection bits which, once enabled, will not allow access to the program memory. These bits are actually programmed into the program memory, but user access to it is not available. (Note. For more information on EEPROM programming of PIC16C84, datasheet DS30189D in PDF format, available on Microchip Website, can be used.)

Besides this, the device has some code protection bits which, once enabled, will not allow access to the program memory. These bits are actually programmed into the program memory, but user access to it is not available. (Note. For more information on EEPROM programming of PIC16C84, datasheet DS30189D in PDF format, available on Microchip Website, can be used.)

www.electronicsforu.com

a portal dedicated to electronics enthusiasts

TABLE III

Look-up table of sine values in decimal and equivalent Hex values (within parenthesis) at 10 degree interval

100(64)	187(BB)	19(13)
117(75)	177(B1)	6(6)
134(86)	164(A4)	2(2)
150(96)	150(96)	0(0)
164(A4)	134(86)	2(2)
177(B1)	117(75)	6(6)
187(BB)	100(64)	19(13)
194(C2)	88(58)	29(1D)
198(C6)	71(47)	41(29)
208(D0)	55(37)	55(37)
198(C6)	41(29)	71(47)
194(C2)	29(1D)	88(58)

The 8-bit port-B of this device has been used as an output port, which is directly connected to the DAC. The 5-bit port-A has been used both to input key-press data and to output display data to the LEDs. Actually, the I/O pins on this port are time-shared/multiplexed between the keys and the LEDs. This means the same lines are used at one time for reading the keys and at another time for outputting data to drive the LEDs directly. The time-sharing is so fast that the display through LEDs appears to be stable, or any key closure is detected error-free.

The circuit works on 5V power supply, which can be derived from a 9V PP3 battery (or any other source capable of supplying 7.5V to 9V DC) by using commonly available 7805 regulator. The current drain of the circuit is less than 10 mA.

Although the circuit of Fig. 5 can be easily assembled using a general-purpose PCB, a proper actual-size single-sided PCB for the same is given in Fig. 6 along with its component layout in Fig. 7.

Software

The waveform generation technique is pretty easy and one can implement it with any other microprocessor or microcontroller system (e.g. 8085, 8032, Z80, 6800, etc). The program flowcharts for generation of various waveforms are shown in Fig. 8. One can write one's software for the purpose. However, source program for generation of various waveforms using the circuit of Fig. 5, employing PIC16C84 microcontroller, is given in Appendix 'A'.

For programming PIC microcontroller, including the complete development of a system, Microchip offers an integrated development environment (IDE) software

called Mplab. It is available on Technical Library CD-ROM offered (free, on request) from its India Liaison Office, Bangalore. The latest version of this software can also be downloaded from the Microchip Website 'microchip.com'.

The Mplab IDE comes with editor, assembler, and programmer software to support Microchip's device programmers and a software simulator. It also supports programs written in 'C' language.

For the present device (PIC 16C84), the author has used Microchip PICSTART PLUS development programmer. The software for the same, in PDF format, is also available on the Internet.

Operation

As stated earlier, the present circuit can produce all standard waveforms. After power-up, by default the circuit produces squarewave signal. The LED marked 'square' also lights up to indicate that function. When the 'select' key is pressed once, the output changes to tri-wave. The waveforms are selected sequentially on every depression of the 'select' switch and then repeated. Tested frequency range is 1 Hz to 100 Hz (all waveforms).

Sinewave generation. For waveforms other than sinewave, the data to the DAC changes in binary ascending or descending order. But since sine function is not a linear function, each data is predefined and a value table is used in this case. The value for each step of the sinewave is read and sent to the output port. The resolution depends upon the number of steps. The higher the step-count, the greater is the resolution, or vice-a-versa. A simple look-up table (values at 10° intervals), comprising 36 values

TABLE IV

Address (Hex)	Bank 0 registers	Bank 1 registers	Address (Hex)
00	Indirect	Indirect	80
01	TMR0	Option	81
02	PCL	PCL	82
03	Status	Status	83
04	FSR	FSR	84
05	Port	Tris	85
06	Port	Tris	86
07	—	Not implemented	— 87
08	EEdat	Eecon1	88
09	Eeaddr	Eecon2	89
0A	Pclath	Pclath	8A
0B	Intcon	Intcon	8B
0C	General-purpose RAM area starts		8C
	Bank 1 RAM not implemented		
2F	RAM ends		AF

www.electronicsforu.com

a portal dedicated to electronics enthusiasts

APPENDIX 'A'

Assembly language program for implementation of function generator using PIC16C84

<pre> ERRORLEVEL -302 INCLUDE <P16C84.INC> PCL equ 0x02 ; STATUS equ 0x03 ; FSR equ 0x04 ; PORT_A equ 0x05 ; PORT_B equ 0x06 ; EEDATA equ 0x08 ; EEADDR equ 0x09 ; PCLATH equ 0x0A ; INTCON equ 0x0B ; INDF equ 0x00 ; OPTION_REG equ 0x81 ; TRISA equ 0x85 ; TRISB equ 0x86 ; EECON1 equ 0x88 ; EECON2 equ 0x89 ; ; ; RAM 0x0C TO 0x2F (36 BYTES) ; RP0 equ 0x05 ; FN_KEY equ 0x18 ; SQR equ 0x01 ; TRI equ 0x02 ; P_RAMP equ 0x04 ; N_RAMP equ 0x08 ; FN_STATUS equ 0x0C ; KEY equ 0x0D ; TEMP1 equ 0x0E ; TEMP2 equ 0x0F ; FN_VAL equ 0x10 ; ON_DELAY equ 0x11 ; OFF_DELAY equ 0x12 ; ; ;-----; ; ORG 0x00 ; START CLRF STATUS ; CLRF INTCON ; BSF STATUS, RP0 ; MOVLW B'10000000' ; MOVWF OPTION_REG ; CLRF TRISB ; BCF STATUS, RP0 ; CLRF PORT_B ; CLRF PORT_A ; CLRF EEDATA ; CLRF EEADDR ; INCF FN_STATUS ; CLRF FN_VAL ; MOVLW 0x0F ; ; ;-----; ; NORMAL CALL KEY_SEEK ; ; SHOW_FN BSF STATUS, RP0 ; CLRF TRISA ; BCF STATUS, RP0 ; MOVF FN_STATUS,W ; MOVWF PORT_A ; ; </pre>	<pre> MOVF FN_STATUS,W ; XORLW SQR ; BTFSC STATUS,Z ; GOTO SQR_WAVE ; ; MOVF FN_STATUS,W ; XORLW TRI ; BTFSC STATUS,Z ; GOTO TRI_WAVE ; ; MOVF FN_STATUS,W ; XORLW P_RAMP ; BTFSC STATUS,Z ; GOTO PRAMP ; ; MOVF FN_STATUS,W ; XORLW N_RAMP ; BTFSC STATUS,Z ; GOTO NRAMP ; ; GOTO NORMAL ; ; MOVLW 0xFF ; MOVWF PORT_B ; CALL DELAY_ON ; CLRF PORT_B ; CALL DELAY_OFF ; GOTO NORMAL ; ; MOVF FN_VAL,W ; MOVWF PORT_B ; XORLW 0xFF ; BTFSC STATUS,Z ; GOTO LO ; INCF FN_VAL,F ; GOTO HI ; ; MOVF FN_VAL,W ; MOVWF PORT_B ; INCF FN_VAL,F ; GOTO NORMAL ; ; MOVF FN_VAL,W ; MOVWF PORT_B ; DECF FN_VAL,F ; GOTO NORMAL ; ; MOVF FN_VAL,W ; MOVWF PORT_B ; DECF FN_VAL,F ; GOTO NORMAL ; ; BSF STATUS,RP0 ; MOVLW 0x0F ; MOVWF OFF_DELAY ; ; BSF STATUS,RP0 ; MOVLW 0x1F ; MOVWF ON_DELAY ; ; DECF ON_DELAY,F ; MOVF ON_DELAY,W ; BTFSC STATUS,Z ; RETLW 0 ; GOTO DL1 ; ; BCF STATUS,RP0 ; MOVLW 0x1F ; MOVWF OFF_DELAY ; ; DECF OFF_DELAY,F ; MOVF OFF_DELAY,W ; BTFSC STATUS,Z ; RETLW 0 ; GOTO DL2 ; ; BSF STATUS,RP0 ; MOVLW 0x1F ; ; </pre>	<pre> MOVWF TRISA ; BCF STATUS,RP0 ; MOVF PORT_A,W ; ANDLW 0x1C ; XORLW 0x1C ; BTFSC STATUS,Z ; RETLW 0 ; ; MOVF PORT_A,W ; ANDLW 0x1C ; MOVWF KEY ; ; KEY_LUP MOVF PORT_A,W ; ANDLW 0x1C ; XORLW 0x1C ; BTFSS STATUS,Z ; GOTO KEY_LUP ; ; CHK_FN MOVF KEY,W ; XORLW FN_KEY ; BTFSC STATUS,Z ; GOTO FN_CHANGE ; ; RETLW 0 ; ; FN_CHANGE RLF FN_STATUS,F ; MOVF FN_STATUS,W ; BTFSS FN_STATUS,4 ; RETLW 0 ; CLRF FN_STATUS ; INCF FN_STATUS,F ; RETLW 0 ; ; ;-----; ; DELAY_ON BCF STATUS,RP0 ; MOVLW 0x1F ; MOVWF ON_DELAY ; ; DL1 DECF ON_DELAY,F ; MOVF ON_DELAY,W ; BTFSC STATUS,Z ; RETLW 0 ; GOTO DL1 ; ; ; DELAY_OFF BCF STATUS,RP0 ; MOVLW 0x1F ; MOVWF OFF_DELAY ; ; DL2 DECF OFF_DELAY,F ; MOVF OFF_DELAY,W ; BTFSC STATUS,Z ; RETLW 0 ; GOTO DL2 ; ; ;-----; ; END ; ; ;*****; </pre>
--	---	---

covering complete 360°, is shown for this purpose. The look-up table (Table III) is to be implemented as per the flowchart

for sine wave generation as shown in Fig. 8.

Various registers implemented in the

internal RAM area of microcontroller, along with their addresses, are shown in Table IV.

SIMPLE SWITCH MODE POWER SUPPLY

DEEPU P.A.



The SMPS described here is suitable for high-wattage stereos and other similar equipment. The circuit employs two high-voltage power transistors (BU208D) which have built-in reverse-connected diodes across their collectors and emitters. It can supply about 250-watt output.

The circuit uses a ferrite core transformer of 14mm width, 20mm height, and 42mm length of E-E cores. An air gap of 0.5 mm is required between E-E junction. Good insulation using plastic-insulating sheets (Mylar) is to be maintained between each layer of winding.


The number of primary turns required is 90 with 26 SWG wire. The secondary winding employs 17 SWG wire (for 4A load current). Each turn of the secondary develops approximately 2 volts. The reader can decide about the output voltage and the corresponding secondary turns, which would work out to be half the desired secondary voltage. The volt-

age rating of capacitors C7 and C8 should be at least twice the secondary output of each secondary section. BY396 rectifier diodes shown on the secondary side can be used for a maximum load current of 3

secondary (output). Ensure that each winding is separated by an insulation layer.

Two separate heat sinks are to be provided for the two transistors (BU208D). The filter capacitor for mains should be of at least 47 μ F, 350V rating. It is better to use a 100 μ F, 350V capacitor. If the output is short-circuited by less than 8-ohm load, the SMPS would automatically turn off because of the absence of base current.

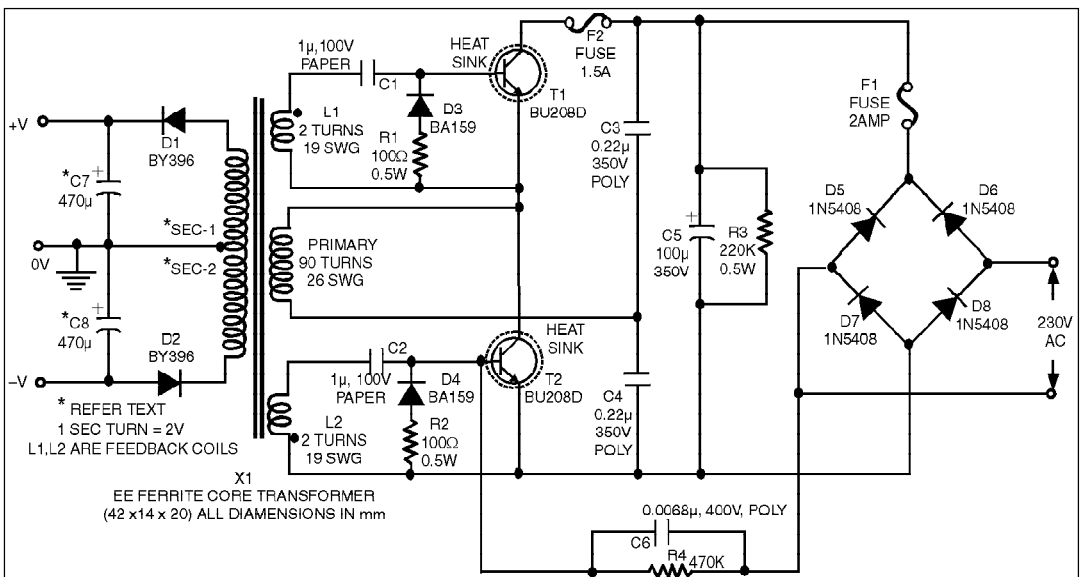The $h_{fe_{min}}$ (current amplification factor) of BU208D is 2.5. Thus, sufficient



amperes.

Two feedback windings (L1 and L2) using two turns each of 19 SWG wire are connected to transistors T1 and T2 with a phase difference of 180°, as shown by the polarity dots in the figure. First wind the primary winding (90 turns using 26 SWG wire) on the former. Then wind the two feedback windings over the

base current is required for fully saturated operation, otherwise the transistors get over-heated.

At times, due to use of very high value of capacitors C7 and C8 (say 2200 μ F or so) on the secondary side or due to low load, the oscillations may cease on the primary side. This can be rectified by increasing the value of capacitor C6 to 0.01 μ F.

TOILET INDICATOR

K.S. SANKAR





The circuit shown here displays the message 'toiLEt' or 'bUSY', using just six 7-segment common-anode displays. Such a display can be fixed

on the toilet door and operated using a reed switch and a ferrite magnet pair, suitably fixed on toilet door and its frame, such that the reed switch is closed when

the toilet is busy.

 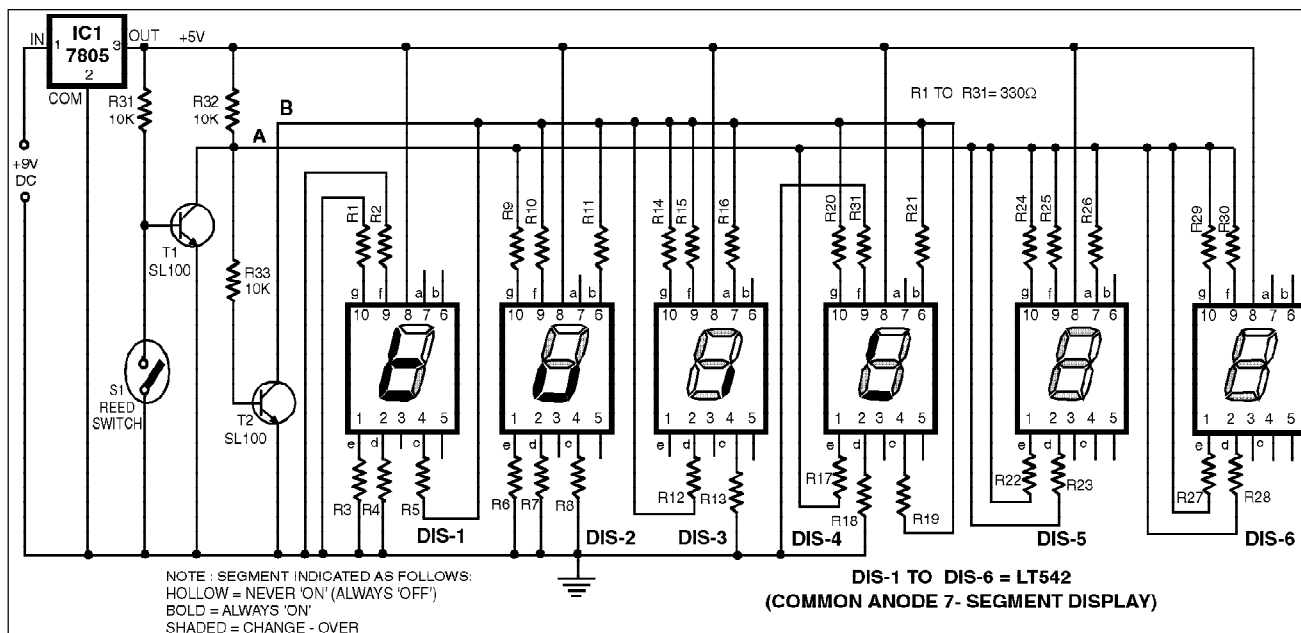Those segments of the displays for each letter that are common to both the display words 'toiLEt' and 'bUSY' are connected through resistors to ground (indicated by bold lines in the figure). These segments are permanently lit. 'A' rail is connected to segments that make up the word 'toiLEt' and 'B' rail for the word



'bUSY'. The last two displays are not used in the word 'bUSY'. Rails 'A' and 'B' are active low for the common-anode displays used here. Segments that are to be always 'off' are left disconnected and are shown as hollow lines. Those segments which are either lit during 'toiLEt' display (pulled 'low' via bus 'A') or during 'bUSY' display (pulled 'low' via bus 'B') are shown shaded in the figure.

Connect a +5V supply rail to the common anode pin of all the displays. To test the circuit at this stage,

'toiLEt' and 'busy'. Use a 9V DC adapter as the power supply source and stabilise it through a 7805 regulator.

Normally, switch S1 is open and transistor T1 is forward biased. T1 conducts and thus rail 'A' goes to near 0V, to display the word 'toiLEt'. If switch S1 is closed, T1 switches 'off' and turns 'on' transistor T2 to take point 'B' to near ground potential, and thus the display changes over to indicate the word 'bUSY'.

Thus, when toilet door is open, the magnetically-

temporarily ground either rail 'A' or rail 'B' (but not both), and check whether the display shows

operated (or micro-switch operated) reed switch is open and the display indicates 'toiLEt'. Now to make the message changeover to 'bUSY', when someone goes inside and locks the door, the switch needs to be closed on closure of the toilet door. One may also use other methods to achieve the same results.

FEATHER-TOUCH SWITCHES FOR MAINS

D.K. KAUSHIK





An ordinary AC switchboard contains separate switches for switching 'on'/'off' electric bulbs, tubelights, fans, etc. A very simple, interesting circuit presented here describes a feather-touch switchboard which may be used for switching 'on'/'off' four or even more devices. The membrane or micro-switches (push-to-on type) may be used with this circuit, which look very elegant.

By momentary depression of a switch, the electrical appliance will be 'on'/'off', independently.

To understand the principle and design of the circuit, let us consider an existing switchboard consisting of four switches. One live wire, one neutral wire, and four wires for four switches are connected to the switchboard, as shown in the illustration below the circuit diagram.

The switches are removed and the above-mentioned wires (live, neutral, L1, L2, L3, and L4) are connected to the circuit, as shown in the main diagram.

The circuit comprises four commonly available ICs and four micro-relays, in addition to four micro-switches/membrane switches (push-to-on type) and a few other passive components. IC 7805 is a 5-volt regulator used for supplying 5V to IC2 and IC3 (7476 ICs). These ICs are dual J-K flip-flops. The four J-K flip-flops being used in toggle mode toggle with each clock pulse. The clock pulses are generated by the push-to-on switches S1 through S4 when these are momentarily depressed. When a switch is momentarily depressed, its corresponding output changes its existing state (i.e. changes from 'high' to

 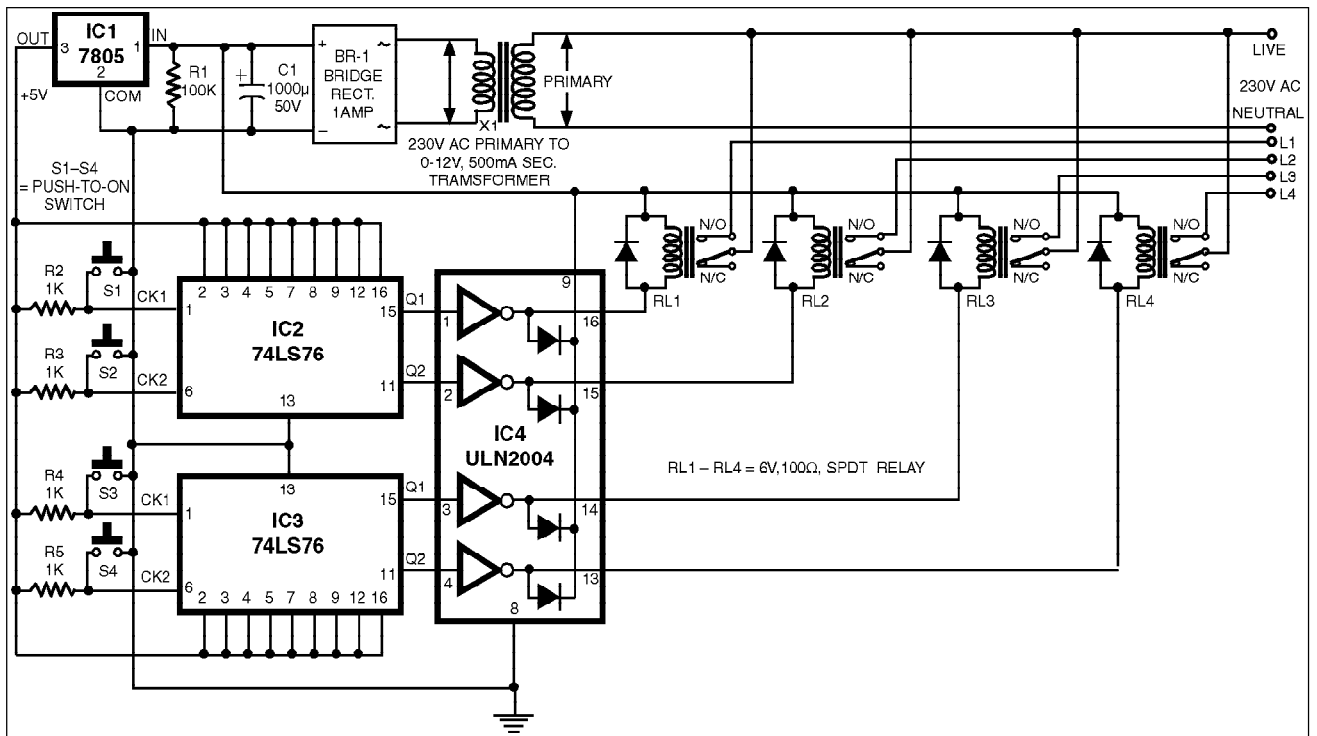

'low' or vice versa). The outputs of flip-flops drive the corresponding relays, in conjunc-

tion with the four relay driver transistors SL100. The wires earlier removed are connected to this circuit. On the switch panel board, the micro-switches are connected, and under the board the connections are wired as suggested above.

Relays RL1 though RL4 are 9V, SPST-type micro-relays of proper contact ratings.

The circuit may be expanded for six switches by using one more IC 7476, and

an IC ULN 2004 which has an array of seven Darlington's for driving the relays. So two more micro-switches and relays may be connected in a similar fashion.

This circuit can be assembled on a general-purpose PCB and the total cost should not exceed Rs 300. It is suggested that the circuit, after assembly on a PCB, may be housed in a box of proper size, which may be fitted on the wall in place of a normal switchboard.

DIGITAL FAN REGULATOR

C.K. SUNITH



The circuit presented here is that of a digital fan regulator, variable to provide five speed levels as catered for in ordinary fan regulators. The circuit makes use of easily available components. An optional 7-segment display with its associated circuitry has been provided to display your choice of fan speed.


The heart of the circuit is a modulo-6 binary counter, built around IC2 and IC3 (IC 7476) which are dual JK flip-flops. The counter counts up in a straight binary progression from 000 to 101 (i.e. from


0 to 5) upon each successive clock edge and is reset to 000 upon next clock. The count sequence of the counter has been summarised in Table I.

Each flip-flop is configured to toggle

Displayed count	Counter count	IC4's active low output	Relay activated
0	000	Q0	NIL
1	001	Q1	RL1
2	010	Q2	RL2
3	011	Q3	RL3
4	100	Q4	RL4
5	101	Q5	RL5
0	000	Q0	NIL

 when the clock goes from high to low. Let us begin with the assumption that the counter reads 000 at power on. The monoshot built around IC1 (NE 555) provides necessary pulses to trigger the



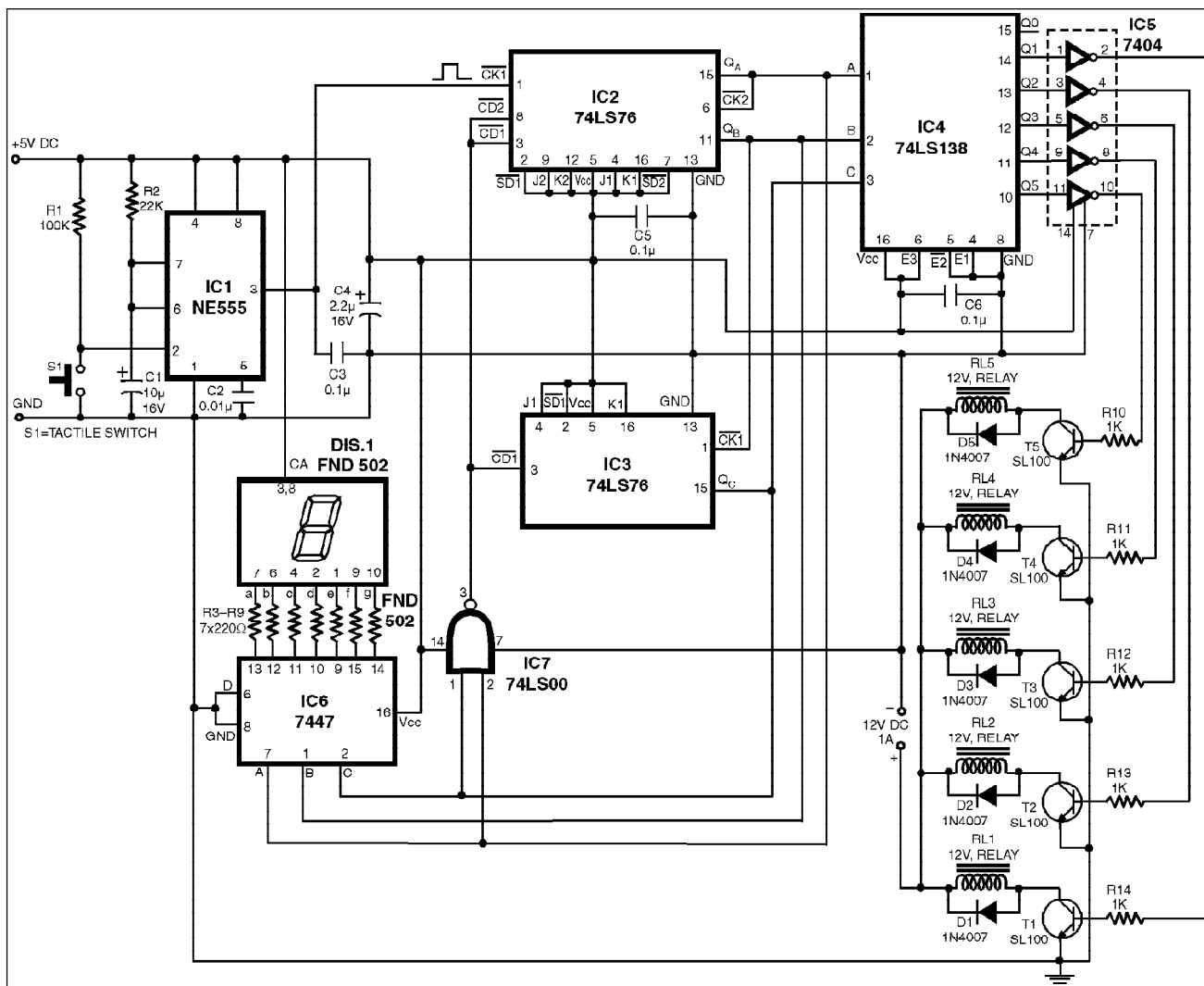

counter upon every depression of switch S1. Upon the arrival of first clock edge, the counter advances to 001. The outputs of the counter go to IC4 (IC 74138), which is a 3-line to 8-line decoder. When IC4 receives the input address 001, its output Q1 goes low, while other outputs Q0 and Q2 through Q7 stay high. The output Q1, after inversion, drives transistor T1, which actuates relay RL1. Now power is delivered to the fan through the N/O contact RL1/1 of relay RL1 and the tapped resistor R_T . For the tapped resistor R_T , one can use the resistance found in conventional fan

regulators with rotary speed regulation.

The outputs of the counter also go to IC6 (IC 7447), a BCD to 7-segment code converter, which, in turn, drives a 7-segment LED display. When switch S1 is depressed once again, the counter advances to count 010. Now, the output Q2 of IC4 goes low, while Q0, Q1 and Q3 through Q7 go high or remain high. This forces transistor T2 to saturation and actuates relay RL2. The display indicates the counter output in a 7-segment fashion.

The counter proceeds through its normal count sequence upon every depres-

sion of switch S1 up to the count 101. When switch S1 is depressed once again, normally the counter should read 110. But the two most significant bits of the counter force the output of NAND gate (IC7) to go low to reset the counter to 000. The counter now begins to count through its normal sequence all over again, upon every key depression.

The circuit does not provide the facility to memorise its previous setting once it is powered off or when there is a mains failure.

www.electronicsforu.com

a portal dedicated to electronics enthusiasts

TELEPHONE RINGER USING TIMER ICs

PRABHASH K.P.



Using modulated rectangular waves of different time periods, the circuit presented here produces ringing tones similar to those produced by a telephone.

The circuit requires four astable multivibrators for its working. Therefore two 556 ICs are used here. The IC 556 contains two timers (similar to 555 ICs) in a single package. One can also assemble this circuit using four separate 555 ICs. The first multivibrator produces a rectangular waveform with 1-second 'low' duration and 2-second 'high' duration. This waveform is used to control the next multivibrator that produces another rectangular waveform.


A resistor R7 is used at the collector of transistor T2 to prevent capacitor C3 from fully discharging when transistor T2 is conducting. Preset VR1 must be set at such a value that the two ringing tones are heard in one second. The remaining two multivibrators are used to produce ringing tones corresponding to the ringing pulses produced by the preceding multivibrator stages.

When switch S1 is closed, transistor T1 cuts off and thus the first

multivibrator starts generating pulses. If this switch is placed in the power supply path, one has to wait for a longer time

for the ringing to start after the switch is closed. The circuit used also has a provision for applying a drive voltage to the circuit to start the ringing.

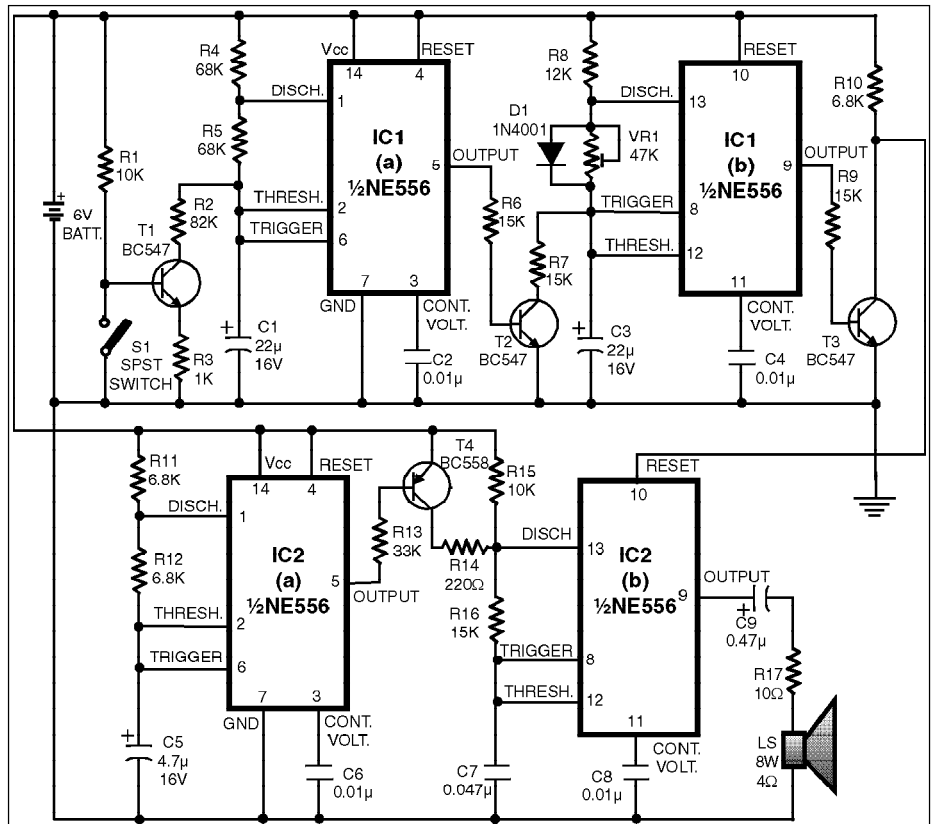Note that the circuit is not meant for connecting to the telephone lines. Using appropriate drive circuitry at the input (across switch S1) one can use this circuit with intercoms, etc. Since ringing pulses are generated within the circuit, only a constant voltage is to be sent to the called party for ringing.



www.electronicsforu.com

a portal dedicated to electronics enthusiasts

November

2000

PC-TO-PC COMMUNICATION USING INFRARED/LASER BEAM

K.S. SANKAR



Serial communication between two PCs has been covered earlier too in EFY. However, two separate ICs (1488 and 1489) were used in those projects (for TTL to RS-232C and vice-versa level conversion), using wireless radio wave technology. This level conversion required use of three different voltages, i.e. +12V, -12V and +5V.

Here is a novel circuit using MAXIM Corporation's IC MAX232, which needs only a single power supply of 5V for level conversion. Fig. 1 shows the internal functional diagram of MAX232 IC. The communication over the short distance of 2 to 3 metres is established using infrared diodes, as shown in Fig. 2. The range could be increased up to hun-

dred metres, using a laser diode module in place of infrared LEDs.

The laser module used is easily available as laser pointer (having about 5 mW power output). It is to be used with its three battery cells removed and positive supply terminal soldered to the casing and 0V point to the contact inside the laser module.

Assemble the two prototypes on PCBs or breadboards and connect them to COM-1 (or COM-2) port of each PC. Point the laser beam of one module to fall on the photodiode of the module connected to the other PC, and vice versa.

Load PROCOMM or TELIX serial communication software and set the port parameters to 9600 n 8 1 (here, 9600 refers to the baud rate, n stands for parity-none, 8 represents bits per character, and 1 indicates number of stop bits) to establish the communication. File transfer is also possible. The prototype was tested (by the author) between speeds of 1200 and 9600 bauds, including file transfer between the two PCs. The software program for the purpose was written in 'C' language. The source code of the program is given on page 49 for COM-1 port.

Circuit

Transmitter. Data signals transmitted through pin 3 of 9-pin (or pin 2 of 25-pin) 'D' connector of RS232 COM port are sent to pin 8 of MAX232 and it converts these EIA (Electronic Industry Association) RS232C compatible levels of $\pm 9V$ to 0/5V TTL levels, as given in Table I. The output pin 9 of MAX232 IC drives the pnp transistor SK100 and pow-

ers the IR LEDs. Output pin 9 also drives an LED indicator (LED2) during the positive output at its pin 9. At logic '0' output at pin 9, LED2 goes 'off', but drives the pnp transistor through a bias resistor of 1 kilo-ohm (R5), to switch 'on' IRLED1 and IRLED2 and also a visible LED3. Since very low drive current is used, use of high-efficiency visible LEDs, which light up at 1 mA, is needed. The electrical pulses sent by the COM port are now converted into corresponding modulated pulses of IR light.

Receiver. The IR signals are detected by a photodiode (D1). (A photodiode is reverse biased and breaks down when IR light falls on its junction.) The detected TTL level (0/5V) signals are coupled to pin 10 of MAX 232 IC. These TTL levels are converted to $\pm 9V$ levels internally (as per Table 1) and output at pin 7.

A visible LED1 at pin 7 of MAX232 IC indicates that the signals are being

TABLE I

Max 232 Conversion Levels	
TTL +5V	to -9V RS 232
TTL 0V	to +9V RS 232
RS 232 +9V	to 0V TTL
RS 232 -9V	to 5V TTL

PARTS LIST	
<i>Semiconductors:</i>	
IC1	- MAX232A +5V powered multichannel RS232 driver/receiver
IC2	- NE555 timer
IC3	- IR RXR module; Siemens SFH-506-38 or Telefunken TS0P-1838
T1	- BC547 npn transistor
T2	- BC548 npn transistor
D1	- 1N4148 diode
LED1-LED3	- Red LED
IRLED1, IRLED2	- Infrared light emitting diode
<i>Resistors (all 1/4-watt, $\pm 5\%$ carbon, unless stated otherwise):</i>	
R1,R2	- 47-ohm
R3,R4	- 4.7-kilo-ohm
R5,R9	- 1-kilo-ohm
R6	- 1.2-kilo-ohm
R7	- 10-ohm
R8	- 330-ohm
R10	- 2.2-kilo-ohm
R11	- 10-kilo-ohm
VR1	- 4.7-kilo-ohm preset
<i>Capacitors:</i>	
C1-C5	- 1 μ , 25V electrolytic
C6	- 470 μ , 25V electrolytic
C7,C8	- 0.01 μ ceramic disk
<i>Miscellaneous:</i>	
	- 9/25-pin 'D' connector (male/female)

Note: Parts List pertains to circuit in Fig. 3.

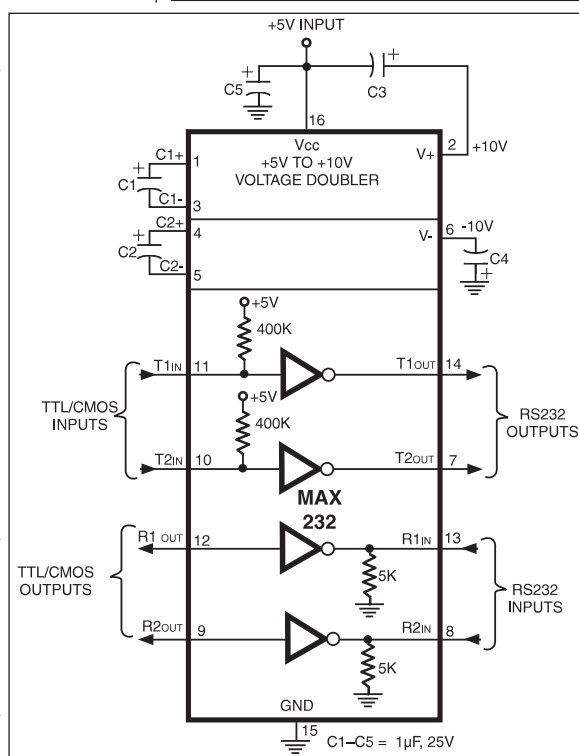


Fig. 1: Internal functional diagram of IC MAX232

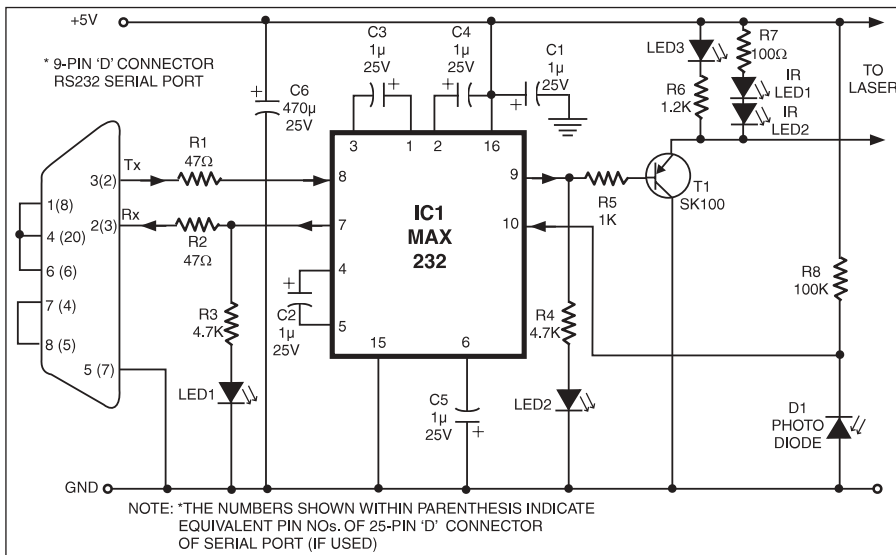


Fig. 2: Communication between two PCs for a short range using IR diodes, or longer distance using laser

and both PCs 'think' that there is a null modem cable connected between them. Table II shows the correspondence between the various pins of a 9-pin (or 25-pin) 'D' connector of serial port of PC. In some PCs, the serial port is terminated into a 9-pin 'D' connector and in some others into a 25-pin 'D' connector.

Testing

Assemble two transceiver modules and connect each of them, using 3-core cables, to Com-1 ports of the two PCs. Place them 15 to 20 cms apart so that the IR LEDs of each module face the photodiode detector of the other.

Power 'on' both the circuits to operate at stabilised 5V DC. You may alternatively use a 7805 regulator IC with a

9V DC source to obtain regulated 5V supply.

Check if the MAX232 IC is working properly by testing pin 2 for 9 to 10V positive supply and pin 6 for -9V supply. MAX232 (refer Fig. 1) uses 1µF, 25V capacitors C1-C5 as a charge pump to internally generate ±9V from 5V supply. Generally, defective MAX232 ICs will not show a voltage generation of +9V and -9V at pins 2 and 6, respectively. Replace ICs, if required. Although 1µF, 25V capacitors are recommended in the datasheet, the circuit works well even with

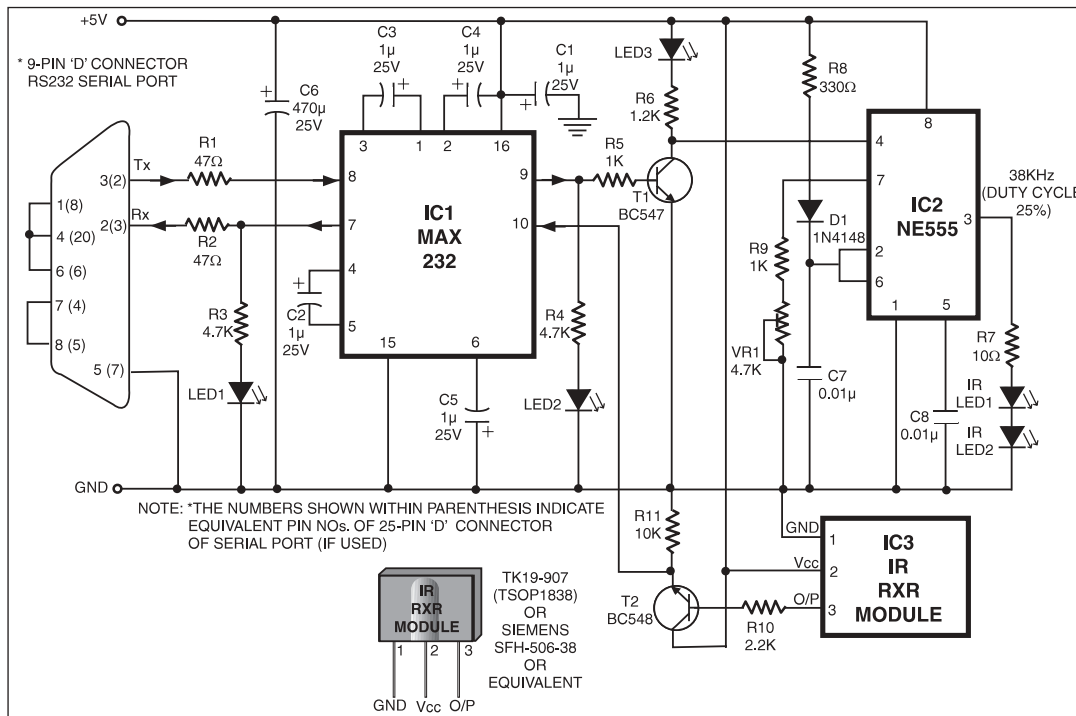


Fig. 3: Modified circuit diagram for PC-to-PC communication using 38kHz modulated pulses

received. Pin 7 is also connected to pin | 2 (receiver pin) of 9-pin (or pin 3 of 25-pin) 'D' connector used for the serial port in the PC, so that the data may be read. The optical signals received by the photo-diodes are in fact converted to electrical pulses

10µF, 25V capacitors, which are easily available.

With both the PCs and supply to the transceiver modules 'on', throw some light

TABLE II

DB 9 Pin	DB25 Pin	Signal Direction	Description
1	8	In	DCD (data carrier detect)
2	3	In	RX (receiver data)
3	2	Out	TX (transmit data)
4	20	Out	DTR (data terminal ready)
5	7	—	GND (signal ground)
6	6	In	DSR (data set ready)
7	4	Out	RTS (request to sent)
8	5	In	CTS (clear to send)
9	22	In	RI (ring indicator)

TABLE III

Base Address for the Communication Ports	
Communication	Base address port
COM1	03F8H
COM2	02F8H
COM3	03F8H
COM4	02F8H

with the torch on the photodiode. LED1 should flicker at the burst frequency rate of the transmitter. This proves that the IR signals are being detected by photodiodes and converted into RS232-compatible levels by the MAX232 and output at pin 7 of MAX232 ICs is available for the PC to read the pulses.

To test the transmitter side, disconnect the module from COM-1 (or COM-2) port of the PC, and with the device pow-

ered 'on', use a short jumper wire from +5V and touch it at pin 8 of MAX232 IC to simulate a positive pulse. LED2 should turn 'off' and IRLEDs and LED3 should turn 'on' if the wiring is correct. IRLEDs would also be glowing, although one cannot see them glowing. Remove the link wire from +5V to pin 8 of MAX232 IC and connect back the 'D' connector to PC's COM-1 (or COM-2) port.

Run a simple communication software

like PROCOM or TELIX. Set the baud rate, parity, bits per character, and stop bits to 9600, n, 8, 1, respectively, and send a few characters from the keyboard through COM-1 (or COM-2) port. You should be able to see LED3 flickering for a few seconds, indicating data transmission.

Connect both PCs to the circuits and set the software to chat mode. You should be able to transfer data between the PCs, as if a cable was connected.

Depending on the sensitivity setting and power/angle of IRLEDs, increase the distance to about 35 cms (12 inches) and try again for better distance.

For more power, use metal-can type IRLEDs and reduce the value of resistor R7 for more drive

TABLE V
AL Register Bits

Bit								Use
7	6	5	4	3	2	1	0	
X	X	X	•	•	•	•	•	Baud-rate code
•	•	X	X	•	•	•	•	Parity code
•	•	•	•	X	•	•	•	Stop-bit code
•	•	•	•	•	•	X	X	Character-size code

TABLE VI
Baud Rate

Bit			Value	Bits per second
7	6	5		
0	0	0	0	110
0	0	1	1	150
0	1	0	2	300
0	1	1	3	600
1	0	0	4	1200
1	0	1	5	2400
1	1	0	6	4800
1	1	1	7	9600

TABLE VII
Parity

Bit		Value	Meaning
4	3		
0	0	0	None
0	1	1	Odd Parity
1	0	2	None
1	1	3	Even Parity

TABLE VIII
Stop Bits

Bit	Value	Meaning
2	0	One
0	1	Two

TABLE IX
Character Size

Bit		Value	Meaning
1	0		
0	0	0	Not used
0	1	1	Not used
1	0	2	7-bit*
1	1	3	8-bit

current. If you use a laser beam, as explained earlier, remove the IRLEDs and the device will track up to 10 metres without any data loss.

Hints

1. Aligning the laser beam is a problem, but once it is aligned carefully and fixed, the data transmission and reception would be error-free. Transmitter and receiver alignment routines have been included in this software program to aid in the alignment process.

2. Ordinary clear photodiodes should be used for detector. If you use dark-red plastic-encapsulated diodes, you may have problems, as these react only to very bright natural light or infrared light.

EFY Lab Note. While testing, we did face problems with red plastic-encapsulated diodes as well as clear Darlington detectors (GE's L14F1), probably because of various light sources in the room caus-

TABLE IV
8250 Registers: Offset from Base Address

Offset	LCR Bit 7	Meaning	Read/write
0	0	Transmitter holding register (THR) [when written to port]	Write
0	0	Receiver data register (RDR) [when read from port]	Read
0	1	Baud rate divisor-low byte (BRDL)	Read/write
1	0	Interrupt enable register (IER)	Read/write
1	1	Baud rate divisor-high byte (BRDL)	Read/write
2	x	Interrupt identification register (IIR)	Read only
3	x	Line control register (LCR)	Read/write
4	x	Modem control register (MCR)	Read/write
5	x	Line status register (LSR)	Read only
6	x	Modem status register (MSR)	Read only

 


Fig. 4: Actual-size, single-sided PCB for the circuit in Fig. 3

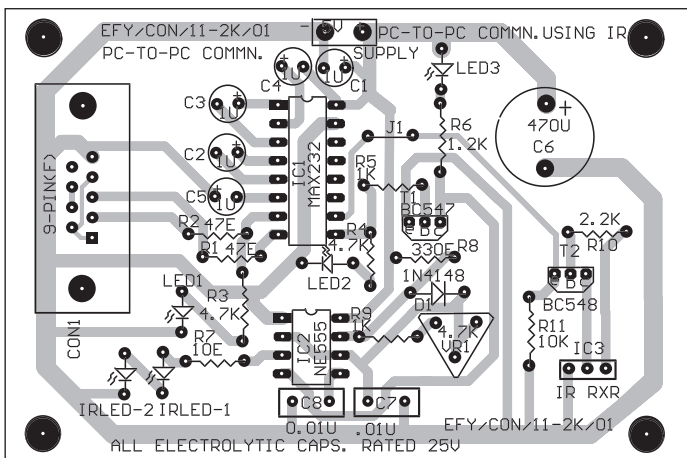


Fig. 5: Component layout for the PCB

Program Listing for PC-to-PC Communication in 'C'

```

/* PROGRAM FOR LASER / IR COMMUNI-
CATION BETWEEN TWO PCs */

/* by K.S.Sankar for EFY Nov/Dec'2000 */

#include <stdio.h> /* Header Files */
#include <dos.h>
#include <conio.h>
#include <graphics.h>
#include <stdlib.h>
#define DEL 25 /* Preprocessor - Delay Vari-
able */
#define COM 0X03F8 /*0x02f8 -com2,0x03f8-
com1 */
char gra='Y'; /* Global Variables */
int flag=0;
union REGS inregs,outregs; /* Union declara-
tion for registers */
FILE *fp; /* File declaration */
int status;
char temp='\n',t2;
int t1=10;
/* The Main Function */
void main(void)
{
char ch,chr,chs; /* Local Variable */
clrscr();
if(flag==0)
/* splash0; /* Calling Splash routine */
flag++;
textcolor(4);gotoxy(26,6);
printf("INFRARED/LASER COMMUNICA-
TION");
gotoxy(34,9);textcolor(10);
printf("R");textcolor(7);printf("eceive mode");
textcolor(14);gotoxy(35,12);
printf("S");textcolor(7);printf("end mode");
textcolor(6);gotoxy(37,15);
printf("E");textcolor(7);printf("xit");
ch = getch(); /* Select Mode */
switch(toupper(ch))
{
case 'R': R:clrscr();
textcolor(4);gotoxy(26,6);
printf("INFRARED/LASER COMMUNI-
CATION");
textcolor(138);gotoxy(33,9);
printf("RECEIVE MODE");
textcolor(9);gotoxy(33,12);
printf("A");textcolor(7);printf("lign de-
vice");
textcolor(11);gotoxy(33,15);
printf("F");textcolor(7);printf("ile receive");
textcolor(6);gotoxy(36,18);
printf("Q");textcolor(7);printf("uit");
chr = getch();
switch(toupper(chr))
{
case 'A': raln();break;
case 'F': f_rcv();break;
case 'Q': main();
default : clrscr();
printf("Wrong Key Pressed");
goto R;
}
break;
case 'S': S:clrscr();
textcolor(4);gotoxy(26,6);
printf("INFRARED/LASER COMMUNI-
CATION");
textcolor(142);gotoxy(36,9);
printf("SEND MODE");
textcolor(9);gotoxy(34,12);
printf("A");textcolor(7);printf("lign de-
vice");
textcolor(11);gotoxy(34,15);
printf("T");textcolor(7);printf("ransfer
file");
textcolor(6);gotoxy(38,18);
printf("Q");textcolor(7);printf("uit");
chs = getch();
switch(toupper(chs))
{
case 'A': salgn();break;
case 'T': f_snd();break;
case 'Q': main();
default : clrscr();
printf("Wrong Key Pressed");
goto S;
}
break;
case 'E': clrscr();
textcolor(143);
gotoxy(35,13);
printf("GOOD BYE");
exit(1);
default : clrscr();
printf("Wrong Key Pressed");
main();
return ;
}
}
/* Function for receive (For Device Alignment)
*/
ralgn(void)
{
char st = ' '; /* Local variables */
clrscr();
gotoxy(30,2);
textcolor(10);
printf("RECEIVE MODE .");
textcolor(9);printf(" ALIGN DEVICE");
printf("\n");
initial(); /* Call Initialisation routine */
loop:if(!kbhit())
{
if(st==0x04) /* Check for end of Transmis-
sion */
{
clrscr();
textcolor(140);
gotoxy(30,12);
printf("ALIGNED PROPERLY");
gotoxy(48,24);
printf(" Press any key to quit .");
getch();
main(); /* Got to main function after aligning
properly */
}
status = inp(0X3fd); /*Checking status at
com1 port */
if((status & 0x01)==0x00) /* Check for Data
Ready */
goto loop;
else if(!kbhit())
{
st = inp(COM); /*Get character from
com1 port till */

printf("%c",st); /* key hit or end of
transmission */
goto loop;
}
else
main(); /*Call main function if key hit */
}
return;
}

/*Function for File Receive */
f_rcv()
{
int flag=0,bytecount=0,count; /* Local Vari-
ables */
float ot = 0.00,nt = 0.00;
char ch,st[55000],fnn[30];
clrscr();
initial(); /*Calling Initialisation Routine */
ot = clock() / 18.2; /*Calculate exec time in
secs from start of program */

gotoxy(2,2);
printf(" FILE NAME ? : ");
fp=fopen(gets(fnn),"wb"); /*Get file name in
write mode */
gotoxy(26,10);
printf("Ready for) RECEIVING DATA ....");
gotoxy(50,24);
textcolor(138);
printf("Don't KEY IN may loss data");
loop: nt = clock()/18.2; /*Calculate exec time in
secs from start of
program */
status = inp(0X3FD); /*Get character from
com1 port */
if((status & 0x01)==0x00) /* Check for Data
Ready */
{
/* Check for no data reception for five seconds
after
start of reception if no data is received con-
tinue other process */
if((bytecount>0) && (nt-ot)>5.0)
{
clrscr();
for(count=0;count<flag;count++)
{
gotoxy(26,10);
textcolor(11);
printf(" Saving data in");
gotoxy(43,10);
textcolor(12);
printf(" %s",fnn);
/*Dump the data received in a File */
fprintf(fp,"%c",st[count]);
}
fclose(fp);
gotoxy(26,13);
textcolor(11);
printf(" File %s of %d bytes created
",fnn,count);
gotoxy(50,24);
textcolor(7);
}
}
}
}

```

```

printf(" Press any key to quit .");
getch();
main();
}
goto loop;
}
else if(!kbhit())
{
st[flag] = inp(COM);/*Get character from
Com1 port */
flag++;
bytecount++;
ot = clock()/18.2; /*Calculate exec time during
receiving */
goto loop;
}
else
{
/* If transmission is cut terminate abnormally */
clrscr();
for(count=0;count<flag;count++)
{
gotoxy(26,3);
textcolor(140);
cprintf(" TERMINATED ABNOR-
MALLY ");
gotoxy(26,10);
textcolor(11);
cprintf(" Saving data in");
textcolor(12);
cprintf(" %s",fnm);
fprintf(fp,"%c",st[count]);
}
fclose(fp);
gotoxy(26,13);
textcolor(11);
cprintf(" File %s of %d bytes created
",fnm,count);
sleep(5);
main();/*Go to main after dumping in file */
}
return;
}

/* Function for send align ( for device align-
ment) */
salgn(void)
{
int flag=0; /* Local Variables */
char st[127];
clrscr();
initial();
textcolor(14);
cprintf("Type the sentence ( < 127 chars)");
puts("\n");
gets(st); /* Get string to send */
loop:status = inp(0X3FD); /* Get com1 port sta-
tus */
if((status & 0x20)==0x00) /* Check Trans-
fer holding register empty */
goto loop;
else
do
{
if(kbhit()) /* Check for key hit */
{
outport(COM,0X0D); /* Send carriage return
*/
outport(COM,0X0A); /* Send line feed */
if(flag==strlen(st) /* Check for length of
string*/
{

```

```

printf("\n");
flag=0;
outport(COM,0X0D);
/* Send carriage return */
delay(5);
outport(COM,0X0A); /* Send carriage return
*/
delay(5);
}
else
{
outport(COM,st[flag]); /* Send character to
com1 port*/
printf("%c",st[flag]);
flag++;
delay(DEL);
}
}
}
if(kbhit()) /* Check key hit */
{
delay(1);
outport(COM,0x04);/*Send End of
transmission */
main();
}
while(!kbhit());
}

/*Function for file transfer*/
f_snd()
{
int flag=0,count=0,fl; /* Local Variables */
char ch,st[55000],fnn[20];
clrscr();
initial(); /* Calling Initialisation Routine */
gotoxy(2,2);
printf("FILE NAME ? : ");
fp = fopen(gets(fnn),"rb"); /* Get file name to
be sent */
if(fp==NULL)
{
clrscr();
gotoxy(35,13);
printf(" FILE NOT FOUND !");
delay(1000);
main();
}
else
{
fl = filelength(5); /* Calculate file length */
gotoxy(23,20);
printf("File being transferred has %u
bytes",fl);
do
{
ch = fgetc(fp);
st[count] = ch;
count++;
}
while(count<=fl);
}
fclose(fp);

loop: status = inp(0X3FD); /*Check com1 port
status */
if((status & 0x20)==0x00)/* Check Trans-
fer holding register empty */
goto loop;
else
do
{
if(flag==fl) /*Check for file length */

```

```

{
gotoxy(50,24);
printf(" Press any key to exit !");
getch();
main(); /*Call main function */
}
else
{
outport(COM,st[flag]);/*Send each character
in the file*/
printf("\t%004x",st[flag]);
flag++;
delay(DEL);
}
}
while(!kbhit()); /* Check for key hit */
}

/*Initialisation Function */
initial()
{
inregs.h.ah = 0; /*Initialisation of port */
inregs.h.al = 0X63; /* Baudrate , Parity ,
Databits , Stopbit(s) */
inregs.x.dx = 0; /*Select port COM1 */
int86(0x14, &inregs, &outregs); /*Complete
Communication service Interrupt*/
}

/*Function for Splash screen*/
splash(void)
{
int d=DETECT,m,j,i;
struct palette type pal; /* Structure for palette
colours */
initgraph(&d,&m,""); /*Initialisation for splash
screen */
getpalette(&pal); /*Get palette colours*/
for(i=0;i<=pal.size;i++)
setrgbpalette(pal.colors[i],i*5,i*4,i*4);/*Combi-
nation of RGB colours*/
setfillstyle(8,8);
setcolor(15);
settextstyle(1,0,4);
setbkcolor(4);
for(i=0;i<17;i++) /* Writing text with RGB
palette colors */
{
setcolor(i);
outtextxy(45+i,200+i,"PC to PC Laser/IR
Communication");
}
sleep(1);
cleardevice();
for(i=0;i<17;i++) /* Writing text with RGB
palette colors */
{
setcolor(i);
outtextxy(175+i,200+i,"Mostek Electronics");
}
sleep(1);
cleardevice();
for(i=0;i<17;i++) /* Writing text with RGB
palette colors */
{
setcolor(i);
outtextxy(160+i,175+i,"K.S.Sankar");
}
sleep(1);
cleardevice();
closegraph();
}
/*-----end-----*/

```

TABLE X
Line Status Register Bits

Bit	Meaning
7	1 = DATA READY
6	1 = OVERRUN ERROR (OE)
5	1 = PARITY ERROR (PE)
4	1 = FRAMING ERROR (FE)
3	1 = BREAK INTERRUPT (BI)
2	1 = TRANSMITTER HOLDING REGISTER EMPTY (THRE)
1	1 = TRANSMITTER SHIFT REGISTER EMPTY (TSRE)
0	1 = 16550 PE/FE/BREAK IN FIFO QUEUE, 0 FOR 8250 AND 16450

ing corruption of the data. Finally, we succeeded, after modification of the circuit as shown in Fig. 3. We were able to flawlessly transfer files, from about 5-metre distance, between two 386-based PCs. We included a 38kHz modulator in the transmitter section and used IR receiver module, which includes a bandpass filter and demodulator for 38kHz carrier. Please refer to the author's circuit idea captioned 'Proximity Detector' in this issue for the working principle etc. For better understanding of the software program given by the author, we have included certain additional information in the succeeding paragraphs.

The base addresses for the serial communication ports in a PC are shown

in Table III. The offset address of the registers used in serial communication is given in Table IV.

For serial port initialisation, the program makes use of BIOS interrupt 14H service 00H. It initialises the serial port pointed to by the contents of dx register (0 for Com-1 and 1 for Com-2 port). The contents of 'al' register initialise the specific communication port for baud rate, parity, stop-bit code, and character-size code as per Table V (and expanded in Tables VI through IX respectively).

The transmitter holding register (THR) and receiver data register (RDR) both at address Base+0 (the former being write(only) and latter being read(only)) act as buffers during transmission and reception, respectively, of a character. The other most important register, which is referred to in the software program frequently, is the line status register (LSR) at Base+5 (i.e. 03FDH for COM-1 port or 02FDH for COM-2 port).

Meaning of each of the bits of line status register is given in Table X. Its bit 0 is set when a byte is logged in the receiver buffer register and cleared when the byte is read by the CPU. Its bit 6 is set when both the transmitter holding register and the transmitter shift register are empty.

Presently, the software program is meant for COM-1 port initialised for 600 bauds. It can be changed for 1200, or 2400, or 4800, etc by changing the contents of 'al' register in the initialisation function to 83H, or A3H, or C3H, etc in place of 63H. Similarly, for using COM-2 port, change all register addresses starting with 0X3f. to 0X2f. etc in the program.

With the information included in the tables and some knowledge of 'C' programming, the readers would be able to understand the program with the help of comments already included at various places in the program. The executable file as well as the source code will also be included in the CD available (optionally) with EFY Dec. 2000 issue.

The source code as well as executable files are proposed to be included in next month's EFY-CD. □

www.electronicsforu.com

a portal dedicated to electronics enthusiasts

MULTI-EFFECT CHASER LIGHTS USING 8051 MICROCONTROLLER

ADITYA U. RANE



The 8051 microcontroller, first developed by Intel, finds many applications in small development systems such as speed control of DC motors, timers, process-control applications, and temperature controllers. One of its simple applications as multi-effect chaser lights is described in this project.

Here the microcontroller 8051 controls the switching sequence of eight triacs (TR1 through TR8) via the buffer transistors T1 through T8, as shown in the schematic diagram of Fig. 1. Each triac, in turn, may be used to control a series of bulbs (with a total voltage drop of 230V AC and the current drawn through BT136 triacs not exceeding 4 amp).

Features of 8051 microcontroller. The heart of the circuit is the 8051 microcontroller. Some of the important features of the controller are as

follows:

- 8-bit CPU with register A (accumulator) and register B.
- 16-bit program counter (PC).
- 16-bit data pointer (DPTR).

- 8-bit program status word (PSW).
- 8-bit stack pointer.
- 128 bytes of internal RAM.
- No ROM for 8031, 4k ROM for 8051, and 4k EPROM for 8751.
- Two external and three internal interrupt sources.
- Four programmable input-output ports/registers.

One of the important parts of the 8051 CPU is its oscillator section. The oscillator section is present on the chip itself, only quartz crystal has to be con-

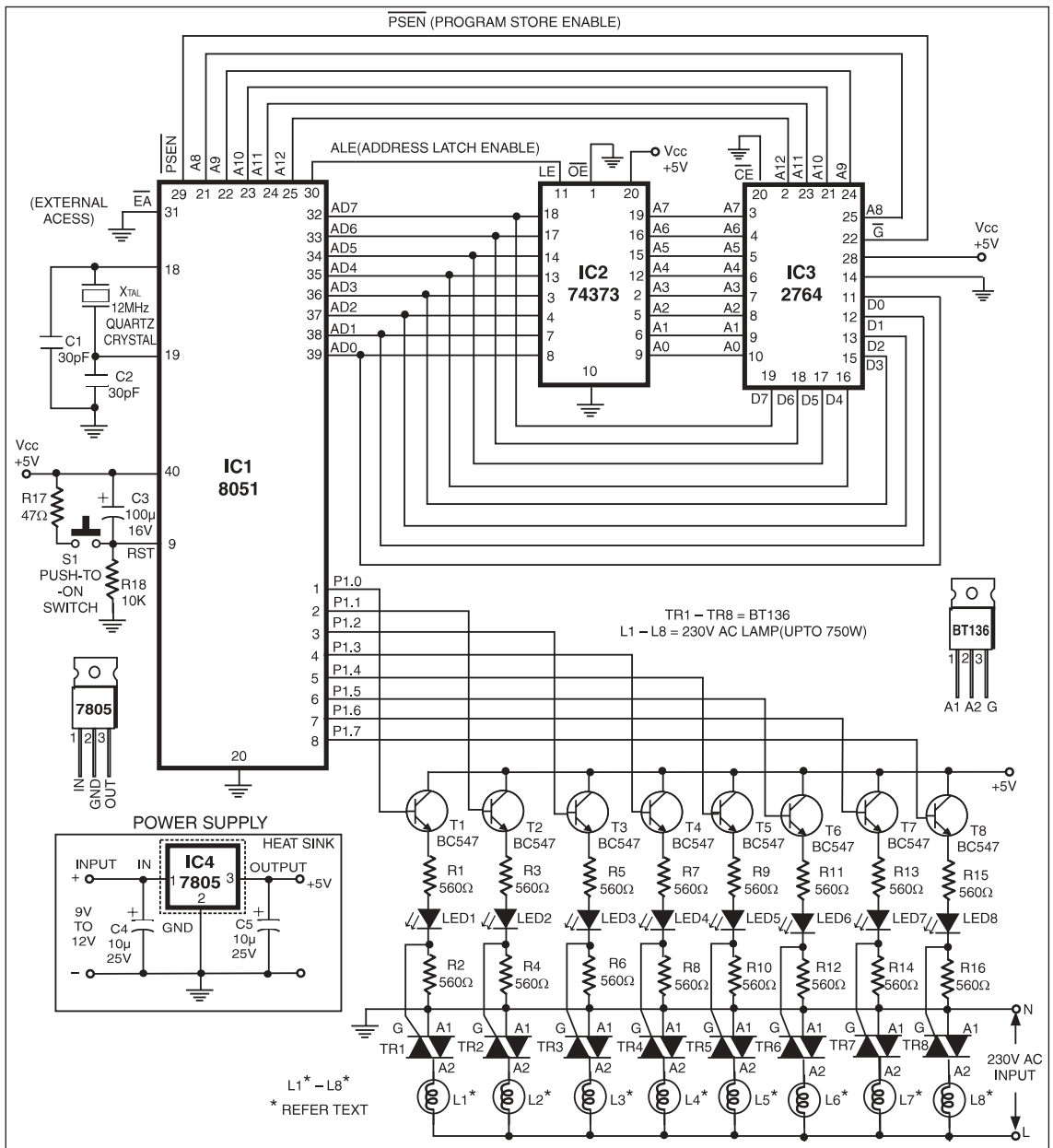


Fig. 1: Schematic diagram of multi-effect chaser lights

Pins	Use
P3.0 (RXD)	Receive data serially
P3.1 (TXD)	Transmit data serially
P3.2 (INT0)	External interrupt zero
P3.3 (INT1)	External interrupt one
P3.4 (T0)	I/P pin for timer 0
P3.5 (T1)	I/P pin for timer 1
P3.6 (WR)	External memory write pulse
P3.7 (RD)	External memory read pulse

nected externally between pins 18 and 19. The crystal frequency should range between 1 MHz and 16 MHz for proper functioning of the controller. If this frequency is taken below 1 MHz, there is a chance of losing data of its internal RAM.

Pin 31 happens to be the external access pin for the controller. If this particular pin is grounded, 8051 fetches program from the externally connected ROM/EPROM. And if it is connected to Vcc, it starts executing the program from the internal ROM that has 4k address space (0000H-0FFFH). For 8031, there is no internal ROM present, and hence this pin has to be grounded for its proper operation.

When internal ROM is used, and if the program exceeds the 4k internal ROM address space, then after the last address 0FFFH, it starts executing the program from externally connected ROM/EPROM. The externally connected ROM/EPROM can be increased up to 64k, i.e. 0000H-FFFFH. In the case of RAM, the same can be extended up to 64k.

It should be noted that the 8051 is organised such that data memory and program memory can be two entirely different physical memory entities. Another important aspect to be dis-

cussed relates to its input-output (I/O) ports. The 8051 has a total of four 8-bit ports, namely, P0, P1, P2, and P3.

P0. The P0 port may be used as input, output, or as combined low-order address and a bidirectional data bus for external memory, which is an alternate function.

P1. Port P1 does not have any alternate function. It means that these pins are used for interfacing input-output devices like ADC, DAC, 7-segment displays, LCD, keyboard, etc.

P2. Port P2 happens to be the high-order address lines, i.e. A8-A15. This port can be used for interfacing I/O devices. It should be noted that port 2 is changed momentarily by the address signals when supplying the byte of a 16-bit address.

P3. Port 3 functions in a fashion similar to that of port 1. Each pin of port P3 performs different operations as shown in Table I.

Hardware

The controller is interfaced with the external memory (EPROM) via the oc-

 


Fig. 2: PCB layout for the circuit

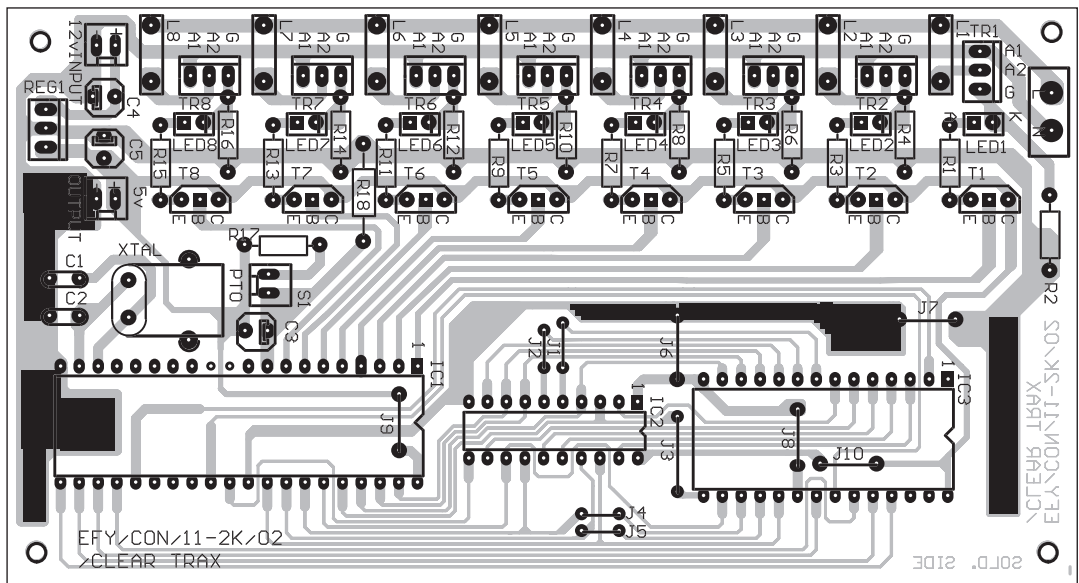


Fig. 3: Component layout for the PCB

 


Fig. 4: Output code format from port P1

 


Fig. 5: Output code format for setting only P1.0

tal 'D' latch 74LS373. The purpose of using 74LS373 is to demultiplex the address

lines and the data lines. Hence, after de-multiplexing, AD0-AD7 forms two sets of lines—address lines A0-A7 and data lines D0-D7. The higher-order address lines A8 to A15 are directly available from 8051 pins.

During the memory access cycle, port P0 first outputs lower bytes of 16-bit memory address and then the same port acts as bidirectional data bus to read a byte of memory, whereas port P2 provides the higher byte of memory address during the read cycle. It is further seen that the lower-order address byte of port P0 gets latched into external register of 74373 (IC2) to save the particular byte. The ALE (Address latch enable) pulse provides the precise timing to the 74LS373 for latching the low-order address.

If the memory access is meant for the program memory, the PSEN signal goes low and enables the EPROM to output the code on the data bus. The purpose of using PSEN (program store enable) is that it provides the output signal for the program memory/code memory. When this signal goes low, con-

 


Fig. 6: Hex code for Fig. 3

 


Fig. 7: Hex code for setting P1.0 and P1.7 bit

troller can read instruction byte from the program memory.

Under the program control, 8051 provides the output to port P1, which is further coupled to the base of driver transistors T1 through T8 (BC547). A logic 1 at any of the output pins of port P1 will drive the corresponding LED as well as the gate of the triac. The corresponding triac therefore fires to drive the lamp/lamps connected between its terminal A2 and the neutral line (N). If you use, say, 12V lamps, you may connect about 20 lamps in series. If each lamp is of 25-watt (passes about 2A current) rating, you may connect two rows of 20 such bulbs across A2 terminal of each triac and neutral line. The software program determines the triggering sequence of the triacs to provide the lighting effects.

Software

As mentioned earlier, lighting of bulbs is controlled by port P1 output code format. During the execution of the program, the code stored from memory location 0023H up 007CH (total locations are thus 59H or 89 decimal) will get loaded into the accumulator one by one and will get transferred to port P1. If the format of these codes or their sequence is changed, the output too will get altered in same manner. Please note that outputting logic 1 from any pin (equivalent to setting a specific bit) will switch 'on' the corresponding triac (and the series of bulbs connected across its terminals A2 and N), whereas outputting logic 0 from the same pin of port P1 (equivalent to clearing/resetting the specific bit) will switch it 'off'. The output code format from port P1 is shown in Fig. 4.

Example 1: If there is a requirement to set only P1.0 bit, the output format from port P1 will be as shown in Fig. 5.

For converting the above format to

PARTS LIST

Semiconductors:

- IC1 - 8051 microcontroller
- IC2 - 74373 octal 'D' type latches
- IC3 - 2764 EPROM 8-kbytes
- IC4 - 7805 regulator +5V
- T1-T8 - BC547 npn transistors
- TR1-TR8 - BT 136, triac
- LED1-LED8 - Red LED

Resistors (all 1/4-watt, ±5% carbon, unless stated otherwise):

- R1-R16 - 560-ohm
- R17 - 47-ohm
- R18 - 10-kilo-ohm

Capacitors:

- C1, C2 - 30pF ceramic disk
- C3 - 100µF, 16V electrolytic
- C4, C5 - 10µF, 25V electrolytic

Miscellaneous:

- X_{TAL} - 12MHz quartz crystal
- L1-L8 - L1 through L8 could each be a series of bulbs with total voltage-drop of 230V AC
- Heat-sink
- S1 - Push-to-on switch

www.electronicsforu.com

a portal dedicated to electronics enthusiasts

Program Listing For Multi-effect Chaser Lights

Add.	Code	Label	Mnemonics	Comments	Add.	Code	Label	Mnemonics	Comments
			ORG 0000H	;ROM starting address	003F	01		DB 01H	
0000	E4		CLR A	;Clear contents of accumulator	0040	11		DB 11H	
0001	759000		MOV P1,#00H	;Clear port 1 (off all LEDs)	0041	22		DB 22H	
0004	900023		MOV DPTR,#0023H	;Moving immediate DPTR	0042	44		DB 44H	
				;with 0023 (starting address of	0043	88		DB 88H	
				;O/P codes)	0044	44		DB 44H	
0007	7B00	LABEL2:	MOV R3,#00H	;Clearing the contents of	0045	22		DB 22H	
				register R3	0046	11		DB 11H	
0009	E4	LABEL1:	CLR A	;Clear accumulator	0047	33		DB 33H	
000A	2B		ADD A,R3	;Adding the contents of	0048	77		DB 77H	
				accumulator and register R3	0049	FF		DB FFH	
000B	0B		INC R3	;Incrementing the contents of	004A	77		DB 77H	
				register R3 by 1	004B	33		DB 33H	
000C	93		MOVC A,@A+DPTR	;Copy the code byte, found at	004C	11		DB 11H	
				;ROM address formed by adding	004D	81		DB 81H	
				;A dn the DPTR, to A	004E	42		DB 42H	
000D	F590		MOV P1,A	;Move the content the contents	004F	24		DB 24H	
				;of accumulator to port 1	0050	18		DB 18H	
000F	1116		ACALL DELAY	;Calling delay	0051	24		DB 24H	
0011	BB59F5		CJNE R3,#59H, LABEL1	;compare the contents of regis- ter R3 with 59H and jump to label1 if not equal else continue	0052	42		DB 42H	
				;Short jump to label2	0053	81		DB 81H	
0014	80F1		SJMP LABEL2		0054	C3		DB C3H	
0016	7801	DELAY:	MOV R0,#01H	;Move immediate register R0	0055	E7		DB E7H	
				;with 01H	0056	FF		DB FFH	
0018	7900	LABEL5:	MOV R1,#00H	;Move immediate register R1	0057	E7		DB E7H	
				;with 00H	0058	C3		DB C3H	
001A	7A00	LABEL4:	MOV R2,#00	;Move immediate register R2	0059	81		DB 81H	
				;with 00H	005A	01		DB 01H	
001C	DAFE	LABEL3:	DJNZ R2,LABEL3	;Decrement the content of	005B	02		DB 02H	
				register R2 till it becomes zero	005C	04		DB 04H	
001E	D9FA		DJNZ R1,LABEL4	;Decrement R1 till zero	005D	08		DB 08H	
0020	D8F6		DJNZ R0,LABEL5	;Decrement R0 till zero	005E	10		DB 10H	
0022	22		RET	;Return	005F	20		DB 20H	
0023	01	DB 01H	;DB(Define Byte) is		0060	40		DB 40H	
0024	02	DB 02H	;the assembler directive		0061	80		DB 80H	
0025	04	DB 04H			0062	40		DB 40H	
0026	08	DB 08H			0063	20		DB 20H	
0027	10	DB 10H			0064	10		DB 10H	
0028	20	DB 20H			0065	08		DB 08H	
0029	40	DB 40H			0066	04		DB 04H	
002A	80	DB 80H			0067	02		DB 02H	
002B	40	DB 40H			0068	01		DB 01H	
002C	20	DB 20H			0069	03		DB 03H	
002D	10	DB 10H			006A	0C		DB 0CH	
002E	08	DB 08H			006B	30		DB 30H	
002F	04	DB 04H			006C	C0		DB C0H	
0030	02	DB 02H			006D	30		DB 30H	
0031	01	DB 01H			006E	0C		DB 0CH	
0032	03	DB 03H			006F	03		DB 03H	
0033	07	DB 07H			0070	0F		DB 0FH	
0034	0F	DB 0FH			0071	F0		DB F0H	
0035	1F	DB 1FH			0072	FF		DB FFH	
0036	3F	DB 3FH			0073	00		DB 00H	
0037	7F	DB 7FH			0074	FF		DB FFH	
0038	FF	DB FFH			0075	00		DB 00H	
0039	7F	DB 7FH			0076	FF		DB FFH	
003A	3F	DB 3FH			0077	AA		DB AAH	
003B	1F	DB 1FH			0078	55		DB 55H	
003C	0F	DB 0FH			0079	AA		DB AAH	
003D	07	DB 07H			007A	55		DB 55H	
003E	03	DB 03H			007B	AA		DB AAH	
					007C	55		DB 55H	

normal hex level, you have to apply 8421 logic (Fig. 6) and you get 01H.

Example 2: To set P1.0 and P1.7, you have to output 81H from port P1 (Fig. 7).

In the software program, total codes to be displayed are 007CH-0023H = 0059H, as mentioned earlier, and hence 59H is loaded in the main program at memory location 0012H. Further, register R3 being an 8-bit register, the

maximum count is restricted to FFH (255 decimal). Since we are comparing the contents of register R3 with 59H, when register R3 reaches that count, the compare instruction gets satisfied and it jumps to label 2 (in the program). In case you wish to extend the codes to be output from port P1, the loaded count at memory location 0012H has to be altered correspondingly. The program, when run, produces an eye-catching

lighting effect. The complete program listing is given in the box above.

An actual-size, single-sided PCB for the circuit in Fig. 1 is shown in Fig. 2 and its component layout is shown in Fig. 3. It is important that neutral and phase (live) lines of 230V AC are not interchanged, because only the neutral line is required to be grounded to PCB common ground and not the live line. □

AUTOMATIC BATTERY CHARGER

YASH DEEP



Normally, chargers available in the market do not have any sort of control except for a rotary switch that can select different tapings on a rheostat, to vary the charging current. This type of control is not adequate because of the irregular fluctuations in the mains supply, rendering the control ineffective.

A simple circuit intended for automatic charging of lead-acid batteries is presented here. It is flexible enough to be used for large-capacity inverter batteries. Only the rating of transformer and power transistor needs to be increased.

The circuit has been basically designed for a car battery (about 40 Ah rating), which could be used for lighting two 40W tubelights. The circuit includes Schmitt trigger relay driver, float charger, and battery voltage monitor sections.

The Schmitt trigger is incorporated to


avoid relay chattering. It is designed for a window of about 1V. During charging, when the battery voltage increases beyond 13.64V, the relay cuts off and the float charging section continues to work. When battery voltage goes below 11.66V, the relay is turned on and direct (fast) charging of the battery takes place at around 3A.

In the Schmitt trigger circuit, resistors R1 and R2 are used as a simple voltage divider (divide-by-2) to provide battery voltage sample to the inverting input terminal of IC1. The non-invert-

ing input terminal of IC1 is used for reference input derived from the output of IC2 (7806), using the potentiometer arrangement of resistors R3 (18 kilo-ohm) and R4 (1 kilo-ohm).

LED1 is connected across relay to indicate fast charging mode. Diodes D3 and D6 in the common leads of IC2 and IC3 respectively provide added protection to the regulators.

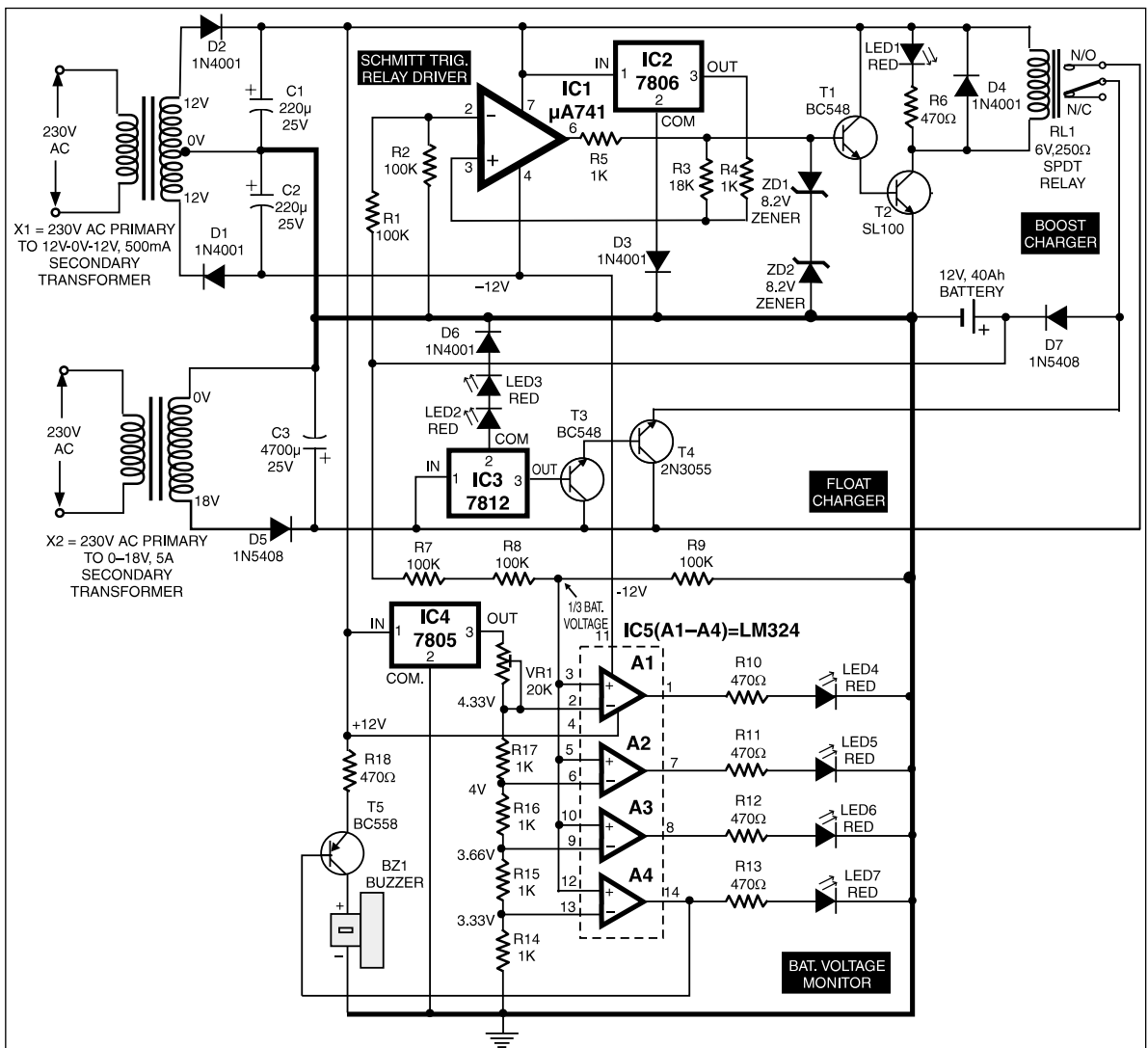The float charging section, comprising regulator 7812, transistors T3 and T4, and few other discrete components, becomes active when the battery voltage goes above 13.64V (such that the relay RL1 is de-energised). In the energised state of the relay, the emitter and collector of transistor T4 remain shorted, and hence the float charger is ineffective and direct charging of battery takes place.



The reference terminal of regulator (IC3) is kept at 3.9V using LED2, LED3, and diode D6 in the common lead of IC3 to obtain the required regulated output (15.9V), in excess of its rated output, which is needed for proper operation of the circuit. This output voltage is fed to the base of transistor T3 (BC548), which along with transistor T4 (2N3055) forms a Darlington pair. You get 14.5V output at the emitter of transistor T4, but be-

cause of a drop in diode D7 you effectively get 13.8V at the positive terminal of the battery. When Schmitt trigger switches 'on' relay RL1, charging is at high current rate (boost mode). The fast charging path, starting from transformer X2, comprises diode D5, N/O contacts of relay RL1, and diode D7.

The circuit built around IC4 and IC5 is the voltage monitoring section that provides visual display of battery volt-

age level in bar graph like fashion. Regulator 7805 is used for generating reference voltage. Preset VR1 (20 kilo-ohm) can be used to adjust voltage levels as indicated in the circuit. Here also a potentiometer arrangement using resistors R7, R8, and R9 is used as 'divide by 3' circuit to sample the battery voltage. When voltage is below 10V, the buzzer sounds to indicate that the safe discharge limit has been exceeded.

TEMPERATURE MEASUREMENT INSTRUMENT

ANANTHA NARAYAN




If wires of two dissimilar metals are joined at both the ends and the junction formed at one of the ends is heated more than the other junction, a current flows in the circuit due to Seebeck thermal emf. This effect is used in thermocouple (TC) temperature sensors.

The Peltier effect is converse of the Seebeck effect, which means that if a current is forced through junctions of dissimilar metals, one junction starts getting hot while the other starts getting cold, depending on direction of the applied emf. This effect is used to make small portable refrigerators.

It is known that one of the junctions is the sensing or hot junction (T_{mes}) and the other junction is the terminating or cold junction (T_{ref}). The voltage between terminals 'a' and 'b' is proportional to $T_{mes} - T_{ref}$ (as given in the Table I). The formula being $V_{ab} = a(T_{mes} - T_{ref})$, where a is the Seebeck coefficient of the thermocouple.

In the circuit, use only metal film

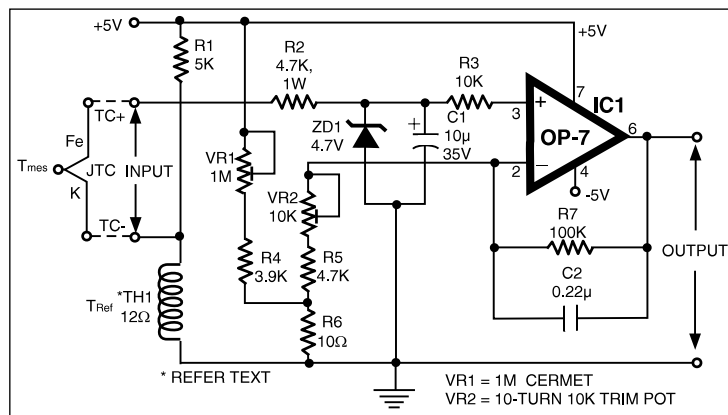resistors (MFRs) of 1 per cent tolerance, as this is an instrumentation application. Power supply should be a stable +5V, -5V supply, for which one can use 7805 and 7905 regulators.



The input terminals TC+ and TC- should go to a 4-way barrier terminal block. Two extra terminals are used to mount TH1 Cu thermistor. This forms an isothermal block, which is good

enough.

A simple way to make a TH1 Cu thermistor is to take a 1meg-ohm, 2W resistor as a former and wind 2 metres of 46 SWG enameled copper (Cu) wire (5.91ohm/metre) over it. This gives a 12-ohm value. Terminate wire ends on resistor leads.

For calibration, you will need a DMM/DPM and a millivolt source (as shown in the figure below). First connect source between terminals TC+ and TC-, then set source to 0.00 mV (verify with DMM for zero). The output across +out and -

out terminals must be in mV (use DMM), representing the room temperature (RT). For example, if RT is 30°C (use a glass thermometer), +out should be 30mV. At 0mV input, adjust VR1 till 30mV is read at +out terminal. This is

 
 


Table I

MV Thermocouple	Temperature in °C	Remarks
0	0	As cold junction is not zero but is at room temperature (RT), add RT to temperature.
2.585	50	
5.268	100	
10.777	200	
16.325	300	
21.846	400	
27.338	500	
33.096	600	
Example		
Feed 10.777mV between the TC+ and TC- terminals. If RT is 30°C, reading on 2V DPM will be 230 counts i.e. 230mV.		
Reference junction or cold junction at 0°C.		

'zero cal'. Now increase mV input to 21.85 (corresponding to 400°C). Then vary VR2 till +out terminal is at 430mV (temp. +RT). This is 'gain cal'. Now, as VR1 and VR2 are interdependent, you may have to repeat 'zero cal' and 'gain cal' a few times till you get the above values.

Properties of J thermocouple and design aspects of gain block used in the temperature measurement instrument are summarised below:

J Thermocouple (ANSI Symbol 'J')

1. J is a thermocouple made of iron (positive) and constantan (negative).
2. Constantan is an alloy of copper and nickel.
3. Full range of use is from -200°C to +700°C.
4. It is practical to use it only from 0°C to 400°C.
5. It is useful in reducing and alkali-

line atmosphere.

6. It corrodes/rusts in acidic and oxidising atmosphere.
7. Colour codes of wires are negative-red and positive-white.
8. J type is popular because of low price and high mV output.
9. J type TC is used in rubber/plastic forming and for general purpose.

Design of gain block

1. Minimum input from thermocouple is as low as 1 to 2 mV. Hence ultra-low offset (<100µV) op-amp OP07 is used.
2. Inputs may be subjected to wrong connections or high voltage. Use of resistor R2 limits current and zener ZD1 clamps voltage to a safe level.
3. Gain required is 400mV/21.8mV, which is approximately 18 at 400°C.

Gain $A_v = (R_f + R_i) / R_i$. Here R_f is R_7 and $R_i = R_5 + R_6 + VR_2$ (in circuit-value).

Design of TH1 cold junction compensation copper thermistor

1. J Type TC output changes by 0.052mV per °C as per Table I. Copper has a temperature coefficient of 0.0042 ohm per ohm/°C. For example, for a copper wire of 12 ohms, it is $12 \times 0.0042 = 0.05$ ohm/°C.

2. For R_1 of 5k, current through TH1 = $5V/5k = 1mA$. Change of voltage across TH1 with temperature is $0.05 \times 1mA = 0.05$ mV/deg.

3. This rate is the same as that of J type thermocouple and hence it simulates cold junction.

Lab Note. During lab testing the value of VR1 had to be very much increased. However, as per author, it should be kept at 1 kilo-ohm only.

VOICE BELL

MUKESH KUMAR SONI



This circuit consists of two parts as shown in the figure. The upper circuit should be assembled in a box along with regulated 9V power supply (not shown in figure), while lower circuit may be assembled on a small general-purpose PCB and fixed inside the doorbell switch enclosure. Connect points A and B of one module to the similar points of the other, using a simple 2-core electric cable. The polarity need not be adhered to, because the bridge rectifier used inside the switch circuit automatically ensures proper polarity.


In the normal condition, any voice or sound in the vicinity of the door, where the lower circuit (module 2) is installed, will be heard on module 1 inside your home. However, as soon as the door bell switch is pressed by someone, a distinct bell sound will be heard in the loudspeaker, inside the house.

With switch S1 in open condition, module 2, which is a simple condenser mic amplifier, amplifies the sound/audio in its vicinity and the audio output is available across points A and B. In module 1, this audio is developed across preset VR1, which acts as a volume control. The audio from the wiper of the preset is coupled to the input of

low-power (1.2-watt) audio amplifier TBA820M, which after amplification is fed into a 4-ohm loudspeaker. (The combination of resistor R9 and capacitor C7

introduced by EFY Lab in the path of Vcc pin 6, during actual testing, helps in noise reduction and limits the power dissipation in IC2.)

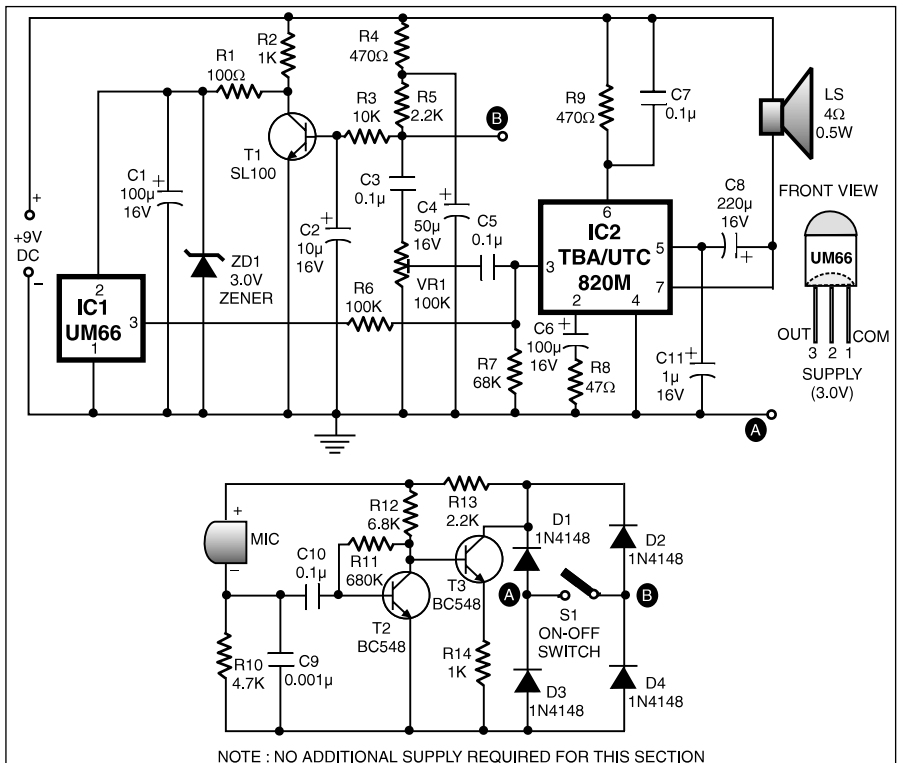Transistor T1 is normally conducting due to its base pulled to the positive supply rails via resistors R3, R5, and R4. Therefore collector of transistor T1 is at near ground potential, and



hence the melody generator UM66 (IC1) does not get any power supply and is thus off.

When bell switch S1 is pushed (closed), the audio output from module 1 is shorted to ground and at the same time transistor T1 base is pulled to ground via resistor R3. As a result, transistor T1 is cut off, to pull

its collector high. The voltage at collector of transistor T1, after limiting by zener ZD1 to 3V, serves as power supply for melody generator UM66. The output of melody generator is directly coupled to the input of audio amplifier and hence only melody is reproduced in the speaker, when switch S1 is pushed.

The main advantage of this bell is

that if there are strangers outside the door, conversing before gaining entry by pressing the bell switch, you can eavesdrop and hear their conversation to guess their intentions.

Lab Note. This circuit can be easily modified to act as door-phone cum door-bell. So try it out!

MOVING CURTAIN DISPLAY



K.P. VISWANATHAN

Several circuits have been published in earlier issues of EFY for producing eye-catching lighting effects, such as lighting up of characters one-by-one and their going off one-by-one in same direction, i.e. first character goes off first and so on (first-in first-out, or FIFO). In the present circuit, an attempt is made for changing this sequence, i.e. the first character to go off last (last-in first-out, or LIFO).

Easily available ICs are used and the number of characters is limited to


five. Effects like 'curtain opening and closing' and 'peacock feathers spreading and closing' can be produced. Wiring of the same is shown in separate figures. Each line is lit up by 6-volt or 12-volt bulbs connected in series for 230V AC operation and controlled via triacs. LEDs can also be used with proper driving circuits. (Please ensure that sum of voltage drop across the series-connected bulbs is equal to around 230V.)


Flip-flops formed by NOR gates are used for controlling the sequence. NOR

gates N1 and N2 form an oscillator whose period can be controlled using preset VR1. Oscillator's output is fed to clock input pin 14 of IC1 (CD4017), which is a decade counter.


Initially when output Q0 of IC1 is high, the output of flip-flop formed by NOR gates N3 and N4 goes high, thus triggering triac-1 through driving transistor T1. In the same way, when Q1 to Q4 outputs go high sequentially, corresponding triacs get triggered and all the five groups of bulbs light up. The first part of the sequence is over.

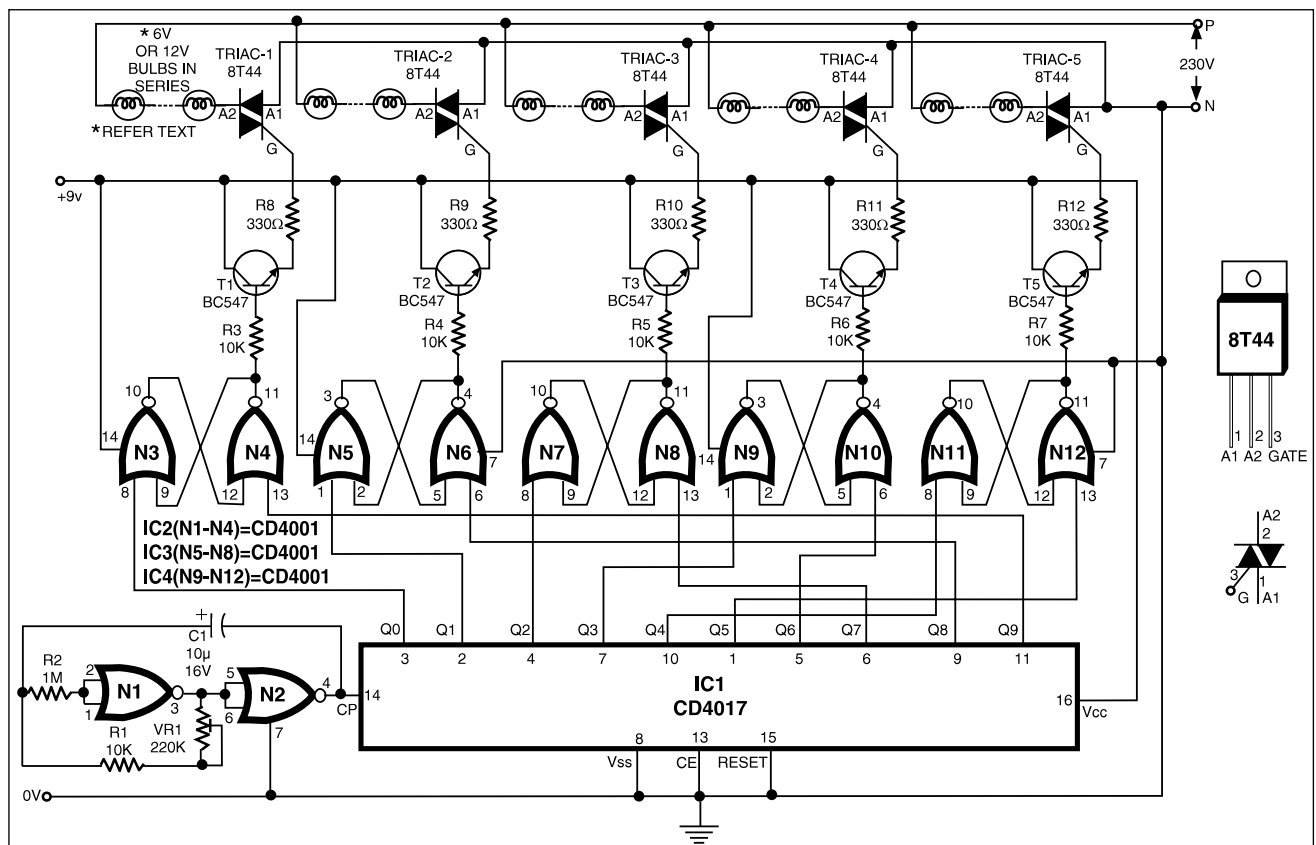When output Q5 of IC1 become high, the flip-flop formed by NOR gates N11 and N12 is toggled and the output is pulled to logic 0, removing the neces-



 

 sary drive given to triac-5. Similarly, when outputs Q6 through Q9 become high, triac-4 through triac-1 go off one by one and the earlier lit up bulbs go off last. The second part of the sequence is also over and then the



cycle repeats itself endlessly.

PROXIMITY DETECTOR

K.S. SANKAR



This proximity detector is constructed using an infrared diode detector. Infrared detector can be used in various equipment such as burglar alarms, touch-free proximity switches for turning on a light, and solenoid-controlled valves for operating a water tap. Briefly, the circuit consists of an infrared transmitter and an infrared receiver (such as Siemens SFH506-38 used in TV sets).

The transmitter part consists of two 555 timers (IC1 and IC2) wired in astable mode, as shown in the figure, for driving an infrared LED. A burst output of 38 kHz, modulated at 100 Hz, is required for the infrared detector to sense the transmission; hence the set-up as shown is required. To save power, the duty cycle of the 38kHz astable multivibrator is maintained at 10 per cent.

The receiver part has an infrared detector comprising IC 555 (IC3), wired for operation in monostable mode, followed by pnp transistor T1. Upon reception of infrared signals, the 555 timer (mono) is turned 'on' and it re-

mains 'on' as long as the infrared signals are being received.

When no more signals are received, the mono goes 'off' after a few seconds (the delay depends on timing resistor-capacitor combination of R7-C5). The delay obtained using 470kilo-ohm resistor and 4.7µF capacitor is about 3 seconds. Unlike an ordinary mono, the capacitor in this mono is allowed to charge only when the reception of the signal has stopped, because of the pnp transistor


T1 that shorts the charging capacitor as long as the output from IR receiver module is available (active low).

This setup can be used to detect proximity of an object moving by. Both transmitter and receiver can be mounted on a single breadboard/PCB, but care should be taken that infrared receiver is behind the infrared LED, so that the problem due to infrared leakage is obviated.

An object moving nearby actually reflects the infrared rays from the infrared LED. As the infrared receiver has a sensitivity angle of 60°, the IR rays are sensed within this lobe and the mono in the receiver section is triggered. This principle can be used to turn 'on' the light, using a relay, when a person comes nearby. The same automatically turns 'off' after some time, as the person moves away.

The sensitivity depends on the current-limiting resistor in series with the infrared LED. It is observed that with in-circuit resistance of preset VR1 set at 20 ohms, the object at a distance of about 25 cms can be sensed.

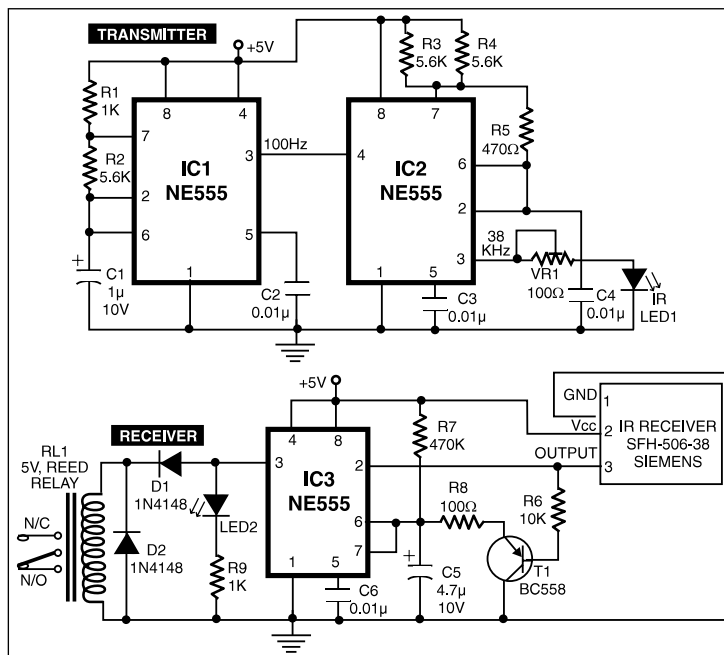This circuit can be used for burglar alarms based on beam interruption, with the added advantage that the transmitter and receiver are housed in the same enclosure, avoiding any wiring problems.



December

2000

ELECTRONIC BELL SYSTEM

Dr D.K. KAUSHIK

In this innovative project, a simple electronic bell system using commonly available ICs is presented for use in educational institutes. This simple and easy-to-fabricate project has the following features:

- It sounds the bell automatically after every period of 40 minutes.
- It displays in digital form the current time and period number of the class going on.
- The system automatically switches off after the last period (11th period). The digital clock showing the current time,

PARTS LIST

Semiconductors:

IC1	- 7805 +5V regulator
IC2	- 7474 dual 'D' flip-flop
IC3	- MM5369 oscillator/driver
IC4	- MM5387/LM8361 clock chip or equivalent
IC5, IC6	- CD4026 decimal up-counter with 7-segment driver
IC7-IC10	- CD4017 decade counter
T1, T2	- BC107 npn transistor
T3, T4	- 2N2222 npn switching transistor
D1-D8	- 1N4001 rectifier diode
LED1, LED2	- Red LED

Resistors (all 1/4-watt, $\pm 5\%$ carbon, unless stated otherwise):

R1, R2	- 2.2-kilo-ohm
R3, R44, R50	- 1.5-kilo-ohm
R4	- 4.7-kilo-ohm
R5, R6, R45	- 10-kilo-ohm
R46, R48	- 330-ohms
R7-R43	- 56-kilo-ohm
R47	- 20-mega-ohm
R49	- 20-mega-ohm

Capacitors:

C1, C4	- 100 μ F, 25V electrolytic
C2	- 30pF ceramic disk
C3	- 30pF trimmer

Miscellaneous:

S1-S4	- Tactile switch (SPST)
S5	- Tactile switch (DPDT)
X _{TAL}	- 3.57945MHz crystal
RL1-RL2	- 12V, 200-ohm relay (SPST)
DIS.1-DIS.6	- LT543 common-cathode 7-segment display
	- Power amplifier with loudspeaker



intervals drive transistor T4 (see Fig. 2) into saturation for a few seconds (the exact duration being decided by the delay circuit comprising 56-kilo-ohm resistor R47, 100 μ F capacitor C4, and diode D7). When the transistor goes into saturation, relay RL2 is energised and the bell sounds for a few seconds.

Any electronic horn/siren using an

audio power amplifier of desired wattage may be used for the bell. In the prototype, the author used an audio tape recorded with the usual sound of brass bell, with tape recorder/player of 150 watts rating, driving four 20-watt speaker units. It was found adequate for the campus of any educational institute. The readers may, however, use any other sound system according to their requirements.

 


Fig. 1: Block diagram of the electronic bell system

however, continues working as usual.

The principle

Fig. 1 shows the block diagram of the system, which has three parts. Part I has the usual digital clock comprising quartz crystal oscillator cum frequency divider IC MM5369, clock chip MM5387, and 7-segment common-cathode displays.

The 1Hz pulse (i.e. one pulse per sec.) is taken from the digital clock and used in part II of the circuit. The accuracy of the system depends on this 1Hz pulse, obtained from the standard digital clock circuit. In part II of the system, the 1Hz pulse is used to obtain one pulse after every 40 minutes, by employing a four-stage counter circuit.

The pulses obtained at 40-minute in-

tervals drive transistor T4 (see Fig. 2) into saturation for a few seconds (the exact duration being decided by the delay circuit comprising 56-kilo-ohm resistor R47, 100 μ F capacitor C4, and diode D7). When the transistor goes into saturation, relay RL2 is energised and the bell sounds for a few seconds.

Part III consists of the period counter and display. It displays the current period in progress. The number of pulses received at 40-minute intervals are counted by this counter circuit and the display unit displays the period number.

One additional relay circuit is used so that the power supply given to parts II and III of the system is automatically interrupted at the end of the eleventh period. Next day the system has to be reset, and the cycle repeats.

The circuit

Fig. 2 shows the detailed circuit diagram. The clock circuit of part I of the system is designed using 3.58MHz quartz crystal, MM5369 crystal oscillator and divider (IC3), MM5387 clock chip (IC4), four com-

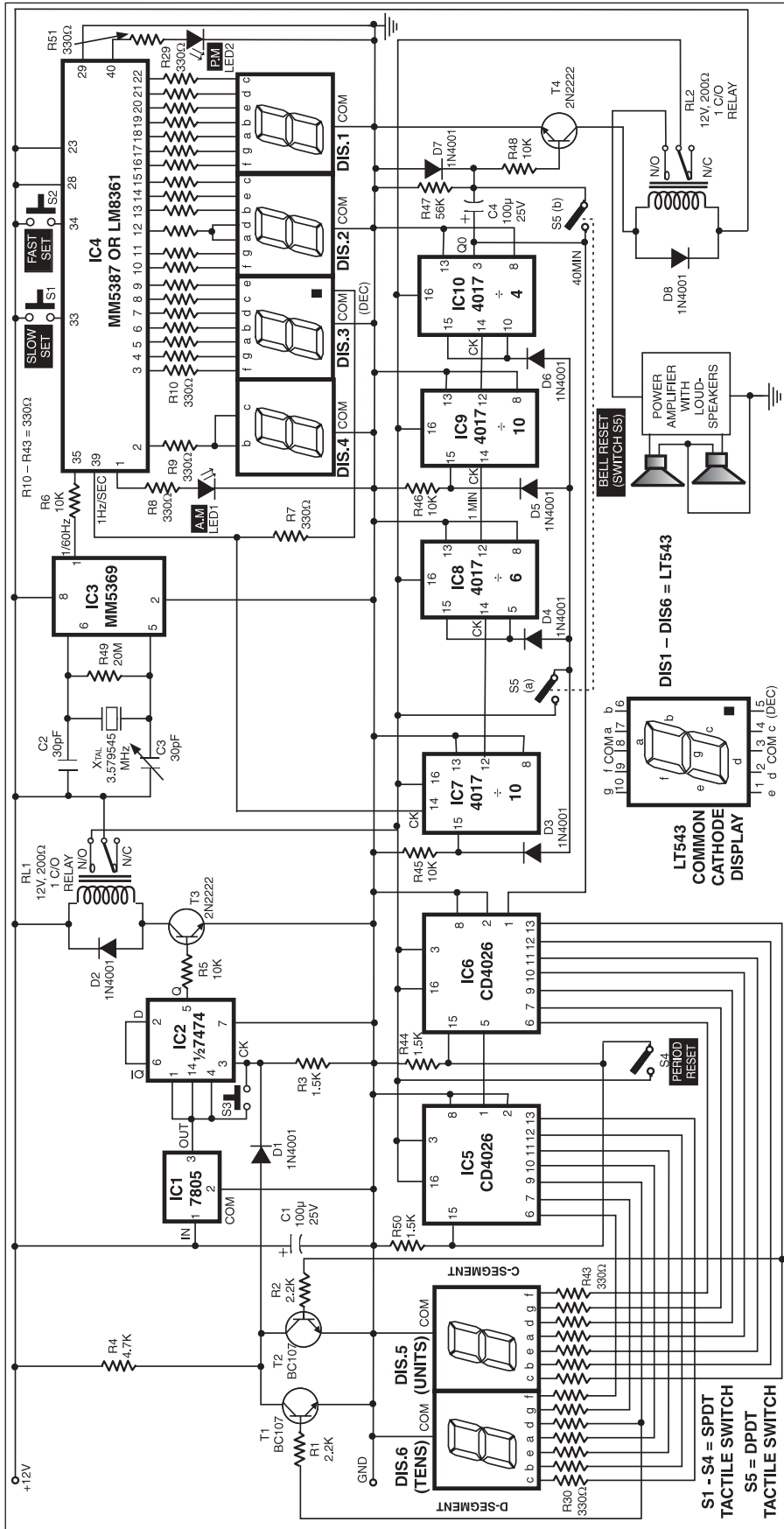


Fig. 2: Schematic diagram of electronic bell system for institutes

mon-cathode 7-segment displays, and a few passive components. For more details of the digital clock, the readers may consult 'Car Clock Module' project in September 1986 issue or Electronics Projects (Vol. 7) published by EFY. Push-to-on switches S1 and S2 (slow and fast time set) may be used to set the time of the digital clock.

(Note. For ready reference, pin configurations of ICs MM5369 and MM5387/LM8361 are reproduced here in Figs 3 and 4, respectively.)

The standard 1Hz pulse is taken from pin 39 of IC4 and connected to clock input pin 14 of decade counter IC7 (CD4017). The carry pin 12 of IC7 outputs a pulse every 10 seconds, which is connected to clock pin 14 of the next CD4017 decade counter (IC8). The reset terminal (pin 15) of IC8 is connected to pin 5 (output No. 6) of the same IC. This IC thus divides the signal by a factor of 6 and its pin 12 (carry pin) gives an output of one pulse every minute. This pulse is applied to IC9 (CD4017), where it is further divided by a factor of 10 to produce an output pulse at every 10-minute interval. Finally, a pulse at every 40-minute interval is obtained from IC10 (CD4017), which is configured as divide-by-four counter, since its reset pin 15 is shorted to Q4 output pin 10 of IC10.

The output pulse at pin 3 of IC10 remains high for ten minutes and low for 30 minutes. This output pulse (every 40 minutes) is connected to the base of transistor T4 through a combination of capacitor C4 and resistance R47, to energise the relay and sound the bell. The capacitor-resistor combination of C4-R47 acts as a differentiator circuit, while diode D7 clips off the negative going portion of the pulse. The delay time may be adjusted by choosing proper C4-R47 combination values.

After the preset time delay of a few seconds, the transistor goes into cut-off and the relay gets de-energised, to switch off the bell. However, the clock circuit of part I around IC4 and divider circuit formed by IC7 through IC10 con-

 


Fig. 3: Pin configuration of MM5369

tinue to work as usual and hence the accuracy of the periods is not affected by the 'on' and 'off' times of transistor T4.

To count and display the current period, a two-digit counter is designed using two CMOS decade counter cum 7-segment decoder/driver CD4026 ICs (IC5 and IC6) and two 7-segment common-cathode displays (LT543). The pulse obtained every 40 minutes from pin 3 of IC10 is also connected to the input of this two-digit counter. This counter counts these pulses and displays them via the LT543 (showing the current period number in progress). The two-digit counter counts and displays the period number up to 11.

The segment 'd' output for most significant digit (MSD) and segment 'c' output for least significant digit (LSD) from IC5 and IC6 are connected to the bases of transistors T1 and T2 respectively, via 2.2-kilo-ohm resistors R1 and R2. The collectors of the two transistors are connected together, working as a NOR gate. When 'd' and 'c' segment driving outputs from IC5 and IC6 respectively, go low simultaneously (just at the beginning of 12th period), the output (com-

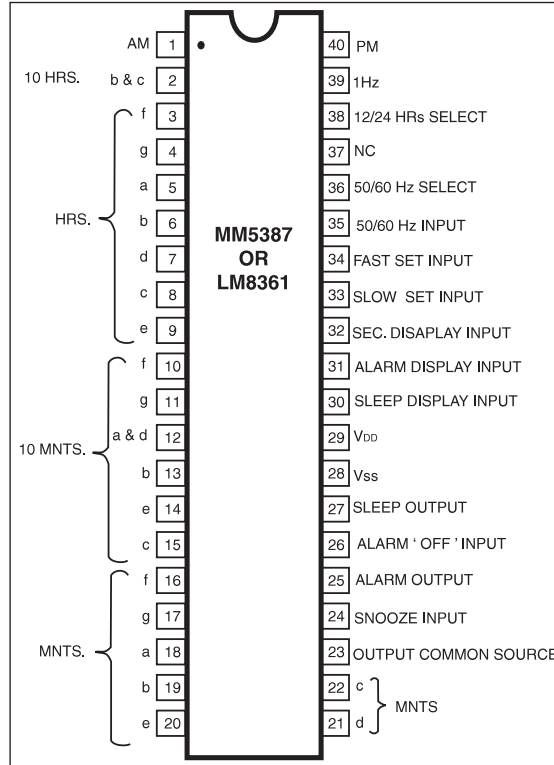


Fig. 4: Pin configuration of IC MM5387/LM8361

mon collector voltage of transistors T1 and T2) goes high. This output is also connected to clock pin 3 of IC2 (IC 7474), which is a dual 'D' flip-flop.

Only one of the two flip-flops is used here in toggle mode by connecting its \bar{Q} pin 6 to data (D) pin 2. The flip-flop toggles after every clock pulse.

circuit description, as discussed above. For operation of the circuit, switch S3 is momentarily pressed for resumption of the supply to parts II and III of the circuit, as relay RL1 is energised. Period-displaying 7-segment displays DIS.5 and DIS.6 will display any random number, which is reset to 00 by momentary depression of switch S4.

Further, switch S5 (DPDT) is pressed and then released exactly at the time when the first period is to start. This resets IC7 through IC10. The output Q0 at pin 3 of IC10 will go high, to energise the relay and thus switch on the bell for a few seconds and advance

The 'Q' output of this flip-flop drives relay RL1 through transistor T3, and thus switches off the supply to parts II and III of the system, just at the beginning of 12th period (i.e. at the end of 11th period). Resumption of the supply may take place the next day after momentarily pressing switch S3. For power supply, a 12V car battery with charging facility is recommended.

An actual-size, single-sided PCB for the circuit (Fig. 2) is shown in Fig. 5 and the component layout for the PCB in Fig. 6. The total cost of the system, excluding cost of audio amplifier, tape recorder, horn, etc, is about Rs 1,000.

Operation

After completing the circuit, test the circuit according to

 


Fig. 5: PCB layout

 


Fig. 6: Component layout

the period display from 00 to 01 (indicating that the first period has started). Hereafter, the circuit works automatically, sounding the bell for a few

seconds after every 40 minutes. In the evening after the eleventh period is over and the institute is to be closed, the power supply to parts II and III of the

exhibition where it was appreciated and liked by most of the visitors—especially those from the educational institutes.

circuit gets automatically switched off. Though the ringing of bell and display of periods discontinue, the digital clock continues to work as usual. Next morning, the above operation needs to be repeated. This system was successfully demonstrated by the author in a science and technology

www.electronicsforu.com

a portal dedicated to electronics enthusiasts

SIMPLE TELEPHONE RECORDING/ANSWERING MACHINE



B.B. MANOHAR

This project is intended to provide you with a simple recording and answering machine, which in the absence of the subscriber/owner of the telephone instrument, responds to the incoming calls and also records them automatically.

Description

To understand the overall working of the system, refer to its block diagram shown in Fig. 1. The incoming telephone line pair is terminated into the ring detection unit comprising a monostable flip-flop followed by a ring counter to detect the incoming calls. After counting a predetermined number of rings, it triggers a timer (another monostable flip-flop) via an inverter. The output of the timer is used for energisation of a set of relays, which initiate the following actions:

1. Switch on AC power to the tape recorder.
2. Switch on DC voltage to the tape player.
3. Reset the ring counter in the ring detector section to make it ready for the next incoming call/ring. However, any fresh call/ring will be ignored as long as the timer output stays 'high'. The timer output also controls the 'on' time of

the recorder and player. The 'on' time can be set as per length of the message to be recorded/played; say, two to three minutes.

4. Simulate off-hook state of the telephone, which is initially in on-hook condition.

The schematic diagram incorporating the control circuitry, including power supply and relays, is shown in Fig. 2. The line diagram, including all accessories used in the system, is shown in Fig. 3.

Normally, the telephone lines (in on-hook position of the

handset) carry 50V DC. However, during ringing, the lines carry 133Hz, 80V AC (modulated pulses), as shown in Fig 5.

Ring detection circuit comprises an input sensing section followed by monostable multivibrator and decade counter. In the input sensing section, capacitor C1 is used for DC blocking while 1N4007 diode D1 is used to rectify the AC ringing voltage. The potentiometer formed by resistors R2 and R3 (shunted by base-to-emitter resis-

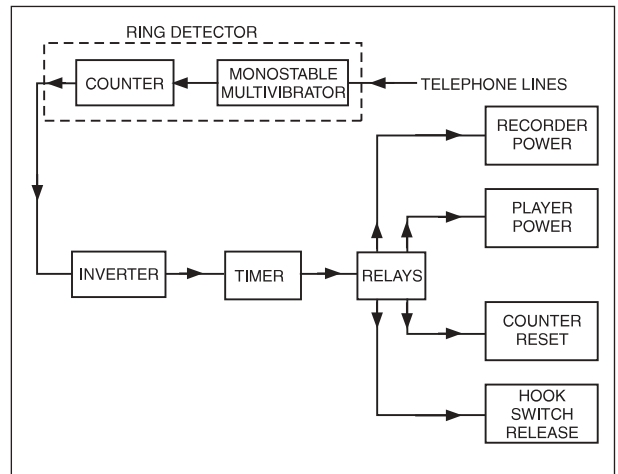


Fig. 1: Block diagram of telephone recording/answering machine

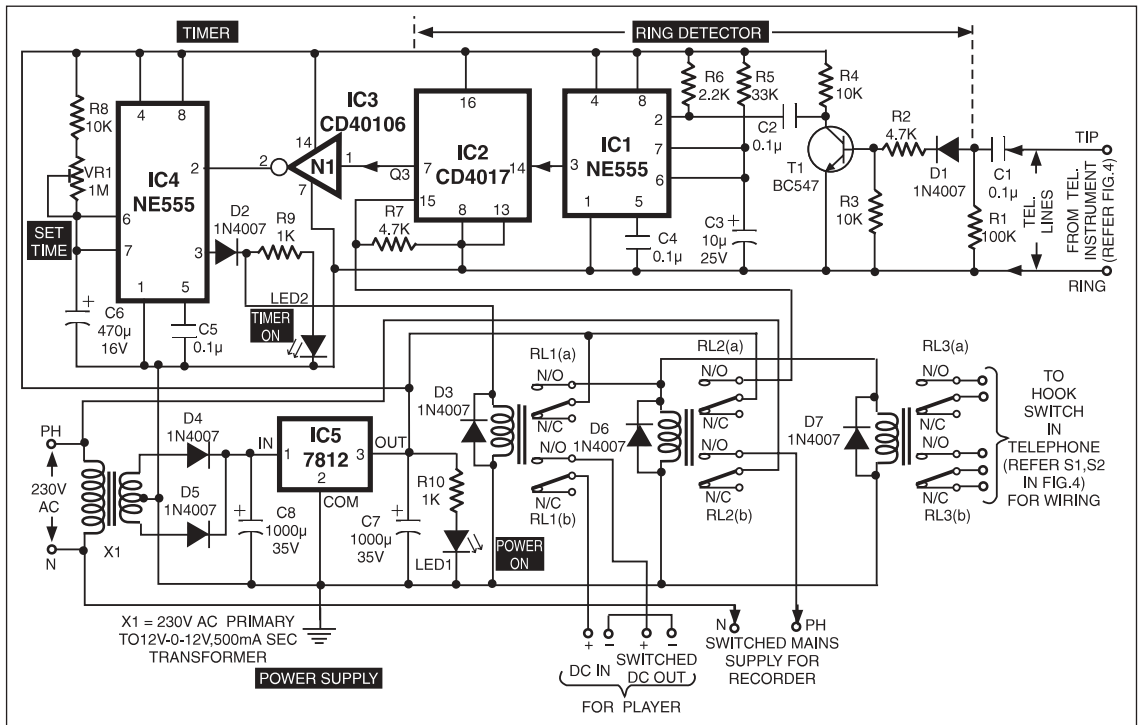


Fig. 2: Circuit diagram of telephone recording/answering machine

 


Fig. 3: Line diagram of telephone recording/answering machine showing interconnection amongst accessories used in the system

tance of transistor T1) acts as voltage/current limiting network for transistor T1. During the positive incursions

of the ringing voltage at the base of transistor T1, it is driven into saturation. As a result, the collector of

transistor T1 is pulled 'low'. This low-going pulse is coupled to trigger pin 2 of timer NE555 (IC1) configured as monostable (retriggerable). The output pulse width of IC1 is given by the relationship

$$\text{Pulse width} = 1.1 R4 \times C3 \text{ ..seconds}$$

where R4 is in ohms and C3 in Farads.

With the component values shown, the pulse width will be roughly 0.36 seconds. This will ensure that the mono pulse does not end during the pause period (0.2 sec.) between two successive rings, so that only one pulse is generated at the output of IC1 for each pair of ring signals separated by 0.2 seconds.

The output of IC1 is coupled to clock input pin 14 of the decade counter IC 4017 (IC2), which is used for counting the rings. From the decade counter one can select any output from Q0 through Q9. But in this project, we take the output from Q3, which goes high at the beginning of third ring

(so you will hear only two rings properly).

The Q3 output at pin 7 of IC2 is inverted by N1 inverter gate of IC3 to trigger timer IC4 (configured as monostable), whose pulse width can be adjusted with the help of preset VR1. The pulse width should be so adjusted that the tape player could replay the required message and the recorder could record the response from the far-end subscriber within the set pulse width period. As stated earlier, timer IC4, when triggered, initiates four different functions. These are

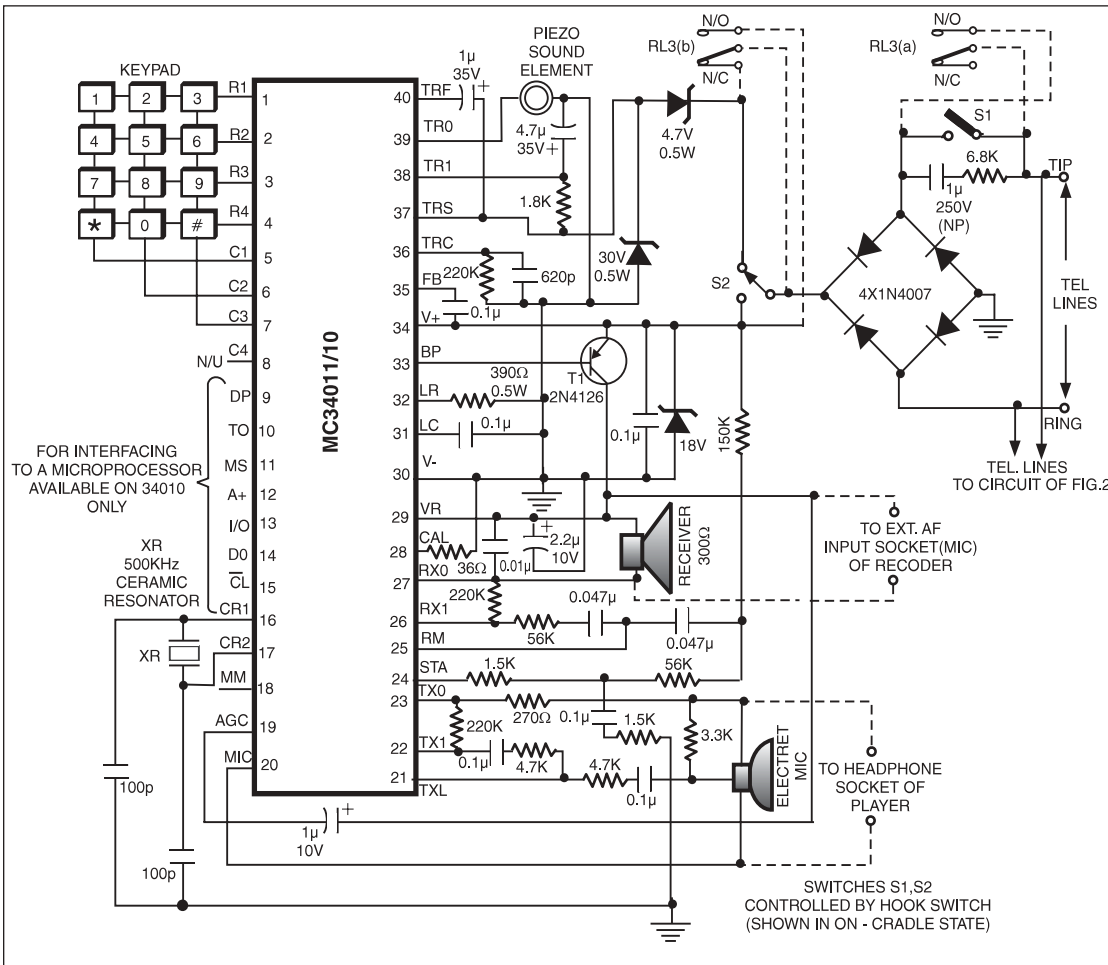


Fig. 4: Telephone circuit diagram using single Motorola IC MC34010/MC34011

 


Fig. 5: Ringing tone timing waveform

microprocessor interface; otherwise both chips are identical.)

Important points

Normally, the player and recorder buttons are always in the pressed or 'on' condition, so that these are automatically switched 'on' by timer

IC4 via relays. If we use C90 cassette tapes for the incoming calls, and assuming that pulse width of timer IC4 is set for 3 minutes, we can record/answer 15 incoming calls, since we can use only one side of the tape in this set-up and hence we can play/record the messages for 45 minutes only. However, one may use each 3-minute duration for message answering (playing) for

accomplished via relays RL1 - RL3 as follows:

1. The output of timer IC4 energises relay RL1. On energisation, contacts RL1(a) of this relay extend +12V to the coils of RL2 and RL3, thereby energising both of them (RL2 and RL3). RL1(b) contacts of relay RL1 (on energisation) switch on the DC supply to the record player, whose play button is supposed to be already depressed. (Please note that DC power supply for the player is not catered to in the circuit. The supply voltage will depend on the 'make' of the player, and may vary from one player to the other. In many cases, battery supply (provided inside the player itself) could be routed via RL2(a) contacts.) Thus, it will start playing the prerecorded message, which would get coupled to the telephone lines, since the hook switch would also be in the released state, simultaneously via relay RL3 (energised) contacts, as described later.

2. RL2(a) contacts of relay RL2, on energisation, extend +12V to reset pin 15 of counter IC2. Thus the counter remains reset until IC4 timer's output goes low again. RL2(b) contacts of relay RL2, on energisation, switch on 230V AC supply to the tape recorder and thus it can record the message received in the earpiece of the telephone.

3. Relay RL3 performs the functions of cradle switch for the telephone in absence of the subscriber (or even during his presence, if he fails to lift his handset off the cradle during ringing). Its contacts RL3(a) and RL3(b) are wired in parallel with the hook switch, as shown in Fig. 4. (This application circuit is based on Motorola single-chip telephone set IC MC34010 or MC34011. The latter chip does not provide

 


Fig. 6: Actual-size, single-sided PCB for the circuit in Fig. 2

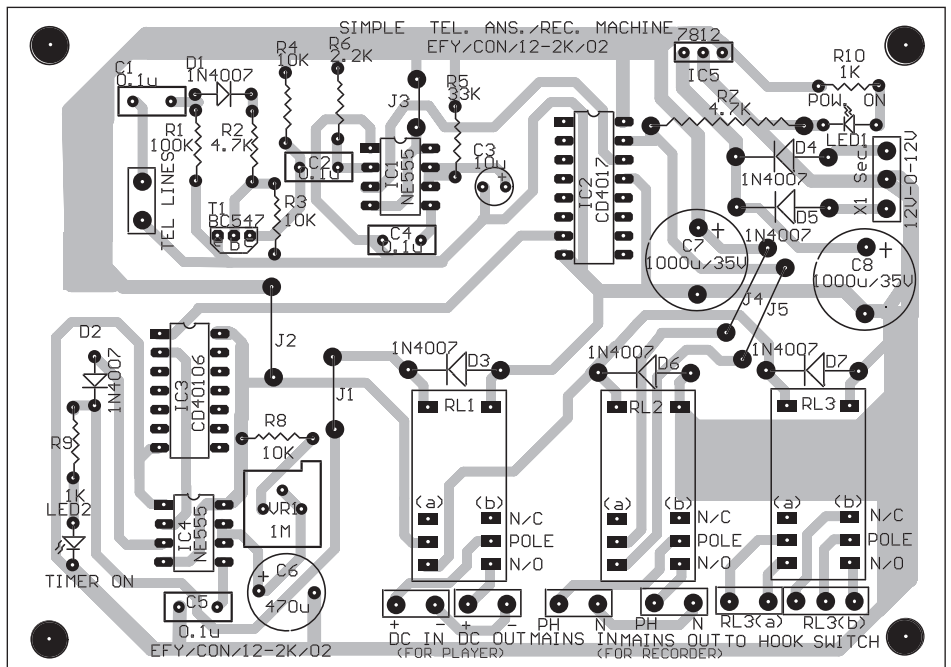


Fig. 7: Component layout for the PCB

PARTS LIST (Fig. 2)*Semiconductors:*

IC1, IC4	- NE555 timer
IC2	- CD4017 decade counter
IC3	- CD40106 inverter
IC5	- 7812 regulator (+12V)
T1	- BC547 npn transistor
D1-D7	- 1N4007 rectifier diode
LED1, LED2	- Red LED

Resistors (all ¼-watt, ±5% carbon, unless stated otherwise):

R1	- 100-kilo-ohm
R2, R7	- 4.7-kilo-ohm
R3, R4, R8	- 10-kilo-ohm
R5	- 33-kilo-ohm
R6	- 2.2-ohms
R9, R10	- 1-kilo-ohm
VR1	- 1-mega-ohm preset

Capacitors:

C1, C2, C4, C5	- 0.1µF, 25V ceramic disk
C3	- 10µF, 25V electrolytic
C6	- 470µF, 16V electrolytic
C7, C8	- 1000µF, 35V electrolytic

Miscellaneous:

X1	- 230V AC primary to 12V-0-12V, 500mA sec. transformer
RL1-RL3	- 12V, 150-ohm, 2C/o relay
	- Tape player with DC supply source
	- Tape recorder
	- Telephone instrument

a minute, with the remaining two minutes reserved for recording other-end subscriber's message (i.e. the tape in the player will run blank for these two minutes). During these two minutes, if other-end subscriber is relaying any message, then the same will be recorded automatically in the tape recorder that is already 'on'.

Whenever the subscriber (owner) intends going out of station, he will have to rewind the player and press the play button 'on'. Similarly, he has to rewind the recorder for recording the 15 incoming messages and also ensure that the recording button is in 'on' (pressed) condition. Both the recorder and the player will be automatically switched 'on' for the preset duration whenever three rings are received, as explained already.

An actual-size PCB for the circuit in Fig. 2 is shown in Fig. 6 and its component layout is shown in Fig. 7. □

The author is proprietor/technical director of VEPCO, Madurai.

www.electronicsforu.com

a portal dedicated to electronics enthusiasts

MULTICHANNEL CONTROL USING SOFT SWITCHES



P. SABARINATHAN


This circuit uses only one octal D-type latch, IC 74LS373, and some associated circuitry to control eight different gadgets. To control more devices, identical circuits, in multiples, can be used. The circuit incorporates the following features:

- (a) Individual 'on/off' control for all channels.
- (b) Emergency 'off' control for all channels.
- (c) Immediate 'on' control for all channels.
- (d) LED indication for 'on' channels.
- (e) Optional push-to-on buttons or tactile switches.


When one presses the 'on' switch (S1) of channel 1, a logic low is applied to data input pin D0. The same level appears on the data output pin Q0, because latch-enable pin LE (active high) is connected to Vcc, and the output-enable \overline{OE} (active low) is pulled down using resistor R9. At the same time, Q0 output is fed back to D0 input, which thus keeps the common

junction of D0 and Q0 (marked 'A' in the figures) at low level, even after releasing 'on' switch S1. This low level is applied to the base of transistor T1 through diode D9 to turn it on, and RL1 is activated. LED1 also glows to indicate that channel 1 is 'on'. The other channels can also be switched on, as desired, in a similar manner.

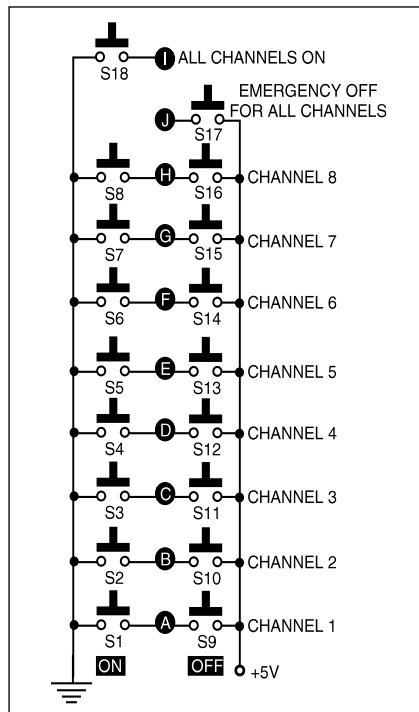To switch off channel 1, 'off' switch S9 of channel 1, is pressed to apply logic high to point 'A'. Because



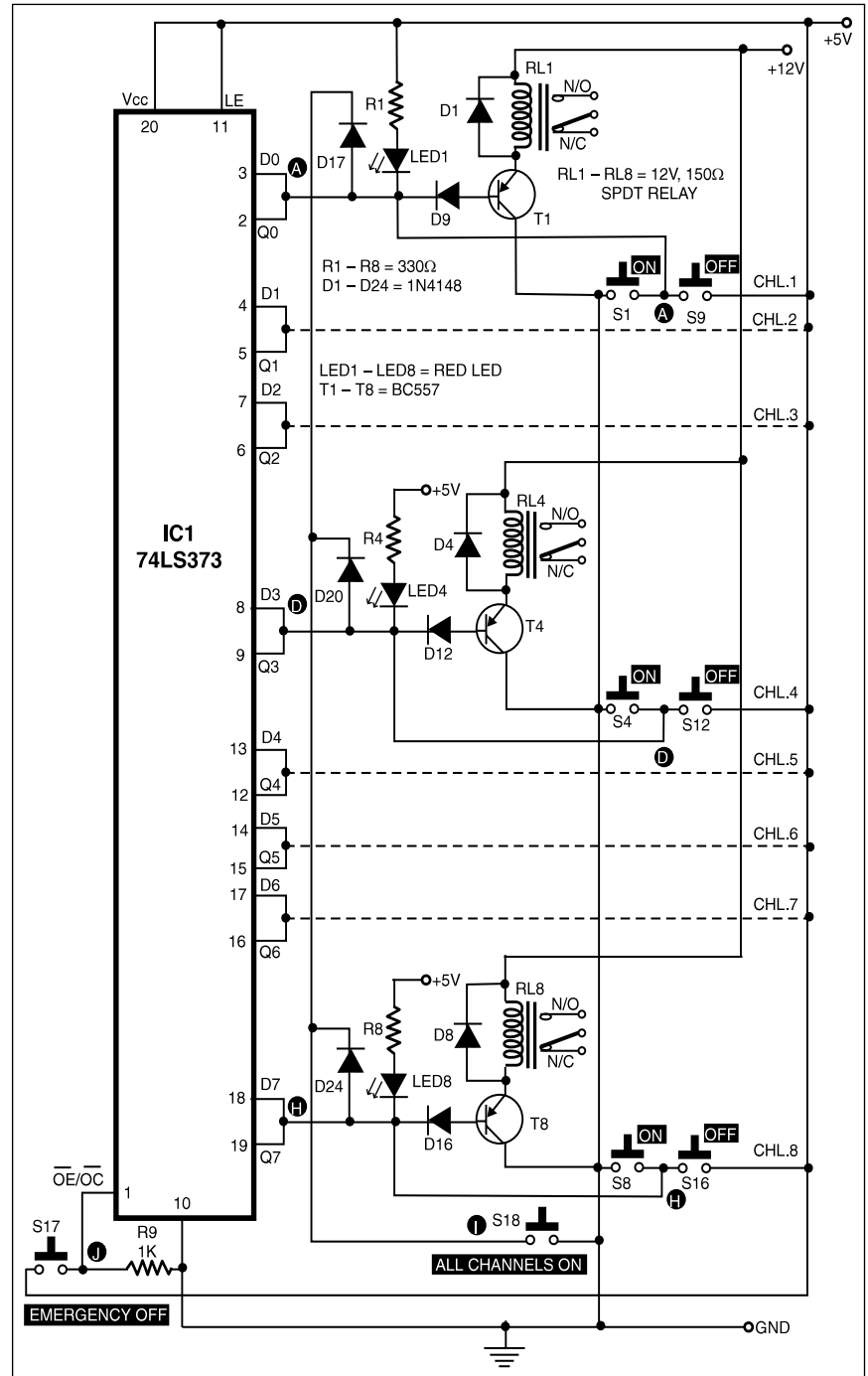junction of D0 and Q0 (marked 'A' in the figures) at low level, even after releasing 'on' switch S1. This low level



of the feedback from Q0 to D0, point 'A' remains high even after releasing the 'off' switch. As a result, relay RL1 is deactivated and LED1 also goes off.

In case of emergency, press the

emergency off switch S17 to disable all the outputs of IC1. In this state, the outputs of IC1 are in high impedance state, and as all transistor bases are almost 'open', all the relays get deactivated.

If all the channels are to be switched on simultaneously, a 'low' logic level is applied via diodes D17 through D24, to data inputs D0 to D7, by pressing switch S18 to activate all the relays.

AN EXCLUSIVE SINEWAVE GENERATOR

J. CHOUDHURY



Many electronic devices depend upon the shape of the signals. It is very easy to produce squarewave signals from sine wave, but reproducing sinewave signals from the square wave is quite difficult. In

case of static squarewave-to-sinewave converter, in low frequency range, we can get accurate sine wave, but in high frequency range the shape will not be a true sine wave. Here is a solution to that problem.

The circuit shown here uses five ICs. The squarewave signal is fed at pin 1 of IC1 (CD 4024). IC1 is a 7-bit counter, but here only 6 bits are made use of. The first four bits are fed as a signal bus to IC3 (CD4066) quad bilateral switch through IC2 (CD4077B) that contains four exclusive NOR gates. It converts the 4-bit signal bus to 'up mode' and 'down mode' hexadecimal signals, simultaneously. The converted signal bus switches on and off the ladder switches inside CD4066. As a result,


the net resistance of ladder varies. This varying resistance varies the charging and discharging current of capacitor C1 in the feedback path of IC5 (LM741).


The charging and discharging mode is controlled by IC4 (CD4011). In fact, capacitor C1 works as an integrator. The sinewave producing circuit needs 64-bit squarewave pulse for 360° sine wave. A missing pulse in this 64-bit sequence produces ramp.

In this circuit, all ICs except IC5 are CMOS ICs and hence the current consumption is very low.

The value of capacitor C1 may be calculated from the relationship: $C1 = 0.27 / f_0 \mu\text{F}$. The value shown in the circuit is for 50Hz output frequency. The shape of the sinewave output may be corrected using presets VR1 and VR2.

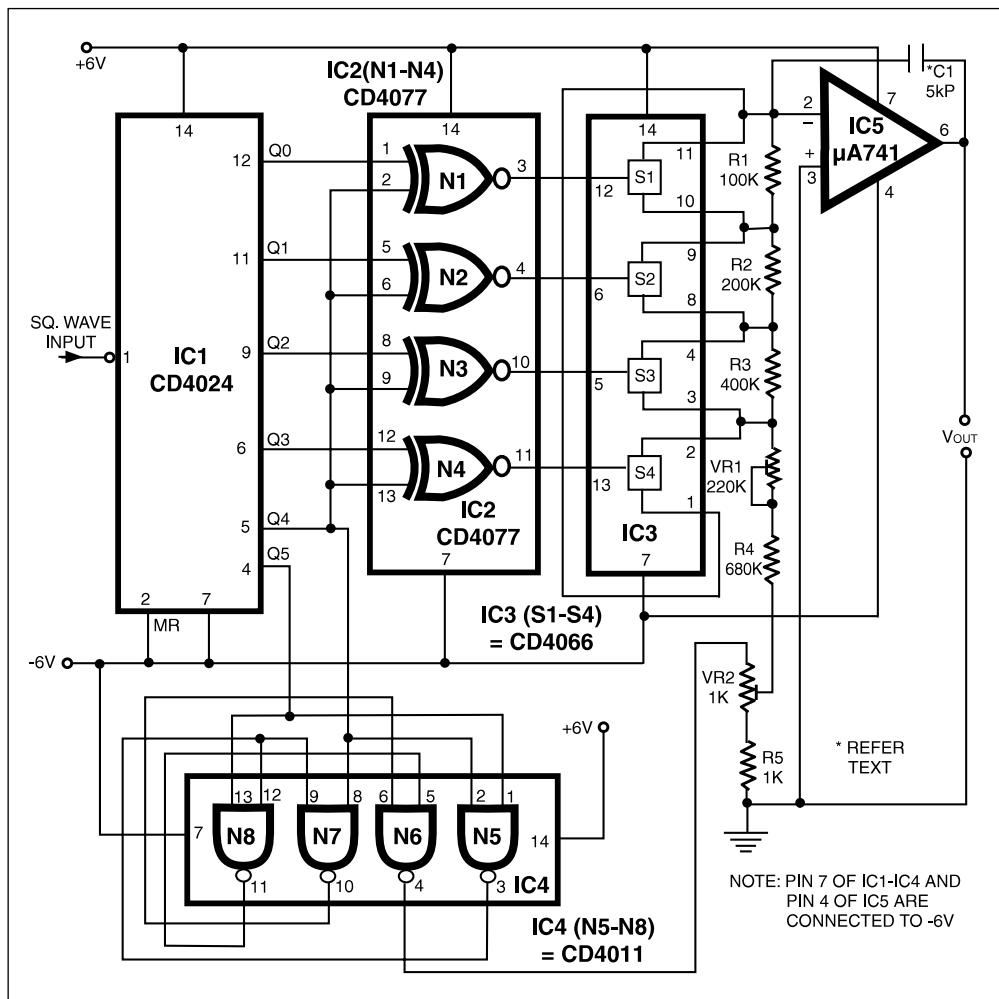(EFY Lab note. Spikes were noticed in the output waveform while operating with higher frequencies in the kilohertz range.)



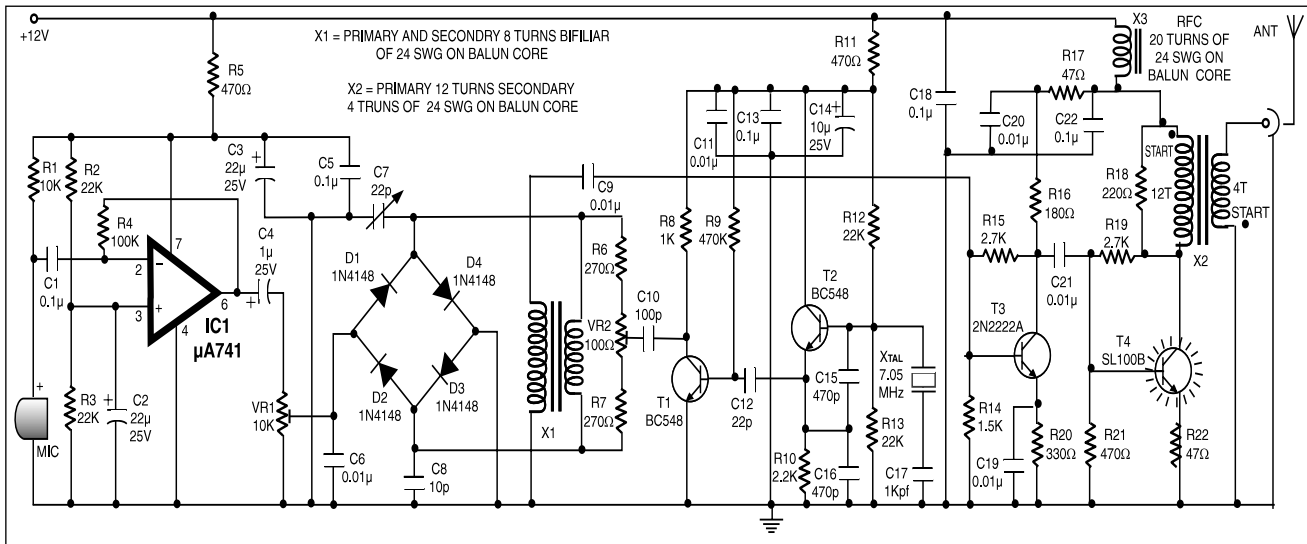

contain some residual carrier. This is known as carrier leakage. By adjusting the 100-ohm preset (VR2) and trimmer (C7) you can null the scariest leakage.

To receive DSB signals you need a beat frequency oscillator to reinsert the missing carrier. If you don't have a beat frequency oscillator, or want to transmit only AM signal, adjust preset VR2 to leak some carrier so that you can receive the signals on any ordinary radio receiver. In AM mode 100% modulation can be attained by adjusting pre-

sets VR1 and VR2.

The DSBSC signal available at the output of the balanced modulator is amplified by two stages of RF linear amplifiers. Transistor 2N2222A (T3) is used as an RF amplifier, which provides enough signal amplification to drive the final power amplifier around transistor SL100B. The output of the final power amplifier is connected to the antenna.

All coils are to be wound on ferrite balun core (same as used in TV balun transformer of size 1.4 cm x 0.6 cm)

using 24SWG enameled copper wire. Proper heat-sink should be provided for SL100B transistor used as final power amplifier.


Range of the order of a few kilometres can be easily achieved by proper choice of site, type of antenna (such as a resonant half-wave dipole of length 20 metres for 7.05 MHz frequency) and proper matching of transmitter to the antenna. Use good-quality shielded wire of short length to connect the crystals.

GROUND CONDUCTIVITY MEASUREMENT

PRASAD J.

The circuit presented here provides the simplest way to measure earth conductivity. Using

 this, radio hobbyists can choose a suitable site for the erection of antennae that require good grounding; for example,



industrial sheds or housing. With a little ingenuity and experimentation, one can even predict the availability of underground water at a site. It should be noted that geologists employ a similar probe, but in place of 50Hz AC mains used here, they employ RF for this purpose.

Though electronics hobbyists having a flair for gardening can measure the salinity or the fertility of soil to be used for their special plants, using the method described here, it however needs a lot of experimentation and study.

The circuit presented here employs a simple AC measurement technique. The efficiency of the circuit and results improve as the frequency of AC increases. With regular mains voltage source of 230 volts, 5-amp current capacity, and 50Hz frequency available, the measurements result in 25 per cent

accuracy, which is quite reasonable and adequate for some practical applications.

The bulb (which is 230V, 100W, filament type) shown in the figure is mounted on a wooden box with a bulb holder. Connection to the mains supply is obtained using long wires, which are terminated into a 3-pin power plug that ensures non-reversibility of live and neutral leads. The bulb drops the voltage to a safer level at the terminating probe. Resistor R1 limits the current. Voltage V1 is measured across resistor R1 using AC voltmeter.

The probes, which are equidistant from each other (about 45.7 cm, or 18-inches, apart) have a height (below ground level) of about 30.5 cm (12 inches) and a diameter of 1.25 cm (or ½-inch). The probes may be made of iron, stainless steel, or copper. (The au-

thor used copper probes.)

The ends of the probes are connected securely to the wires by means of battery terminal lugs (generally used in automobiles) or power supply terminals (used in UPS, DC-AC converters, etc). The probes P2 and P3 can be fixed on hylam strips measuring 75cm(20-inch)x5cm(2-inch)x5mm(0.2-inch). Hylam strips are generally available from switchboard dealers.

To measure the conductivity (σ), the probes are driven into the ground, as shown in the figure, and the circuit is powered with adequate safety measures against any electric hazard. Voltages V1 across resistor R1 and V2 across probes P2 and P3 are measured and noted.

The earth conductivity is then calculated as:

Conductivity = $21 \times V1/V2$ millimhos/metre ($m\sigma/m$)

Please note:

- For poor soil with very little moisture and bio-fertility, the conductivity ranges from 1 to 8 millimhos per metre.

- For average soil, the values range from 10 to 20 millimhos per metre.

- For fertile and good conductive soil, the conductivity ranges from 80 to 100 millimhos per metre.

- For very saline soil, or salt water with very good conductivity, the values might be as high as 5,000 millimhos per metre.


Caution. It should be noted that the polarity of the AC (phase and neutral) leads should never be reversed, to prevent any dangers to human/animal lives.

STEPPER MOTOR CONTROL VIA PARALLEL PORT

SHOBHAN KUMAR DUTTA

To better understand the circuit, one needs to have some knowledge of electronics, computer programming, and the computer's parallel port.

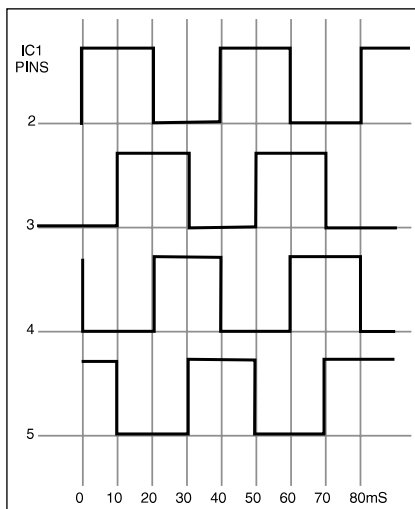You will of course need a computer, 12-volt power supply (preferably a battery eliminator), stepper motor, ULN2003 chip, and some connecting wires.




The circuit can be easily assembled on a breadboard. It is very important that you work with the smallest stepper motor available in the market, such as the one used in a floppy drive. If you go in for the large ones used in CNC machines, there is a chance of damaging the PC's parallel port. The second thing to mention is that the colours of the wires of the stepper motor are non-standard.

The parallel port of the PC is the most flexible way of getting the

computer to communicate with the outside world.

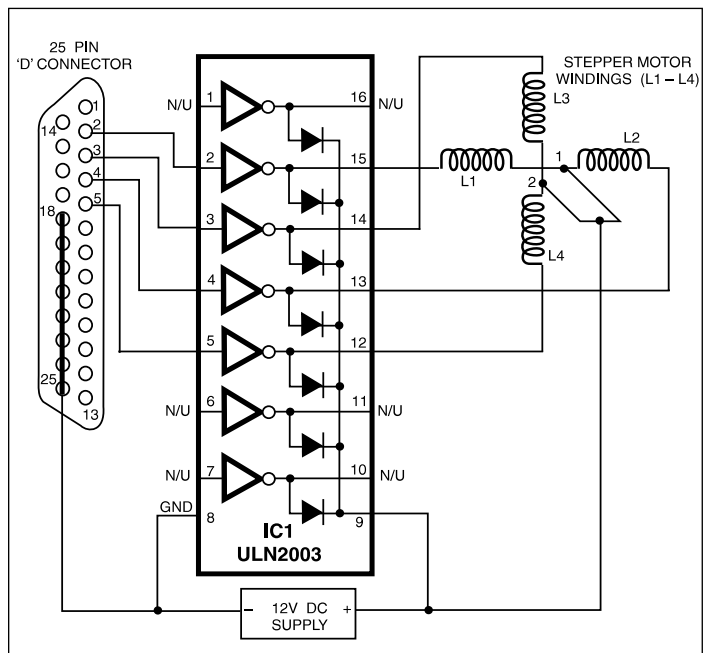The parallel port is generally used to interface printers, but we have used it to interface the stepper motor. The parallel port consists of 25 pins, but it can only transmit 8 bits of data at a time. The reason for the large number of pins is that every data pin has its own ground return pin. There are other pins for various other functions. We have used only four data pins and a ground pin.



The functions of the various pins are given in Table I. Pins 2 through 9 are data pins. Here, we will use data pins 2 to 5, corresponding to data bits D0 through D3 of port 378(hex) for LPT1 or 278(hex) for LPT2. Also, pin 25 is used as the ground pin.

The PC's parallel port cannot sink much current. At the most, it can handle a few milliamperes. So, if the parallel port is connected directly to an electrical device, it will damage the parallel port. Thus, we need a current amplifier in between the parallel port and the electrical device. The ULN2003, used precisely for this purpose, has an array of Darlington transistor pairs. A Darlington configuration is a way of connecting two transistors in order to amplify current to many times the input current value.

The stepper motor has various advantages over other motors, as far as controlling by a computer is concerned. It includes high precision of angular movement, speed of rotation, and high moving and holding torque. It comes in various flavours. We are dealing with unipolar permanent magnet stepper motor that has four coils arranged as follows:

Terminals 1 and 2 are common terminals (connected to ground or the positive supply) and the other four terminals are fed to the appropriate signals. When a proper signal is applied, the shaft turns by a specific angle, called

the step resolution of the motor. On continuous application of the same signal, the shaft stays in the same position. Rotation occurs only when the signal is changed in a proper sequence. There are three modes of operation of a stepper motor, namely, single-coil excitation mode, dual-coil excitation mode, and half-step modes.

- **Single-coil excitation.** Each coil is energised successively in a rotary fashion. If the four coils are assumed to be in a horizontal plane, the bit pattern will be 0001, 0010, 0100, 1000, and 0001.

- **Dual-coil excitation.** Here, two adjacent coils are energised successively in a rotary fashion. The bit pattern will be 0011, 0110, 1100, 1001, and 0011.

- **Half-step mode.** Here, the stepper motor operates at half the given step resolution. The bit pattern is 0001, 0011, 0010, 0110, 0100, 1100, 1000, 1001, and 0001.

Two software control programs, one for DOS and another for Linux, are included here. The program for DOS can be used to run the motor in full- or half-step mode, or in single-coil or double-coil excitation mode.

(EFY Lab note. The method used at EFY for correct identification of the

TABLE I

Pin No (D-type 25)	Signal	Direction In/Out	Register	Hardware Inverted
1	Strobe	In/Out	Control	Yes
2 thru 9	D0 thru D7	Out	Data	—
10	$\overline{\text{Ack}}$	In	Status	—
11	Busy	In	Status	Yes
12	PE	In	Status	—
13	Select	In	Status	—
14	$\overline{\text{AFeed}}$	Out	Control	Yes
15	$\overline{\text{Error}}$	In	Status	—
16	$\overline{\text{Initialise}}$	Out	Control	—
17	$\overline{\text{SLCT}}$ (Printer)	Out	Control	Yes
18 thru 25	Ground	—	—	—

stepper motor coils involved measuring the windings' resistance as well as their continuity in ohmsx1 scale, using any good multimeter. The resistance of individual coils with respect to the middle points will roughly be half the resistance of the combined coil pairs (L1 and L2 or L3 and L4 in the figure). After having identified the coils in this fashion, connect them to the circuit as shown in the figure. Now, if the sequence of input to the coils happens to be wrong, the shaft, instead of moving (clockwise or anti-clockwise), will only vibrate. This can be corrected by trial and error, by interchanging connection to the coils. The output waveforms for full-step single-coil mode, as seen on the oscilloscope, are shown in the figure.)

DOS PROGRAM

```
#include <conio.h>
#include <dos.h>
#define FULLSTEP_SINGLECOIL
#define FULLSTEP_DOUBLECOIL
#define HALFSTEP
unsigned char fullstep_singlecoil_val[]={1,2,4,8};
unsigned char fullstep_doublecoil_val[]={3,6,12,9};
unsigned char halfstep_val[]={8,12,4,6,2,3,9};
void main()
{
```

```
    unsigned int i=0;
    while(!kbhit())
    {
        #ifdef FULLSTEP_SINGLECOIL
        outportb(0x378,fullstep_singlecoil_val[i%sizeof(fullstep_singlecoil_val)]);
        #elif defined(FULLSTEP_DOUBLECOIL)
        outportb(0x378,fullstep_doublecoil_val[i%sizeof(fullstep_doublecoil_val)]);
        #elif defined(HALFSTEP)
```

```
        outportb(0x378,halfstep_val[i%sizeof(halfstep_val)]);
    }
    #endif
    delay(10);
    i++;
    if(i==65535u) i=0;
}
outportb(0x378,0);
}
Compile and run the program under any compiler like turboc for dos or Borland C++.
```

LINUX PROGRAM

```
#include <sys/io.h>
#include <unistd.h>
#include <stdlib.h>
#define FULLSTEP_SINGLECOIL
#define FULLSTEP_DOUBLECOIL
#define HALFSTEP
unsigned char fullstep_singlecoil_val[]={1,2,4,8};
unsigned char fullstep_doublecoil_val[]={3,6,12,9};
unsigned char halfstep_val[]={8,12,4,6,2,3,9};
void main()
{
```

```
    unsigned int i=0;
    if(ioperm(0x378,1,1)==-1) exit(1);
    while(1)
    {
        #ifdef FULLSTEP_SINGLECOIL
        outb(fullstep_singlecoil_val[i%sizeof(fullstep_singlecoil_val)],0x378);
        #elif defined(FULLSTEP_DOUBLECOIL)
        outb(fullstep_doublecoil_val[i%sizeof(fullstep_doublecoil_val)],0x378);
        #elif defined(HALFSTEP)
        outb(halfstep_val[i%sizeof(halfstep_val)],0x378);
```

```
    }
    #endif
    usleep(5000);
    i++;
    if(i==65535u) i=0;
}
outb(0,0x378);
}
Compile and run the program as follows:
#gcc -O6 -o motor motor.c
#./motor
The -O6 flag is necessary for using the 'outb' function.
```

The End